

# 國立成功大學 工程科學系 試題

電子學 (總分 110 分)

學號 E9406063 姓名 張凱淳 5/20/2016

計算題 6 題(110 分，共三頁)。推導過程須要詳細寫出來，若觀念正確，才能斟酌給分。

1. Assuming that the diodes in the circuits of Fig.1, are ideal, find the value of labeled voltages and currents.(20%)

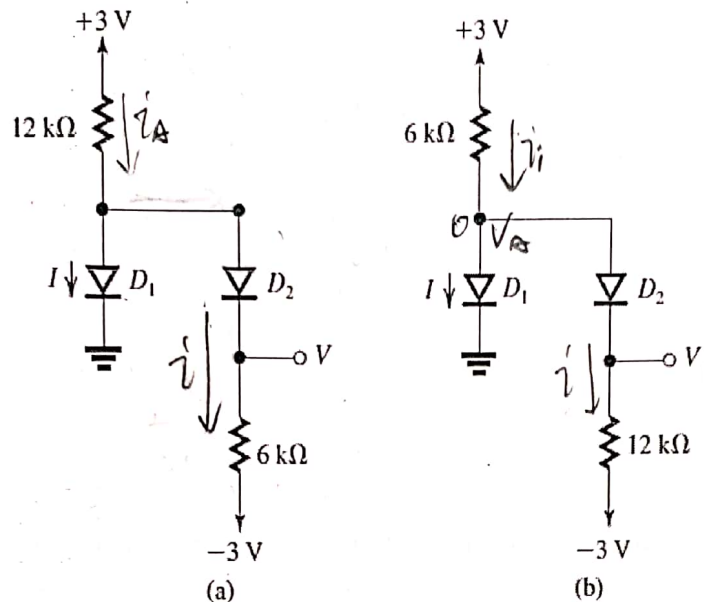


Fig.1

2. For the circuits shown in Fig.2, using the constant-voltage-drop ( $V_D = 0.7V$ ) diode model, find the voltages and currents indicated.(20%)


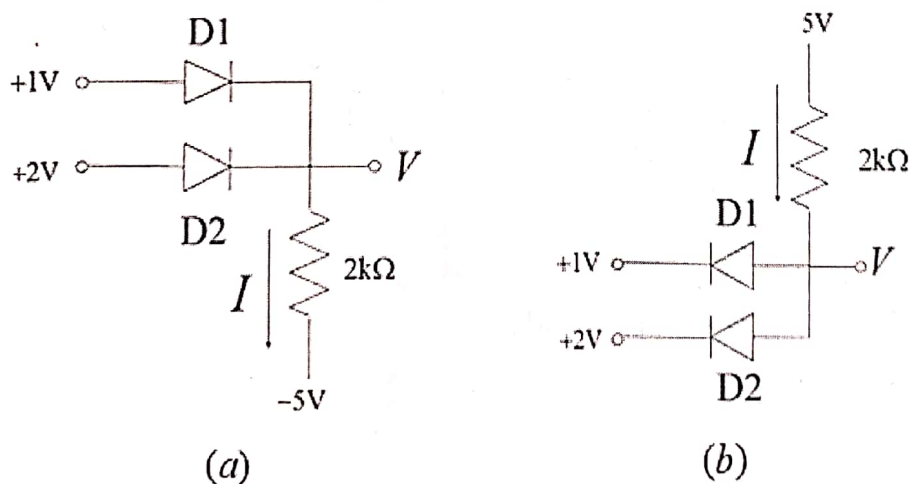


Fig.2

下頁還有題目

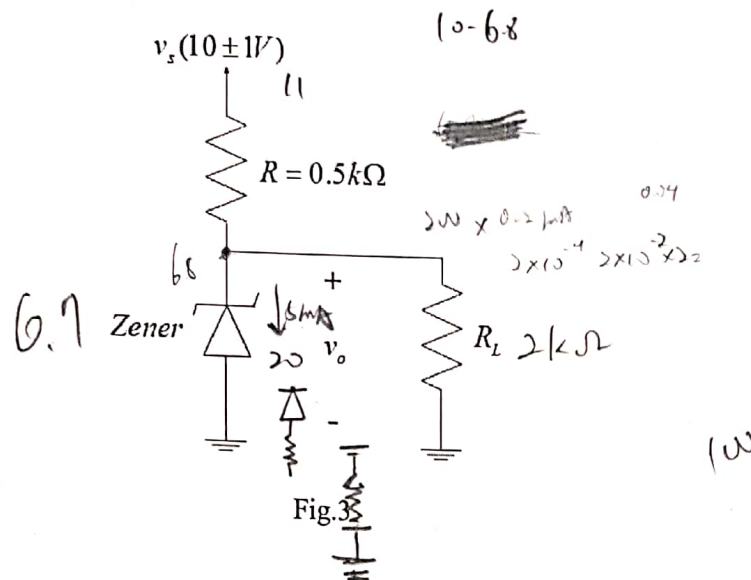3. The 6.8 V zener diode in the circuit of Fig.3 is specified to have  $V_Z = 6.8$  V at  $I_Z = 5$  mA,  $r_Z = 20\Omega$ , and  $I_{ZK} = 0.2$  mA. The supply voltage  $v_s$  is nominally 10 V but can vary by  $\pm 1$  V.
- (a) Find the change in  $v_o$  resulting from connecting a load resistance  $R_L = 2$  k $\Omega$ . (10%)
- (b) What is minimum values of  $R_L$  for which the diode still operates in the breakdown region? (10%)



4. The NMOS transistor in the circuit of Fig.4 has  $V_t = 0.4$  V and  $k'_n(W/L) = 4$  mA/V<sup>2</sup>. The voltages at the source and the drain are measured and found to be  $-0.6$  V and  $0.2$  V, respectively. What current  $I_D$  is flowing, and what must the values of  $R_D$  and  $R_S$  be? If we assume  $R_S$  is fixed, and NMOS operates in saturation region. What is the largest value for  $R_D$  for which  $I_D$  remain unchanged from the value found? Assume  $\lambda = 0$ . (20%)

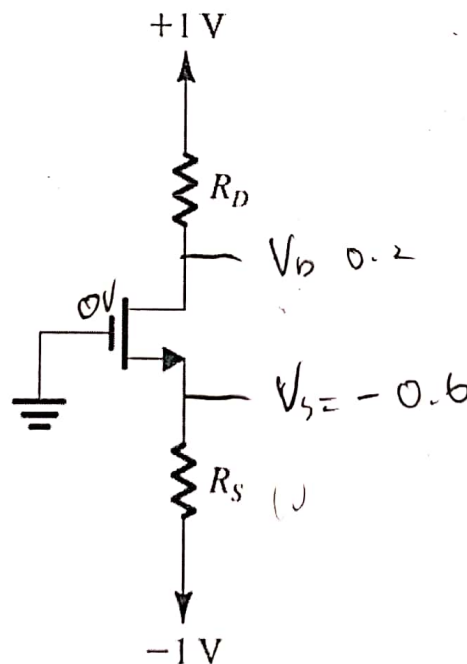


Fig.4

下頁還有題目

5. In the circuit shown in Fig.5, transistors are characterized by  $V_{tp} = -1V$ ,  $k'_n(W/L) = 4mA/V^2$ , find  $V_1$  and  $V_2$ , Assume  $\lambda = 0$ . (20%)

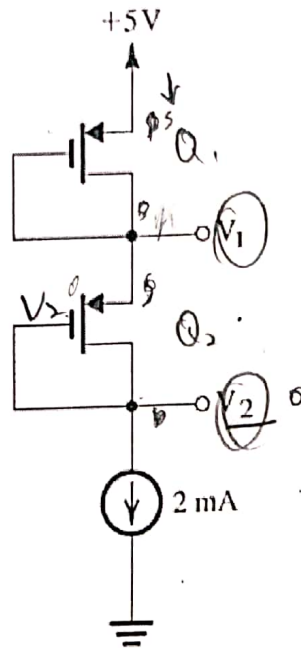


Fig.5

$V_1 = -1$

$V_{GS} = -V_2$

$2 = \frac{1}{2} \times 4 \times (-V_2 + 1)^2$

$-V_2 + 1 = \pm 1$

$V_2 = 2V$

6. For each of the circuits shown in Fig.6, find the labeled nodes voltages. The NMOS transistors have  $k'_n(W/L) = 1.5mA/V^2$  and  $V_t = 0.9V$ , Assume  $\lambda = 0$ . (10%)

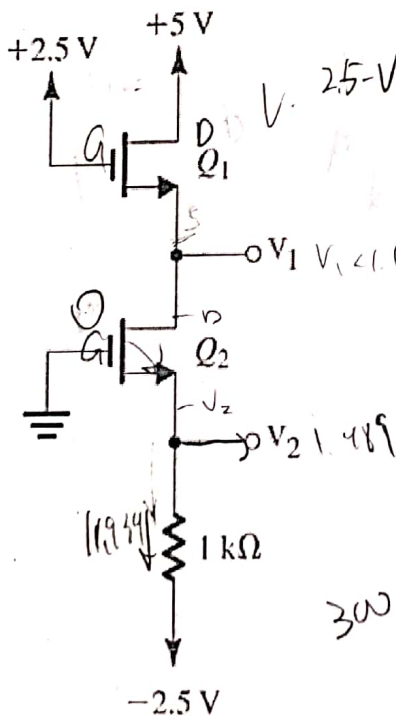


Fig.6

$0 - V_2$

$\frac{1}{2} \times 1.5 (-V_2 - 0.9)^2 = \frac{V_2 + 2.5}{10}$

$3V_2^2 + 5.4V_2 + 2.43 = 4V_2 + 10$

$3V_2^2 + 1.4V_2 - 7.57 = 0$

$3V_2 + 1.4 - 7.57 = 0$

$V_{GS} - V_t = \sqrt{b^2 - 4ac}$

$2.5 - V_1 > 0.9$

$V_1 < 1.6$

$V_2 < 0.9$

$-V_2 > 0.9$

$V_2 < -0.9$

$20 \pm \sqrt{139}$

$20V$

$139$

$11$

$300$

$140$

$757$

$419$

$2.43$

$9.57$