

# Switching Circuit and Logic Design


## Final Exam (2008/6/20)

100 分鐘

Name:

Student ID:

 1. 20% Design a 3-bit counter with counting sequence of 1, 3, 7, 2.  
**Direct ALL illegal states to state 3.**  
**Note: Use the symbol in order of CBA (違者扣分)**  
(1) Draw the resulting circuit using T-type flip flops.  
(2) Draw the complete state diagram corresponding to your circuit.
2. 30% Design a 3-bit counter with counting sequence of 1, 3, 7, 2.  
**Note: Use the symbol in order of CBA (違者扣分).**  
(1) Draw the resulting circuit using JK-type flip flops.  
(2) Draw the complete state diagram corresponding to your circuit.
3. 15% Implement the logic function  $F = \sum m(0, 4, 5, 6, 7, 10, 13) + d(8, 15)$   
Using a 2: 1 Mux
4. 15% Determine the minimized realization of the following Boolean functions.  
 $F(A, B, C, D) = \sum m(0, 2, 8, 9, 13) + \sum d(1, 3)$
5. 10% Complete the waveforms of  $Q_{7474}$  and  $Q_{7476}$



6. 10% 舉兩個實例藉以說明 FSM (有限狀態機器)