



Department of Computer Science and Information Engineering

National Cheng Kung University

數位系統實驗

Thu 9:00 am – 12:00 am

陳培殷

國立成功大學 資訊工程系



Schedule(乙)

- 9/10 Lab - 01 (Logic Gate on Chip)
 - 9/17 Lab - 02 (Logic Gate on Chip)
 - 9/24 Lab - 03 (Logic Gate on Chip)
 - 10/01 Suspension(中秋)
 - 10/7 Mid Exam (Lab - 01 ~ Lab - 02)
 - 9 Lab + 1 Mid Exam (Hardware Description Language, HDL)
 - 12/31 Final Project preparation)
 - 01/07 Final Project Presentation
-



Department of Computer Science and Information Engineering

National Cheng Kung University

LAB - 01

陳培殷

國立成功大學 資訊工程系



Outline

- Video preview for 數位系統簡介+邏輯閘
 - Representations for a circuit
 - 邏輯閘(logic gate), 晶片(chip)
 - 麵包板(Breadboard) for function verification
 - Lab
-

Three representations for a circuit

1. Boolean Algebra


$$F_1 = x + y'z$$

2. Truth Table

真值表

n input variables $\rightarrow 2^n$ combinations

3. Circuit Diagram

 


Inputs					
x	y	z	y'	$y'z$	F_1
0	0	0	1	0	0
0	0	1	1	1	1
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	1	0	1
1	0	1	1	1	1
1	1	0	0	0	1
1	1	1	0	0	1

74LS08

AND gate

Connection Diagram

 

Function Table

$$Y = AB$$

Inputs		Output
A	B	Y
L	L	L
L	H	L
H	L	L
H	H	H

H = HIGH Logic Level

L = LOW Logic Level


Boolean Algebra

$$F = xy$$

74LS32

OR gate

Connection Diagram

 

Function Table

$$Y = A + B$$

Inputs		Output
A	B	Y
L	L	L
L	H	H
H	L	H
H	H	H

H = HIGH Logic Level
L = LOW Logic Level


Boolean Algebra

$$F = x + y$$

74LS04

NOT gate

Connection Diagram

 

Function Table

$$Y = \overline{A}$$

Input	Output
A	Y
L	H
H	L

H = HIGH Logic Level

L = LOW Logic Level

Boolean Algebra


$$F = x'$$

74LS00

NAND gate

Not - AND

Connection Diagram

 

Function Table

$$Y = \overline{AB}$$

Inputs		Output
A	B	Y
L	L	H
L	H	H
H	L	H
H	H	L

H = HIGH Logic Level

L = LOW Logic Level

Boolean Algebra

$$F = (xy)'$$

74LS00 (1/3)

NAND gate

Connection Diagram


Function Table

$$Y = \overline{AB}$$

Inputs		Output
A	B	Y
L	L	H
L	H	H
H	L	H
H	H	L

H = HIGH Logic Level

L = LOW Logic Level

 



V_{CC} (5V)







1 2 3

ground

74LS00 (2/3)

  

74LS00 (3/3)

    



1. Multiple chips (gates) are used to realize a specific circuit
2. A dedicated chip (ASIC, application specific integrated circuit)

Introduction of Solderless Breadboard

- Solderless Breadboard is a convenient kit for laying out circuits without any soldering work. It is very useful for circuit test and modification during practical training.
 - Components in lab can be reused with breadboard.
 - Normally, component's pins are inserted into holes on breadboard. Every five holes are connected together by a brass stripe under plastic cover. One of holes is connected to component's pin and the other holes are for circuit connection with jumpers.
-


Various Breadboards

- Different types of Breadboards

  

The Solderless Breadboard in CSIE NCKU



■ Top view of the breadboard

 

Top View of the Solderless Breadboard

 : connected

 : disconnected

 
 


Example: Connection with 74LS00 Chip(1/7)

■ Board

power supply

Chip(NAND)

  

output


TTL mode

Wire connection
& IC placement


input

Example: Connection with 74LS00 Chip(2/7)

■ Board : wire connection

 

Chip(NAND)

 


Example: Connection with 74LS00 Chip(3/7)


■ Power supply



VCC


 


GND

 


Example: Connection with 74LS00 Chip(4/7)

■ Signal input

  

Example: Connection with 74LS00 Chip(5/7)

■ Signal output

 


Example: Connection with 74LS00 Chip(6/7)

- Input 11
- Output 0

74LS00 truth table

Input		Output
A	B	Y
0	0	1
1	0	1
0	1	1
1	1	0

 


Example: Connection with 74LS00 Chip(7/7)

- Input 00
- Output 1

74LS00 truth table

Input		Output
A	B	Y
0	0	1
1	0	1
0	1	1
1	1	0

 

Equipment

Names	Amount
Solerless Breadboard	×1
74LS00	×1
74LS04	×1
74LS08	×1
74LS32	×1

Lab notice

■ Input




■ Output



Lab I


Please (a) draw the truth table of the following circuit and (b) implement the circuit on the breadboard.

(1)

 

$$F = (x'y')'$$

(2)

 

$$X = ((A + B)C')'$$

Lab II(additional)

- Please draw their Truth Tables and implement the circuits with breadboard.
 - $F_1(A, B) = (A + B)'(A' + B')$
 - $F_2(A, B) = A' + AB$