

Name: Student ID:

1. 15% Design a 5:32 decoder, using some 3:8 decoders and a 2:4 decoder
2. 20% Design a 3-bit counter with sequence of 1, 5, 7, 2. Direct all illegal states to state 7.
Draw the resulting circuit using JK flip flops.
Note: Use the symbol in order of CBA (違者不計分)
3. 30% Design a 3-bit counter with sequence of 1, 5, 7, 2, 3, 4, 6, 8
Draw the resulting circuit using D flip flops.
Note: Use the symbol in order of CBA (違者不計分).
4. 15% Implement the logic function $F = \sum m(0, 4, 5, 6, 7, 8, 10, 13, 15)$, using a 4: 1 Multiplexer.
5. 20% Complete the waveforms of Q_{7474} and Q_{7476}

