

電子電工學

Lecture 4



Midterm Exam Information

Date: Oct 14, 2020

Time: 3:10 ~ 6:00 pm (in class)

Location: 化工系館柏林講堂/93156

Coverage: Textbook Chapters 1-4

LAB 1. Circuit Analysis

Use the online simulator to build the circuit shown in the right figure. Change values of V_s , R_1 , R_2 , R_3 , and R_4 according to your student ID (details as follows.)

1. Export the simulated circuit as a text file.
2. Replace R_L with various resistor values: 1, 2, 3, ..., 10 K Ω . Observe the voltages V_{AB} and draw the curve

V_{AB} vs R_L

ID .txt

ID .JPG
GIF

Submit the above text file and the plot on Moodle.

Suppose your student ID is

$E(nn) 0 (abcde)$

Set the Voltage Source

$$V_s = 5.e \text{ V}$$


Set the resistors

$$R_1 = 1.a \text{ K}\Omega$$

$$R_2 = 2.b \text{ K}\Omega$$

$$R_3 = 4.c \text{ K}\Omega$$

$$R_4 = 3.d \text{ K}\Omega$$

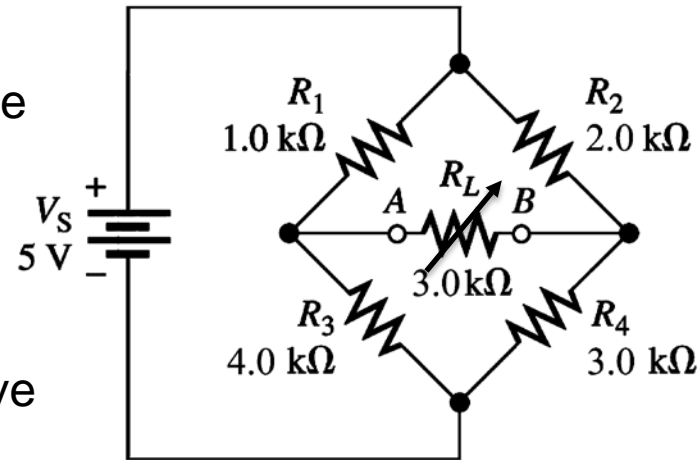

Example: ID E34048156


$$R_1 = 1.4 \text{ K}\Omega$$

$$R_2 = 2.8 \text{ K}\Omega$$

$$R_3 = 4.1 \text{ K}\Omega$$

$$R_4 = 3.5 \text{ K}\Omega$$

$$V_s = 5.6 \text{ V}$$

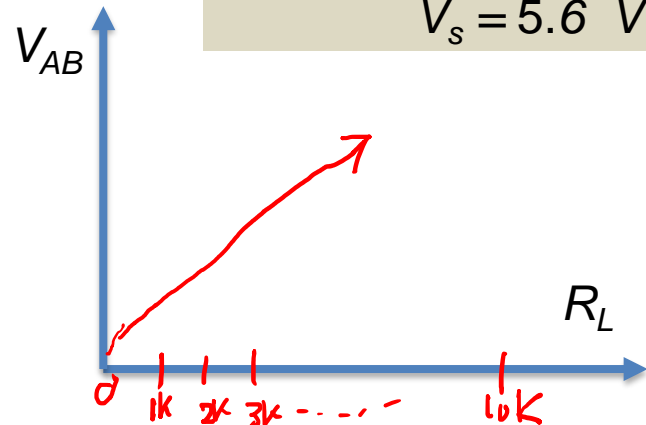


Circuit simulation

- <http://lushprojects.com/circuitjs/circuitjs.html>
- <http://www.falstad.com/circuit/circuitjs.html>

Matrix computation

- <https://octave-online.net/>


Recap: Symbol US vs EU

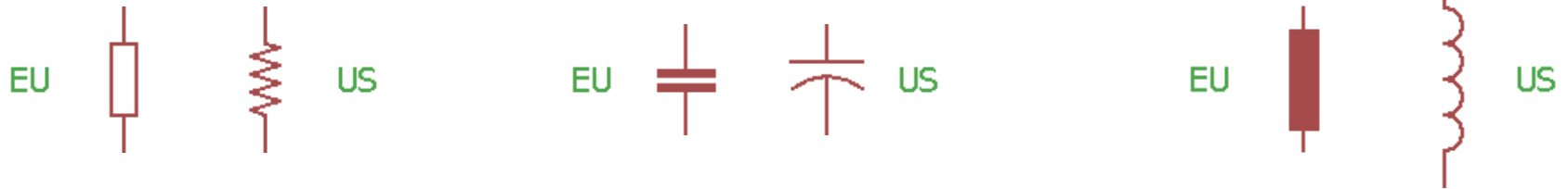

Recap: Voltage direction

$$V_R = i_R \times R$$

$$-2V \quad -1A \quad 2\Omega$$

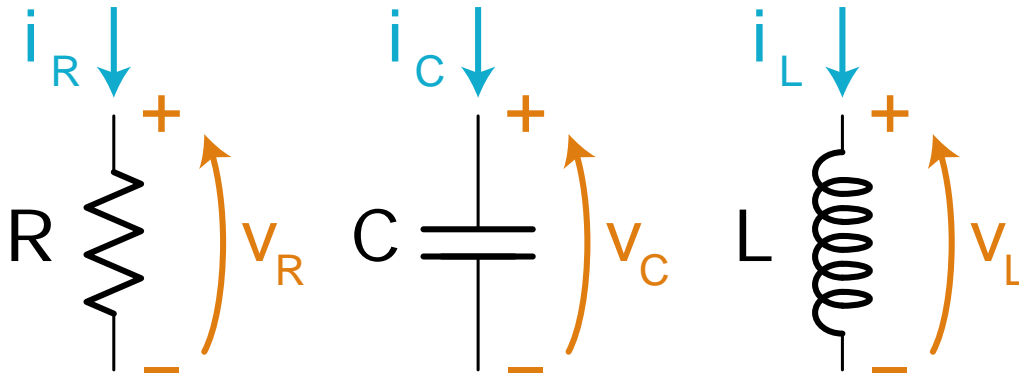

Recap: Circuit analysis

NODAL ANALYSIS

Ohm's law

KCL

KVL

Simplify



1. Labeling Nodes

2. Identifying Ground (earth)

3. Applying KCL \rightarrow eqn's

4. Solving system of equations

$\rightarrow V_A \quad V_B \quad V_C$

System 10 eqn's
 \Rightarrow 10 variables

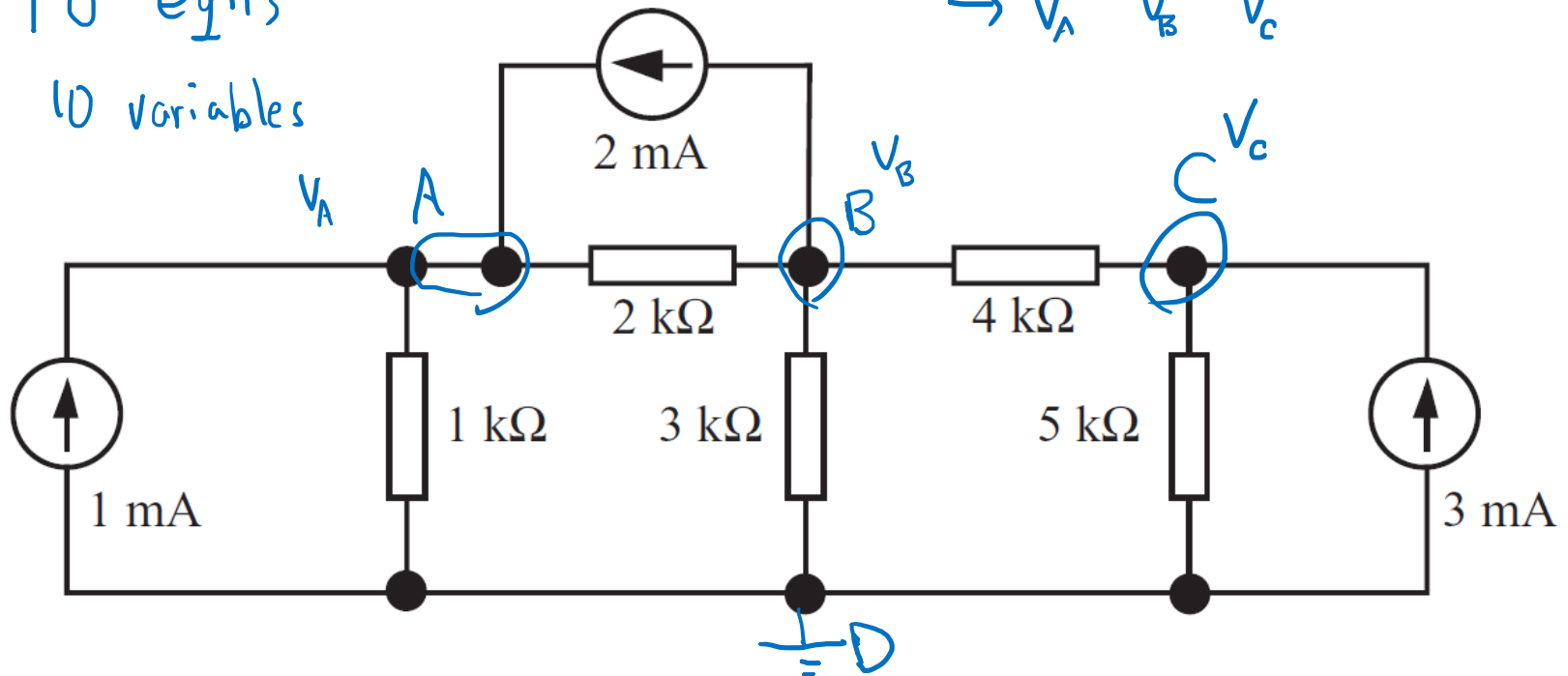


Figure 4.1 The circuit to be analysed

Recap: Nodal analysis with voltage sources

KCL @ A, B \Rightarrow 2 eqns \Rightarrow Solve V_A V_B

$$\begin{cases} V_A = -\frac{320}{21} \text{ V} \\ V_B = -\frac{164}{7} \text{ V} \end{cases}$$

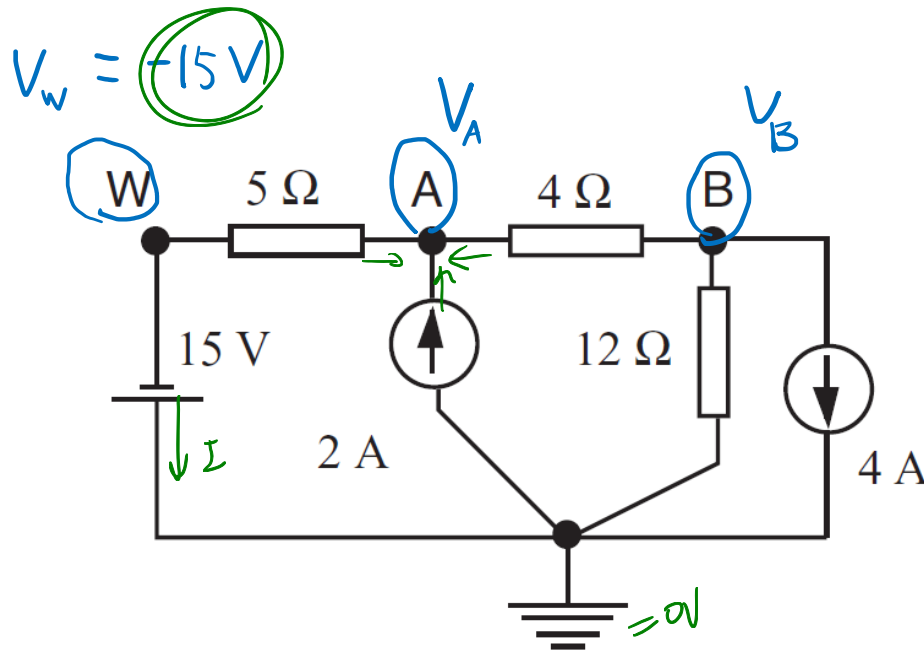


Figure 4.7 A voltage reference node has been chosen and other circuit nodes labelled

Example 4.1

Grounding A

$$\text{KCL @ X: } \frac{0 - V_X}{4} + \frac{V_Y - V_X}{12} + (-4) = 0$$

KCL @ Y:

$$\frac{0 - (V_Y - 15)}{5} + (-2) + \frac{V_X - V_Y}{12} + 4 = 0$$

Solve \Rightarrow

$$\begin{bmatrix} V_X \\ V_Y \end{bmatrix} = \begin{bmatrix} 5 & 172/21 \\ 320 & 121 \end{bmatrix}$$

$$V_X - V_Y = -\frac{164}{7} \text{ V}$$


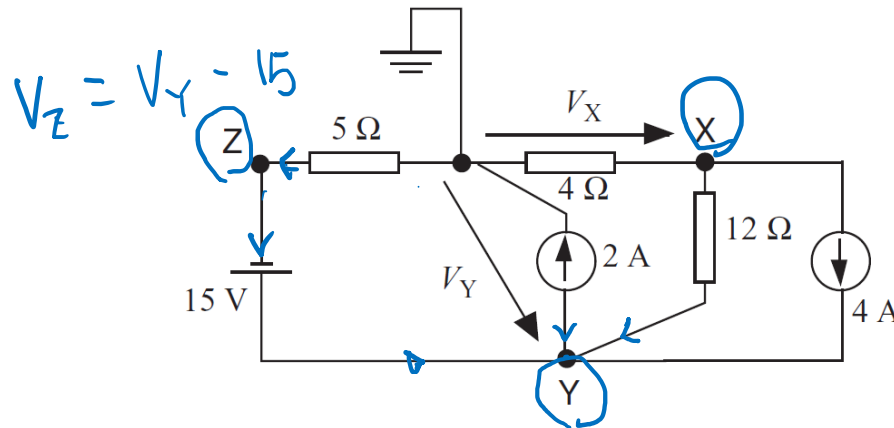


Figure 4.9 Preparation for the analysis of the circuit of Figure 4.7, using a different choice of reference node

Superposition principle

1. Decompose multiple sources
2. Apply only a single src each time
 - * Easier to find an equiv. ckt.
 - * Simpler analysis
 - * Set other src's to \circ
3. Sum up \rightarrow Final case.

Multiple
Sources

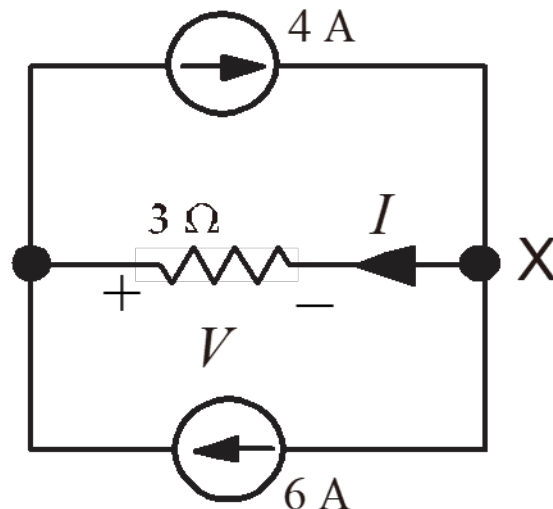


Superposition example

* Apply $S_1 : 4A$ $S_2 : \rightarrow 0$




* Apply $S_2 : 6A$ $S_1 \rightarrow 0$

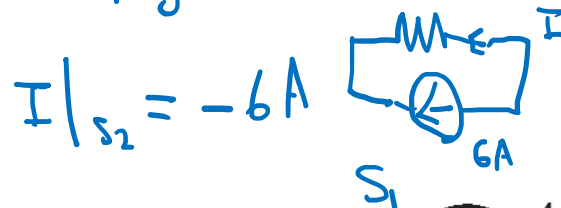

*


$$I|_{S_1, S_2} = 4 + (-6)$$

$$= -2A$$

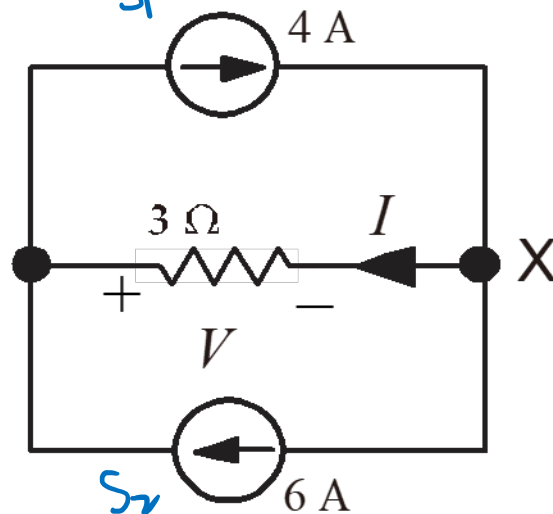

Superposition example

$$\begin{aligned} V &= V|_{s_1} + V|_{s_2} \\ &= -12 + 18 \\ &= 6 \text{ (V)} \end{aligned}$$

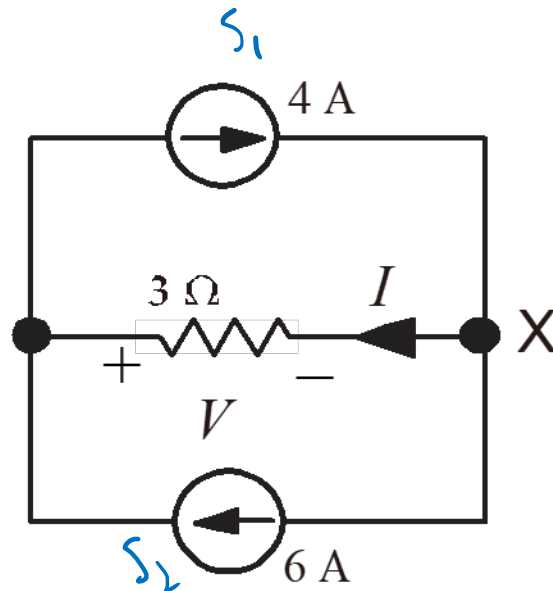

Single source circuit

KCL @ A


$$I_s + \frac{0 - V_A}{R_1} + \frac{0 - V_A}{R_2} + \dots + \frac{0 - V_A}{R_n} = 0$$

$$\left[\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n} \right] [V_A] = [I_s]$$

$$G \cdot \vec{v} = \vec{s}$$

$$\vec{v} = \boxed{G^{-1}} \cdot \vec{s}$$

↳ Solver !

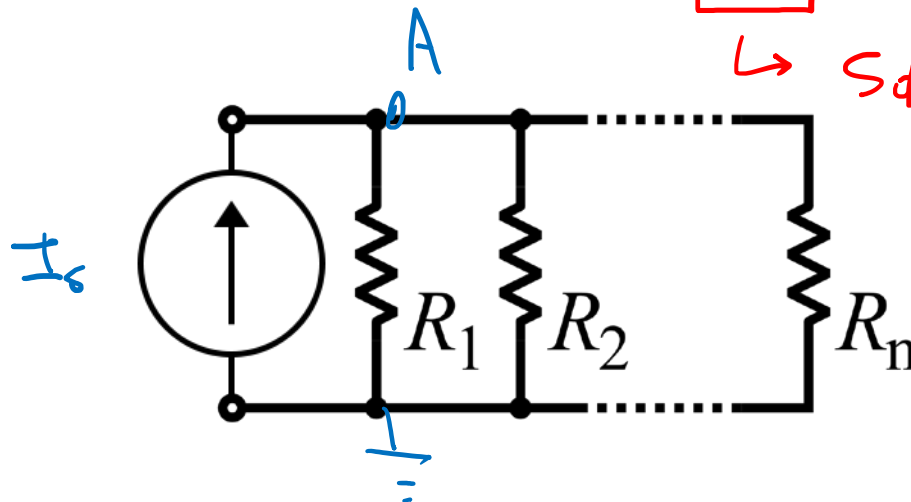

Superposition

$$\begin{bmatrix} -3/2 & 1/2 & 0 \\ 1/2 & -13/12 & 1/4 \\ 0 & 1/4 & -9/20 \end{bmatrix} \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \begin{bmatrix} -I_1 - I_2 \\ I_2 \\ -I_3 \end{bmatrix} = \begin{bmatrix} -I_1 \\ 0 \\ 0 \end{bmatrix} + \begin{bmatrix} -I_2 \\ I_2 \\ 0 \end{bmatrix} + \begin{bmatrix} 0 \\ 0 \\ -I_3 \end{bmatrix}$$

$$\underline{G} \underline{V} = \underline{S} = \underline{S}_1 + \underline{S}_2 + \underline{S}_3$$

$$\underline{V} = \begin{bmatrix} V_A \\ V_B \\ V_C \end{bmatrix} = \underline{G}^{-1} \cdot \underline{S}$$

Solver

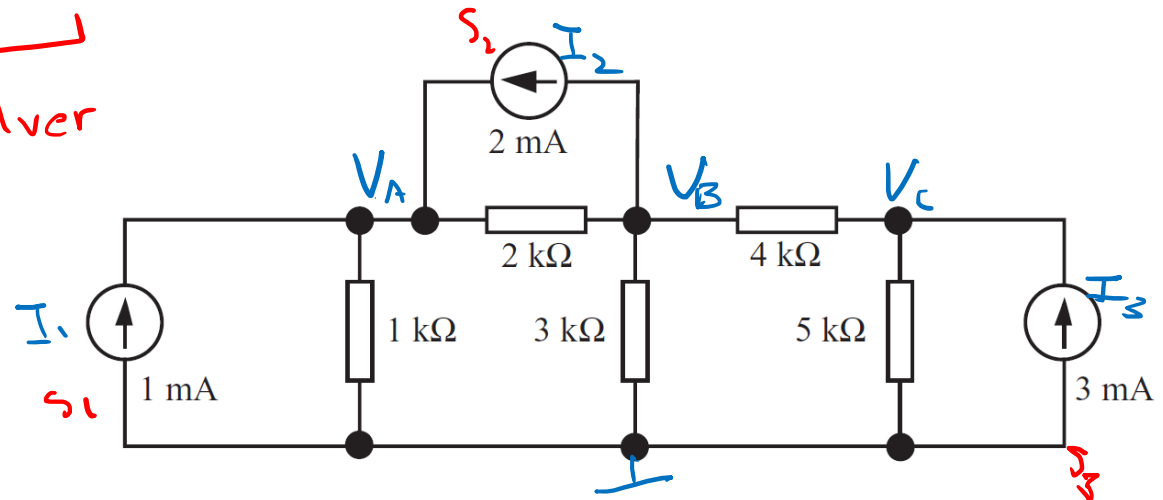


Figure 4.1 The circuit to be analysed

Superposition

Nodal eq

$$G \cdot \vec{v} = I_1 \cdot \begin{bmatrix} -1 \\ 0 \\ 0 \end{bmatrix} + I_2 \cdot \begin{bmatrix} -1 \\ 1 \\ 0 \end{bmatrix} + I_3 \cdot \begin{bmatrix} 0 \\ 0 \\ -1 \end{bmatrix}$$

$$\vec{v} = G^{-1} \vec{s}_1 + G^{-1} \vec{s}_2 + G^{-1} \vec{s}_3$$

$$\vec{v} = \vec{v}_1 + \vec{v}_2 + \vec{v}_3$$

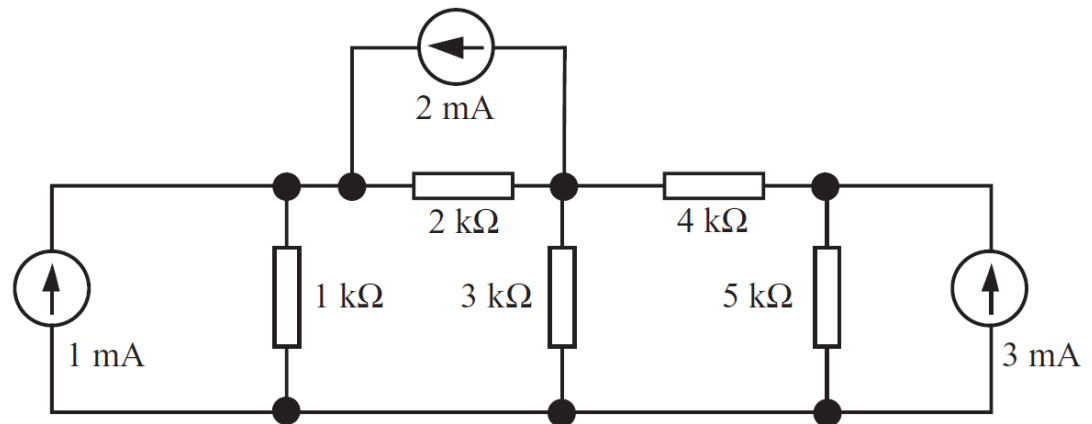


Figure 4.1 The circuit to be analysed

Superposition

$$\vec{V}_1 = \begin{bmatrix} V_{A,1} \\ V_{B,1} \\ V_{C,1} \end{bmatrix} = G^{-1} \vec{s}_1 \rightarrow \text{Apply Src 1 only, } I_2=0, I_3=0$$

$$\vec{V}_2 = \begin{bmatrix} V_{A,2} \\ V_{B,2} \\ V_{C,2} \end{bmatrix} = G^{-1} \vec{s}_2 \rightarrow \text{Src 2 only, } I_1=0, I_3=0$$

$$\vec{V}_3 = \begin{bmatrix} \\ \\ \end{bmatrix} = G^{-1} \vec{s}_3 \rightarrow \text{Src 3 only, } I_1=0, I_2=0$$

$$\vec{V}_1 + \vec{V}_2 + \vec{V}_3 = G^{-1} (\vec{s}_1 + \vec{s}_2 + \vec{s}_3)$$

$$\vec{V} = G^{-1} \vec{s}$$

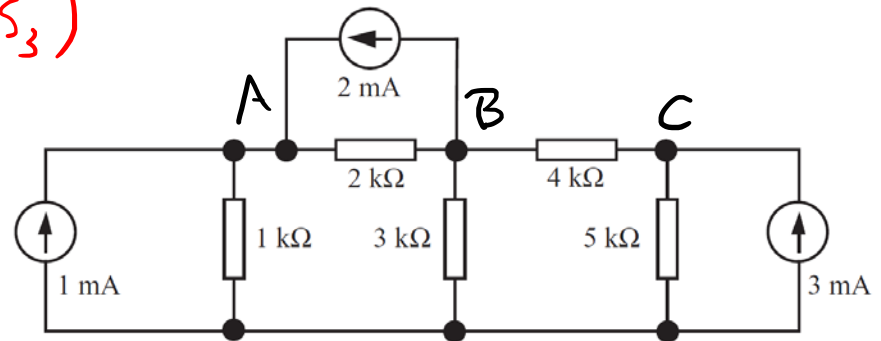


Figure 4.1 The circuit to be analysed

Superposition

Apply S_1 , $S_2 \rightarrow 0 \text{ mA}$ $S_3 \rightarrow 0 \text{ mA}$

$$\Rightarrow V_A | S_1$$

Apply S_2 , $S_1 \rightarrow 0 \text{ mA}$ $S_3 \rightarrow 0 \text{ mA}$

$$\Rightarrow V_A | S_2$$

Apply S_3 , $S_1 \rightarrow 0 \text{ mA}$ $S_2 \rightarrow 0 \text{ mA}$

$$\Rightarrow V_A | S_3$$

$$V_A = V_A | S_1 + V_A | S_2 + V_A | S_3$$


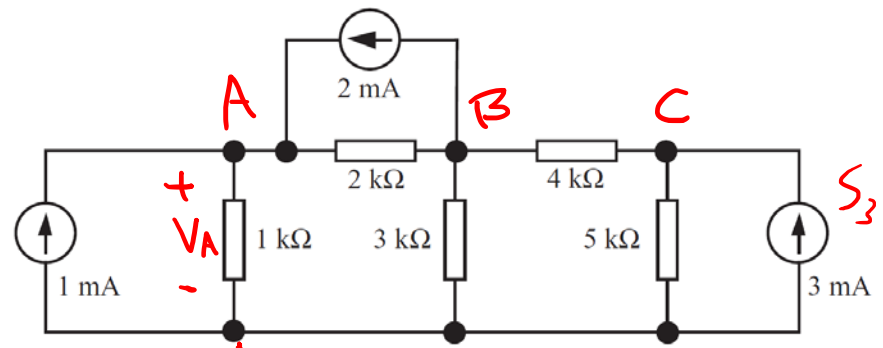


Figure 4.1 The circuit to be analysed

Superposition


$$V_A|_{S_1} = G^{-1} \cdot \vec{S}_1$$

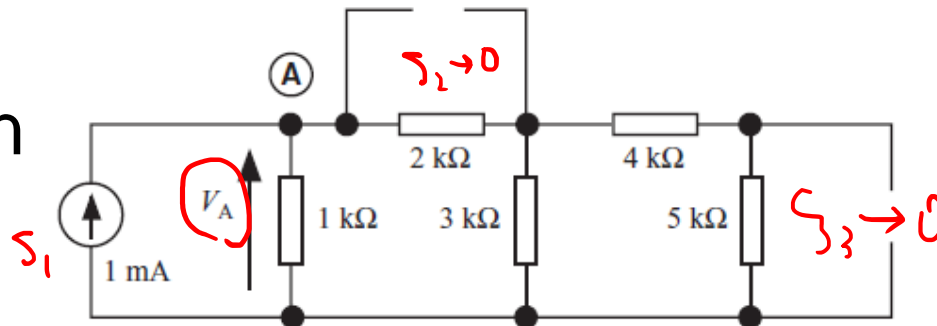

(a)

Analyse to find the value of V_A due to the 1 mA source


$$V_A|_{S_2} = G^{-1} \vec{S}_2$$

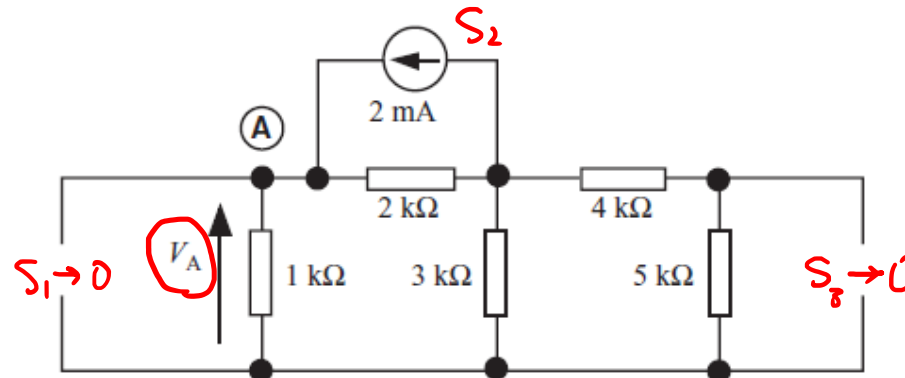

(b)

Analyse to find the value of V_A due to the 2 mA source

$$V_A|_{S_3} = G^{-1} \vec{S}_3$$

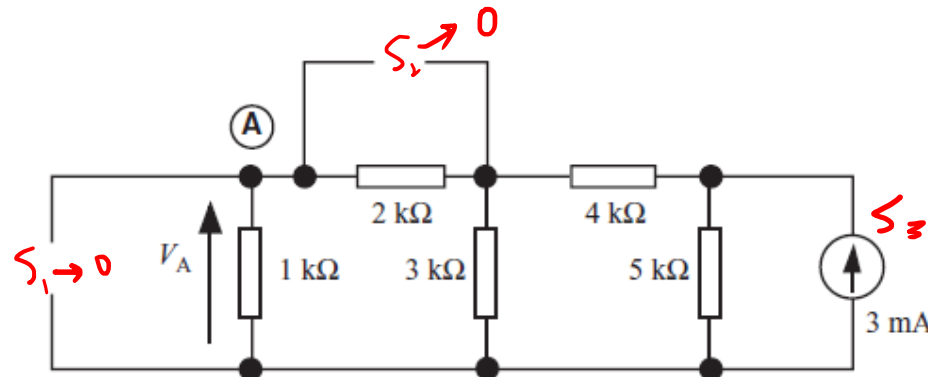

(c)

Analyse to find the value of V_A due to the 3 mA source

Figure 4.10 Illustration of the use of the superposition principle to find the voltage V_A at node A in the circuit of Figure 4.4. The three calculated voltages are added together to find the actual value of V_A .

Review: voltage divider

$$V_A = V \cdot \frac{R_2}{R_1 + R_2}$$

$$R = R_1 + R_2$$

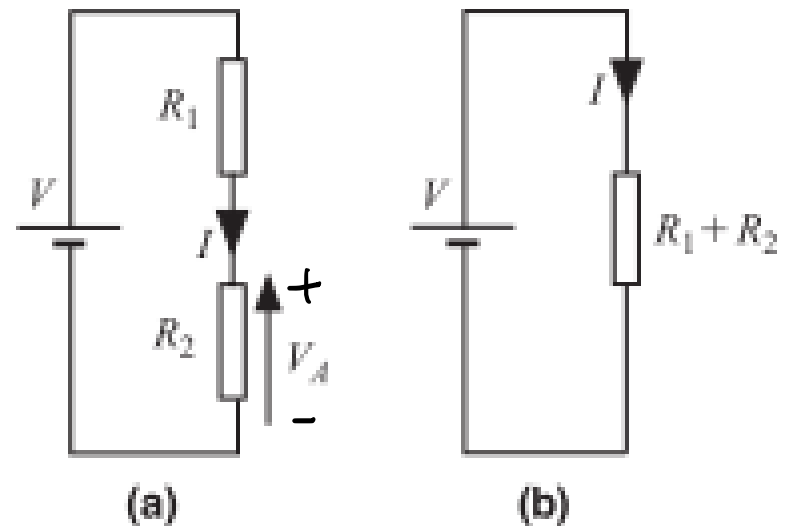


Figure 3.24 Pertinent to Example 3.3

Review: current divider

$$I_1 = I \cdot \frac{R_2}{R_1 + R_2}$$

$$I_2 = I \cdot \frac{R_1}{R_1 + R_2}$$

$$R = R_1 \parallel R_2$$

$$= \frac{1}{1/R_1 + 1/R_2}$$


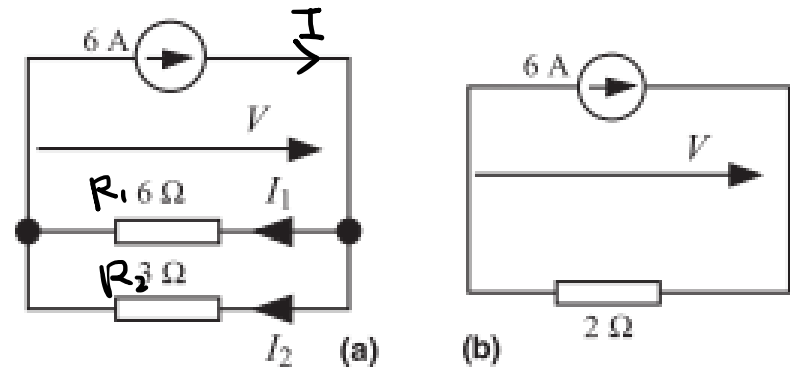


Figure 3.25 Pertinent to Example 3.4


Source (1)

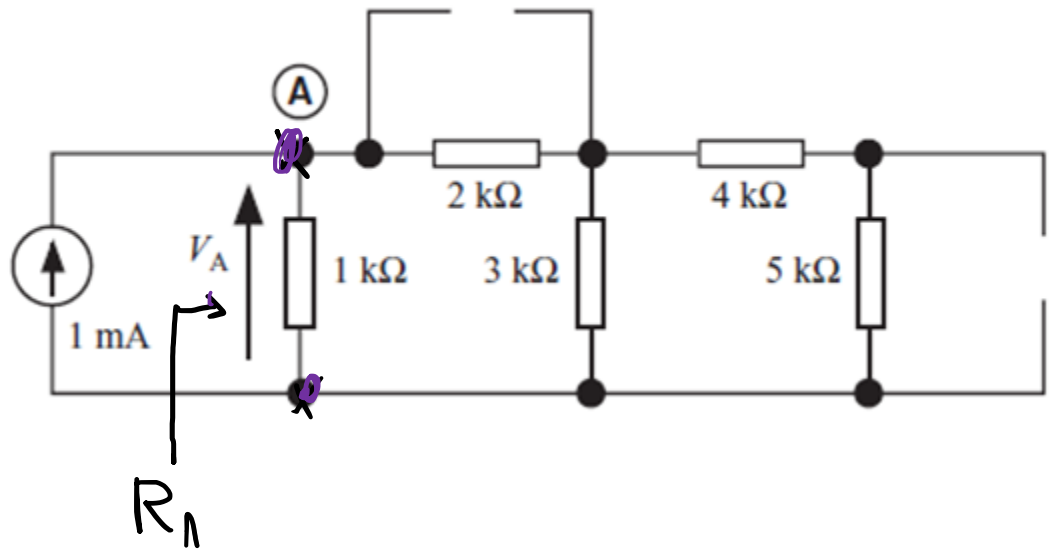

$$R_A = [(4\text{k} + 5\text{k}) \parallel 3\text{k}] + 2\text{k} \parallel 1\text{k}$$
$$= \frac{17}{21} \text{ (k}\Omega\text{)}$$

$$V_A|_{s_1} = I_1 \cdot R_A = \frac{17}{21} \text{ (V)}$$

Source (2)

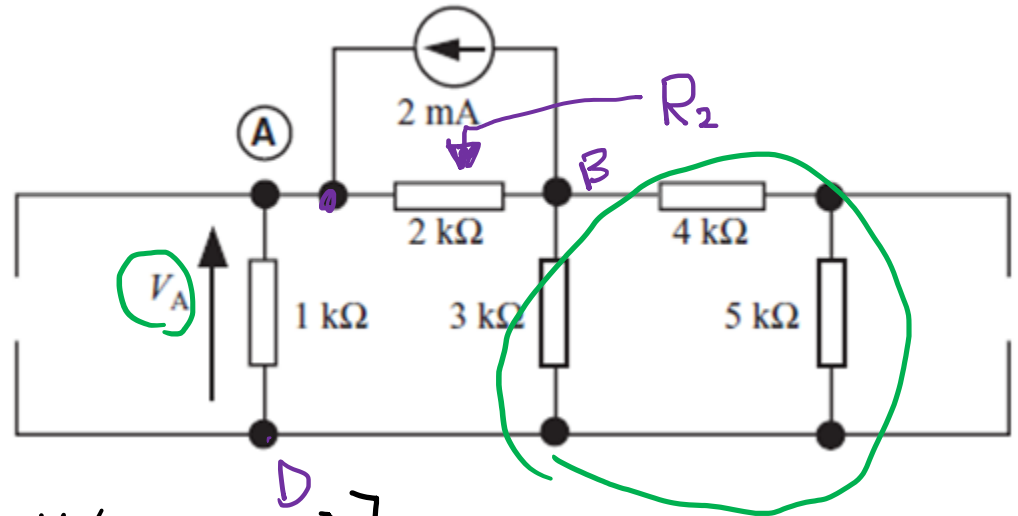



$$R_2 = 2^k // [1^k + (3^k // (4^k + 5^k))]^D$$

$$\Rightarrow V_{AB} = I_2 \times R_2 = 2^{mA} \times R_2$$


$$\Rightarrow V_{AD} = V_{AB} \times \frac{1^k}{1^k + (3^k // (4^k + 5^k))}$$

$$\downarrow$$

$$V_A \uparrow$$

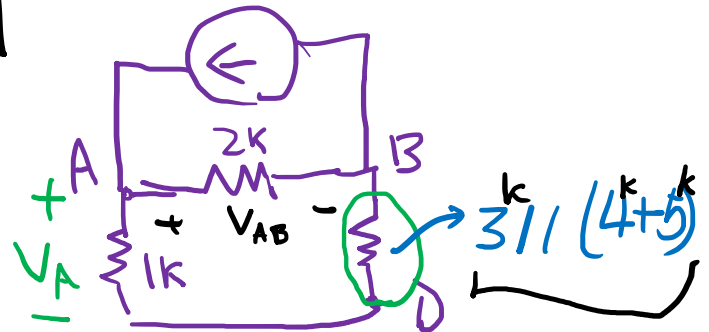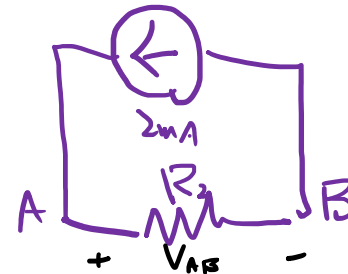

Source (3)

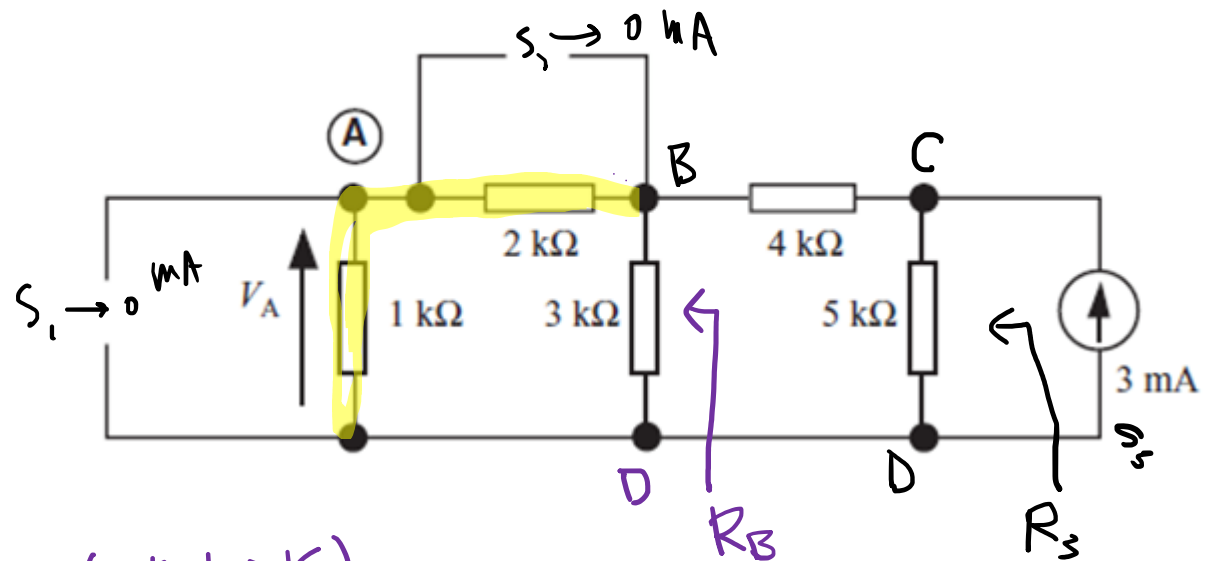

$$R_B = 3k \parallel (1k + 2k)$$

$$\underline{R_3} = 5k \parallel (4k + R_B)$$



$$V_{CD} = I_3 \times R_3 = 3mA \times R_3$$

$$V_{BD} = V_{CD} \times \frac{R_B}{R_B + 4k}$$

$$V_{AD} = V_{BD} \times \frac{1k}{1k + 2k}$$

$$\hookrightarrow V_A |_{S_3}$$
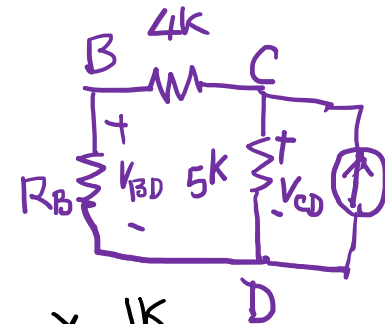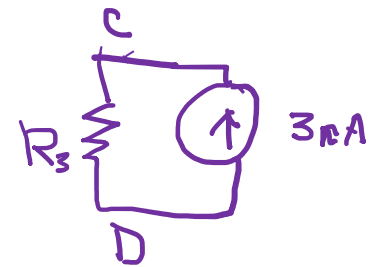
$$= I_3 \times R_3 \times \frac{R_B}{R_B + 4k} \times \frac{1k}{1k + 2k}$$



Superposition

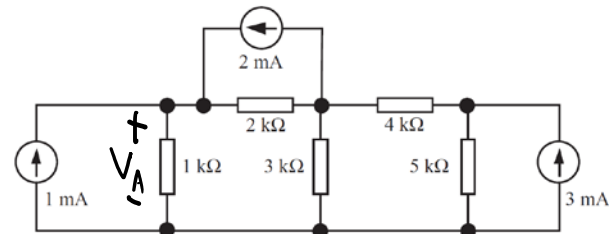


Figure 4.1 The circuit to be analysed


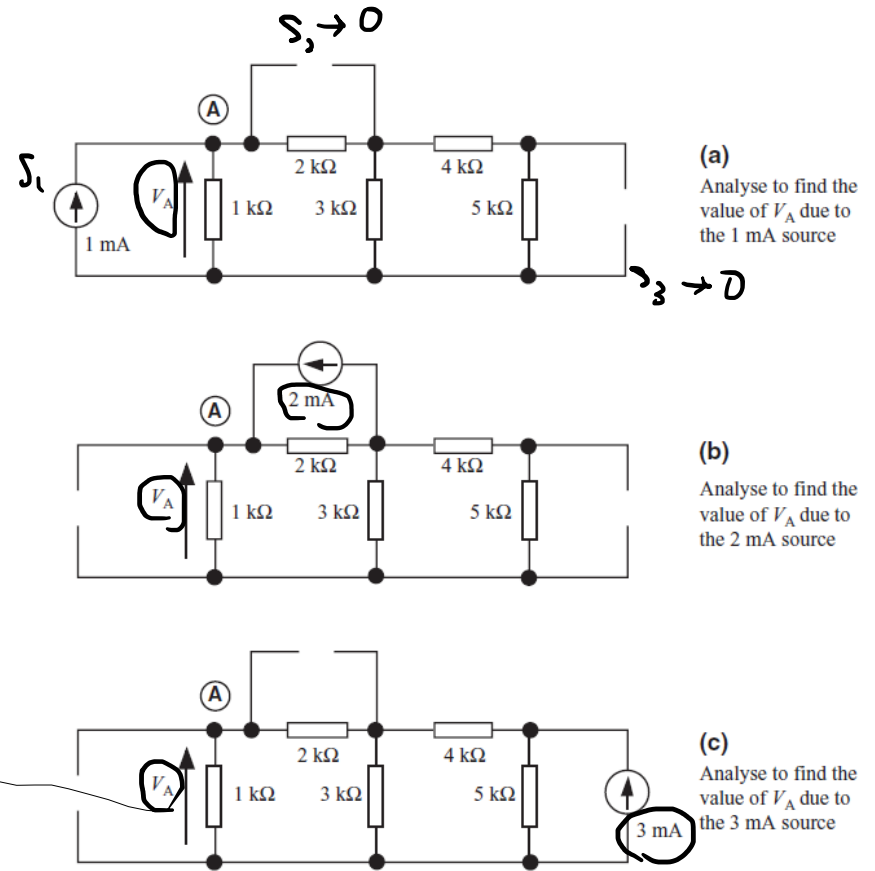
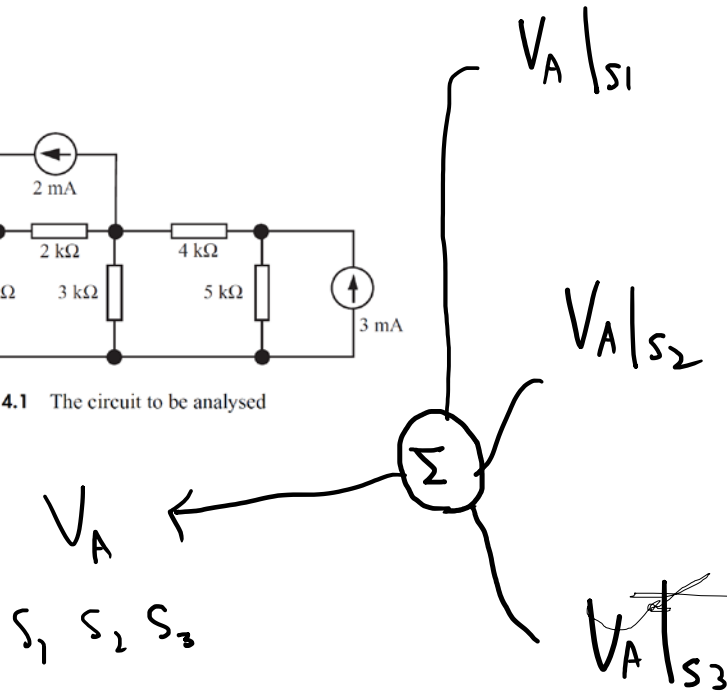


Figure 4.10 Illustration of the use of the superposition principle to find the voltage V_A at node A in the circuit of Figure 4.4. The three calculated voltages are added together to find the actual value of V_A .

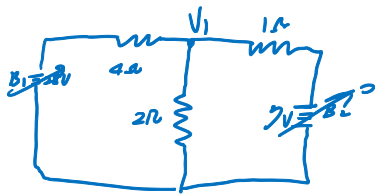

$$B_1 \quad \frac{2}{1+2} = \frac{2}{3}$$

$$\frac{2}{3} + 4 =$$

$20 \times$