





電子電工學

Lecture 14




Change Behaviour

Chapter 12

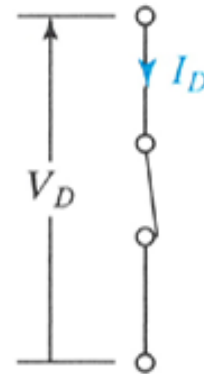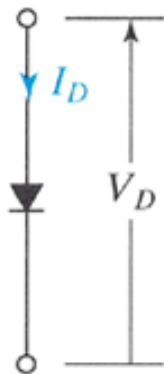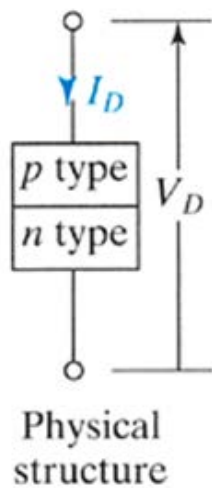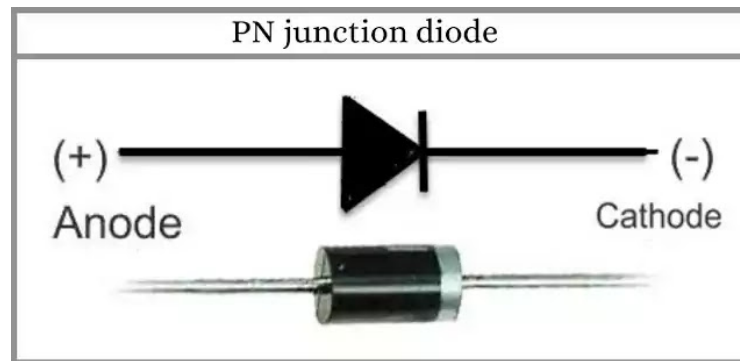

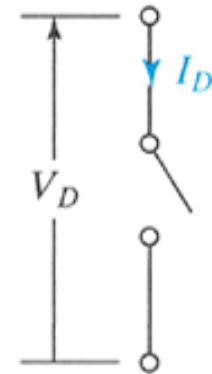Forward bias
 $I > 0$
 $V = 0$
 (closed switch)



Reverse bias
 $V < 0$
 $I = 0$
 (open switch)

(a) Ideal diode symbol

(b) Ideal diode model

FIGURE 10.17 Ideal diode symbol and its switch circuit model.

Idea diode


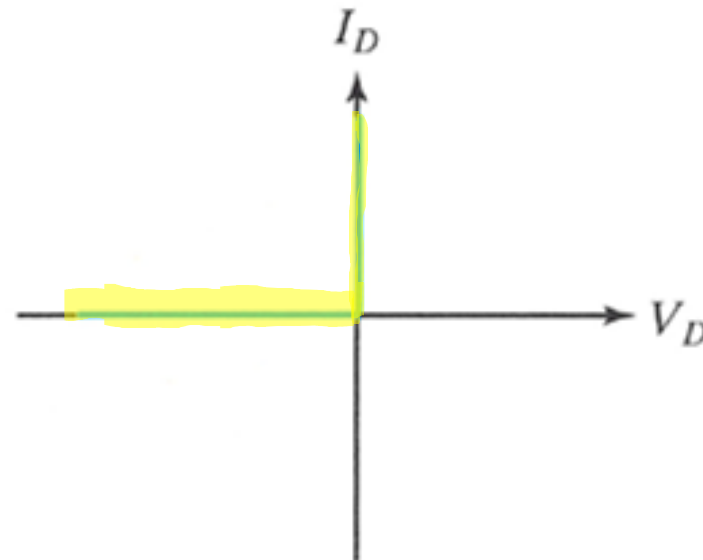
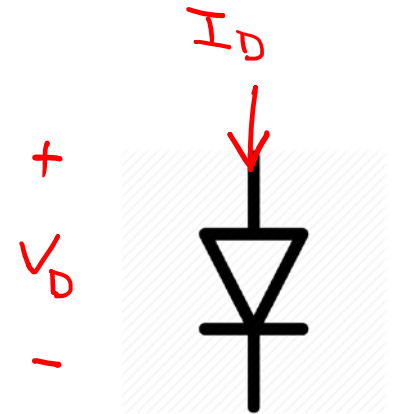


FIGURE 10.16 Plot of current through diode, I_D , versus voltage across diode, V_D , for an "ideal" diode.

Application: Rectifier

整流

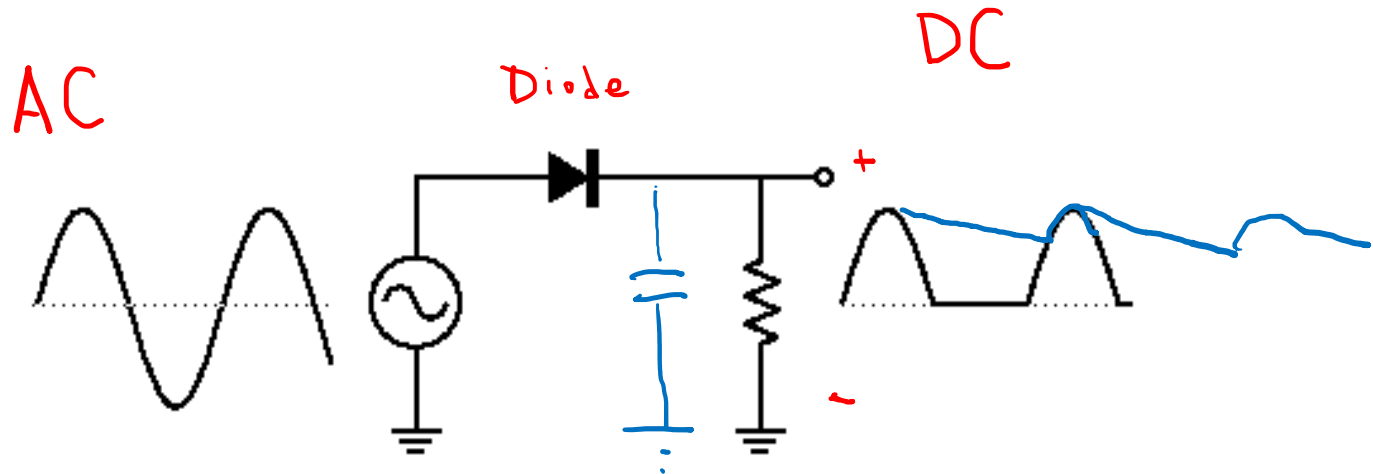

Diode characteristic

Real-world diode (Not ideal)
0V

Stablizer
Regulator

0.7 V voltage
drop

Breakdown

-5V

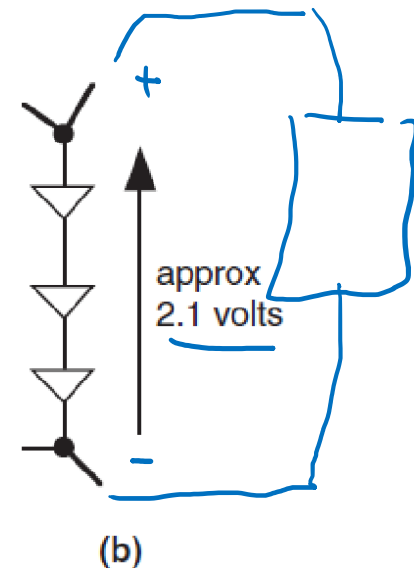
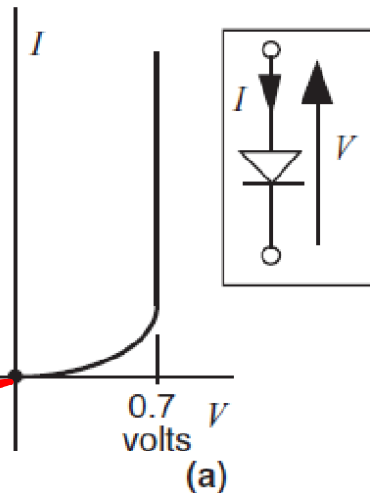


Figure 12.1 A diode characteristic, and the use of diodes to establish a fixed voltage within a circuit

Zener diode characteristic

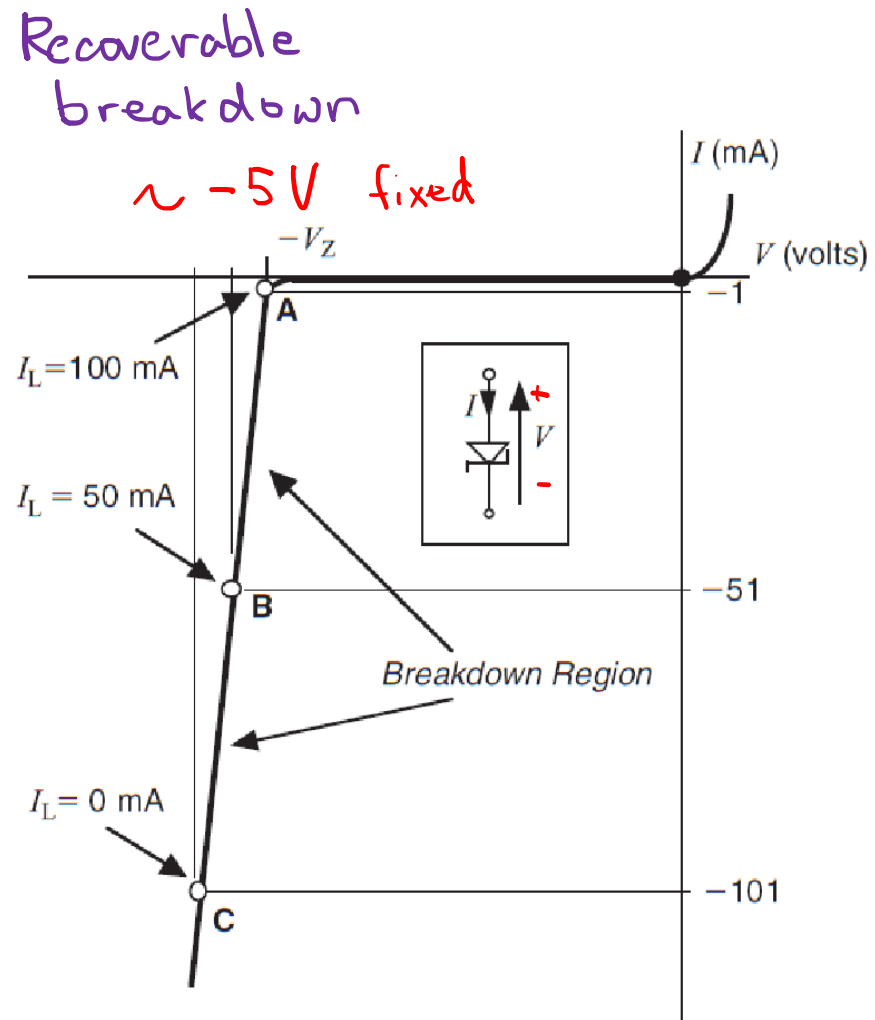


Figure 12.2 The voltage~current characteristic of a Zener diode. Operation in the breakdown region is nondestructive

Stabilizer

Purpose:

To provide stable voltage to load

\sim fixed V

R variable

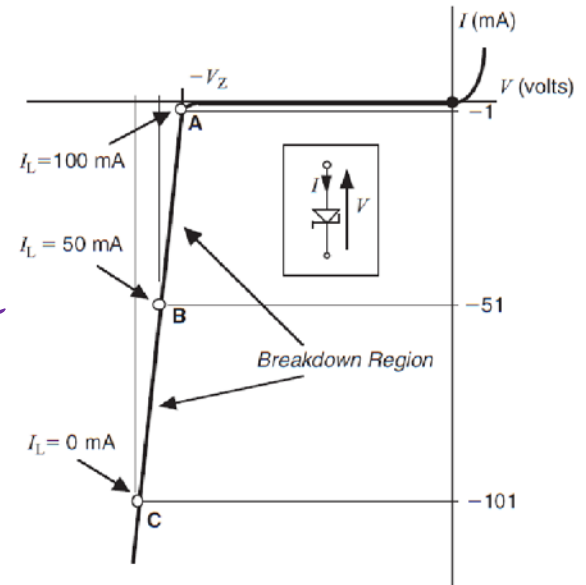


Figure 12.2 The voltage-current characteristic of a Zener diode. Operation in the breakdown region is nondestructive

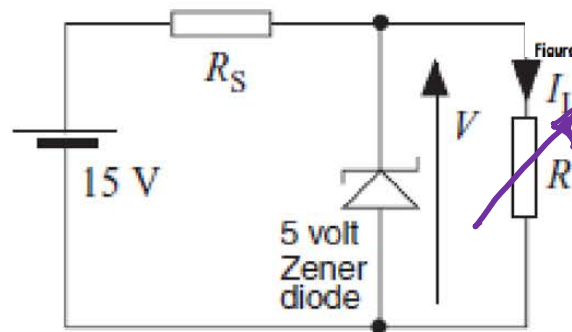


Figure 12.3 A circuit in which the Zener diode helps to maintain the voltage V at approximately 5 V

Stabilizer

Operating point A

Zener diode just turned-on
Least current $I_Z = 1 \text{ mA}$

$$\Rightarrow I = I_L + I_Z \cong 101 \text{ mA}$$

$$\text{Design } R_s = \frac{15 - 5 \text{ (V)}}{101 \text{ (mA)}} = 99 \Omega$$

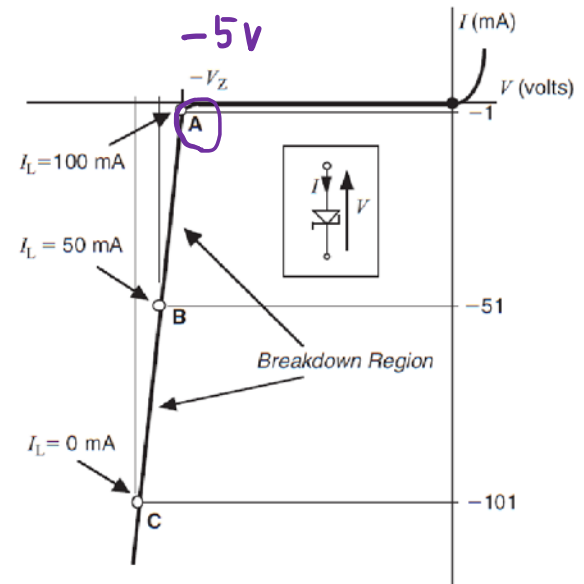
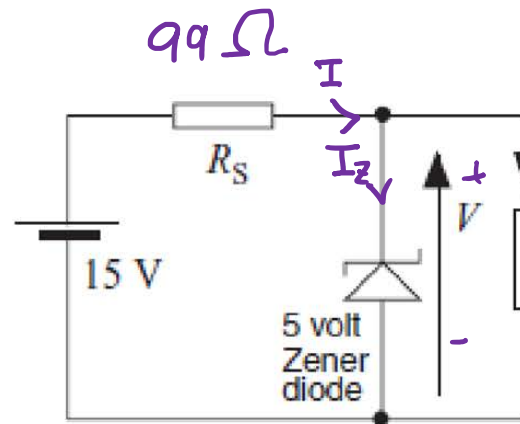


Figure 12.2 The voltage-current characteristic of a Zener diode. Operation in the breakdown region is nondestructive

$I_L = 100 \text{ mA}$

$$R = \frac{5 \text{ V}}{100 \text{ mA}} = 50 \Omega$$

Figure 12.3 A circuit in which the Zener diode helps to maintain the voltage V at approximately 5 V

Stabilizer

Operating point B $R_s = 99 \text{ } \Omega$ fixed

Load extract $50 \text{ mA} = I_L$

$$(R \approx \frac{5 \text{ V}}{50 \text{ mA}} = 100 \text{ } \Omega)$$

$$I = \frac{15 - 5}{99} = 101 \text{ mA}$$

$$\Rightarrow I_Z = I - I_L = 51 \text{ mA}$$

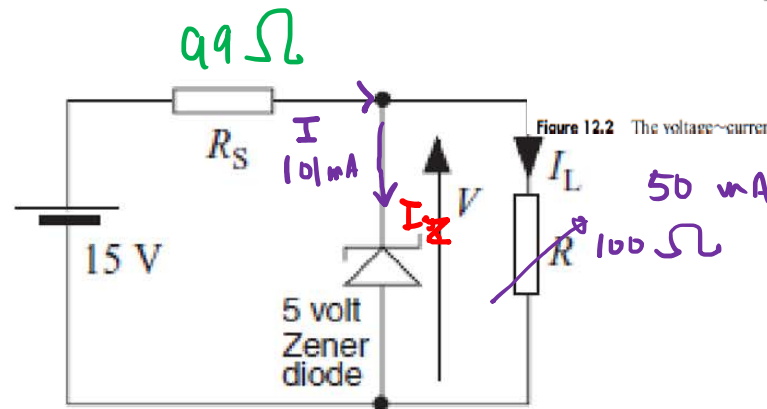
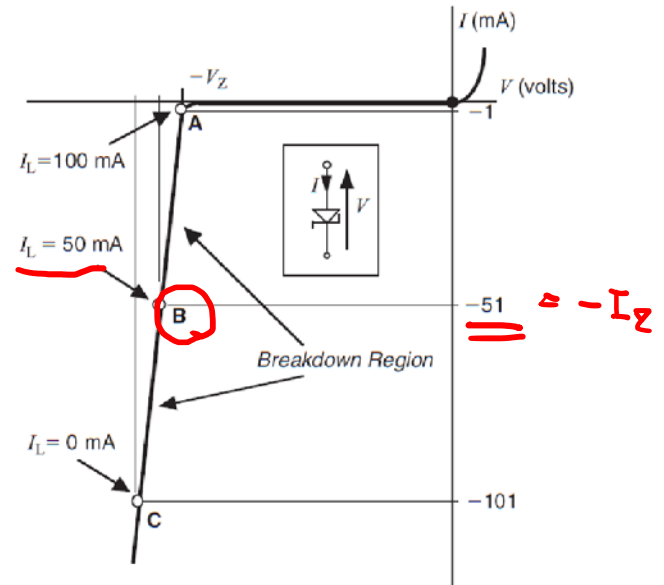


Figure 12.2 The voltage-current characteristic of a Zener diode. Operation in the breakdown region is nondestructive

Figure 12.3 A circuit in which the Zener diode helps to maintain the voltage V at approximately 5 V

Stabilizer

Operating point C

$R \rightarrow \infty$
 Load extracts 0 mA
 $V = 5 \text{ V}$
 $I = 101 \text{ mA}$
 $\Rightarrow I_Z = 101 \text{ mA}$

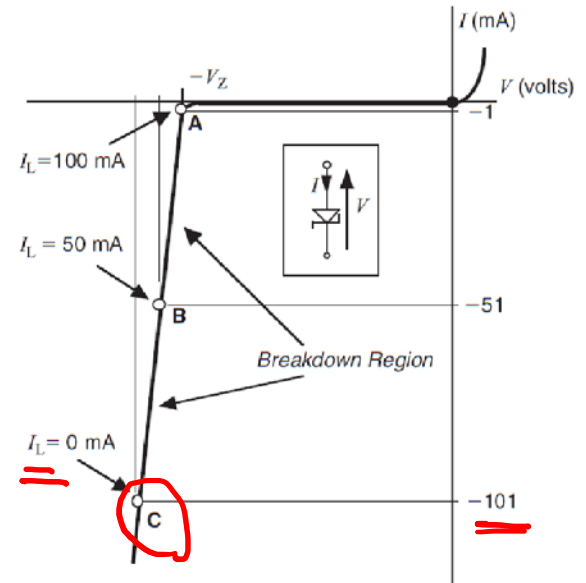
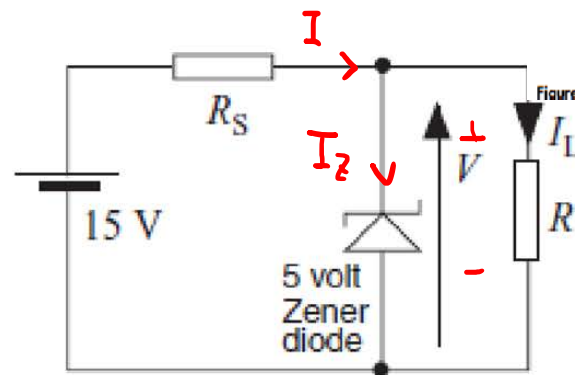


Figure 12.2 The voltage-current characteristic of a Zener diode. Operation in the breakdown region is nondestructive

Figure 12.3 A circuit in which the Zener diode helps to maintain the voltage V at approximately 5 V

Stabilizer summary

1. Maintain essentially a constant voltage

Ideal Zener diode $V = \text{const}$

2. Real-world Zener diode: a small change in $V \rightarrow V + \Delta V$

$$I_L \rightarrow I_L + \Delta I$$

$$V \rightarrow V + \Delta V$$

$$\Delta I \rightarrow \Delta V$$

Change Analysis

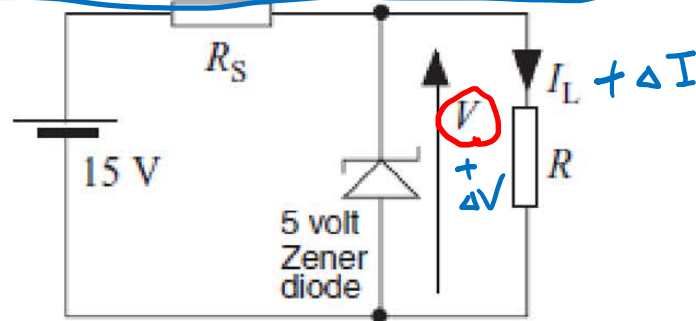


Figure 12.3 A circuit in which the Zener diode helps to maintain the voltage V at approximately 5 V

Connections

Node X

$$I_i \rightarrow I_i + \Delta I_i$$

by KCL at X

$$\begin{cases} I_1 + I_2 + I_3 = 0 \\ (I_1 + \Delta I_1) + (I_2 + \Delta I_2) + (I_3 + \Delta I_3) = 0 \end{cases}$$

$$\Rightarrow \Delta I_1 + \Delta I_2 + \Delta I_3 = 0$$


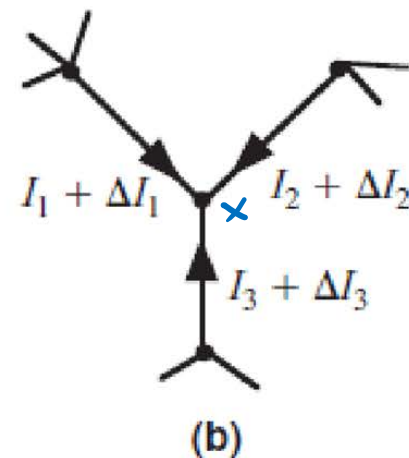
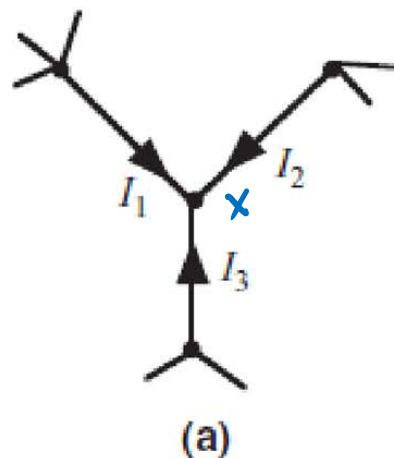


Figure 12.5 (a) The currents flowing into a node and; (b) new values of those currents following a change somewhere in the external circuit

Connections

$$\text{KVL} : V_1 + V_2 + V_3 = 0$$
$$(V_1 + \Delta V_1) + (V_2 + \Delta V_2) + (V_3 + \Delta V_3) = 0$$
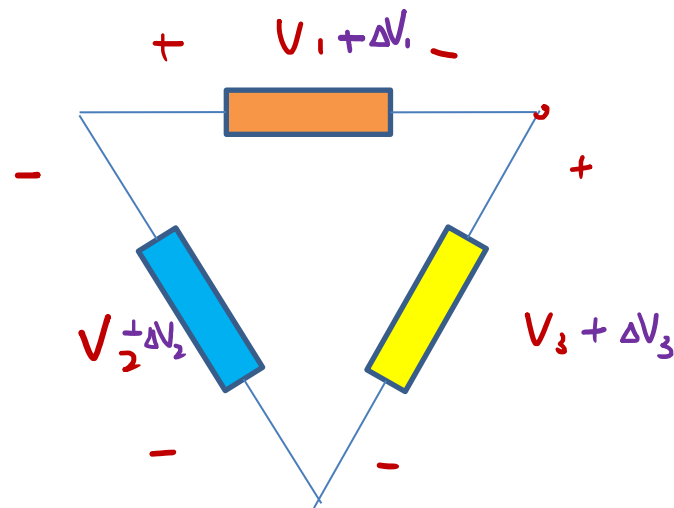
$$\Rightarrow \Delta V_1 + \Delta V_2 + \Delta V_3 = 0$$



Model of Zener diode

$$\begin{aligned} V &\rightarrow V + \Delta V \\ I &\rightarrow I + \Delta I = f(V + \Delta V) \\ \Delta V &\sim \Delta I ? \end{aligned}$$


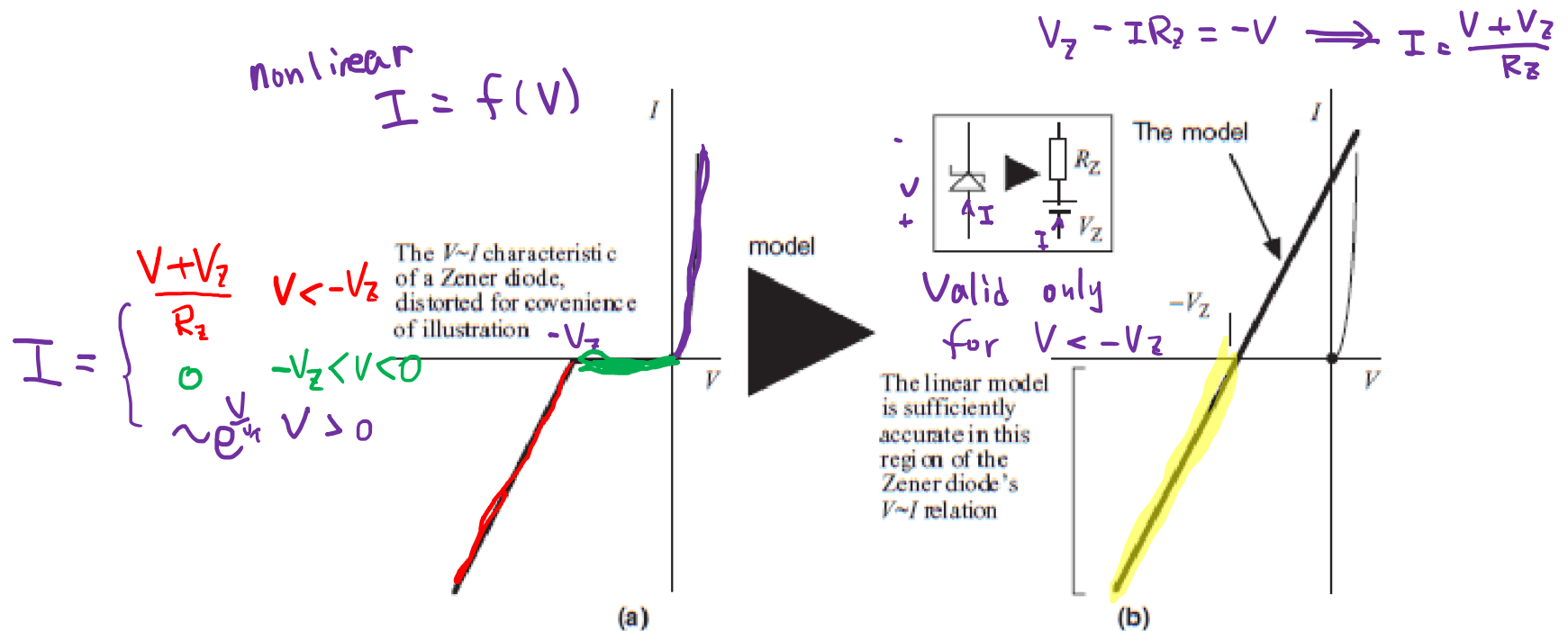


Figure 12.6 (a) The voltage~current characteristic of a Zener diode; (b), a linear model adequately representing the characteristic *in the region in which it is intended to operate*

Model of components

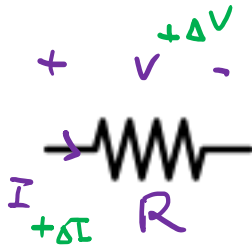

$$V = RI$$

$$V + \Delta V = R(I + \Delta I)$$

$$\Delta V = R \Delta I$$



Const V

$$\Delta V = 0$$

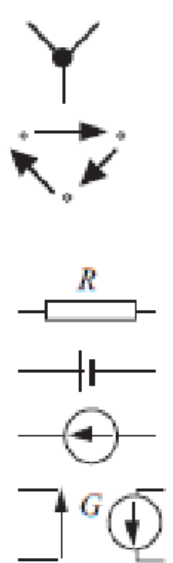
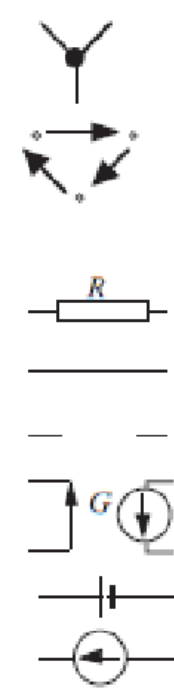


Const I

$$\Delta I = 0$$

Model of changes

Table 12.1 The component and connection relations for changes in current and voltage have the same form as do the same relations for DC currents and voltages

DC Currents and voltages		Changes in current and voltage	
<p><i>representation</i></p> 	<p><i>relation</i></p> $\sum_{\text{node}} I = 0$ $\sum_{\text{loop}} V = 0$ $V = R I$ $V = \text{constant}$ $I = \text{constant}$ $I = G V$	<p>Connections</p> <p><i>at node</i></p> <p><i>around loop</i></p> <p>Components</p> <p><i>resistor</i></p> <p><i>voltage source</i></p> <p><i>current source</i></p> <p><i>vocs</i></p> <p><i>voltage source change</i></p> <p><i>current source change</i></p>	<p><i>relation</i></p> $\sum_{\text{node}} \Delta I = 0$ $\sum_{\text{loop}} \Delta V = 0$ $\Delta V = R \Delta I$ $\Delta V = 0$ $\Delta I = 0$ $\Delta I = G \Delta V$ $\Delta V = \text{constant}$ $\Delta I = \text{constant}$ <p><i>representation</i></p> 

Example 12.1

Voltage source 15V change $\rightarrow (15+2)V$


Load

$V=5V$

$\rightarrow V+\Delta V$

$\Delta V = ?$

Δ -Equivalent ckt:
$$\Delta V = 2 \times \frac{(10 // 100)}{99 + (10 // 100)} = 169 \text{ mV}$$

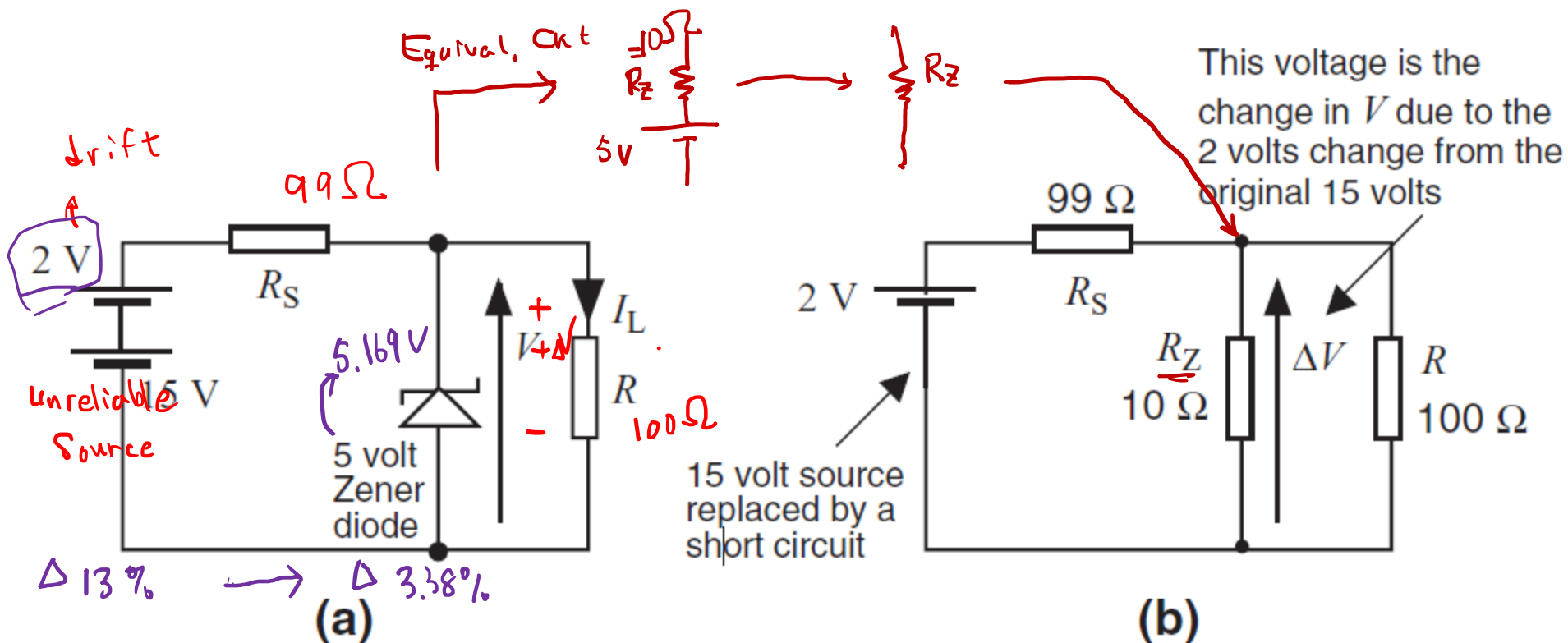

Example 12.2

Increase in load current 10 mA

$$\Delta I_L = 10 \text{ mA} \rightarrow \Delta V = ?$$

Δ -Equivalent Ckt

$$\Delta V = -10 \text{ mA} \times (R \parallel R_Z \parallel R_S)$$

$$= -83.3 \text{ mV}$$

1.67%

Original Load 50 mA
 \downarrow + 20% ΔI
 $+\Delta I_{\text{Load}} = 60 \text{ mA}$


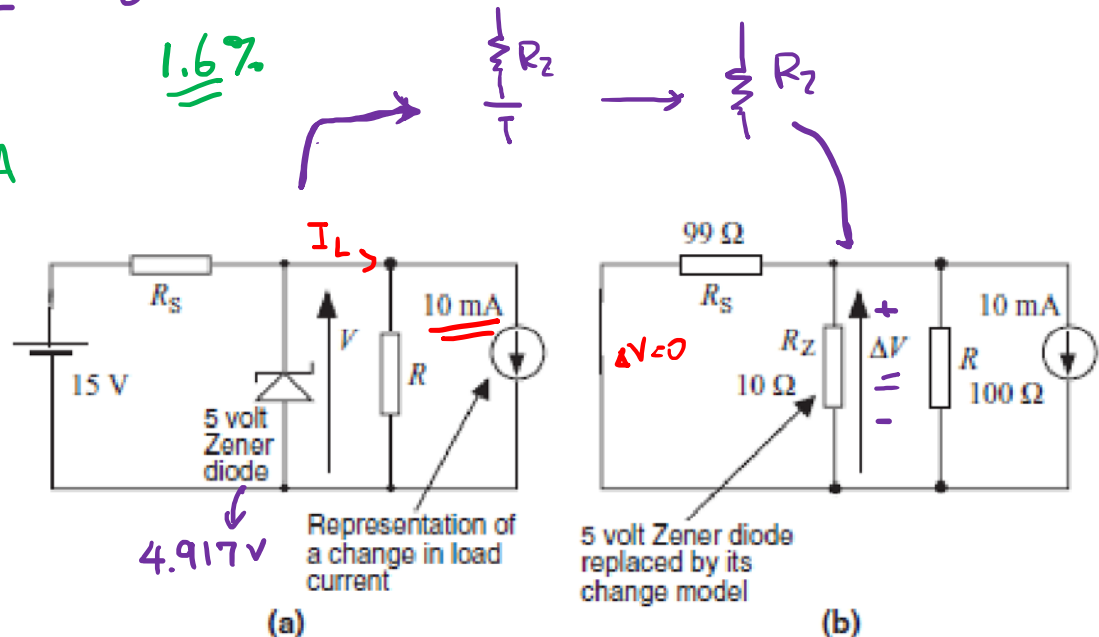
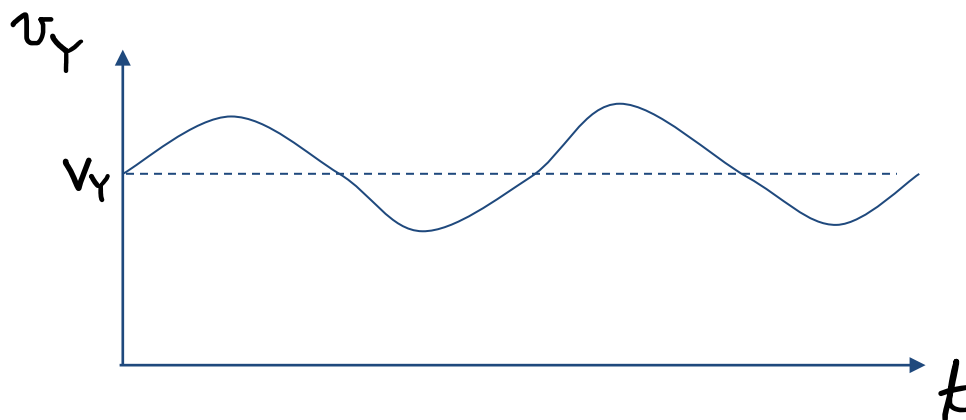


Figure 12.8 An actual circuit (a) and, (b), the change circuit relevant to the calculation of the effect of a 10 mA change in the load current

Chapter 13


Small-Signal Analysis

Notation!

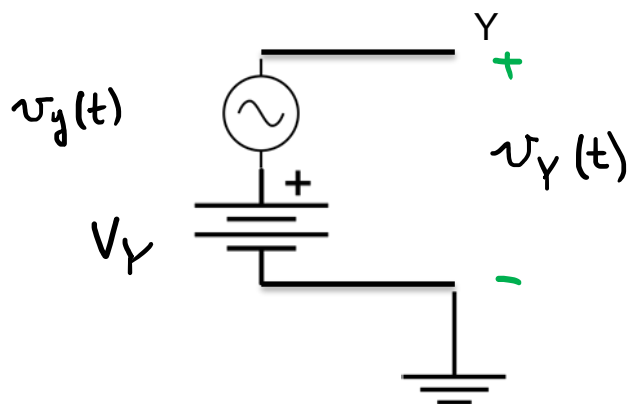


$$v_Y(t) = V_Y + v_y(t)$$

Large-signal DC Bias Small-signal

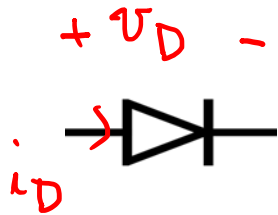

Ideal Diode

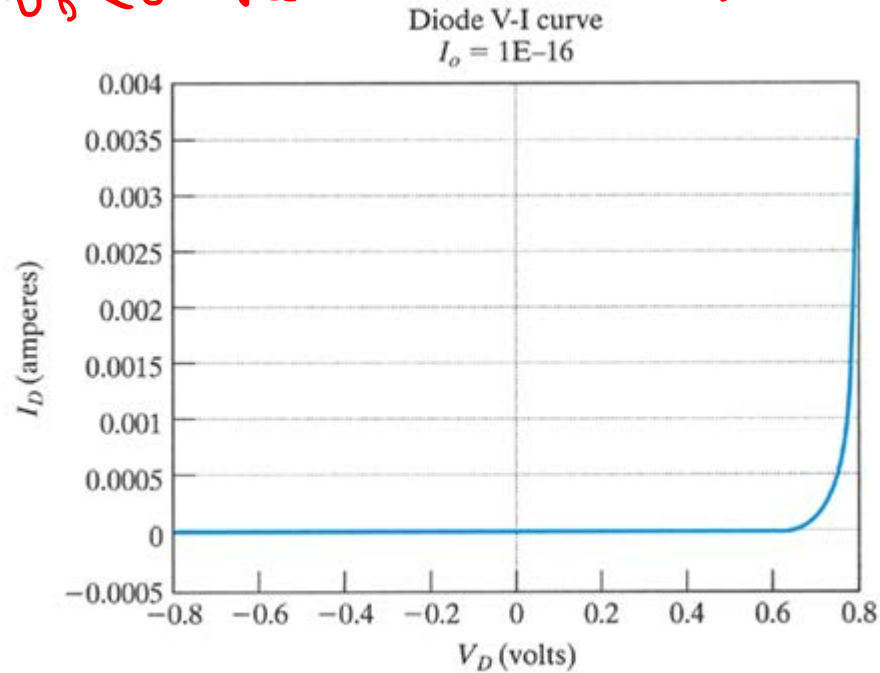If $V_D > 0$ Forward bias $i_D > 0$
 If $V_D < 0$ Reverse bias $i_D = 0$



Real-world Diode

Exponential Diode

FIGURE 10.21 Plot of diode equation for $I_o = 1 \times 10^{-16} \text{ A}$.

$$I_D = I_o \left(e^{\frac{qV_D}{kT}} - 1 \right)$$

$$i_D(t) = I_s \cdot \left(e^{\frac{v_D(t)}{V_T}} - 1 \right)$$

$$\approx I_s \cdot e^{\frac{v_D(t)}{V_T}}$$

$$V_T \approx 25 \text{ mV}$$

Forward bias
 $v_D(t)$ sufficient large

Incremental resistance

$$+ v_D -$$

$$i_D \rightarrow \text{Diode}$$



$$\begin{cases} i_D(t) = I_D + i_d(t) \\ v_D(t) = V_D + v_d(t) \end{cases}$$

$$v_d(t) \xrightarrow{?} i_d(t)$$



SMALL-SIGNAL ANALYSIS

[Bias
Quiescent
Average]

Diode

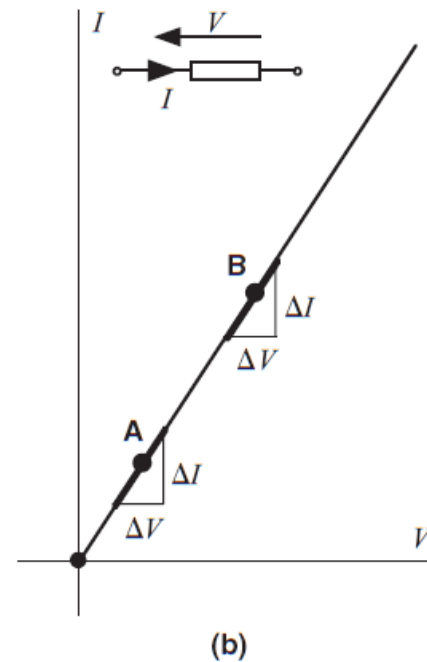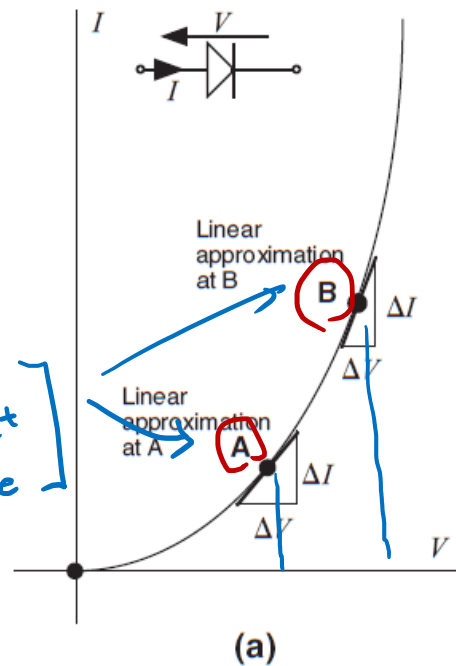

Incremental resistance

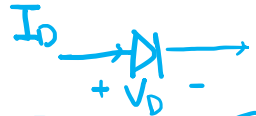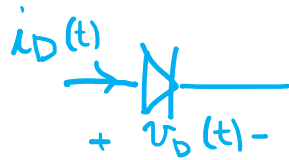

$$I_D = I_s \cdot e^{v_D/v_T}$$


$$i_D(t) \approx I_s \cdot e^{v_D(t)/V_T}$$

$$\begin{aligned} I_D + i_d(t) &= I_s \cdot e^{(v_D + v_d(t))/V_T} \\ &= I_s \cdot e^{v_D/V_T} \cdot e^{v_d(t)/V_T} \\ &= I_D \cdot \left[1 + \frac{v_d(t)}{V_T} + \frac{1}{2} \left(\frac{v_d(t)}{V_T} \right)^2 + \dots \right] \\ &\approx I_D + \frac{I_D}{V_T} v_d(t) \end{aligned}$$

Linearity
Assume

$$\frac{v_d}{V_T} \ll 1$$


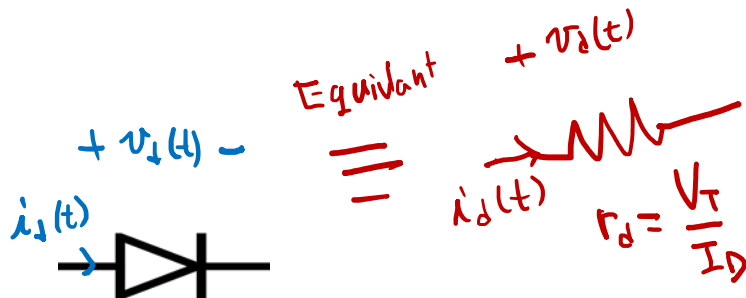
$$\Rightarrow i_d(t) \approx \frac{I_D}{V_T} \cdot v_d(t)$$



Equivalent

$$r_d = \frac{V_T}{I_D}$$

$v_d(t)$

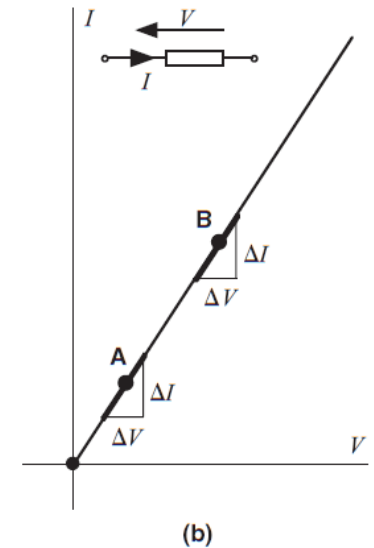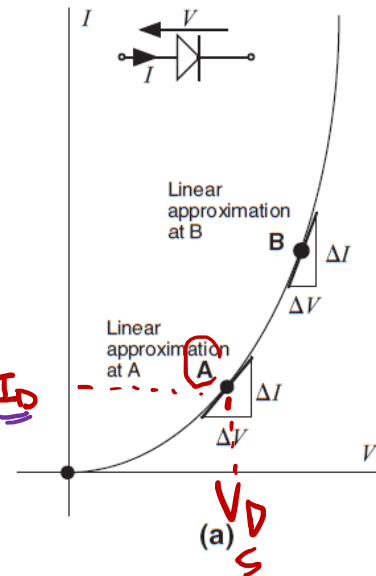

Incremental resistance r_d

Alternative view (change analysis)



$$\left. \begin{array}{l} I_D \rightarrow I_D + \Delta I \\ V_D \rightarrow V_D + \Delta V \end{array} \right\} \text{Relation of } \Delta V \sim \Delta I ?$$

$$\begin{aligned} \frac{\Delta I}{\Delta V} &\approx \frac{dI_D}{dV_D} = \frac{d}{dV_D} \left(\underbrace{I_S \cdot e^{\frac{V_D}{V_T}}}_{I_D} \right) \\ &= \frac{I_D}{V_T} e^{\frac{V_D}{V_T}} \approx \frac{I_D}{V_T} \approx \frac{I_D}{V_T} \end{aligned}$$

define $g_d \equiv \frac{I_D}{V_T}$ [Incremental Conductance]
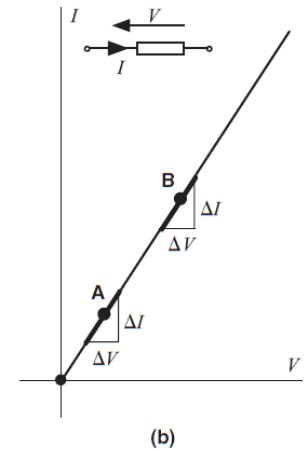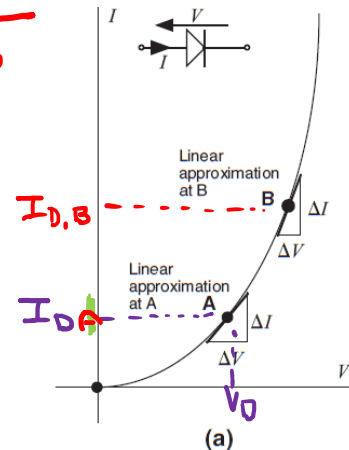
$$r_d \equiv \frac{1}{g_d} = \frac{V_T}{I_D} \approx \frac{25 \text{ mV}}{I_D}$$








$$\Delta V = r_d \cdot \Delta I$$



Small-signal models
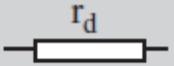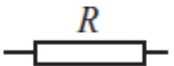
$$v_Y(t) = V_Y + v_g(t)$$

Changes in current and voltage

diode	$\Delta V = r_d \Delta I$	
resistor	$\Delta V = R \Delta I$	
voltage source	$\Delta V = 0$	
current source	$\Delta I = 0$	
VCCS	$\Delta I = G \Delta V$	
voltage source change	$\Delta V = \text{constant}$	
current source change	$\Delta I = \text{constant}$	

$$r_d = \frac{V_T}{I_D}$$

Source Bias

Small-signal source

Example 13.1

Find $v_D(t) = ?$

$$i_D = I_s e^{v_D/V_T}$$


Source $v_S(t) = \underbrace{20}_{V_S: \text{bias}} + \underbrace{1 \sin 100t}_{v_s(t): \text{small signal}}$

Step 1. Find DC bias (quiescent condition)

$$V_D = 0.7 \text{ V}$$

$$V_S = 20 \text{ V}$$

$$I_D = \frac{20 - V_D}{10 \text{ k}} = 1.93 \text{ mA}$$

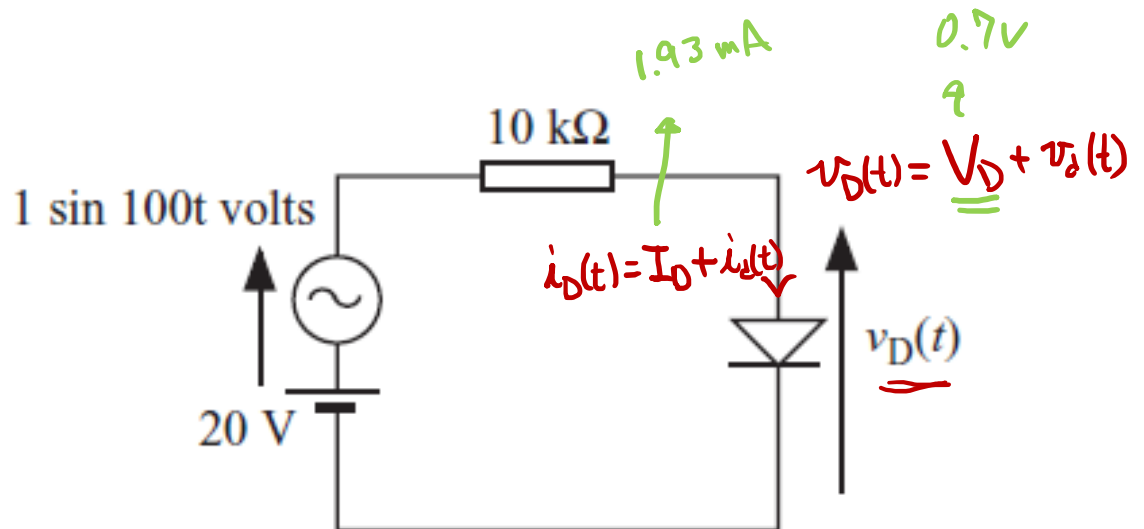

Example 13.1


Step 2. Find small signal model

$$r_d = \frac{1}{g_d} = \frac{V_T}{I_D} = \frac{25 \text{ mV}}{1.93 \text{ mA}} \approx 12.95 \Omega$$

Step 3. Create small-signal equiv. ckt

Step 4. Analyze small-signal ckt

$$v_d(t) = v_s(t) \cdot \frac{r_d}{10 \text{ k}\Omega + r_d} \\ \approx 1.29 \sin(100t) \text{ (mV)}$$

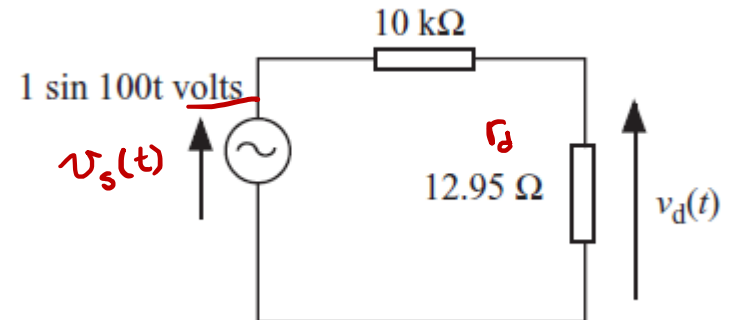


Example 13.1

Step 5. Check linearity assumption


$$\left| \frac{v_d(t)}{V_T} \right| \leq \frac{1.29 \text{ mV}}{25 \text{ mV}} \ll 1$$

Total (large-signal) voltage across diode

$$v_D(t) = 0.7 + 0.00129 \sin(100t)$$

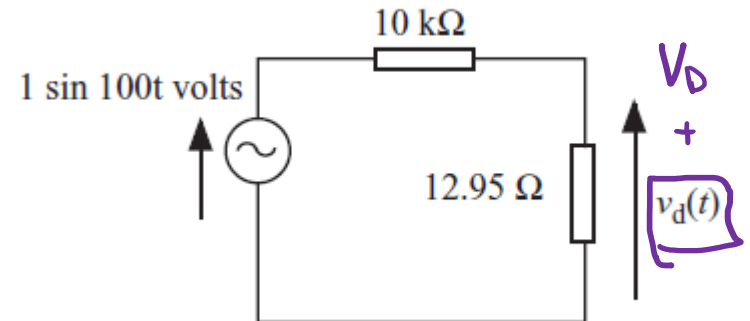

Example 13.1

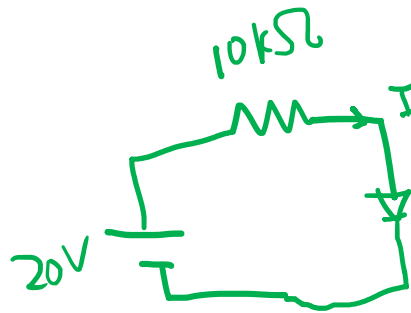


$$I_D = \frac{20 - 0.7}{10k} = 1.93 \text{ mA} \rightarrow$$

$$g_d = \frac{I_D}{V_T} = \frac{1.93 \text{ mA}}{25 \text{ mV}} = 77.2 \text{ S}$$

$$r_d = \frac{V_T}{I_D} = \frac{25 \text{ mV}}{1.93 \text{ mA}} = 12.95 \Omega$$




Small-signal equiv.

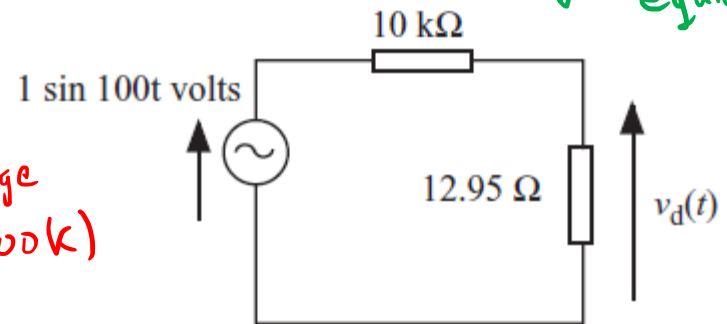V_T : thermal voltage
 $\approx 25 \text{ mV}$ (300K)



$V_D = 0.7 \text{ V}$

$0.7 + 0.00129 \sin(100t)$

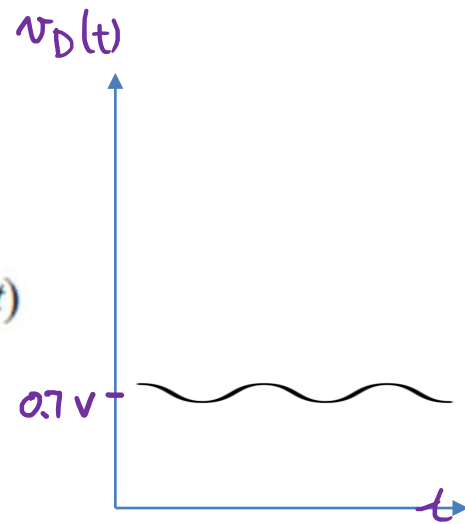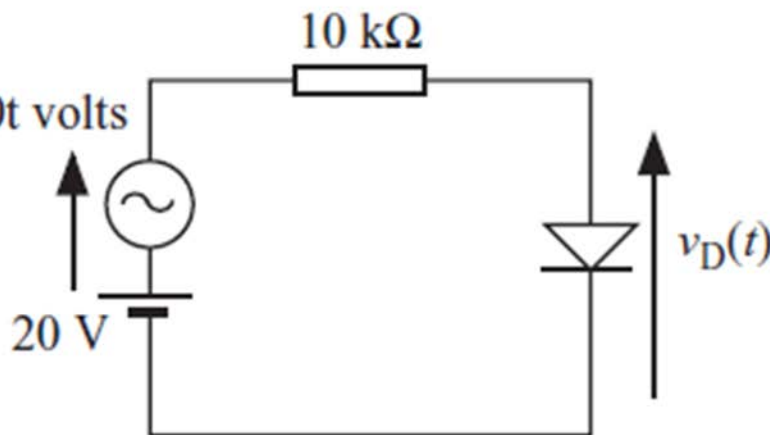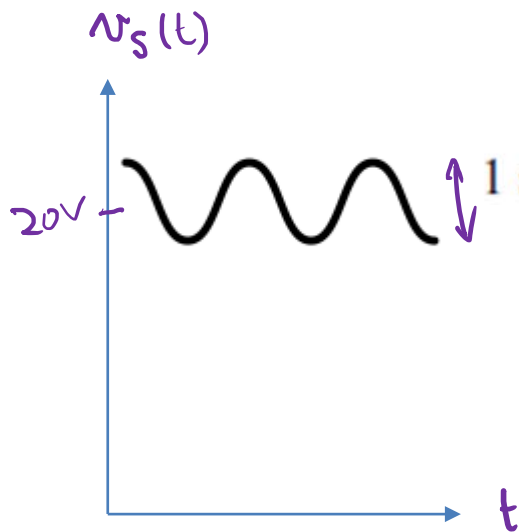

Chapter 13 Summary

Locally Linearization
Nonlinear \rightarrow Approximation \rightarrow Linear Analysis

Small-signal analysis = change analysis

$$I = f(V) \quad I + \Delta I = f(V + \Delta V)$$

$$\Rightarrow \Delta I \approx \left(\frac{df}{dV} \right) \Delta V$$

Diode \downarrow
 $\frac{1}{r_d}$ or g_d

Linear approximation
valid for

V_D : Sufficient high

$$v_d \ll V_T$$

(25 mV)

Course summary

Basic rules

KCL

KVL

Ohm's law

DC circuits

Nodal analysis

Superposition

Thevenin's equiv ckt

Norton's equiv ckt

Non-linear

Change analysis

Small-signal analysis

AC circuits

Phasor diagram

Complex impedance

Frequency response

OP amp

Positive feedback: trigger

Negative feedback: virtual short ckt

(dependent source)



Electronic Systems:

PC, iPhone, iPad, AI, ...

Analog Components:
modulator, oscillator, A/D
converter, RF amp...

Operating System


Program Language

Filters

Computer Arch.

OP Amp abstraction

Digital Abstraction

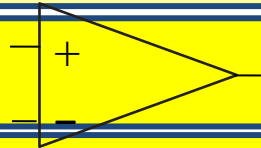

Amplifier

Circuits Abstraction



Physical Laws

Maxwell's, Schrödinger's,...

Natural Phenomena