

# LAB 3. Asymmetrical Oscillator

Build an asymmetrical oscillator on the online simulator. For the opamps, set 'Max Output' to 10 and 'Min Output' to -10. Display  $v(t)$  and  $v_o(t)$ . Export as text file and submit.

Suppose your student ID is  
 $E(NN) 0 (BBB) (CC)$

Set the Voltage Source  
 $V = 1.NN$

Set the resistor  
 $R = 2.CC \text{ K}\Omega$

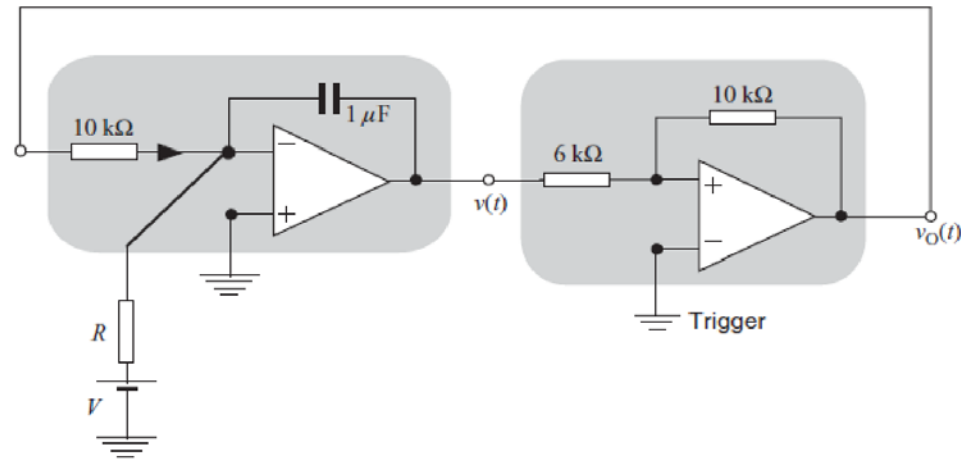


Figure 8.9 Modification to the circuit of Figure 8.7, resulting in asymmetrical waveforms

Example: ID E34048154  
NN=34, Voltage=1.34  
CC=54, R=2.54 K