


一. (30 pts). Given the input and clock transitions in the following figure,

indicate the output of a D device assuming:

(a) It is a positive edge-triggered flip-flop (7474).

 (b) It is a (positive) level-sensitive latch (7476)

Note: You may assume 0 setup, hold, and propagation delays.



二 (30pts) Implement the logic function $F(A,B,C,D)=\sum m(5,7,9,13)+$

$d(1,3,4,14,15)$, using

(a) a 4: 1 Mux

(b) a Decoder

三. (40 pts). Design a self-starting counter that has a normal counting

sequence : 3, 7, 5, 0, 2, and repeat. Direct all illegal states to the state 5. 註: 爲統

一閱卷, 請以 CBA之順序代表狀態 違者此題零分!

(a) Use T flip-flops

(b) Use D flip-flops