

Chapter 12

Field-Effect Transistors


場效電晶體

Field-Effect Transistors (FETs)

- FET (場效電晶體) 是利用 **電場** 來控制 **電流的大小**，而且組成電流的載子僅限 **一種** 極性，即電洞 **或** 是自由電子。
- Metal-Oxide-Semiconductor Field-Effect Transistor (MOSFET, 金氧半場效電晶體) 可分為 NMOS (以 **電子** 為電流載子) 與 PMOS (以 **電洞** 為電流載子)。
- MOSFET 包含 source (源極)、gate (閘極)、drain (汲極) 及 body (基座)。

12.1 NMOS AND PMOS TRANSISTORS

NMOS Transistor (n-p-n)

 



氧化物為絕緣體，沒有電
流能進入閘極端；
控制閘極電壓能夠調整
汲極到源極的電流

場效

(S, 半)

NMOS (n-channel MOS)

- NMOS 之 source (源極) 與 drain (汲極) 為 n-type 半導體，body (基座) 為 p-type 半導體，gate (閘極) 為導體。

  

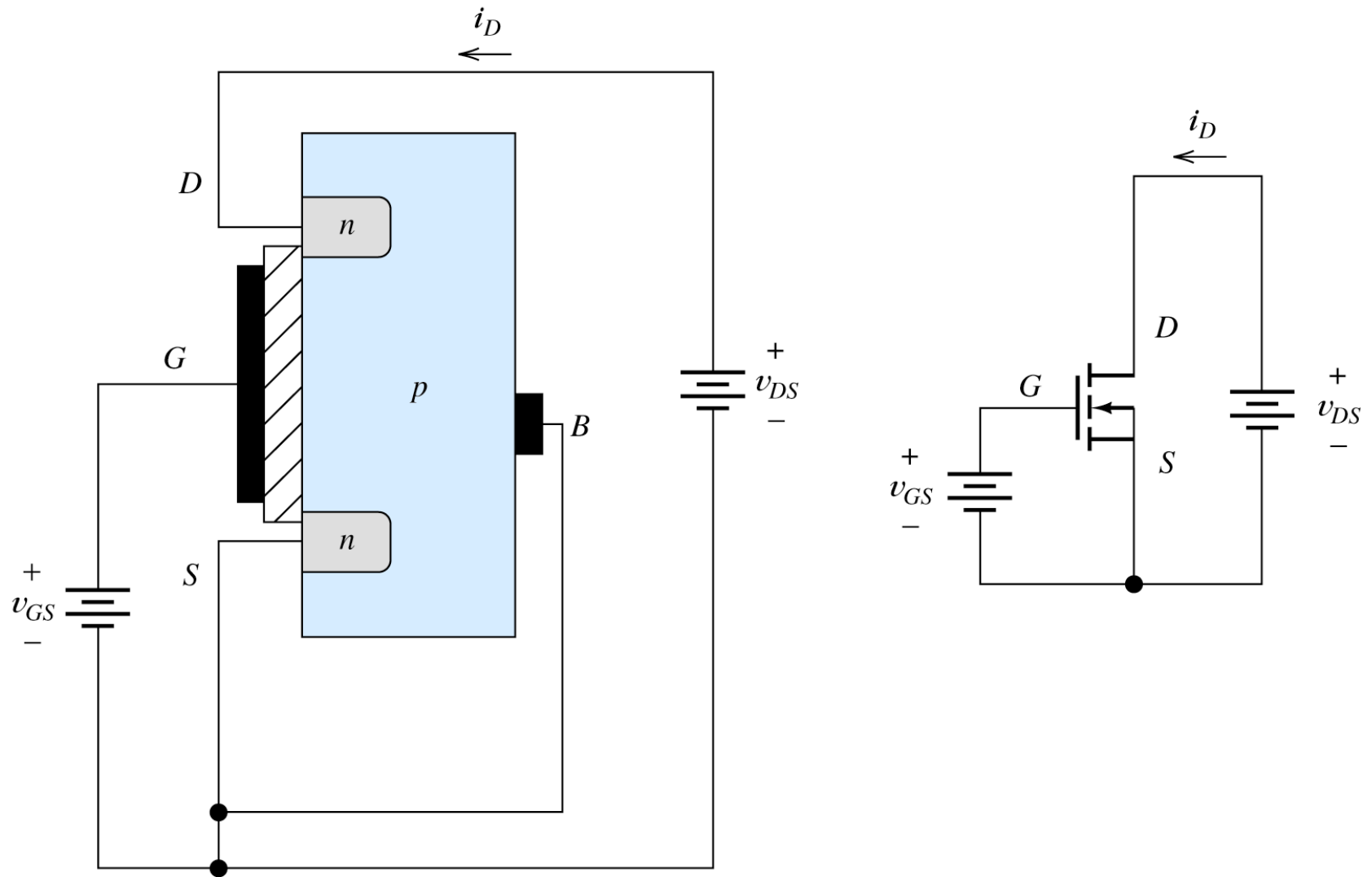


Figure 12.3 For $v_{GS} < V_{to}$, the pn junction between drain and body is reverse biased and $i_D = 0$.

NMOS 的運作 (Operation)

- NMOS 的運作可分為三區(region)

- Cutoff Region (截止區)

$$v_{GS} \leq V_{to}$$

- Triode Region (三極區) or Linear Region (線性區)



$$v_{GS} > V_{to} \text{ and } v_{DS} < v_{GS} - V_{to}$$

- Saturation Region (飽合區)

$$v_{GS} > V_{to} \text{ and } v_{DS} \geq v_{GS} - V_{to}$$

Operation in the Cutoff Region

  - 當閘極(gate)與源極(source)間電壓 $v_{GS} = 0$ ，兩個pn接面(body-source) 與(body-drain)可視為兩個方向相反的二極體，此時MOSFET為截止(cutoff)。
- 當閘極(gate)與源極(source)間電壓 v_{GS} 逐漸上升到 $> V_{to}$ (threshold voltage, 臨限電壓)時，則NMOS才會開始導通。




$$i_D = 0 \text{ for } v_{GS} \leq V_{to}$$

Operation in the Triode Region

$$v_{GS} > V_{to} \text{ and } v_{DS} < v_{GS} - V_{to}$$

 - 當閘極(gate)帶正電時，可逐漸吸引自由電子聚集在絕緣層的下方，並將電洞推離絕緣層下方。



$$\begin{aligned} \begin{cases} v_{GD} > V_{to} \\ v_{DS} > 0 \end{cases} &\equiv \begin{cases} v_{GS} - v_{DS} > V_{to} \\ v_{DS} > 0 \end{cases} \\ &\equiv 0 < v_{DS} < v_{GS} - V_{to} \end{aligned}$$

Operation in the Triode Region

$$v_{GS} > V_{to} \quad \text{and} \quad v_{DS} < v_{GS} - V_{to}$$

- 當閘極(gate)與源極(source)間電壓 v_{GS} 逐漸上升到 $>V_{to}$ (threshold voltage, 臨限電壓), 且在drain和source之間加有電壓 v_{DS} , 則形成n-type通道(channel), 通道中的自由電子受到外加電場的驅動, 形成汲極電流(drain current) i_D , 其方向從drain流向source, 和通道中的電子流方向相反。
- 當 v_{DS} 很小時, i_D 與 v_{DS} 成正比, 亦與 $v_{GS} - V_{to}$ 成正比。
- 由於有氧化絕緣層, 故閘極電流 $i_G = 0$ 。

$$v_{DS} < v_{GS} - V_{to} \equiv v_{GS} - v_{DS} > V_{to} \equiv v_{GD} > V_{to}$$

Operation in the Triode Region




- In the triode region, the NMOS behaves as a **resistor** connected between **drain and source**, but the resistance decreases as v_{GS} increases.

$$i_D = K \left[2(v_{GS} - V_{to})v_{DS} - \cancel{v_{DS}^2} \right]$$

0, if $v_{DS} \sim 0$

$$K = \left(\frac{W}{L} \right) \frac{KP}{2}$$



Device parameter

   

Operation in the Saturation Region


$$v_{GS} > V_{to} \quad \text{and} \quad v_{DS} \geq v_{GS} - V_{to}$$

  - 當drain和source之間電壓 $v_{DS} \geq v_{GS} - V_{to}$ (or $v_{GD} \leq V_{to}$) 則n-type通道在drain端寬度變為0， v_{DS} 再變大， i_D 不再上升，稱為飽合區。



Operation in the Saturation Region

$$i_D = K(v_{GS} - V_{to})^2$$

 

Boundary between Triode and Saturation Regions

At boundary, 使得n-type通道在drain端寬度剛好為0

$$v_{GD} = V_{to}$$

→ $v_{GS} - v_{DS} = V_{to}$

代入I-V equation in **saturation region** $i_D = K(v_{GS} - V_{to})^2$

→ $i_D = Kv_{DS}^2 \quad (\because v_{GS} - V_{to} = v_{DS})$

Boundary between Triode and Saturation Regions

將 $v_{GS} - V_{to} = v_{DS}$ 代入 I-V equation in **triode region**

$$i_D = K \left[2(v_{GS} - V_{to})v_{DS} - v_{DS}^2 \right]$$



$$i_D = K \left[2v_{DS}^2 - v_{DS}^2 \right] = Kv_{DS}^2$$

兩者結果一樣。

 


Figure 12.6 Characteristic curves for an NMOS transistor.

Example 12.1


A NMOS transistor $W=160\mu\text{m}$, $L=2\mu\text{m}$, $KP=50\mu\text{A}/\text{V}^2$, and $V_{to}=2\text{ V}$. Plot the drain characteristic curves to scale for $v_{GS}=0, 1, 2, 3, 4$, and 5 V .

1. 求 K

$$K = \left(\frac{W}{L}\right) \frac{KP}{2} = 2\text{mA}/\text{V}^2$$

 2. 求 boundary

$$i_D = Kv_{DS}^2 = 2 \times 10^{-3} \times v_{DS}^2$$



3. 求 saturation currents

$$i_D = K(v_{GS} - V_{to})^2 = 2 \times 10^{-3} \times (v_{GS} - 2)^2$$




$$i_D = 18\text{mA} \quad \text{for } v_{GS} = 5\text{V}$$

$$i_D = 8\text{mA} \quad \text{for } v_{GS} = 4\text{V}$$

$$i_D = 2\text{mA} \quad \text{for } v_{GS} = 3\text{V}$$
 
$$i_D = 0\text{mA} \quad \text{for } v_{GS} = 2\text{V}$$



4. Plot characteristics in the triode region (parabola 拋物線).

$$i_D = K \left[2(v_{GS} - V_{to})v_{DS} - v_{DS}^2 \right]$$

 


Figure 12.6 Characteristic curves for an NMOS transistor.

PMOS

- PMOS 之 source 與 drain 為 **p**-type 半導體，body 為 **n**-type 半導體，gate (閘極) 為導體。
- 以 **電洞** 為電流載子。


 
 
 
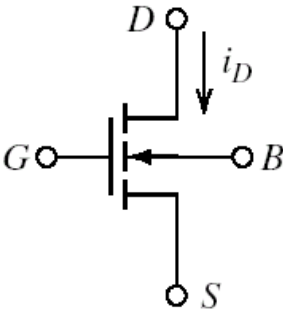



Figure 12.8 Circuit symbol for PMOS transistor.

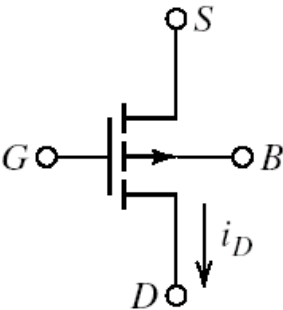

MOSFET Summary

	NMOS	PMOS
Circuit symbol		
KP (typical value)	$50 \mu\text{A/V}^2$	$25 \mu\text{A/V}^2$
K	$(1/2) KP (W/L)$	$(1/2) KP (W/L)$
V_{to} (typical value)	+1 V	-1 V
Cutoff region	$v_{GS} \leq V_{to}$ $i_D = 0$	$v_{GS} \geq V_{to}$ $i_D = 0$
Triode region	$v_{GS} \geq V_{to}$ and $0 \leq v_{DS} \leq v_{GS} - V_{to}$ $i_D = K [2(v_{GS} - V_{to}) v_{DS} - v_{DS}^2]$	$v_{GS} \leq V_{to}$ and $0 \geq v_{DS} \geq v_{GS} - V_{to}$ $i_D = K [2(v_{GS} - V_{to}) v_{DS} - v_{DS}^2]$
Saturation region	$v_{GS} \geq V_{to}$ and $v_{DS} \geq v_{GS} - V_{to}$ $i_D = K (v_{GS} - V_{to})^2$	$v_{GS} \leq V_{to}$ and $v_{DS} \leq v_{GS} - V_{to}$ $i_D = K (v_{GS} - V_{to})^2$
v_{DS} and v_{GS}	Normally assume positive values	Normally assume negative values

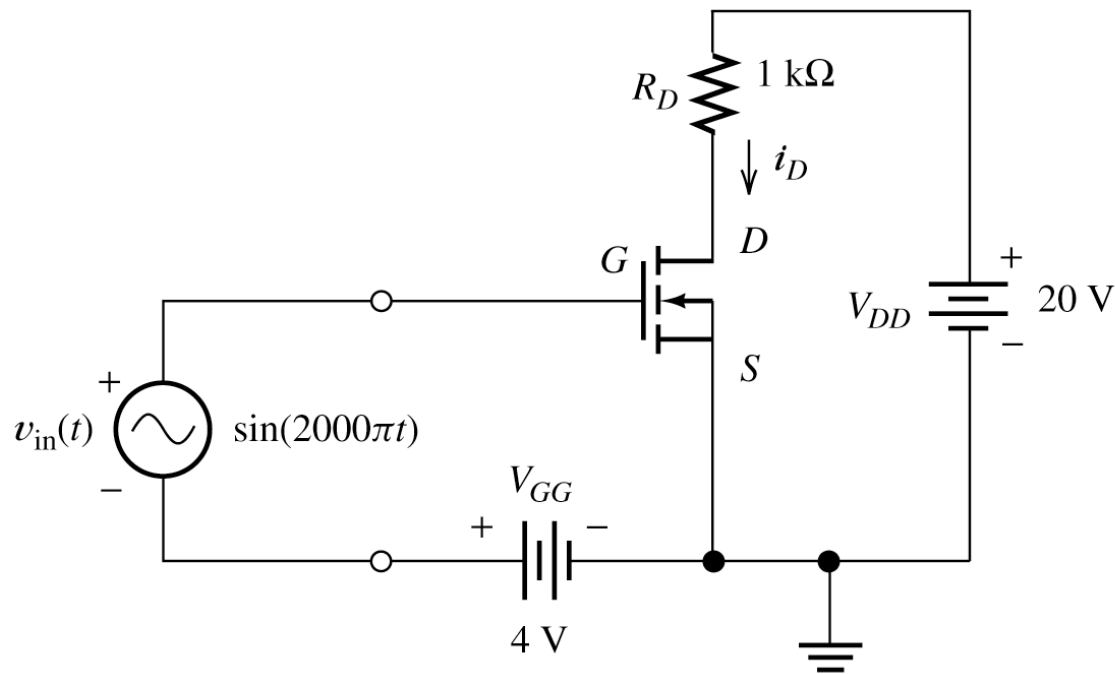12.2 LOAD-LINE ANALYSIS OF A SIMPLE NMOS AMPLIFIER



12.2 LOAD-LINE ANALYSIS OF A SIMPLE NMOS AMPLIFIER

- V_{GG} (dc source) 對NMOS 產生偏壓(bias) , 決定操作點 , 當ac input 在操作點附近隨時間變化 , 導致 v_{GS} , i_D 亦隨時間改變。

 


Figure 12.10 Simple NMOS amplifier circuit.

- i_D 隨時間改變，導致 R_D 亦上的壓降隨時間改變，使得 V_{DS} 產生 ac output。

KVL $v_{GS}(t) = v_{in}(t) + V_{GG} = \sin(2000\pi t) + 4$

Load-line equation $v_{DD} = R_D i_D(t) + v_{DS}(t)$

$$20 = i_D(t)(mA) + v_{DS}(t)$$

Load-line 兩端點

$$(v_{DS} = 0V, i_D = 20mA)$$

$$(v_{DS} = 20V, i_D = 0mA)$$

 


Figure 12.10 Simple NMOS amplifier circuit.

- Quiescent operation point (Q point) is at $v_{in}=0$.

$$v_{GS} = V_{GG} = 4\text{V}$$

 


Figure 12.11 Drain characteristics and load line for the circuit of Figure 12.10.

$$\therefore v_{GS}(t) = v_{in}(t) + V_{GG} = \sin(2000\pi t) + 4$$

→ $V_{GS\max} = 5\text{V (point A)}$

$V_{GS\min} = 3\text{V (point B)}$

 


Figure 12.11 Drain characteristics and load line for the circuit of Figure 12.10.

 


Figure 12.12 v_{GS} and v_{DS} versus time for the circuit of Figure 12.10.

Distortion

Distortion is due to that the characteristic curves for the FET are **not uniformly spaced**.

If a much **smaller input amplitude** was applied we would have amplification **without** appreciable distortion.


12.3 Bias Circuits

Amplifier Analysis

Amplifier analysis has two steps:

1. Determine the **Q point**.
2. Use a **small-signal equivalent circuit** to determine **impedances** and **gains**.


The Fixed- Plus Self-Bias Circuit

 

(a) Original circuit

$v_{DS} ?$

The Fixed- Plus Self-Bias Circuit

 


(a) Original circuit

1. Thévenin equivalent

$$V_G = V_{DD} \frac{R_2}{R_1 + R_2}$$

$$R_G = \frac{R_1 R_2}{R_1 + R_2}$$

 


2. KVL


$$V_G = v_{GS} + R_s i_D \quad (\because i_G = 0)$$

3. Usually, transistor operates in saturation region


$$i_D = K(v_{GS} - V_{to})^2$$

 

4. Load Line Analysis i_D vs. v_{GS}

 


5. Determine v_{DS}

 

$$v_{DS} = v_{DD} - (R_D + R_S)i_D$$

 Example 12.2

Analyze the following circuit. The transistor $KP=50\mu\text{A}/\text{V}^2$, $V_{to}=2\text{ V}$, $L=10\mu\text{m}$, $W=400\mu\text{m}$




1. Determine K

$$K = \left(\frac{W}{L}\right) \frac{KP}{2} = 1\text{mA}/\text{V}^2$$

 2. Thévenin equivalent

$$V_G = V_{DD} \frac{R_2}{R_1 + R_2} = 20 \frac{1}{3 + 1} = 5\text{V}$$



3. Determine V_{GSQ}

$$\begin{cases} V_G = V_{GSQ} + R_s I_{DQ} \\ I_{DQ} = K(V_{GSQ} - V_{to})^2 \end{cases}$$




$$V_G = V_{GSQ} + R_s K(V_{GSQ} - V_{to})^2$$

$$V_{GSQ}^2 + \left(\frac{1}{R_s K} - 2V_{to}\right)V_{GSQ} + V_{to}^2 - \frac{V_G}{R_s K} = 0$$

$$V_{GSQ}^2 - 3.630V_{GSQ} + 2.148 = 0$$

$$V_{GSQ} = 2.886 \text{ or } 0.744$$



 

4. I_{DQ} & V_{DSQ}


$$I_{DQ} = K(V_{GSQ} - V_{to})^2 = 0.784 \text{ mA}$$

$$V_{DSQ} = V_{DD} - (R_D + R_s)I_{DQ} = 14.2 \text{ V}$$

 12.4 SMALL-SIGNAL EQUIVALENT CIRCUITS

$$i_D(t) = I_{DQ} + i_d(t) \quad \text{Small signal (ac)}$$

$$v_{GS}(t) = V_{GSQ} + v_{gs}(t) \quad \text{Small signal (ac)}$$




To determine $v_{gs}(t)$ vs. $i_d(t)$

$$\because i_D = K(v_{GS} - V_{to})^2 \text{ for saturation}$$



$$\begin{aligned} I_{DQ} + i_d(t) &= K[V_{GSQ} + v_{gs}(t) - V_{to}]^2 \\ &= K(V_{GSQ} - V_{to})^2 + 2K(V_{GSQ} - V_{to})v_{gs}(t) + Kv_{gs}^2(t) \end{aligned}$$

SMALL-SIGNAL EQUIVALENT CIRCUITS

 

$$I_{DQ} + i_d(t) = K(V_{GSQ} - V_{to})^2 + 2K(V_{GSQ} - V_{to})v_{gs}(t) + Kv_{gs}^2(t)$$

At Q point

$$I_{DQ} = K(V_{GSQ} - V_{to})^2$$

$$(\because 2K(V_{GSQ} - V_{to})v_{gs}(t) \gg Kv_{gs}^2(t))$$

$$I_{DQ} + i_d(t) = K(V_{GSQ} - V_{to})^2 + 2K(V_{GSQ} - V_{to})v_{gs}(t) + \cancel{Kv_{gs}^2(t)}$$

$$i_d(t) \cong 2K(V_{GSQ} - V_{to})v_{gs}(t) = g_m v_{gs}(t)$$

$$g_m = 2K(V_{GSQ} - V_{to})$$

$$= 2\sqrt{KI_{DQ}}$$

$$= \sqrt{2KP} \sqrt{W/L} \sqrt{I_{DQ}}$$

$$K = \left(\frac{W}{L} \right) \frac{KP}{2}$$

Figure 12.19 Small-signal equivalent circuit for FETs.