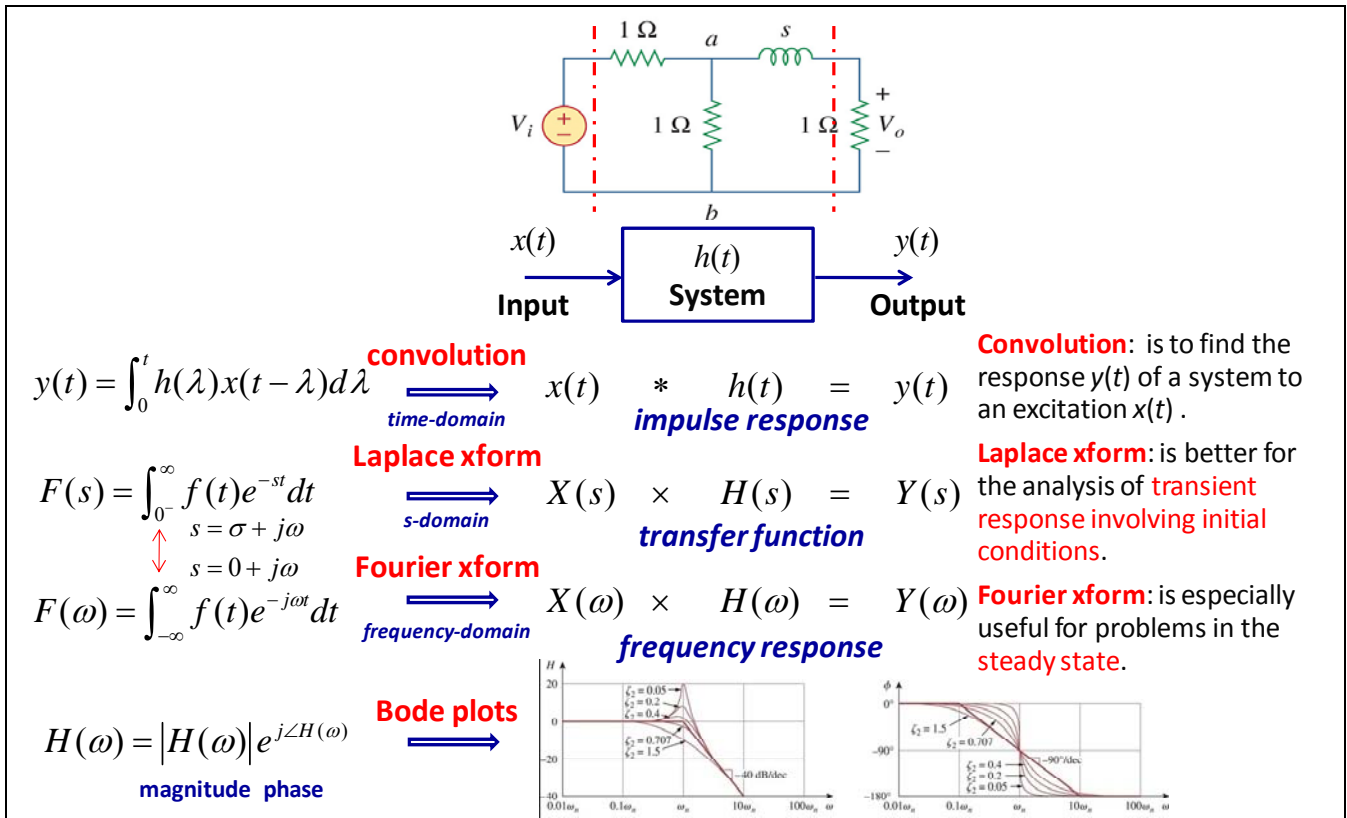


Final Exam

June 25, 2014

- A. Signal & System for Circuit (6×3=18 points):** Describe the relativities among the (a) Figures, (b) Equations, and (c) Terms in the following table.



- B. A RLC Circuit (10+7=17 points):** The input $v_s(t) = 2\sin 2t u(t)$ V in Fig. 1. Also, +1 A flows through the inductor and -5 V is across the capacitor at $t = 0$. (a) Find the output voltage $v(t)$ across the capacitor at $t > 0$. (b) Find the frequency response between the output voltage $v(t)$ and the input voltage $v_s(t)$.

- C. An Op Amp Circuit (8+8+8+4+4=32 points):** $v_i(t) = 10\cos 10t u(t)$ V voltage is applied to the op amp circuit with $R_1 = 100$ k Ω , $R_2 = 100$ k Ω , and $C = 0.5$ μ F from $t = 0$ in Fig. 2. Assume that the initial capacitor voltage was 1 V. (a) Find $v_o(t)$ in the circuit by using Laplace transform. (b) Derive the transfer function $H(s)$ between $V_o(s)$ and $V_i(s)$. And, find the impulse response $h(t)$ between $v_o(t)$ and $v_i(t)$. (c) Find the natural response and the forced response of $v_o(t)$ from (a). (d) Also, indicate the transient response and the steady-state response in $v_o(t)$. (e) Apply the final-value theorem to find the steady-state response in $v_o(t)$.

D. Convolution (6+6=12 points): (a) Please physically and mathematically discuss the “Convolution” according to the equation $y(t) = \int_{-\infty}^{\infty} x(\lambda)h(t-\lambda)d\lambda$! (b) Explain the “Convolution” according to the equation $y(t) = \int_0^t x(\lambda)h(t-\lambda)d\lambda$ with a causal input and a causal system. The following table is for your references.

- **Convolution (folding):** is to find the response $y(t)$ of a system to an excitation $x(t)$.
- It is defined as $y(t) = \int_{-\infty}^{\infty} x(\lambda)h(t-\lambda)d\lambda = \int_{-\infty}^{\infty} h(\lambda)x(t-\lambda)d\lambda$
 $\Rightarrow y(t) = x(t) * h(t) = h(t) * x(t)$ ← **Physics** if $x(t)$ is input & $y(t)$ is output

The **convolution** of two signals consists of time-reversing one of the signals, shifting it, and multiplying it point by point with the second signal, and integrating the product. ← **mathematics**

- It applies to any **linear system** and can be simplified

$y(t) = \int_0^{\infty} x(\lambda)h(t-\lambda)d\lambda$ if $x(t) = 0$ for $t < 0$, i.e., a causal input

$= \int_0^t x(\lambda)h(t-\lambda)d\lambda$ if $h(t) = 0$ for $t < 0$, i.e., a **causal system**

E. Fourier transform (5+6=11 points): (a) Derive the Fourier transform of $10\sin \omega_0 t$. (b) Plot the amplitude spectrum and phase spectrum.

F. MATLAB (5×4=20 points): (a) Find the frequency response $V_o(\omega)/I_i(\omega)$ for the circuit of Fig. 3. And write a MATLAB code to draw (b) a Bode plot, whose x -axis is 100 points from 10^{-2} to 10^2 Hz, (c) a step response, and (d) a time response with a sinusoidal input at 500 rad/s. Function hint: bode(num,den), logspace(a,b,n), step(num,den), lsim(num,den,x,t).

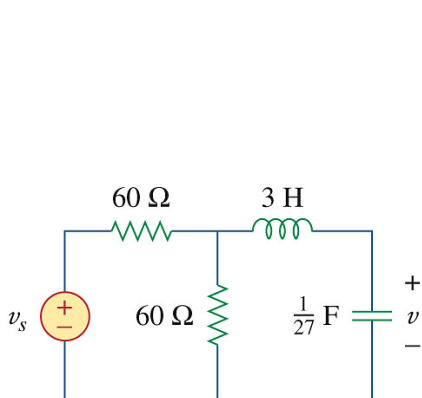


Fig. 1

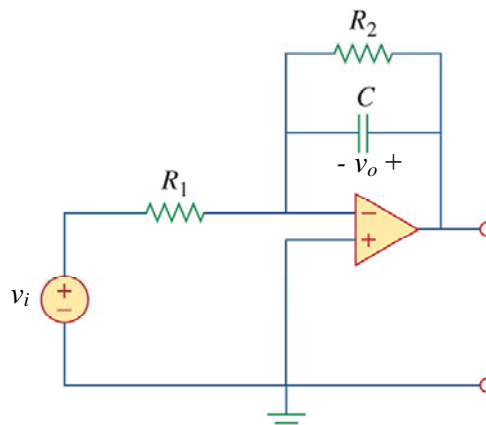


Fig. 2

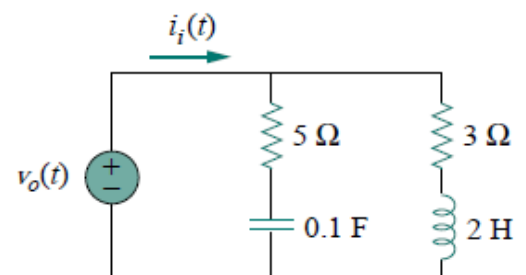


Fig. 3