

1. 單位
2. log10

Midterm Examination II

Electric Circuit

2018/12/2

1. (10%) Find the current I_o of the circuit shown in Fig. 1 by using the superposition theorem.

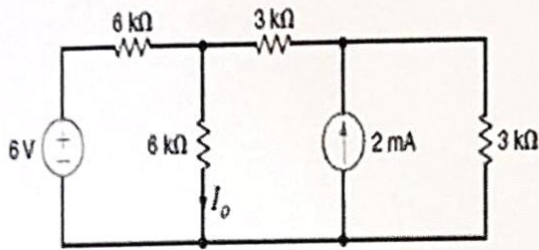


Fig. 1

2. (10%) For the circuit in Fig. 2, Please find its Thevenin's equivalent circuit.

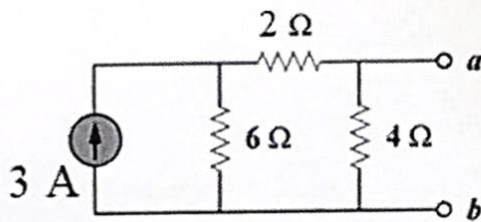


Fig. 2

3. (10%) For the circuit in Fig. 3, please

- (a) find $R_L = ?$ such that the power delivered to R_L is maximum.
(b) determine the maximum power $P_{Lmax} = ?$.

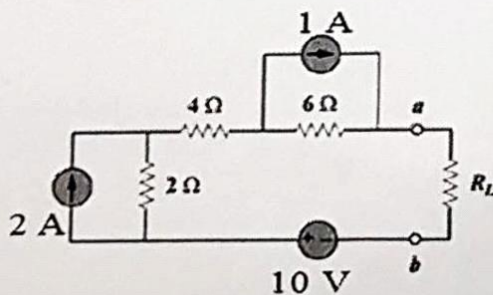


Fig. 3

4. (10%) For the op amp circuit in Fig. 4, determine the value of v_2 such that $v_o = -17.5 V$.

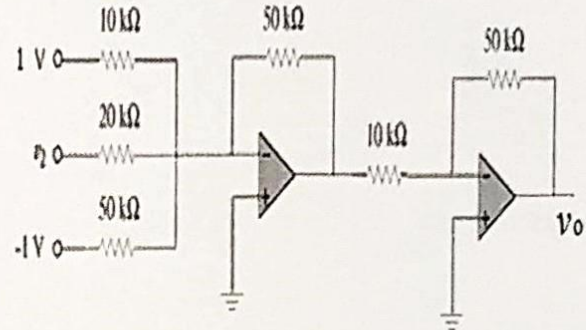


Fig. 4

5. (10%) Obtain the output v_o in the circuit of Fig. 5.

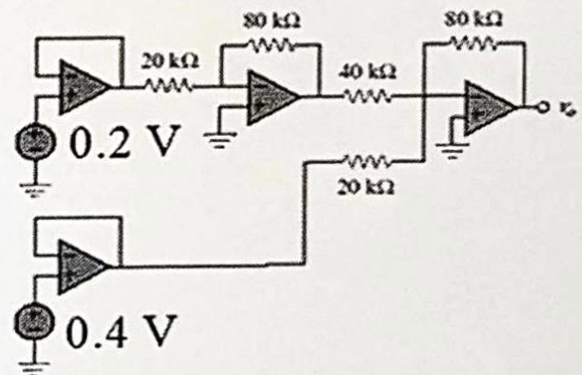


Fig. 5

6. (15%)
(a) - (9%) A 1-mH inductor has the following current

$$i(t) = \begin{cases} 10 A, & t < 0 \\ Ae^{-100t} + Be^{-600t} \text{ (A)}, & t \geq 0 \end{cases}$$

If the inductor has the initial voltage $v_L(0) = 0.5 V$, please find:

- (i) the constants A and B ,