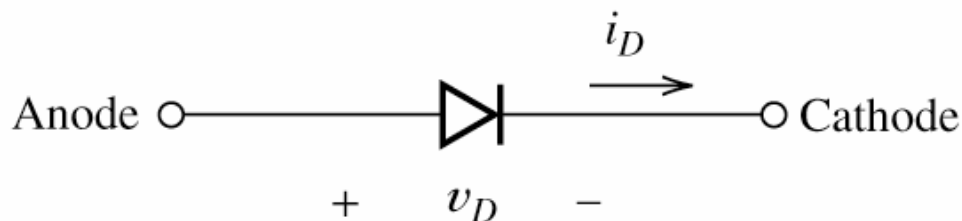



# **Chapter 10 Diodes (二極體)**
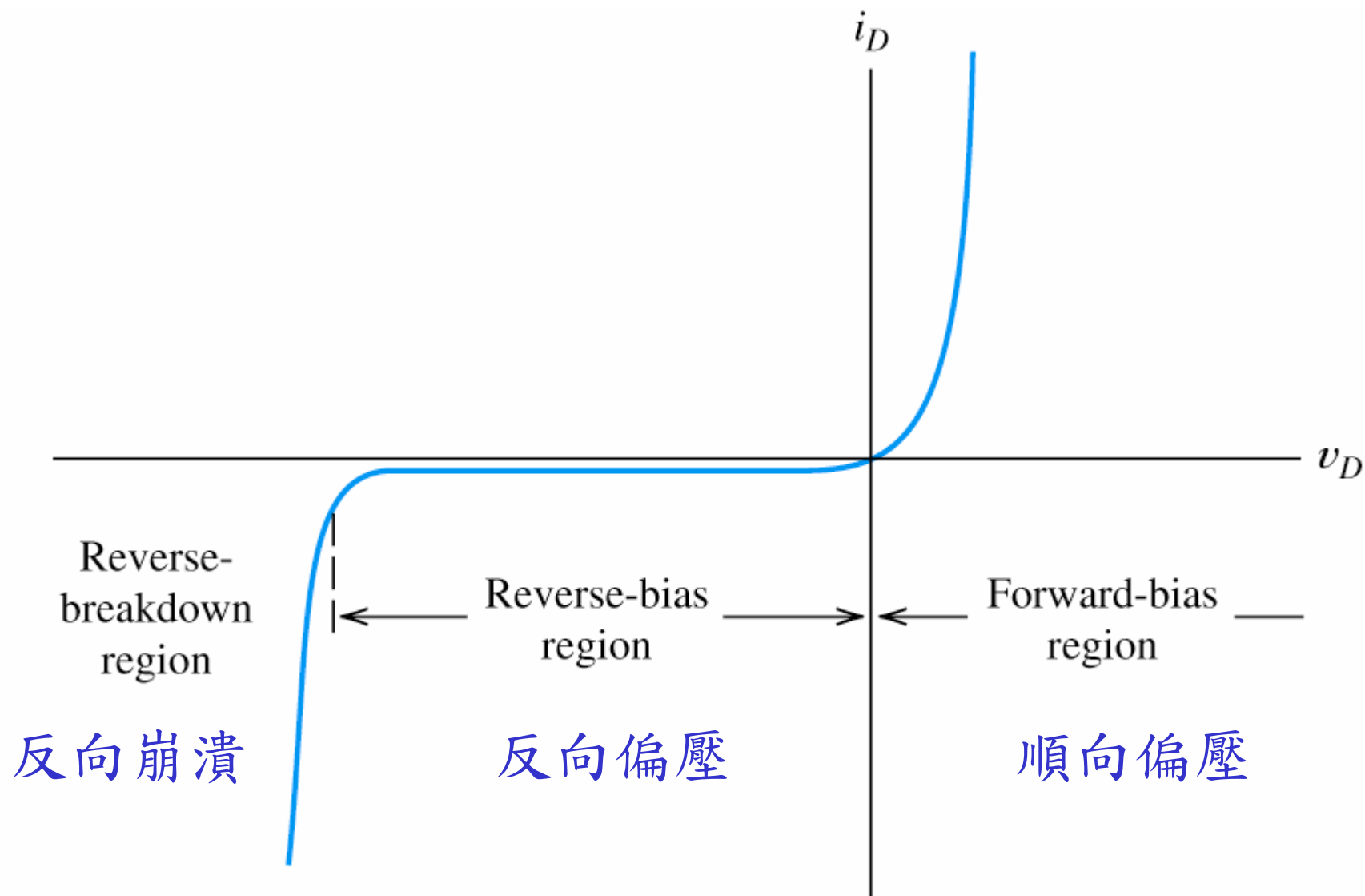
# 10.1 Basic Diode Concept

- The diode has two terminals, the anode (正極) and the cathode (負極)。




- 當二極體正極與負極間給一  $v_D > 0$ , 稱為順向偏壓 (forward bias.)
- 當二極體正極與負極間給一  $v_D < 0$ , 稱為反向偏壓 (reverse bias.)


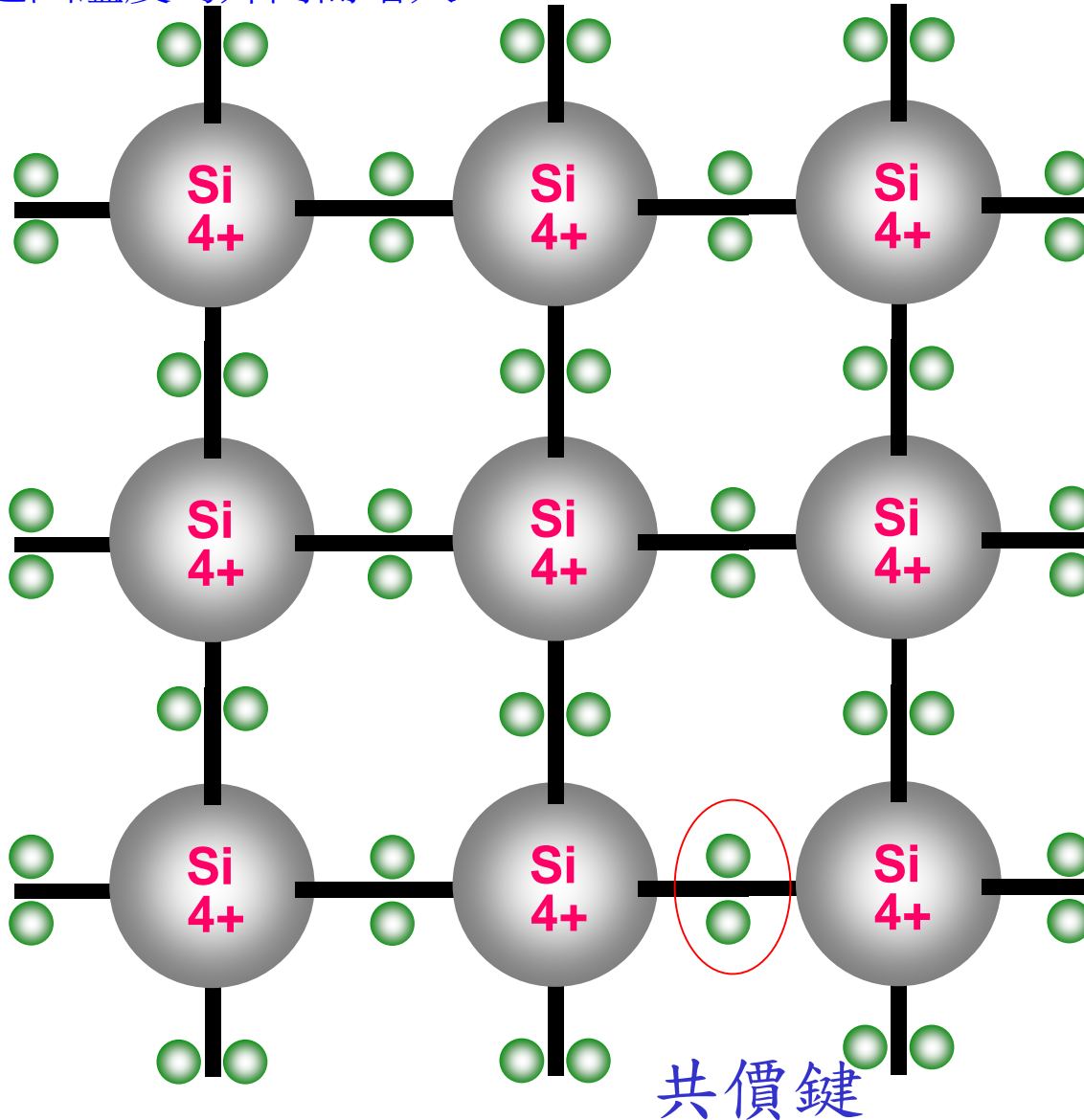
# 本質半導體 (intrinsic semiconductor)

溫度越高，被熱能釋放出來的電子和電洞的數量也越多。因此，本質半導體的導電性遂因溫度的升高而增大




IIB	IIIA	IVA	VA	VIA
	B 硼	C 碳	N 氮	O 氧
	Al 鋁	Si 矽	P 磷	S 硫
Zn 鋅	Ga 鎵	Ge 鍺	As 砷	Se 硒
Cd 鎘	In 銦		Sb 銻	Te 碲
Hg 汞				

四價原子

# 非本質半導體(extrinsic semiconductor)

## n-type

四價原子摻雜  
(doping) 五價原子

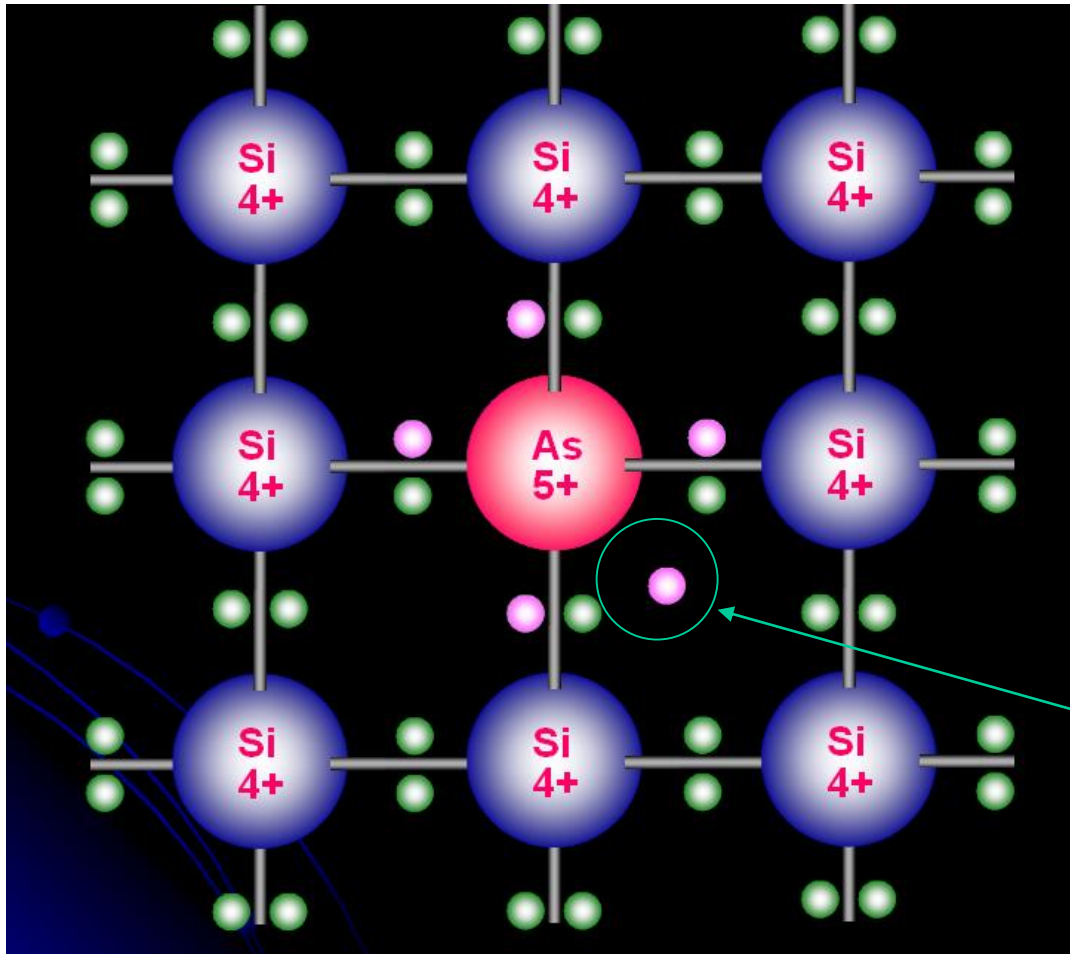


IIB	IIIA	IVA	VA	VIA
	B 硼	C 碳	N 氮	O 氧
	Al 鋁	Si 矽	P 磷	S 硫
Zn 鋅	Ga 鎵	Ge 鍺	As 砷	Se 硒
Cd 鎘	In 銦		Sb 銻	Te 碲
Hg 汞				

具帶負電荷的  
自由電子(由所  
摻雜的五價原  
子提供)

# 非本質半導體(extrinsic semiconductor)

## p-type

四價原子摻雜  
(doping) 三價原子

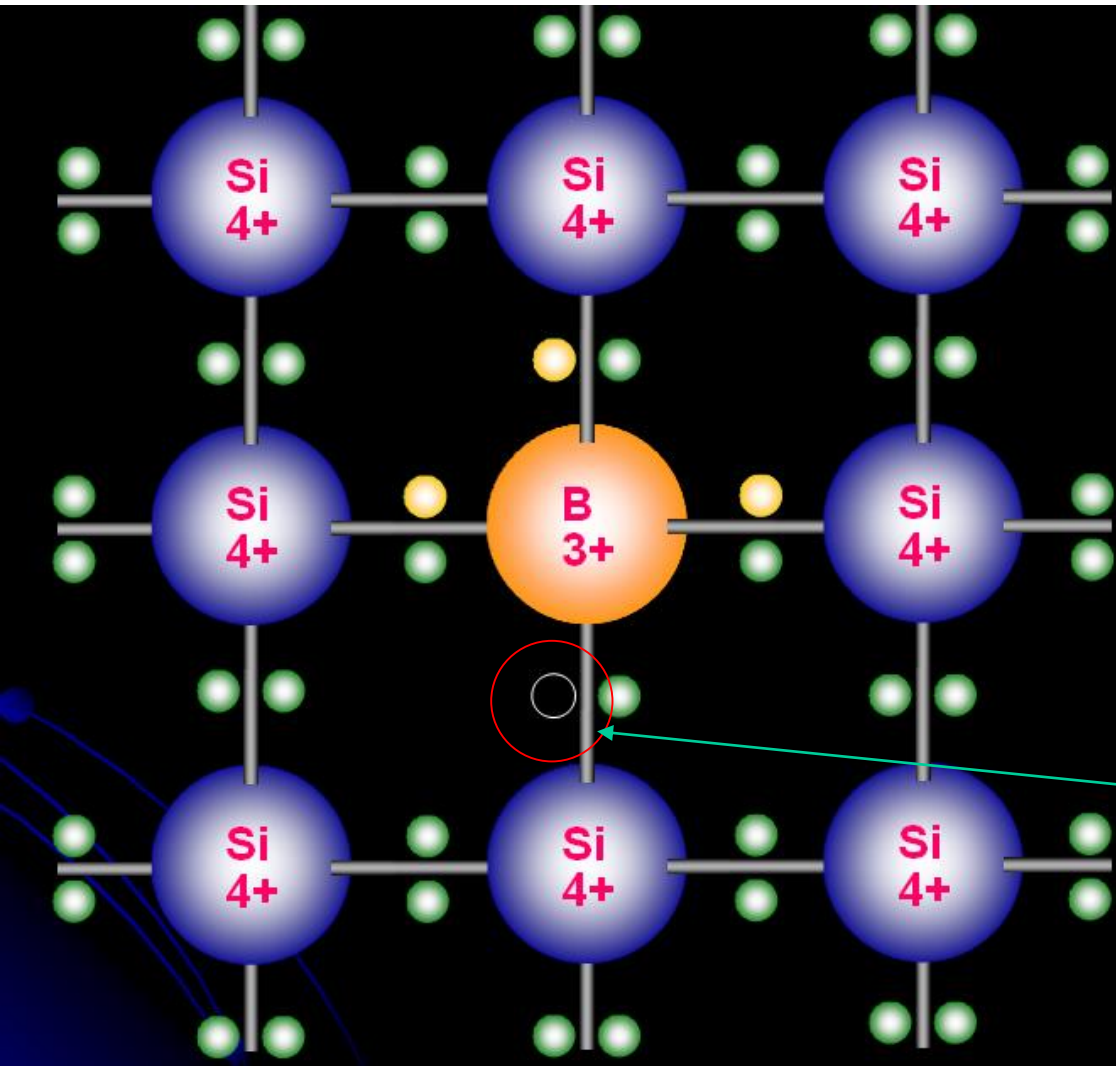

IIB	IIIA	IVA	VA	VIA
	B 硼	C 碳	N 氮	O 氧
	Al 鋁	Si 矽	P 磷	S 硫
Zn 鋅	Ga 鎵	Ge 鍺	As 砷	Se 硒
Cd 鎘	In 銦		Sb 銻	Te 碲
Hg 汞				



具帶正電荷的  
自由電洞(由所  
摻雜的三價原  
子提供)

# Doping

## ■ 摻雜(Doping)

- 將定量雜質加入純質半導體中，就可大幅提升矽與鍺的導電性
- 摻有雜質的半導體有兩種
  - N型：加入五價的雜質原子，砷(As)，磷(P)，鉍(Bi)，銻(Sb)等
  - P型：加入三價的雜質原子，硼(B)，銦(In)，鎵(Ga)等


# PN Junction (PN 接面)

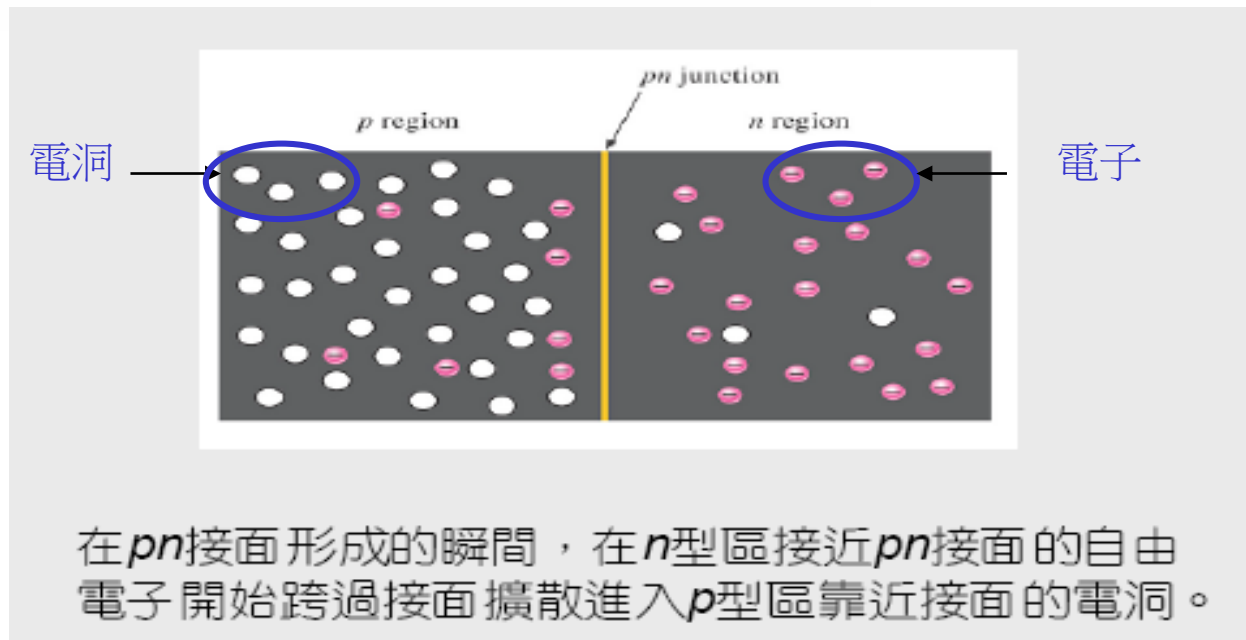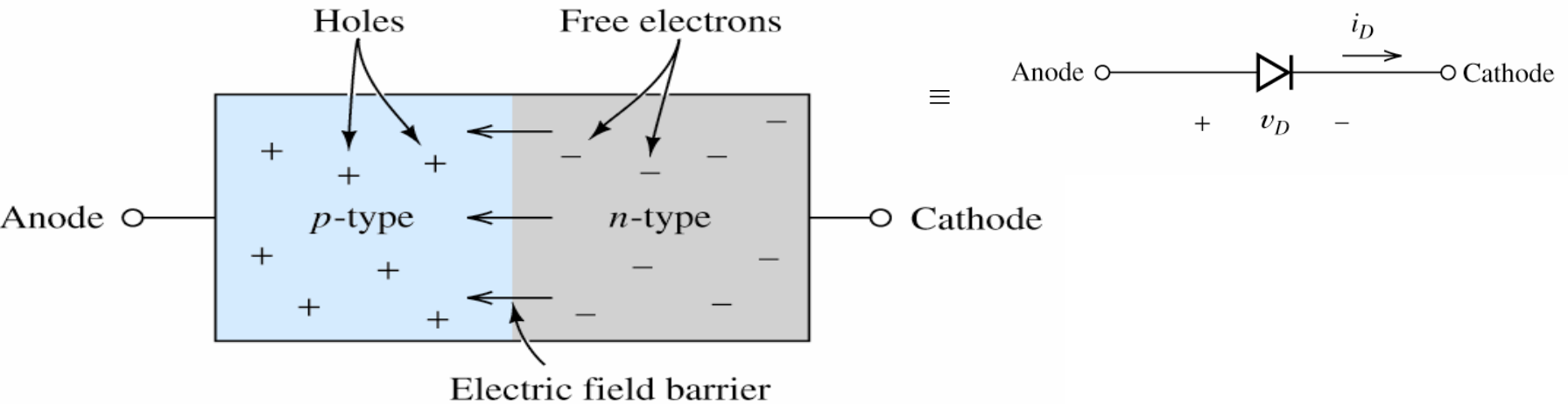



# PN Junction (PN 接面)



## Electric-field barrier

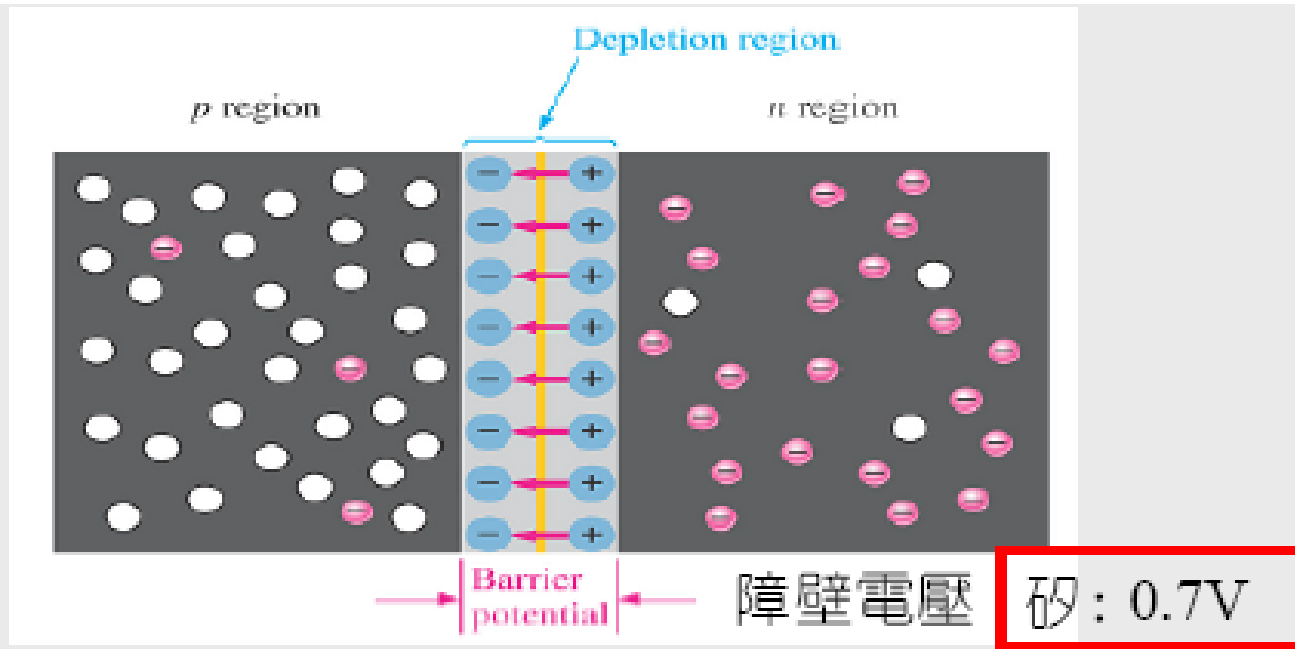


每一個擴散通過接面而與電洞結合的電子，就會在 $n$ 型區留下一個正電荷，並且在 $p$ 型區產生一個負電荷，這樣就形成障壁電壓。這種現象會一直持續，直到產生的障壁電壓大到能夠排斥進一步的擴散作用為止。
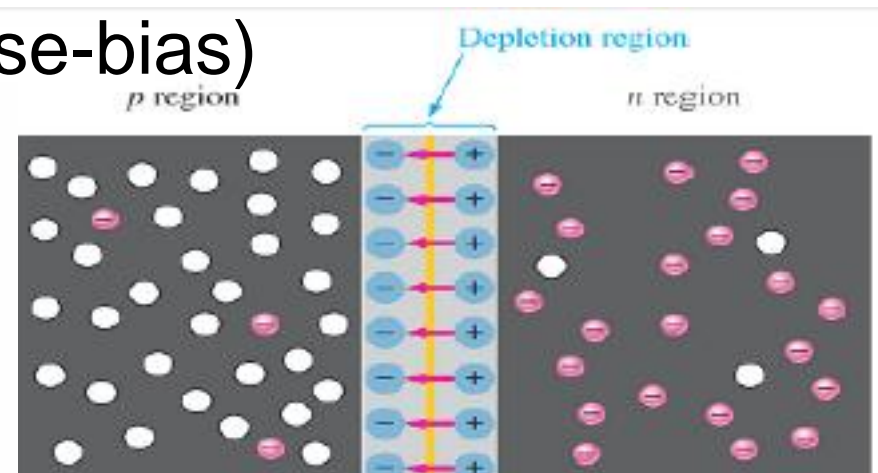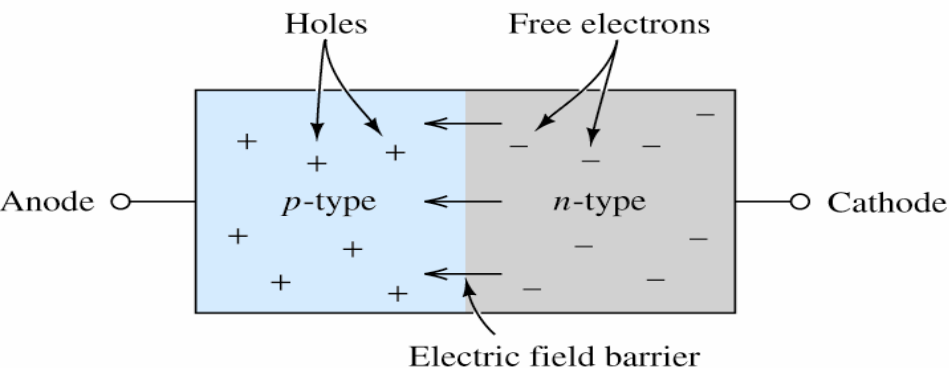
# PN Junction (PN 接面)

- **Electric-field barrier** (電場屏障, P端低, N端高)使得N端自由電子無法到達P端, P端自由電洞無法到達N端。此接面稱為**Depletion region** (空乏區)。
- 當  $V_D > \text{electric-field barrier}$  (順向偏壓, forward-bias), 則二極體導通, 電子(N端)與電洞(P端)向另一端流動。
- 當二極體正  $V_D < 0$  (反向偏壓), 則增強electric-field barrier, 更不導通。(reverse-bias)



# Shockley Equation

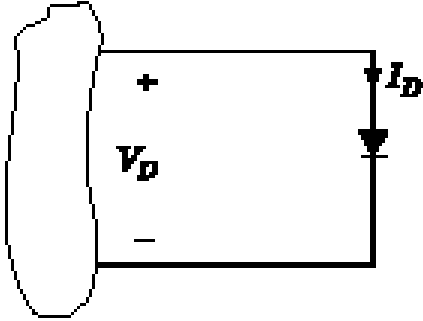

$$i_D = I_s \left[ \exp\left(\frac{v_D}{nV_T}\right) - 1 \right]$$

$I_s$ : (reverse) saturation current ((反向)飽和電流)


$V_T = \frac{kT}{q} \cong 0.026\text{V (at } 300^\circ\text{K)}$ : Termal voltage (熱電位)

$k = 1.38 \times 10^{-23} \text{ (J/K)}$  波茲曼常數

$q = 1.6 \times 10^{-19} \text{ C}$

$T$  ( $^\circ\text{K}$ ) 溫度

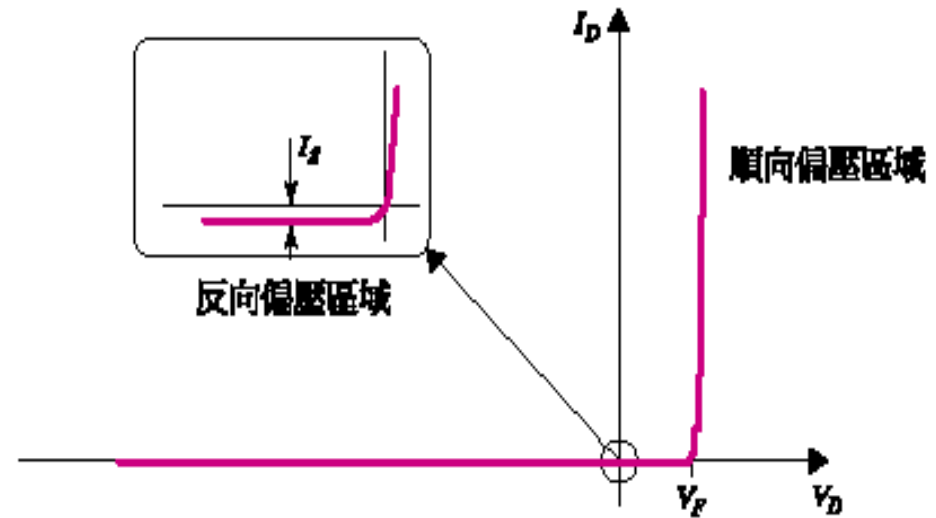$n$ : ideality factor, 理想因子  $1 \leq n \leq 2$




在順向偏壓下，指數項為正指數特性；

在逆向偏壓下， $v_D$ 為負值， $i_D$ 將逼近 $-I_s$

# 二極體完整I-V曲線

順向偏壓時, 當  $v_D \gg nV_T$   $i_D \cong I_s \exp\left(\frac{v_D}{nV_T}\right)$


Breakdown voltage  
崩潰電壓，一般  
diode易燒毀

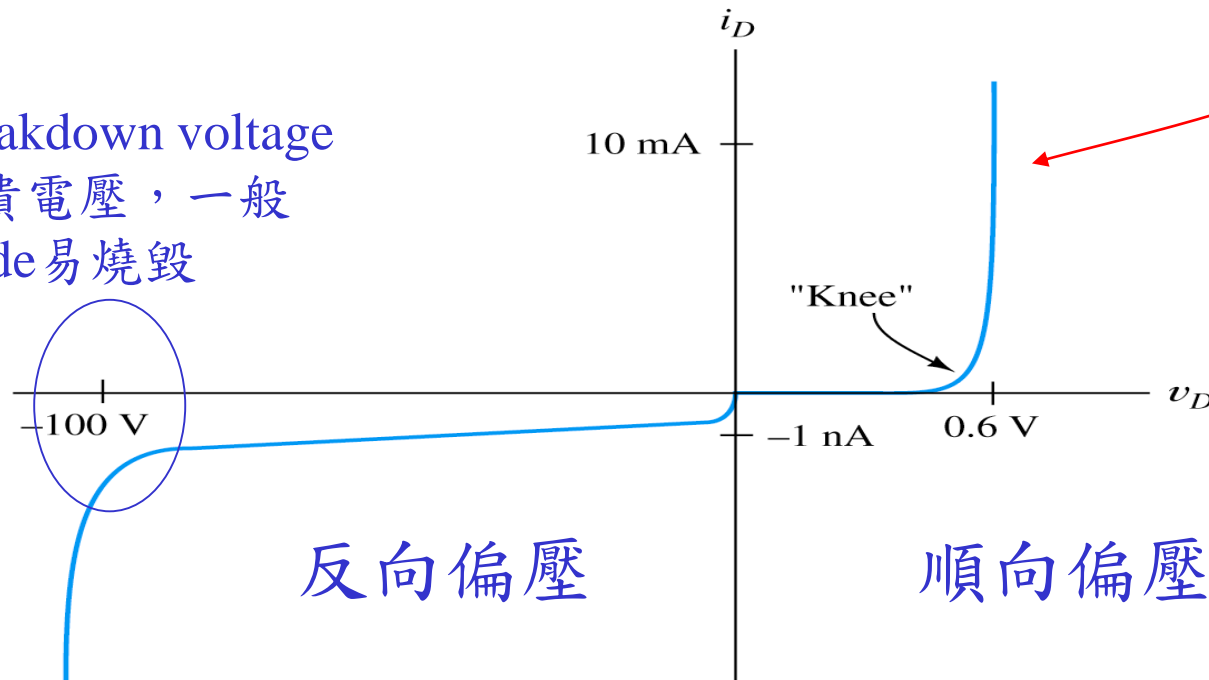


**Figure 10.2** Volt-ampere characteristic for a typical small-signal silicon diode at a temperature of 300 K. Notice the change of scale for negative current and voltage.
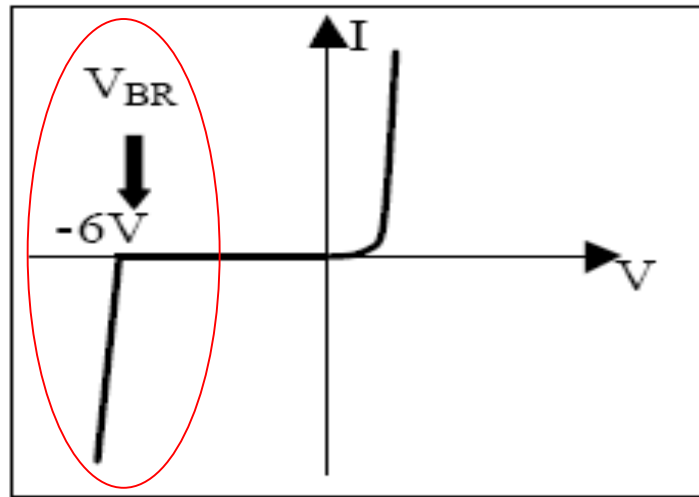
# Zener Diodes (齊納二極體)

Diodes that are intended to **operate in the breakdown region** (崩潰區) are called **Zener diodes**. 其在正向偏壓時與一般diode 一樣。


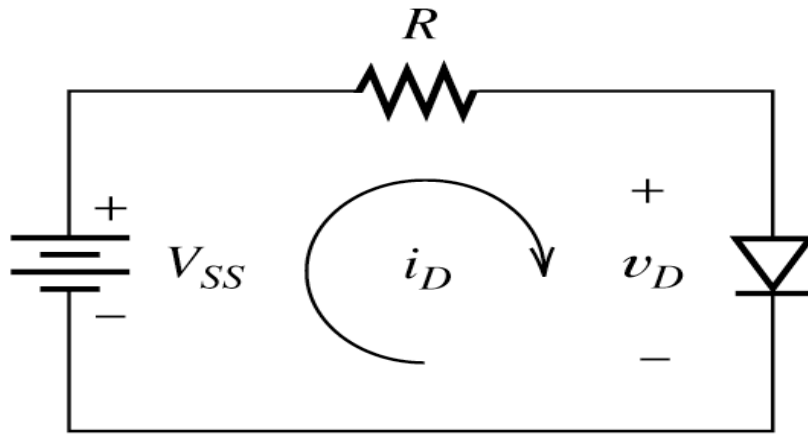
# 10.2 LOAD-LINE ANALYSIS OF DIODE CIRCUITS




KVL

$$V_{SS} = Ri_D + v_D$$

Diode I-V equation

$$i_D = I_s \left[ \exp\left(\frac{v_D}{nV_T}\right) - 1 \right]$$

- 兩條方程式，可解兩個未知數  $i_D$  &  $v_D$ 。
- 將兩條方程式畫在同一張I-V圖上，交點即是解。
- 此成為負載線分析法(load-line analysis)。

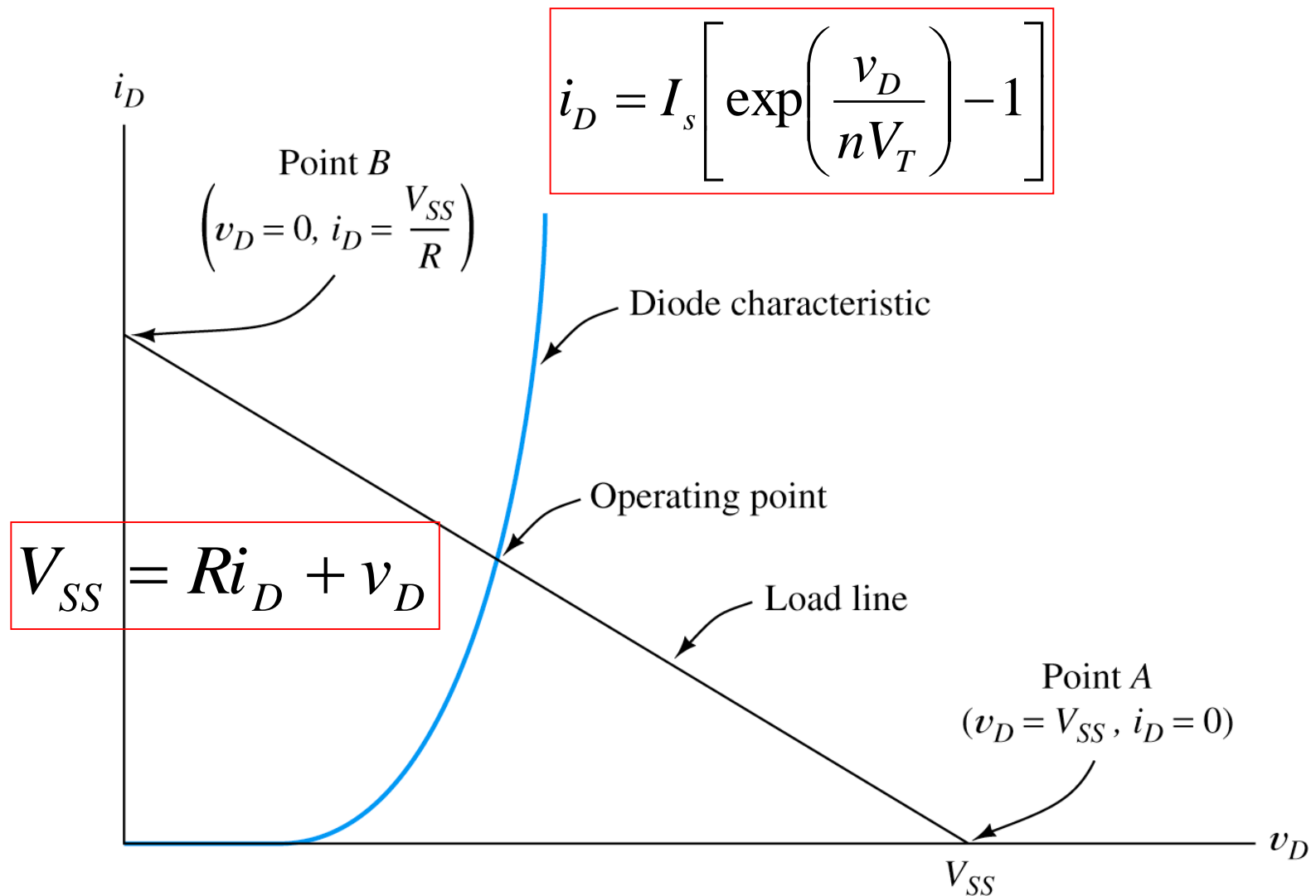

**Figure 10.6** Load-line analysis of the circuit of Figure 10.5.

# Example 10.1 & 10.2 Load line analysis

$V_{ss}=2\text{ V}$ ,  $R=1\text{ k}\Omega$ . (load line 1)

$V_{ss}=10\text{ V}$ ,  $R=10\text{ k}\Omega$ . (load line 2)

Find the diode voltage and current at the **operating point**.


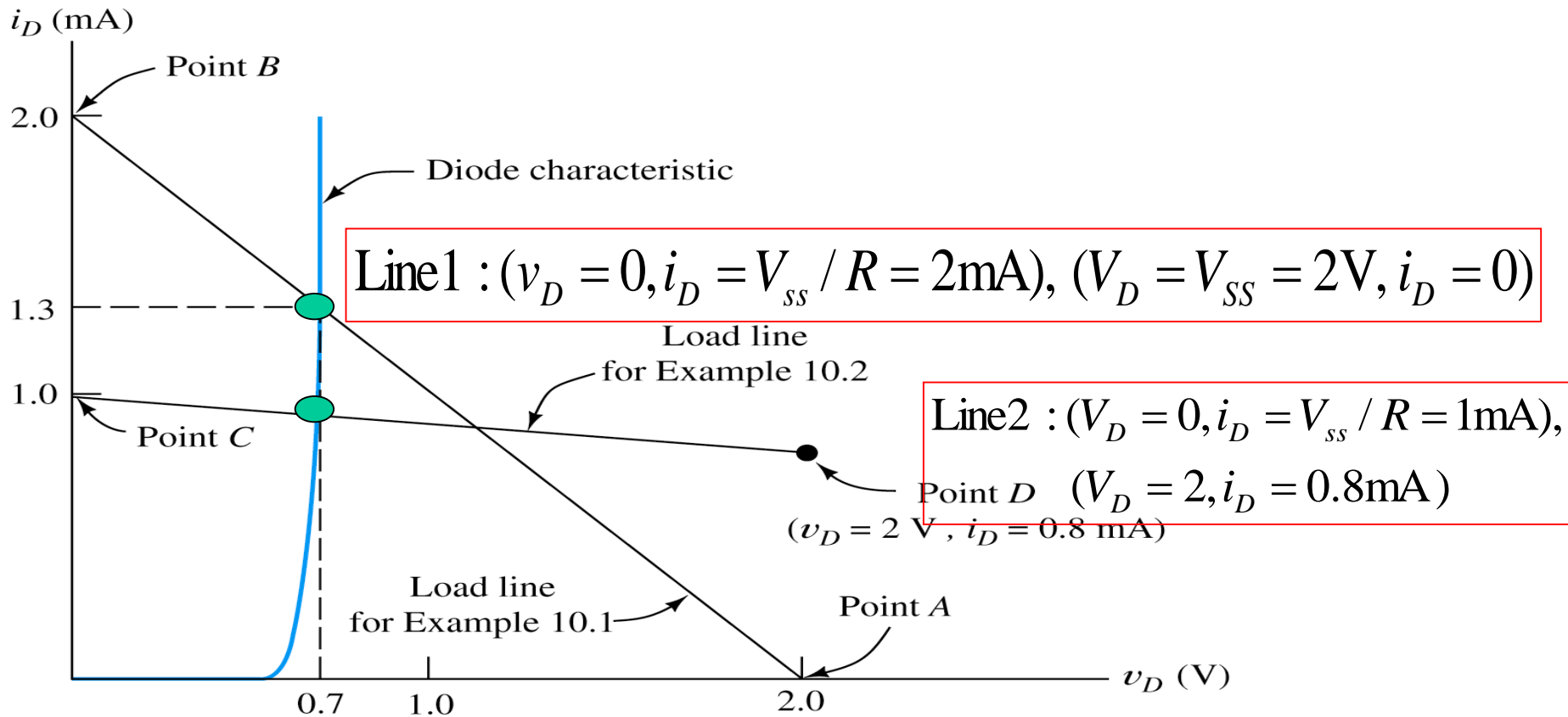


Figure 10.7 Load-line analysis for Examples 10.1 and 10.2.

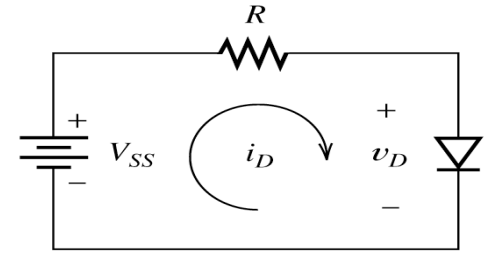

## Exercise 10.3

$V_{ss}=2\text{ V}$ ,  $R=100\ \Omega$ .

Find the diode voltage and current at the **operating point**.


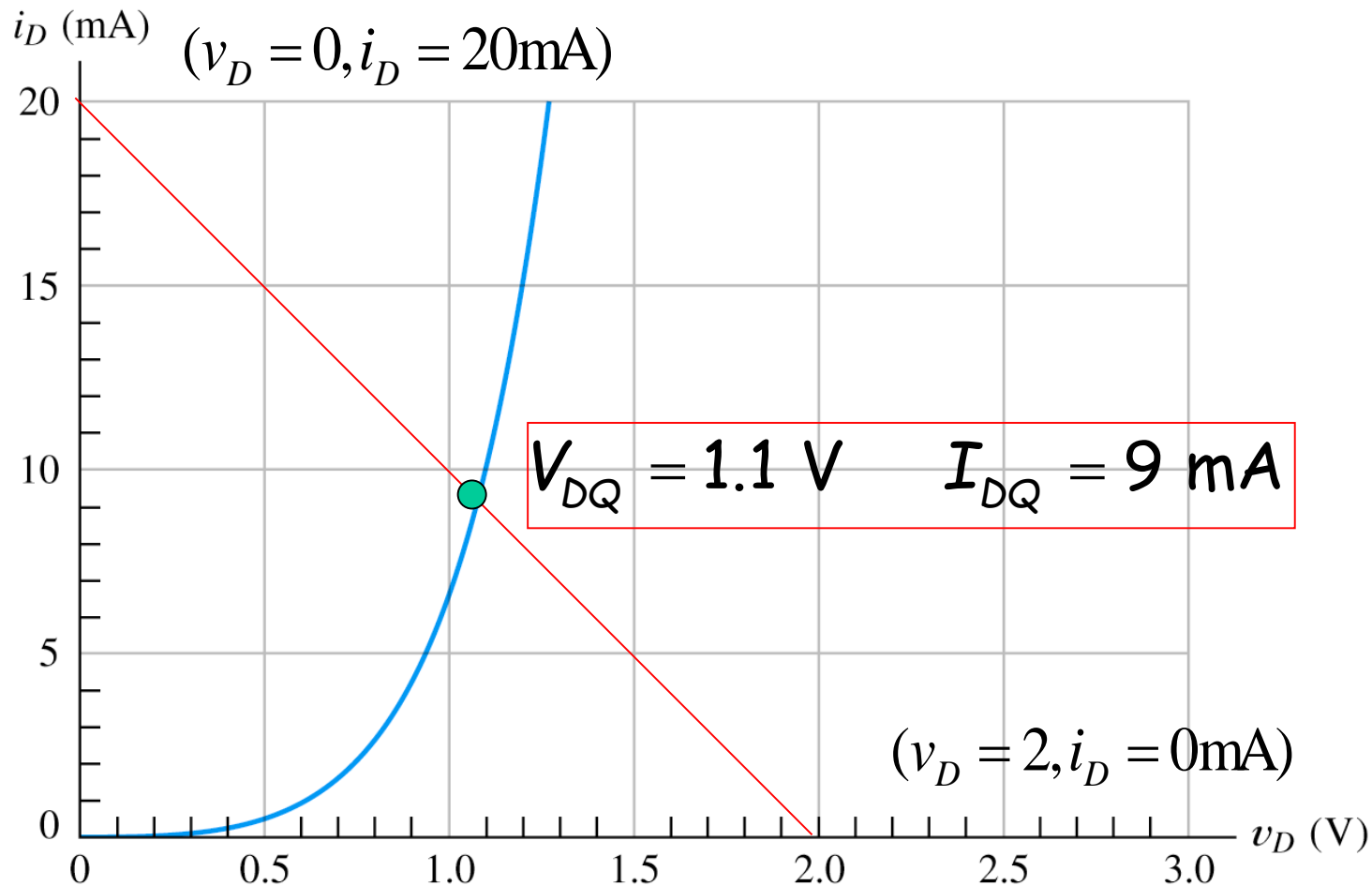


Figure 10.8 Diode characteristic for Exercise 10.3.
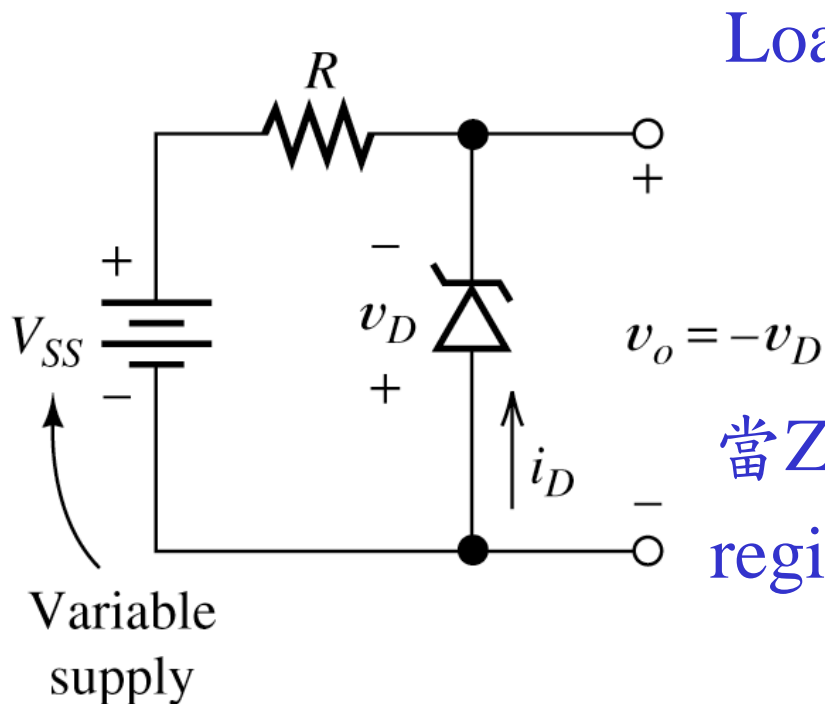
# 10-3 ZENER-DIODE VOLTAGE-REGULATOR CIRCUITS

A **voltage regulator** (穩壓) circuit provides a nearly **constant voltage** to a load from a variable source.



Load line

$$V_{SS} + Ri_D + v_D = 0$$

當 Zener diode 操作在 breakdown region 時,  $v_D$  與  $i_D$  都  $< 0$ .

## Example 10.3

$R=1\text{ k}\Omega$ ,  $V_{ss}=15\text{ V}$ . (load line 1)

$R=1\text{ k}\Omega$ ,  $V_{ss}=20\text{ V}$ . (load line 2)

Find the diode voltage and current at the **operating point**.

$$V_{ss} + Ri_D + v_D = 0$$


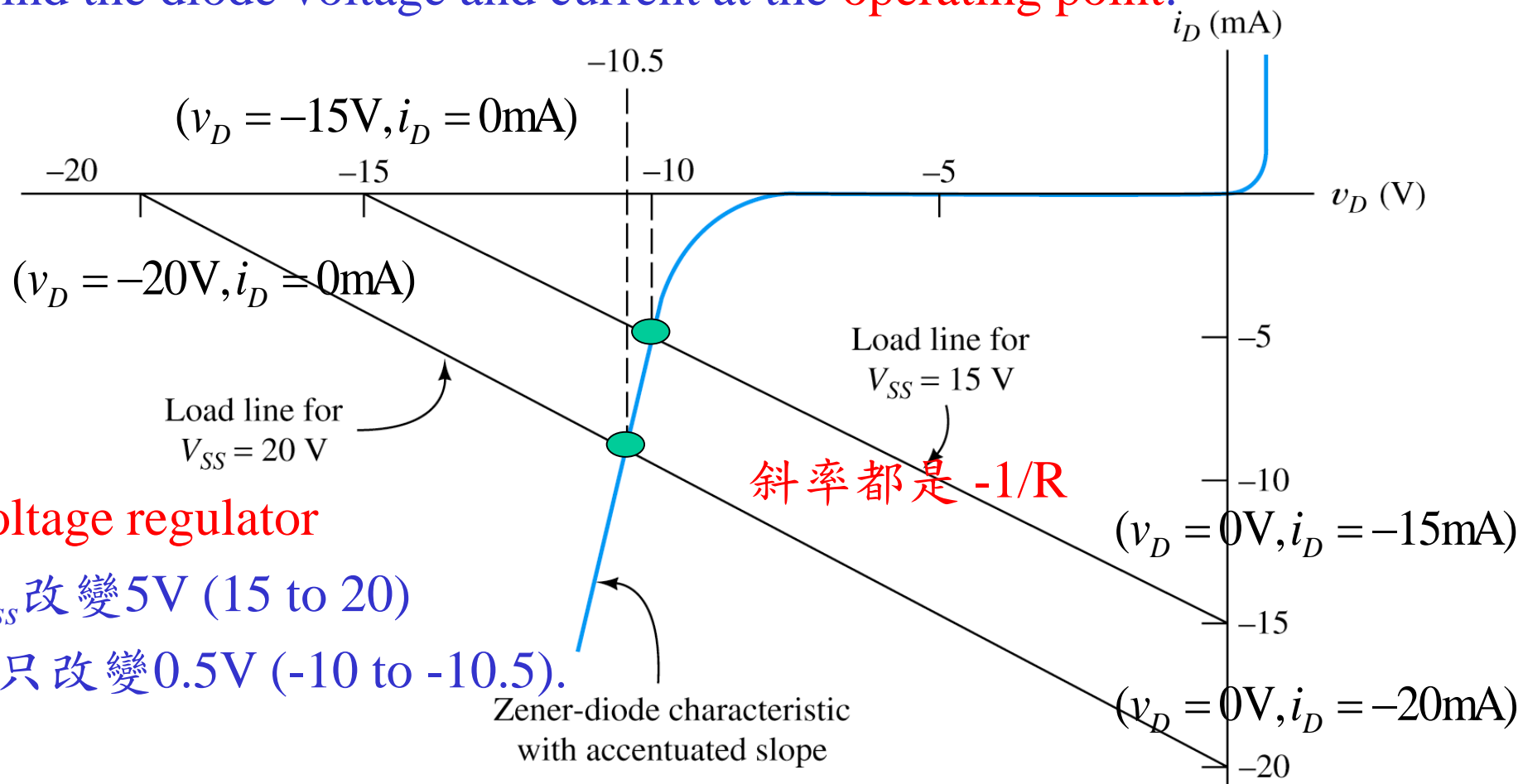



Figure 10.10 See Example 10.3.
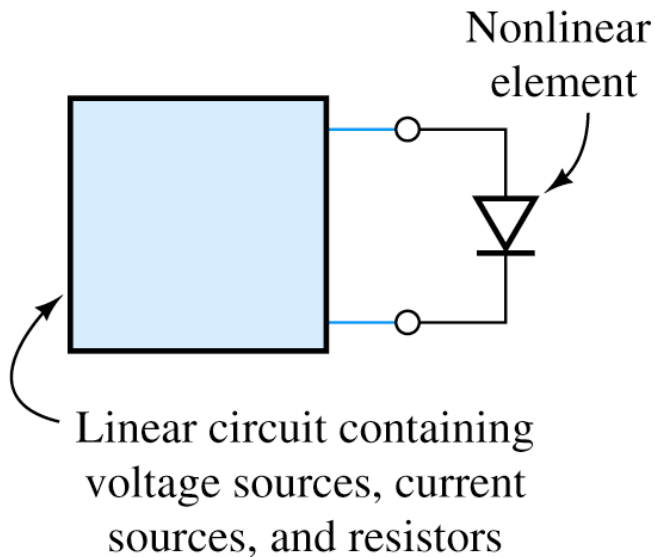
# Load-Line Analysis of Complex Circuits

一個電路包含 **two-terminal 非線性元件** (如 diode)，首先將線性元件部分以戴維寧等效電路簡化後，再利用 load-line analysis 求解。



(a) Original circuit

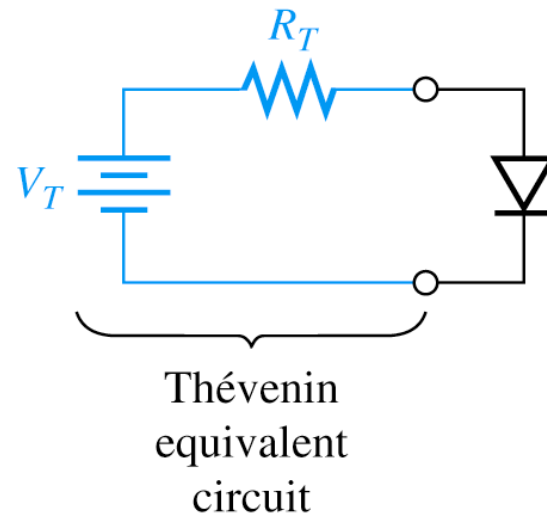


(b) Simplified circuit


## Example 10.4

$V_{SS}=24\text{ V}$ ,  $R=1.2\text{ k}\Omega$ ,  $R_L=6\text{ k}\Omega$ .

Find  $v_L$  and  $I_s$ .

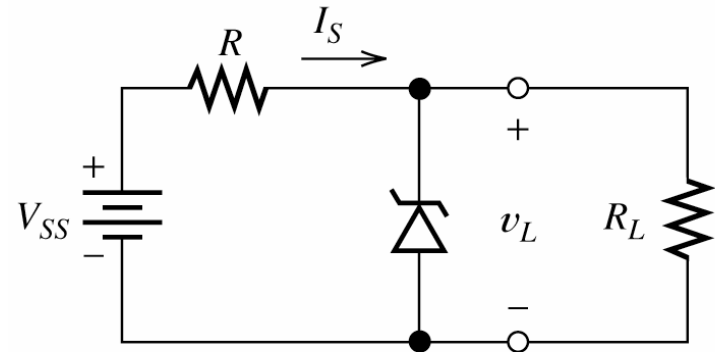


(a) Regulator circuit with load

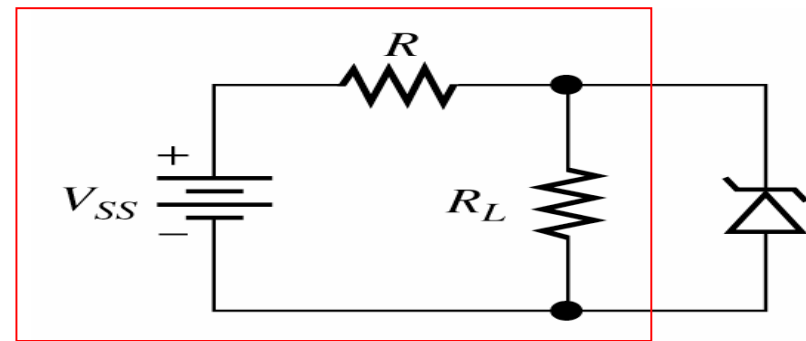

(b) Circuit of (a) redrawn

1. 將線元件與非線性元件分離

2. Thévenin

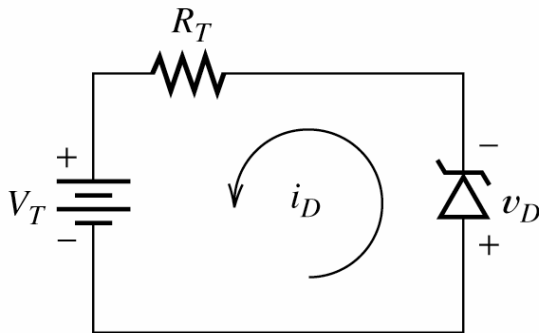

Open-loop voltage


$$V_T = V_{SS} \frac{R_L}{R + R_L} = 20\text{V}$$

Zeroing to find the Thévenin resistance

$$R_T = \frac{RR_L}{R + R_L} = 1\text{k}\Omega$$

### 3. Load-line analysis


$$V_T + R_T i_D + v_D = 0$$

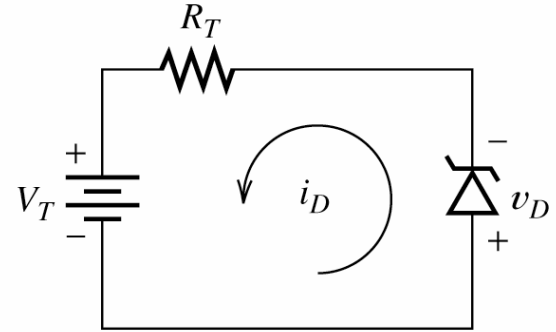

Load-line will pass

$$(v_D = -v_T = -20\text{V}, i_D = 0\text{mA})$$
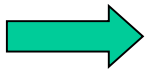
$$(v_D = 0\text{V}, i_D = -\frac{V_T}{R_T} = -20\text{mA})$$



$$V_L = -v_{DQ} = 10.0\text{V}$$

$$I_s = \frac{V_{ss} - v_L}{R} = 11.67\text{mA}$$


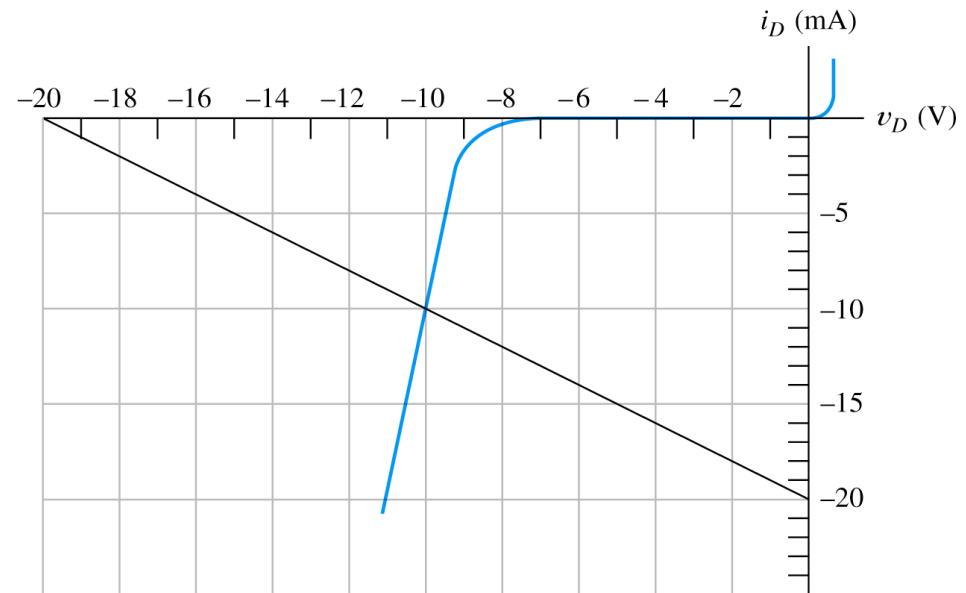


Figure 10.13 Zener-diode characteristic for Example 10.4 and Exercise 10.4.
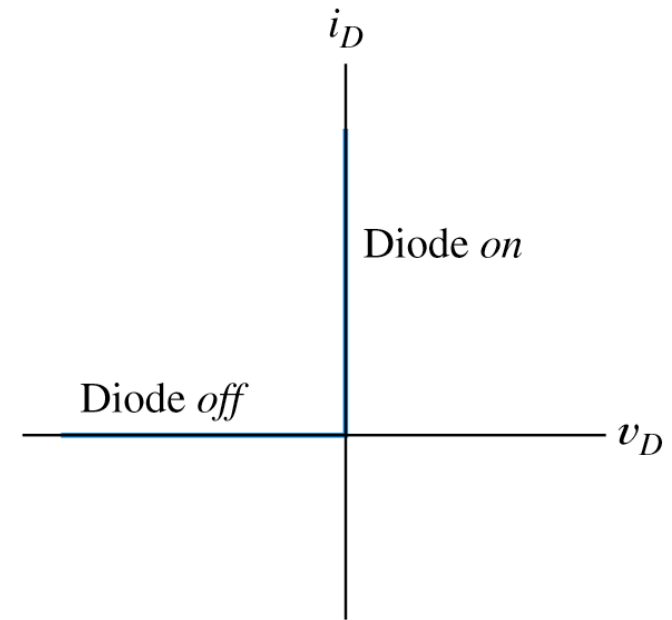
# 10.4 IDEAL-DIODE MODEL

The ideal diode acts as a **short circuit** for **forward** currents and as an **open circuit** with **reverse** voltage applied.



# Assumed States for Analysis of Ideal-Diode Circuits

1. Assume a **state for each diode**, either **on** (i.e., a short circuit) or **off** (i.e., an open circuit). For  $n$  diodes there are  $2^n$  possible combinations of diode states.
2. Analyze the circuit to determine the **current** through the diodes assumed to **be on** and the **voltage** across the diodes assumed to **be off**.




3. **Check** to see if the result is consistent with the assumed state for each diode. **Current** must flow in the **forward** direction for diodes assumed **to be on**. Furthermore, the **voltage** across the diodes assumed **to be off** must be positive at the cathode (i.e., **reverse bias**).

4. If the results are consistent with the assumed states, the analysis is finished. Otherwise, return to step 1 and choose a different combination of diode states.

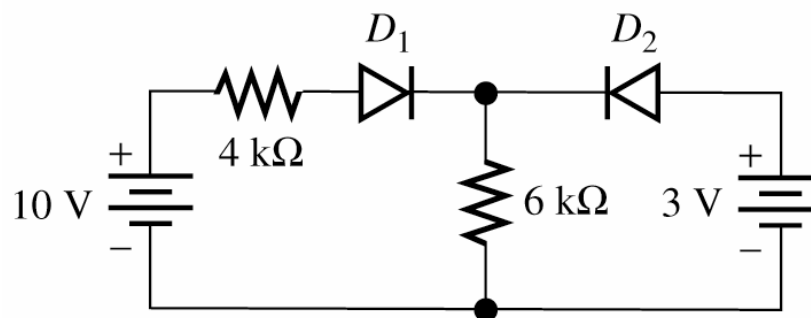
# Example 10.5 Using ideal-diode model to analyze the circuit.

Assuming that  $D_1$  is off and  $D_2$  is on.



(a) Circuit diagram

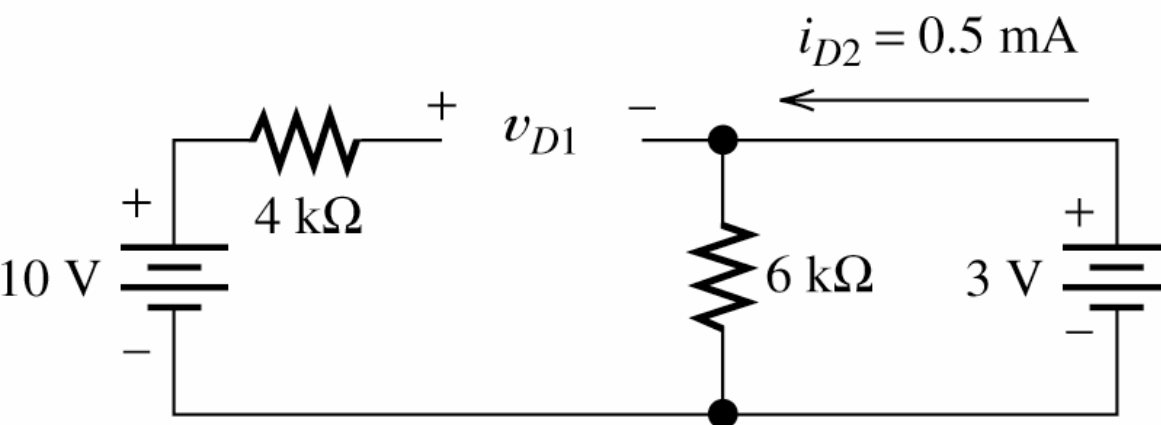1. Assume  $D_1$  is off and  $D_2$  is on



$$i_{D2} = \frac{3}{6k} = 0.5\text{mA}$$


$D_2$  on is correct.

$$v_{D1} = 10 - 3 = 7\text{V}$$


$D_1$  off is NOT correct.

(b) Equivalent circuit assuming  $D_1$  off and  $D_2$  on  
(since  $v_{D1} = +7\text{ V}$ , this assumption is not correct)

2. Assume D1 is on and D2 is off

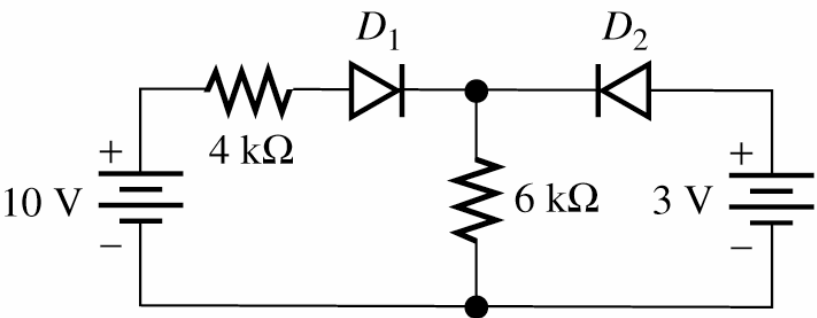

(a) Circuit diagram

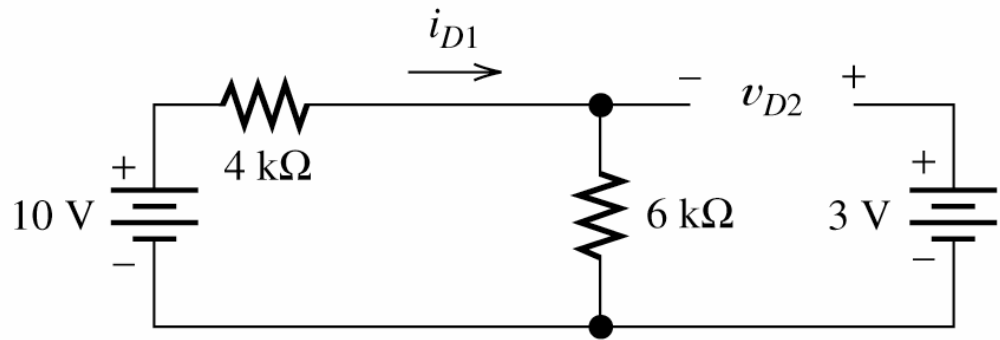

(c) Equivalent circuit assuming  $D_1$  on and  $D_2$  off  
(this is the correct assumption since  $i_{D1}$  turns out to be a positive value and  $v_{D2}$  turns out negative)

$$i_{D1} = \frac{10}{(6 + 4)k} = 1\text{mA}$$

D1 on is correct.

$$6 = -v_{D2} + 3$$

$$v_{D2} = -3\text{V}$$


D2 off is correct.

# 10.5 PIECEWISE-LINEAR DIODE MODELS


一個定電壓與電阻串接，其電壓電流關係式為

$$v = R_a i + V_a$$

I-V圖為斜率 $1/R_a$ 且通過 $(v=V_a, i=0)$ 的直線。

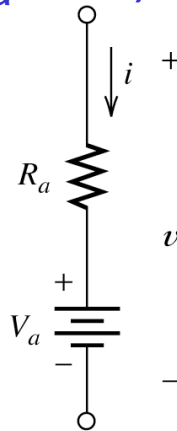


(a) Circuit diagram

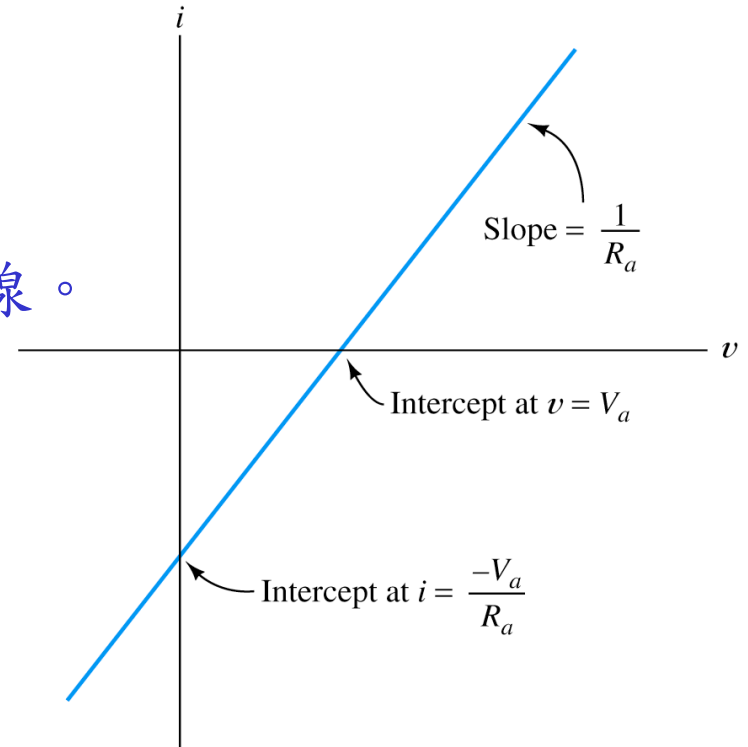


(b) Volt-ampere characteristic

# PIECEWISE-LINEAR DIODE MODELS

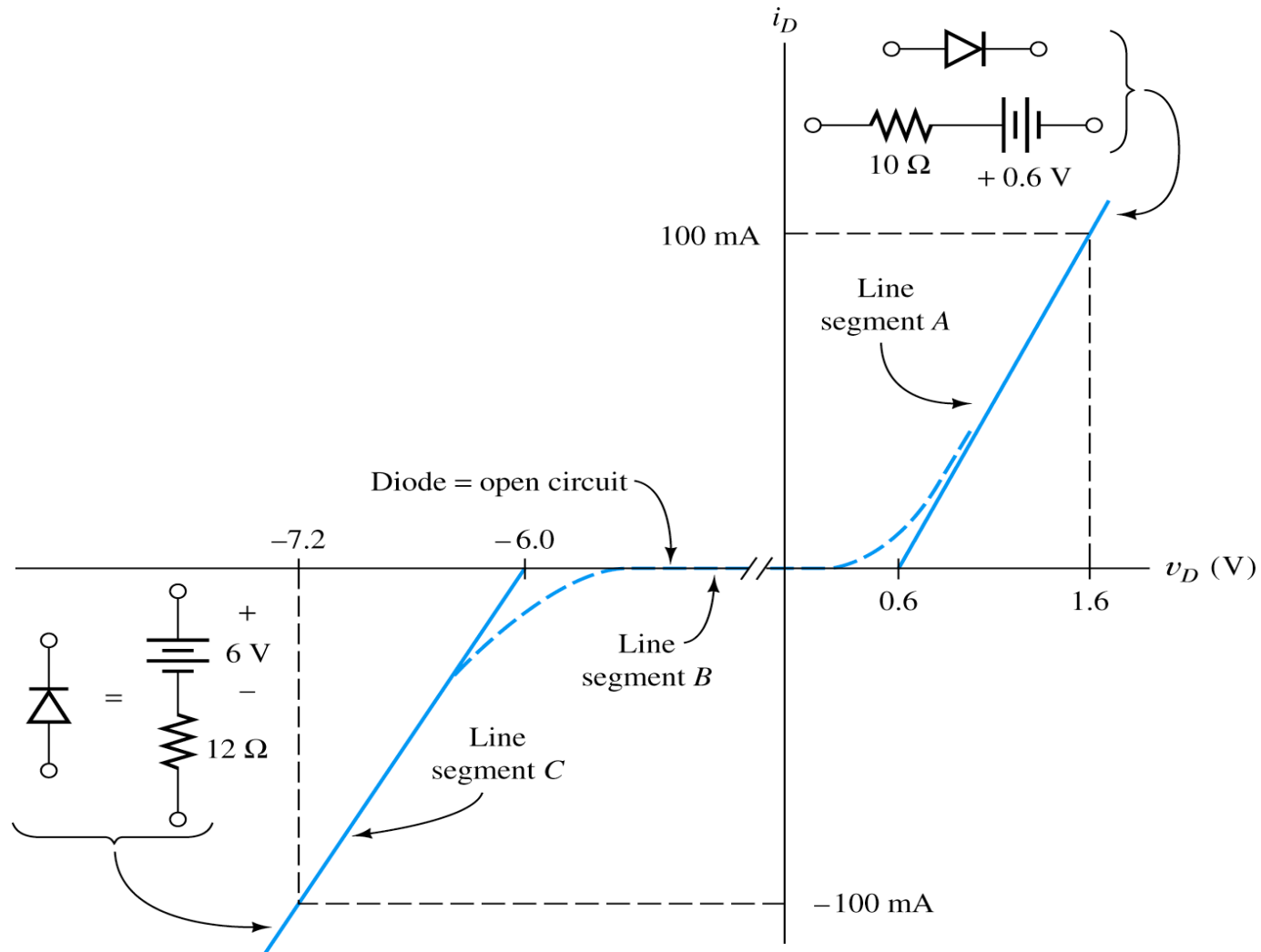

**Figure 10.19** Piecewise-linear models for the diode of Example 10.6.


## Example 10.7

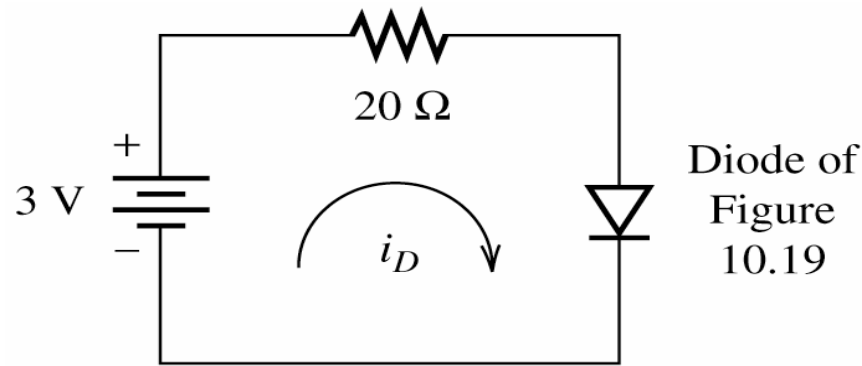

(a) Circuit diagram

1.  $3V > 0.6V$  (turn on voltage of the diode), assume the diode is forward bias.


2. The equivalent circuit

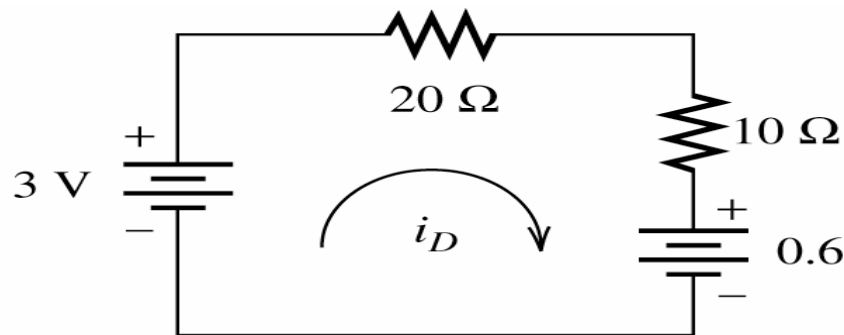

(b) Circuit with diode modeled by the equivalent circuit for the forward-bias region

$$i_D = \frac{3 - 0.6}{20 + 10} = 80\text{mA}$$

# SIMPLE PIECEWISE-LINEAR DIODE MODELS

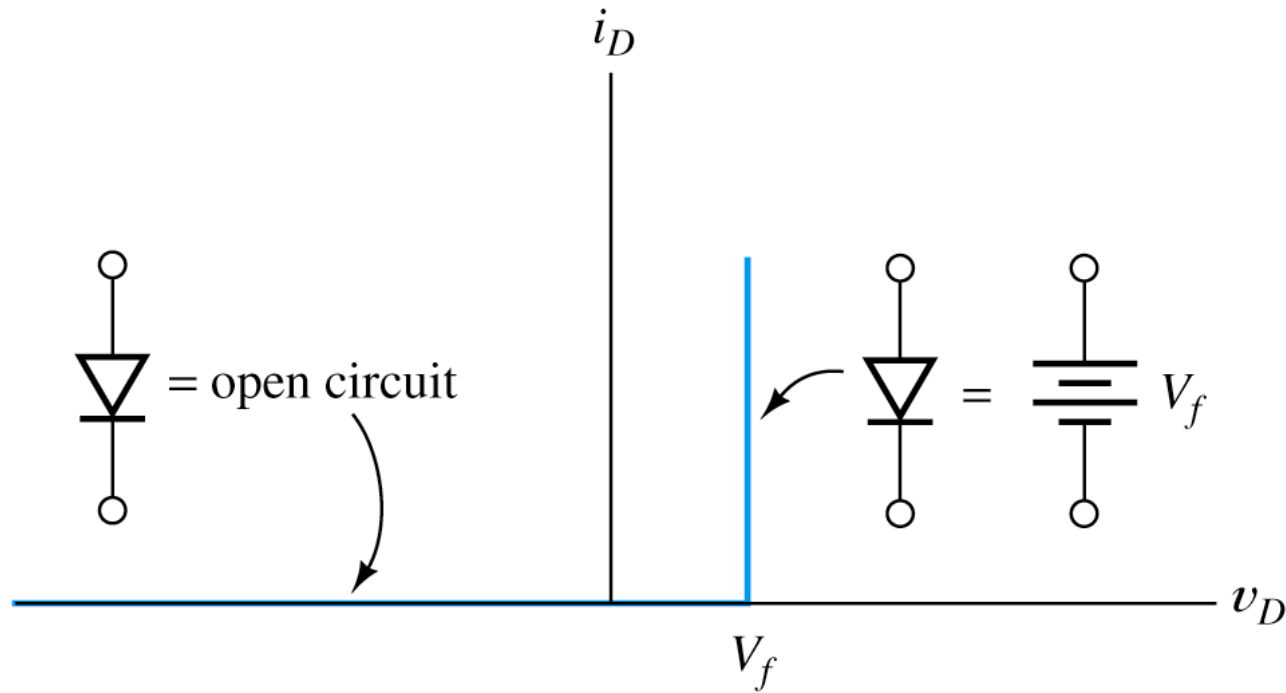

**Figure 10.23** Simple piecewise-linear equivalent for the diode.

# 10.6 Rectifier Circuits (整流器)

## Half-wave rectifier (半波整流器)

只有  $v_s(t) > 0$  才有輸出 (or  $v_s(t) < 0$  時  $v_o(t) = 0$ )

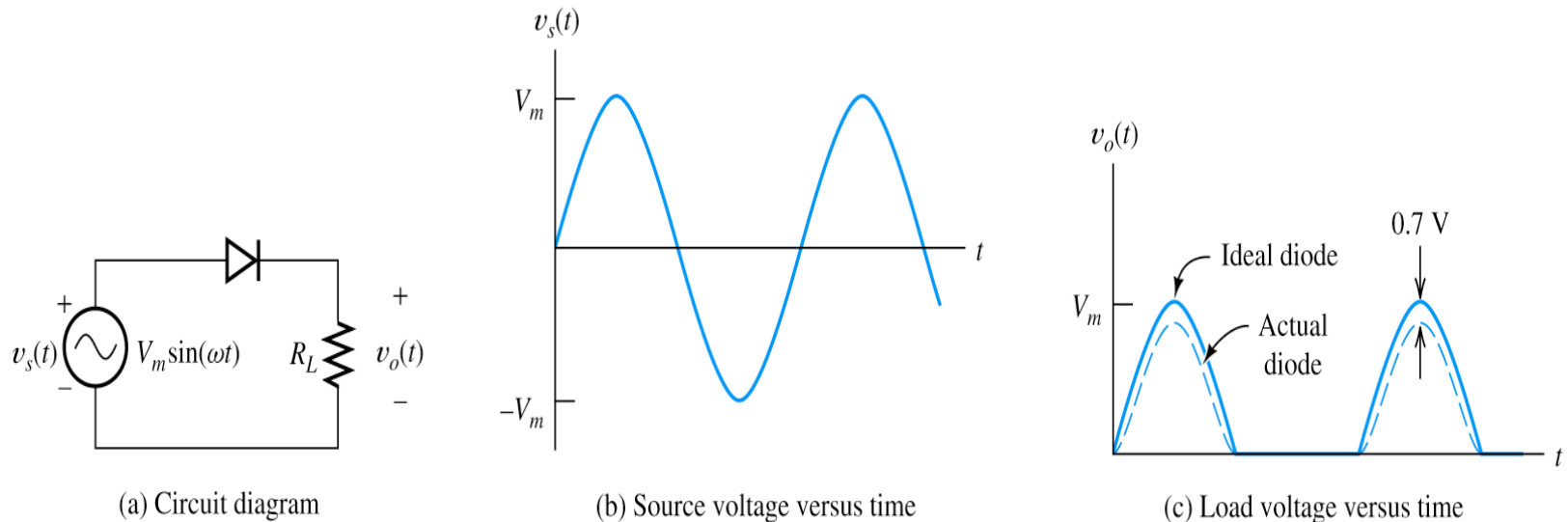


Figure 10.24 Half-wave rectifier with resistive load.



# Battery-Charging Circuit

- 只有  $v_s(t) > V_B$  (battery 電壓) 有電流輸出充電
- 當  $v_s(t) < V_B$ , diode off, 避免電池放電

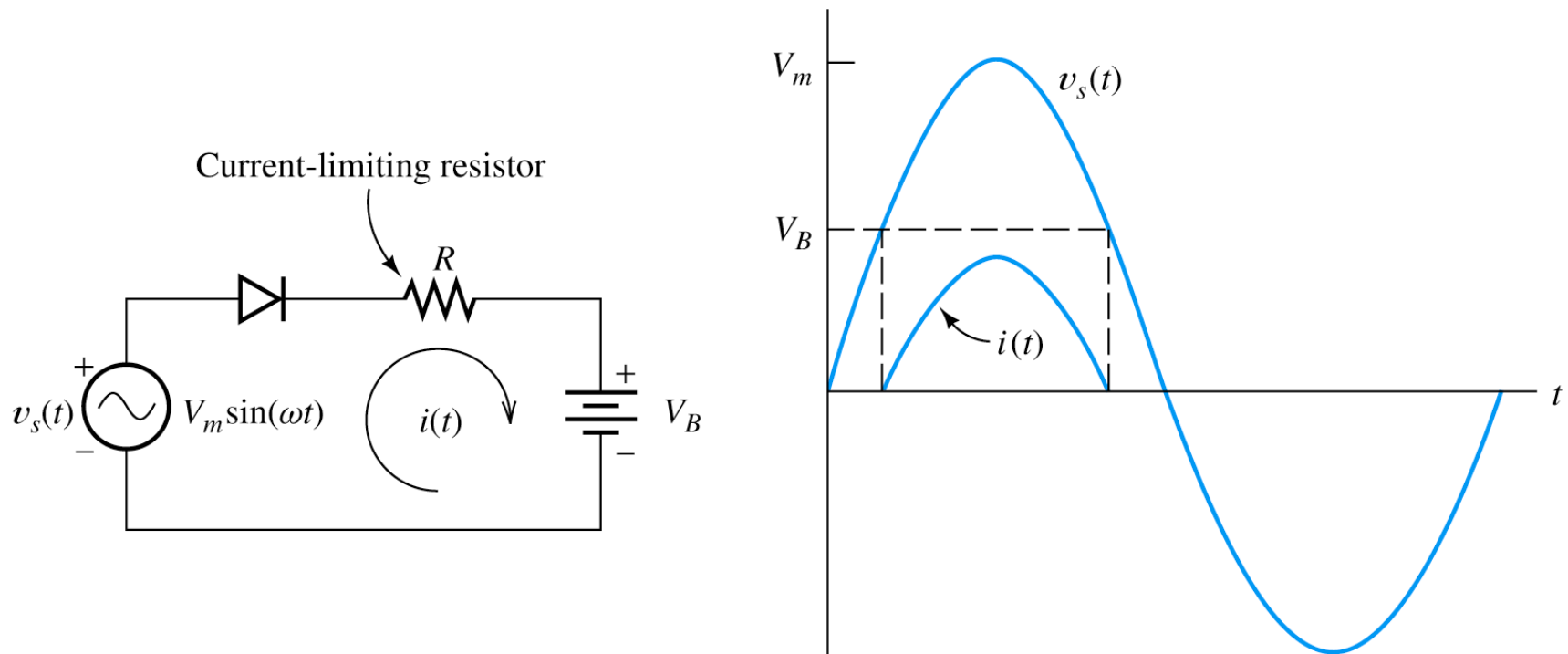


Figure 10.25 Half-wave rectifier used to charge a battery.

# Half-Wave Rectifier (半波整流) with Smoothing Capacitor


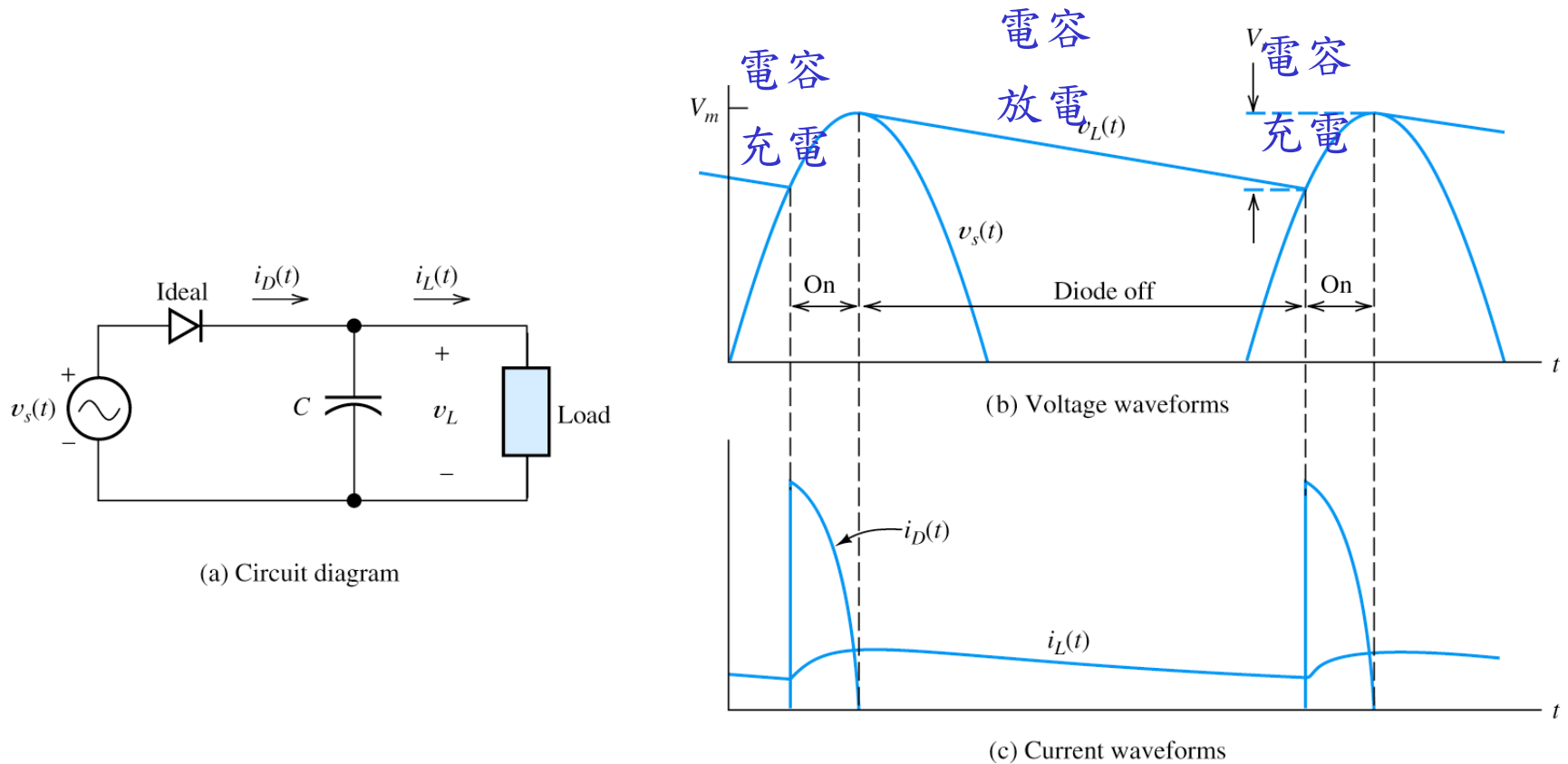



Figure 10.26 Half-wave rectifier with smoothing capacitor.

# Full-Wave Rectifier (全波整流)

- 利用兩個電壓源兩個diode

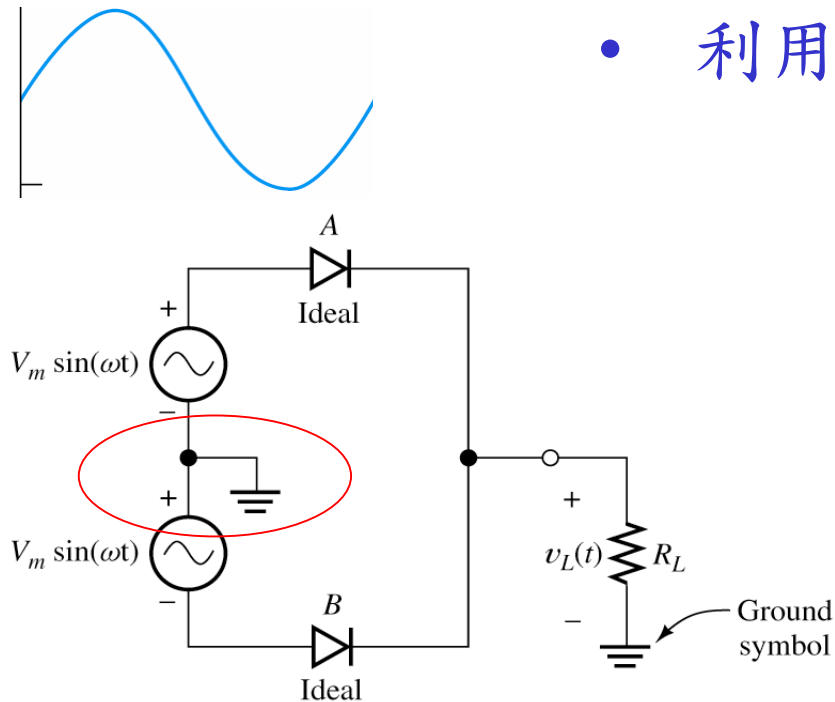

(a) Circuit diagram

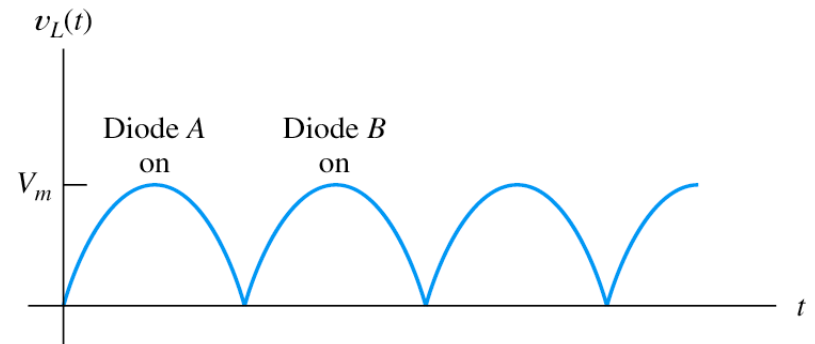

(b)

Figure 10.27 Full-wave rectifier.

- 利用一個電壓源


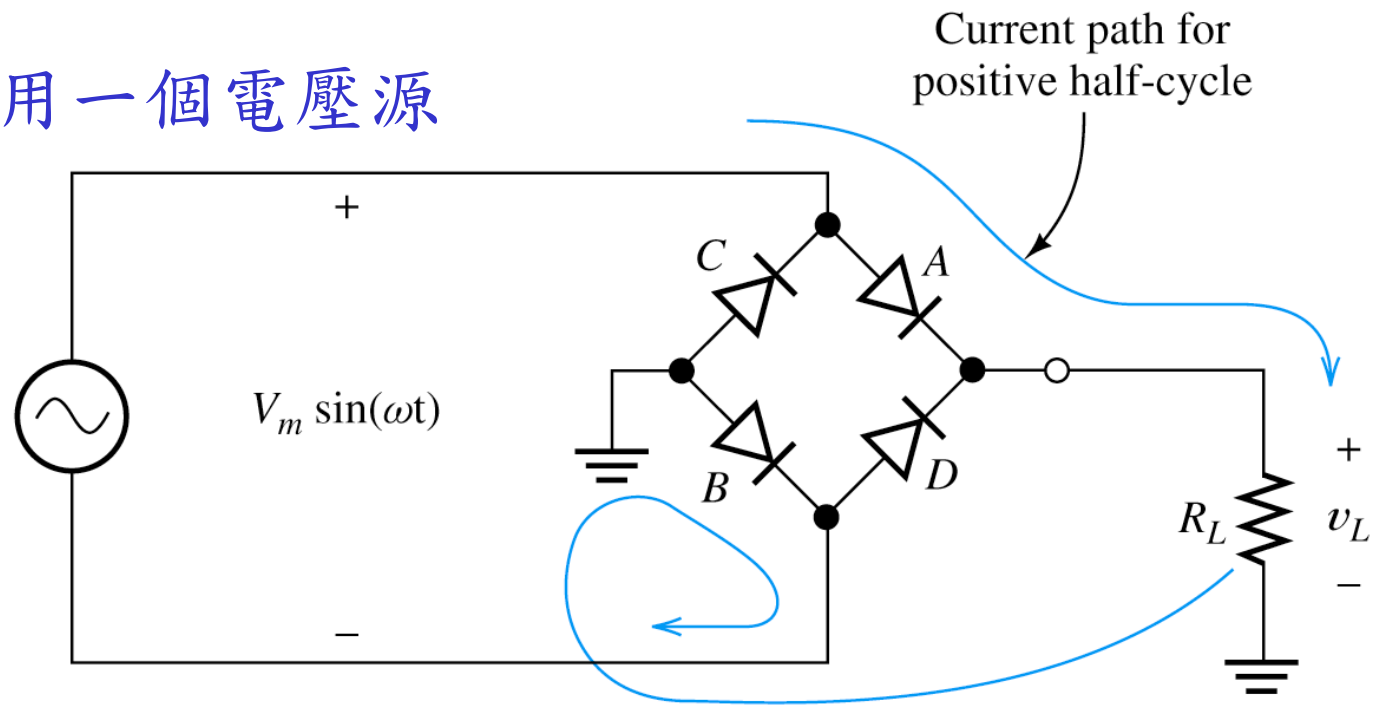


Figure 10.28 Diode-bridge full-wave rectifier.


Full-Wave Rectifier: 用到 4 個 diodes

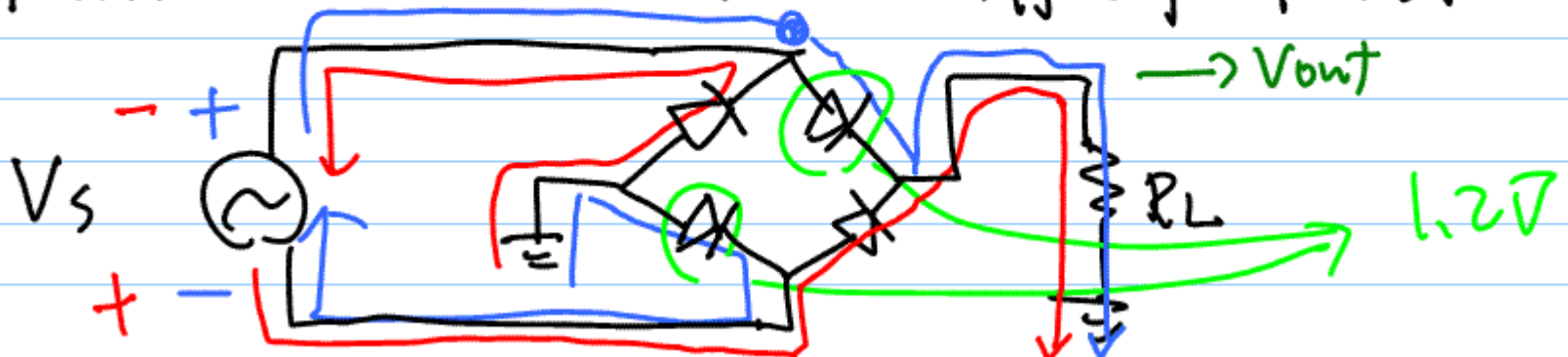


# 10.7 Wave-Shaping Circuits
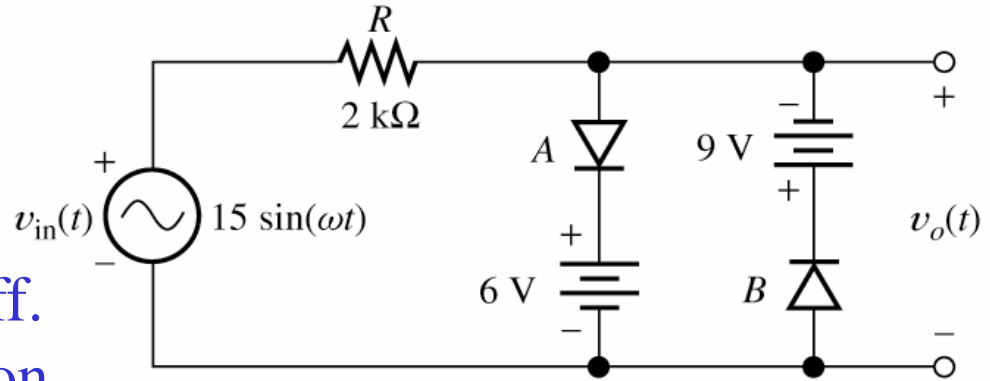
## Clipper Circuits 剪波器


- 當  $v_{in} > 6V$  , DA on, DB off.
- 當  $v_{in} < -9V$  , DA off, DB on.
- 當  $-9V < v_{in} < 6V$  , DA&DB off.



(a) Circuit diagram

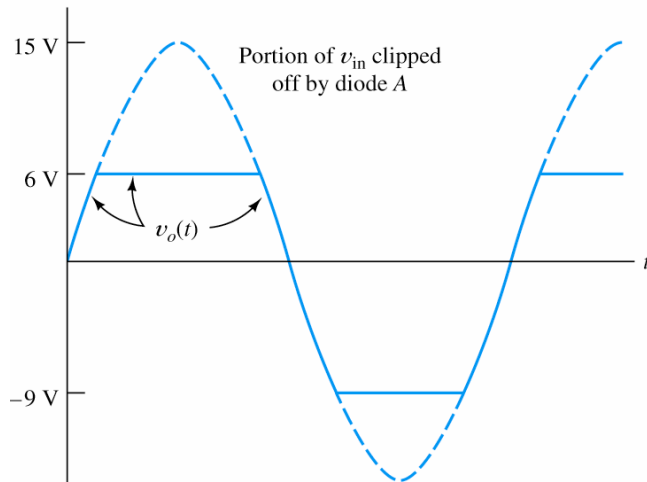


(b) Waveforms

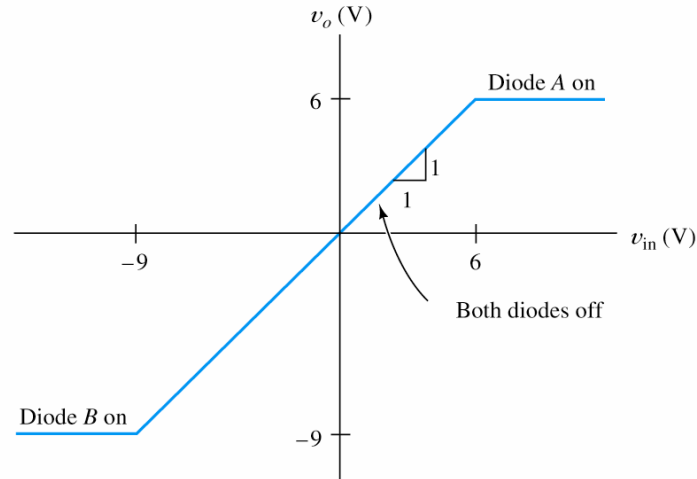

(c) Transfer characteristic
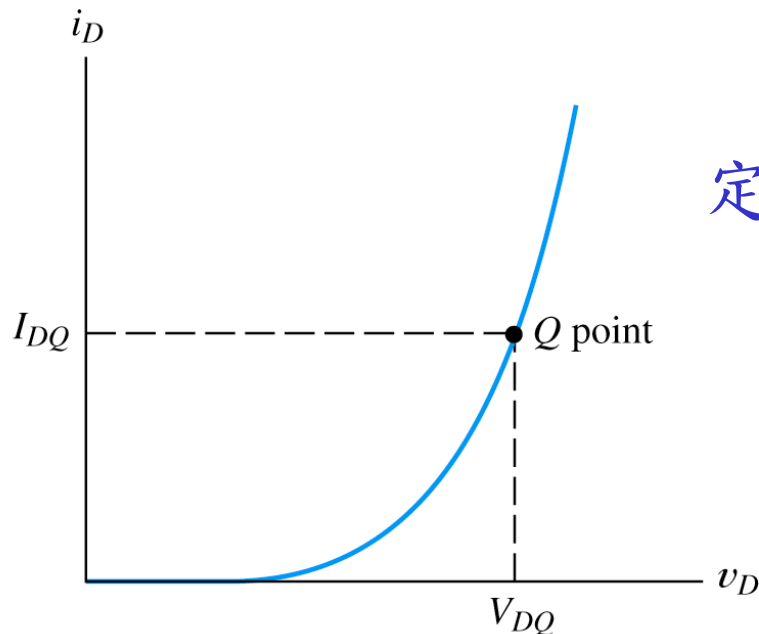
# 10.8 LINEAR SMALL-SIGNAL EQUIVALENT CIRCUITS

- 分析在靜態操作點(quiescent point, Q point)上, 電壓微幅改變(small signal)時, 電流的變化。
- The small-signal equivalent circuit for a diode is a **resistance**.



$$\Delta i_D \cong \left( \frac{di_D}{dv_D} \right)_Q \Delta v_D$$

定義dynamic resistance of the diode

$$r_d \cong \left[ \left( \frac{di_D}{dv_D} \right)_Q \right]^{-1}$$

$$i_d = \frac{v_d}{r_d}$$



$$r_d \cong \left[ \left( \frac{di_D}{dv_D} \right)_Q \right]^{-1} = ?$$

$$i_D = I_s \left[ \exp\left(\frac{v_D}{nV_T}\right) - 1 \right] \quad (\text{Shockley Equation})$$


$$\frac{di_D}{dv_D} = I_s \frac{1}{nV_T} \exp\left(\frac{v_D}{nV_T}\right)$$

At Q-point  $v_D = v_{DQ}$

$$\left( \frac{di_D}{dv_D} \right)_Q = I_s \frac{1}{nV_T} \exp\left(\frac{v_{DQ}}{nV_T}\right)$$

At  $v_D = v_{DQ}$ , determine  $i_{DQ}$
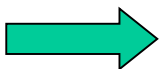
$$I_{DQ} \cong I_s \exp\left(\frac{v_{DQ}}{nV_T}\right) \quad (\text{將 } v_D = v_{DQ} \text{ 代入 Shockley Equation, 且忽略 -1 項})$$




$$\left( \frac{di_D}{dv_D} \right)_Q = I_S \frac{1}{nV_T} \exp\left( \frac{v_{DQ}}{nV_T} \right) = \frac{I_{DQ}}{nV_T}$$

$$r_d = \frac{nV_T}{I_{DQ}}$$

•  $I_{DQ}$  越大，斜率  
( $1/r_d$ ) 越大， $r_d$  越小

• 假設固定 ac voltage  $v_d$ ，  
Q 點越高 ( $v_D$  越大)，ac  
current  $i_d$  越大

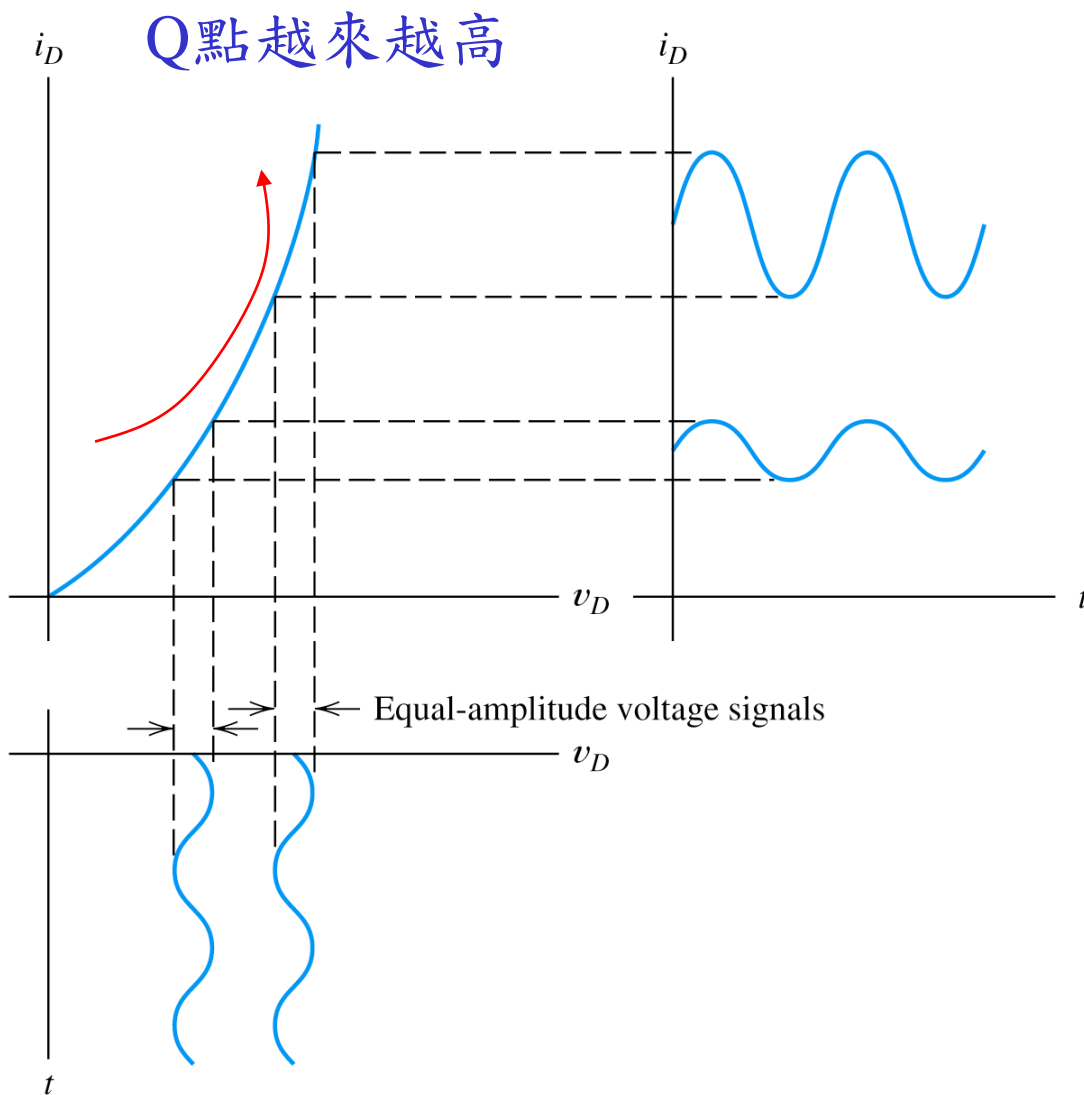

**Figure 10.38** As the  $Q$  point moves higher, a fixed-amplitude ac voltage produces an ac current of larger amplitude.



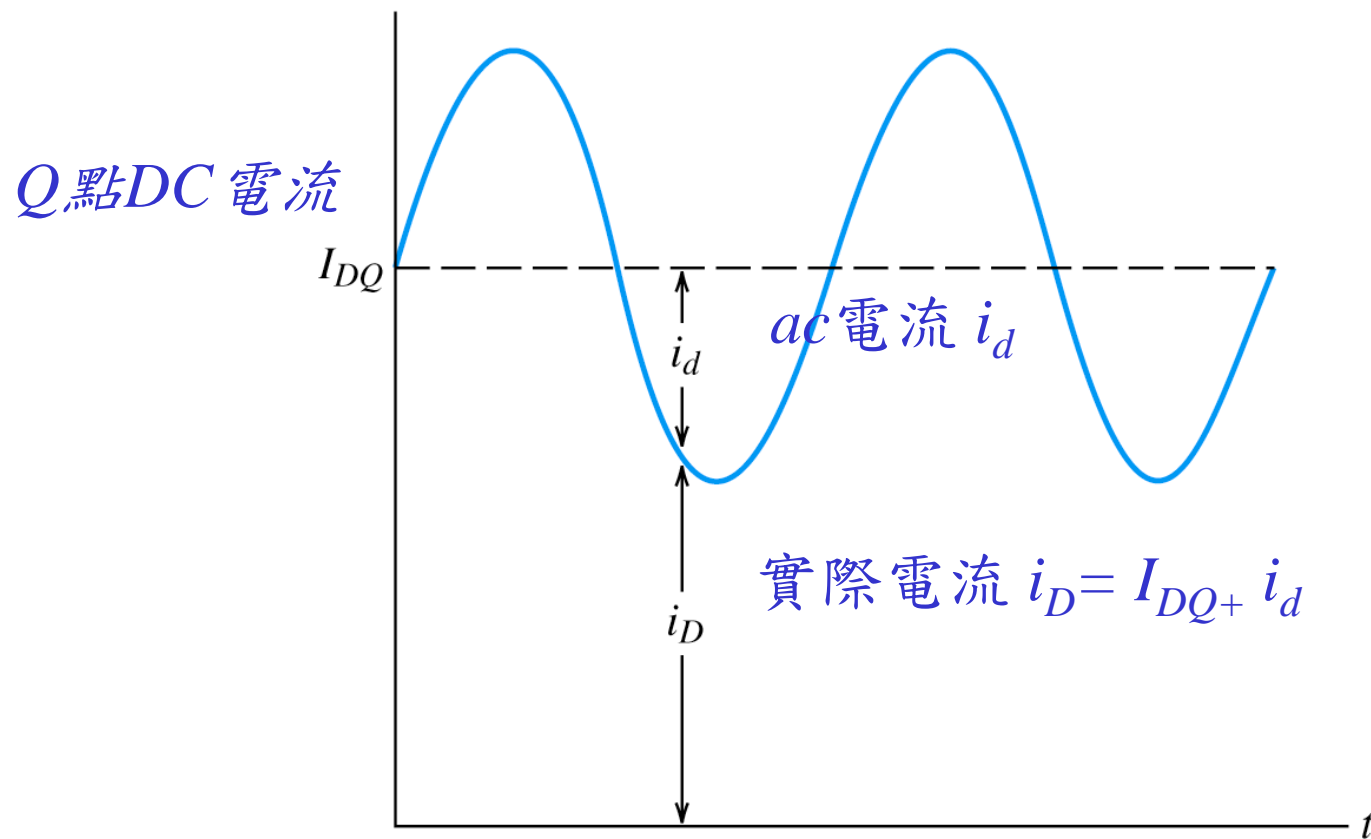


Figure 10.39 Illustration of diode currents.

# Notation for Currents and Voltages in Electronic Circuits

- $v_D$  and  $i_D$  represent the **total instantaneous diode voltage and current**. At times, we may wish to emphasize the time-varying nature of these quantities, and then we use  $v_D(t)$  and  $i_D(t)$
- $V_{DQ}$  and  $I_{DQ}$  represent the **dc diode current and voltage** at the quiescent point.

- $v_d$  and  $i_d$  represent the (small) ac signals. If we wish to emphasize their time varying nature, we use  $v_d(t)$  and  $i_d(t)$ .