

Chapter 5


Steady-State Sinusoidal Analysis

5.1 Sinusoidal Currents and Voltages

A sinusoidal voltage

$$v(t) = V_m \cos(\omega t + \theta)$$

Peak value Phase angle(相位)

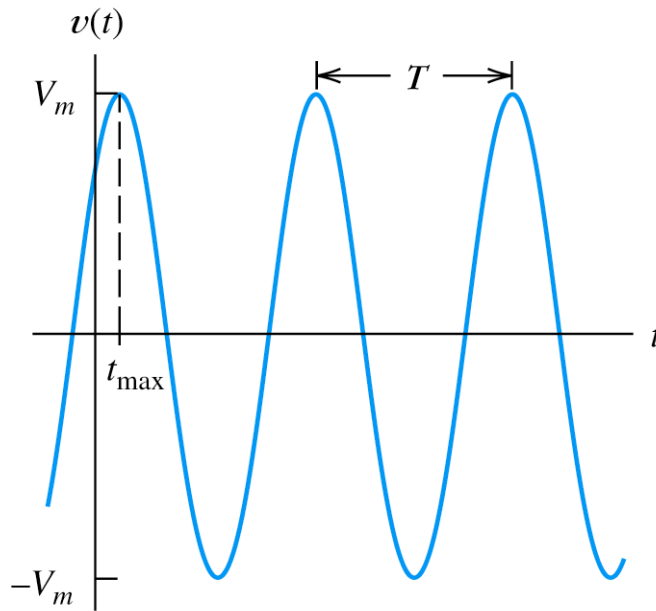

ω Angular frequency
(角頻率, rad/sec)

T Period
(週期)

$$\omega T = 2\pi$$

$f = \frac{1}{T}$ frequency
(頻率, Hz)

$$\omega = 2\pi f = \frac{2\pi}{T}$$

Figure 5.1 A sinusoidal voltage waveform given by $v(t) = V_m \cos(\omega t + \theta)$.

Note: Assuming that θ is in degrees, we have $t_{\max} = \frac{-\theta}{360} \times T$.

For the waveform shown, θ is -45° .

V_m is the **peak value**

ω is the **angular frequency** in radians per second

θ is the **phase angle** ($0^\circ \sim 360^\circ$)

T is the **period**


Frequency $f = \frac{1}{T}$

Angular frequency $\omega = \frac{2\pi}{T} = 2\pi f$

$$\omega t + \theta$$

Radians Degree
 $(0 \sim 2\pi)$ $(0^\circ \sim 360^\circ)$

For uniformity, we express sinusoidal functions by cosine function.

 $\sin(z) = \cos(z - 90^\circ)$

Ex

$$\begin{aligned} v_x(t) &= 10 \sin(200t + 30^\circ) = 10 \cos(200t + 30^\circ - 90^\circ) \\ &= 10 \cos(200t - 60^\circ) \end{aligned}$$

Root-Mean-Square (均方根)Values

$$V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$I_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$

Root-Mean-Square (均方根) Values

假設電壓源($v(t)$)週期為 T , 與電阻連接, 計算其平均功率 P_{avg}

$$p(t) = \frac{v^2(t)}{R}$$

$$E_T = \int_0^T p(t) dt$$

$$P_{avg} = \frac{E_T}{T} = \frac{1}{T} \int_0^T p(t) dt = \frac{1}{T} \int_0^T \frac{v^2(t)}{R} dt = \frac{\left[\sqrt{\frac{1}{T} \int_0^T v^2(t) dt} \right]^2}{R}$$

$$\longrightarrow P_{avg} = \frac{V_{rms}^2}{R} = I_{rms}^2 R$$

RMS Value of a Sinusoid

$$v(t) = V_m \cos(\omega t + \theta)$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V_m^2 \cos^2(\omega t + \theta) dt}$$

$$\because \cos^2(z) = \frac{1}{2} + \frac{1}{2} \cos(2z)$$

$$V_{rms} = \sqrt{\frac{V_m^2}{2T} \int_0^T [1 + \cos(2\omega t + 2\theta)] dt}$$

RMS Value of a Sinusoid

$$V_{rms} = \sqrt{\frac{V_m^2}{2T} \left[t + \frac{1}{2\omega} \sin(2\omega t + 2\theta) \right]_0^T}$$

$$V_{rms} = \sqrt{\frac{V_m^2}{2T} \left[T + \frac{1}{2\omega} \sin(2\omega T + 2\theta) - \frac{1}{2\omega} \sin(2\theta) \right]}$$

$$\omega = \frac{2\pi}{T}$$

$$\begin{aligned} \therefore \quad & \frac{1}{2\omega} \sin(2\omega T + 2\theta) - \frac{1}{2\omega} \sin(2\theta) = \frac{1}{2\omega} \sin(4\pi + 2\theta) - \frac{1}{2\omega} \sin(2\theta) \\ & = \frac{1}{2\omega} \sin(2\theta) - \frac{1}{2\omega} \sin(2\theta) \\ & = 0 \end{aligned}$$

$$\rightarrow V_{rms} = \frac{V_m}{\sqrt{2}}$$

RMS Value of a Sinusoid

$$V_{\text{rms}} = \frac{V_m}{\sqrt{2}}$$

The rms value for a sinusoid is the **peak value divided by the square root of two**. This is **not true for other periodic waveforms** such as square waves or triangular waves.


Example 5.1 Power delivered to a resistance by a sinusoidal source

- **A voltage** $v(t) = 100\cos(100\pi t)$ is applied to a $50\text{-}\Omega$ resistance.

Find

- the rms value of the voltage.
- Find the average power delivered to the resistance.
- Find the power as a function of time and sketch to scale.

1. $\omega = 100\pi = \frac{2\pi}{T} \quad \longrightarrow \quad T = \frac{2\pi}{100\pi} = 20\text{ms}$

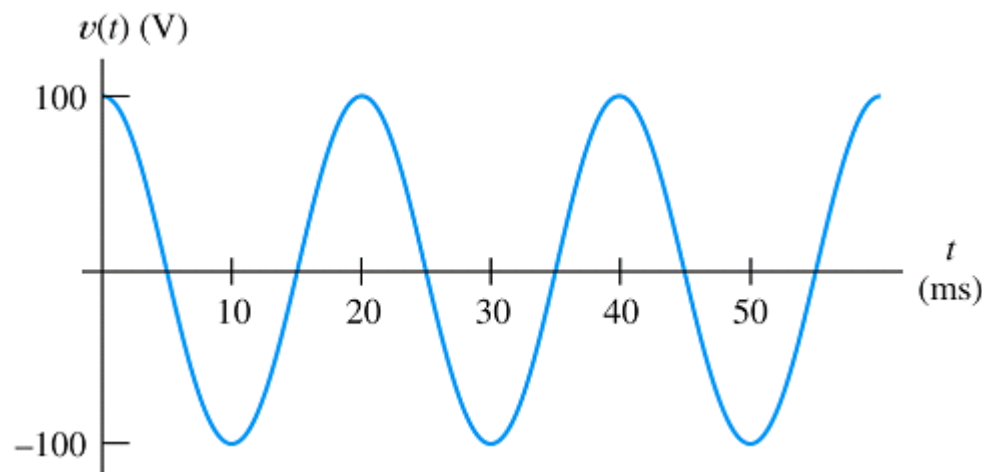

Example 5.1 Power delivered to a resistance by a sinusoidal source

2. The rms value of the voltage

$$\because V_m = 100V \longrightarrow V_{rms} = \frac{V_m}{\sqrt{2}} = 70.71 \text{ V}$$

3. The average power


$$P_{avg} = \frac{V_{rms}^2}{R} = \frac{(70.71)^2}{50} = 100W$$

Example 5.1 Power delivered to a resistance by a sinusoidal source

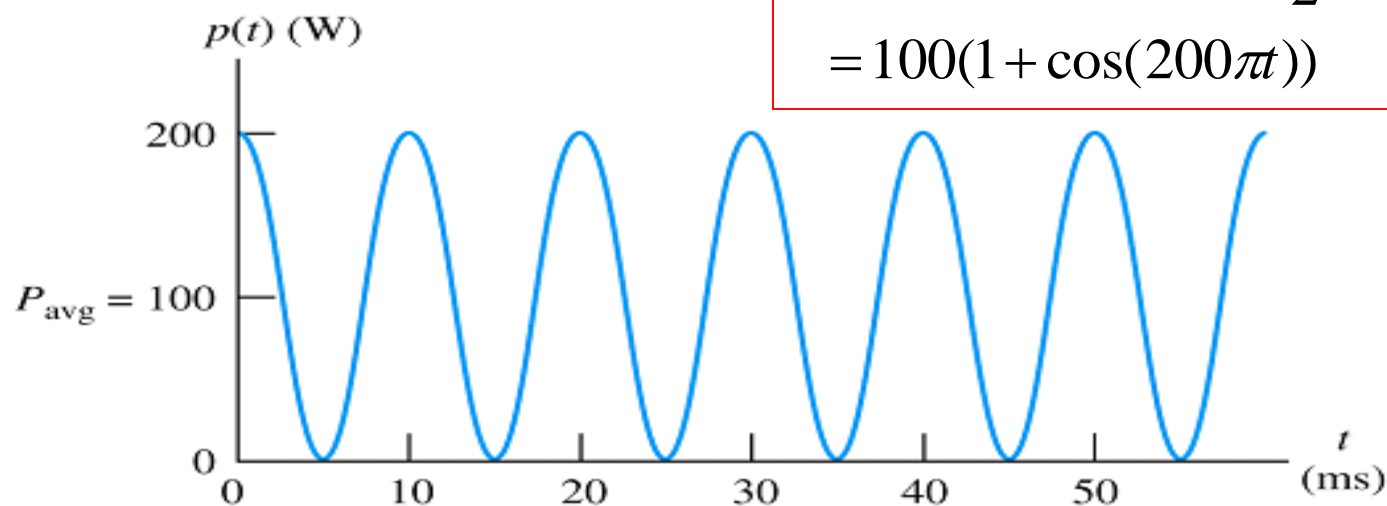4. The power as a function of time is

$$p(t) = \frac{v^2(t)}{R} = \frac{100^2 \cos^2(100\pi t)}{50} = 200 \cos^2(100\pi t) \text{ W}$$

$$\begin{aligned} 200 \cos^2(100\pi t) &= \frac{200}{2} (1 + \cos(200\pi t)) \\ &= 100(1 + \cos(200\pi t)) \end{aligned}$$



5.2 Phasors (相量)

Refer to Appendix A Complex Numbers

Phasor Definition

- Phasor 以複數(complex numbers)來表示 sinusoidal voltages or currents. Ex.

$$\text{Phasor : } \mathbf{V} = V_m \angle \theta$$

- Magnitude (V_1) 代表最大振幅(peak value).
- Angle (θ_1)代表相位(phase).

A sinusoidal **cosine** voltage

$$v_1(t) = V_1 \cos(\omega t + \theta_1) \quad (\text{Time function, 時間函數})$$

其 phasor 為

$$\text{Phasor : } \mathbf{V}_1 = V_1 \angle \theta_1$$

A sinusoidal **sine** voltage

$$v_2(t) = V_2 \sin(\omega t + \theta_2)$$

∴

$$\sin(z) = \cos(z - 90^\circ)$$



$$v_2(t) = V_2 \cos(\omega t + \theta_2 - 90^\circ)$$



$$\mathbf{V}_2 = V_2 \angle \theta_2 - 90^\circ$$

For sinusoidal currents

$$i_1 = I_1 \cos(\omega t + \theta_1)$$

phasor $\mathbf{I}_1 = I_1 \angle \theta_1$

$$i_2 = I_2 \sin(\omega t + \theta_2)$$

phasor $\mathbf{I}_2 = I_2 \angle \theta_2 - 90^\circ$

Adding Sinusoids Using Phasors

Step 1: Determine the phasor for each term.

Step 2: Add the phasors using **complex arithmetic**.

Step 3: Convert the sum to **polar form**.

Step 4: Write the result as a **time function**.

Using Phasors to Add Sinusoids

$$v_1(t) = 20 \cos(\omega t - 45^\circ)$$

$$v_2(t) = 10 \sin(\omega t + 60^\circ)$$

To find $v_s(t) = v_1(t) + v_2(t)$.

1. The phasors

$$\mathbf{V}_1 = 20 \angle -45^\circ \quad \mathbf{V}_2 = 10 \angle -30^\circ$$

2. Complex arithmetic

$$\mathbf{V}_1 = x_1 + jy_1 = 20 \cos(-45^\circ) + j20 \sin(-45^\circ) = 14.14 - j14.14$$

$$\mathbf{V}_2 = x_2 + jy_2 = 10 \cos(-30^\circ) + j10 \sin(-30^\circ) = 8.66 - j5$$

$$\mathbf{V}_s = 14.14 - j14.14 + 8.66 - j5 = 22.80 - j19.14$$

Using Phasors to Add Sinusoids

3. Convert the sum to polar form

$$V_s = 22.80 - j19.14$$

$$V_m = \sqrt{(22.80)^2 + (19.14)^2} = 29.77$$

$$\theta = \arctan\left(\frac{-19.14}{22.80}\right) = -40.01^\circ$$

$$\longrightarrow V_s = 29.77 \angle -40.01^\circ$$

$$v_s(t) = 29.77 \cos(\omega t - 40.01^\circ)$$

Using Euler's formula to Add Sinusoids

$$v_1(t) = 20 \cos(\omega t - 45^\circ) = 20 \operatorname{Re}(e^{j(\omega t - 45^\circ)})$$

$$v_2(t) = 10 \sin(\omega t + 60^\circ) = 10 \cos(\omega t - 30^\circ) = 10 \operatorname{Re}(e^{j(\omega t - 30^\circ)})$$

$$v_s(t) = v_1(t) + v_2(t) = \operatorname{Re}\left[(20e^{-j45^\circ} + 10e^{-j30^\circ})e^{j\omega t}\right]$$

$$20e^{-j45^\circ} + 10e^{-j30^\circ} = 29.77 \angle -40.01^\circ = 29.77e^{-j40.01^\circ}$$

polar form

$$v_s(t) = \operatorname{Re}\left[29.77e^{-j40.01^\circ}e^{j\omega t}\right] = 29.77 \cos(\omega t - 40.11^\circ)$$

Visualization of Sinusoids

A sinusoidal voltage $v(t) = V_m \cos(\omega t + \theta)$

Exponential form $v(t) = \text{Re}[V_m e^{j(\omega t + \theta)}]$

Complex Polar form $V_m e^{j(\omega t + \theta)} = V_m \angle \omega t + \theta$


- Sinusoids 可視為複數向量(complex vectors) 隨時間改變在實數軸的投影量。

$$V_m e^{j(\omega t + \theta)} = V_m \angle \omega t + \theta$$

可視為 Vector with length V_m 以 ω rad/s 角速度 (angular velocity) 在複數平面以逆時針 (counterclockwise) 方向旋轉。

• $v(t)$ 為 $V_m e^{j(\omega t + \theta)}$ 在實數軸的投影量。

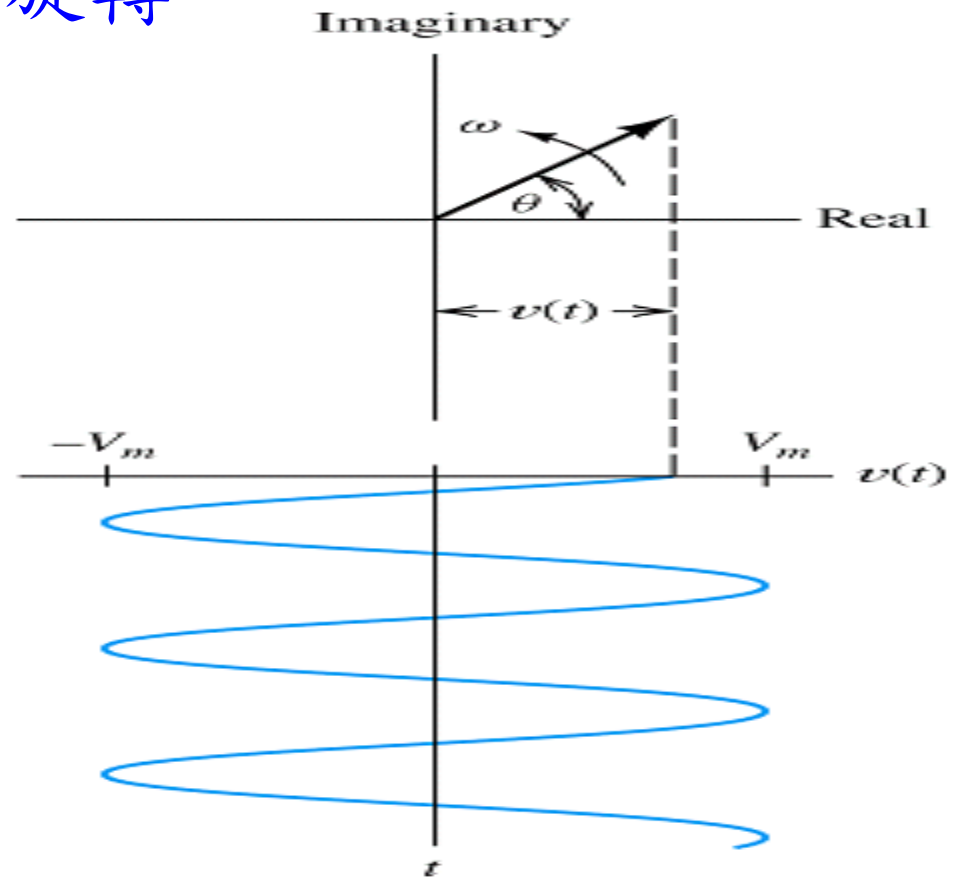• $v(t)$ 的 Phasor $V_m \angle \theta$ 為 $V_m e^{j(\omega t + \theta)}$ 在 $t = 0$ 時的向量。



Phasors as Rotating Vectors

- Sinusoids can be visualized as the **real-axis projection** of vectors **rotating** in the **complex plane**.
- The **phasor** for a sinusoid is a snapshot of the corresponding rotating vector **at $t = 0$** .

Phase Relationships from Phasors

1. To determine phase relationships from a phasor diagram, consider the **phasors to rotate counterclockwise**.
2. Then when standing at a fixed point, if V_1 **arrives first** followed by V_2 after a rotation of θ , we say that **V_1 leads V_2** by θ .
3. Alternatively, we could say that **V_2 lags V_1** by θ . (Usually, we take θ as the smaller angle between the two phasors.)

Phase Relationships from Phasors

V_1 leads V_2 by 60° .

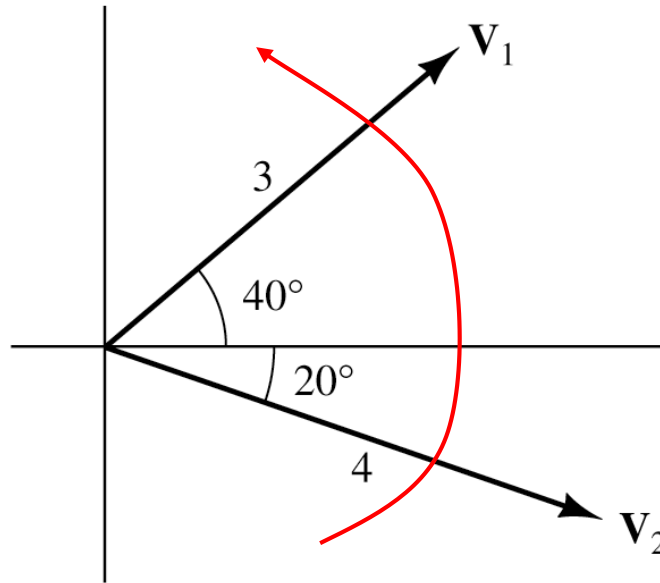


Figure 5.5 Because the vectors rotate counterclockwise, v_1 leads v_2 by 60° (or, equivalently, v_2 lags v_1 by 60° .)

Phase Relationships from Time Functions

To determine **phase relationships** between sinusoids from their **plots versus time**,

1. find the **shortest time interval t_p** between **positive peaks** of the two waveforms.


2. Then, the phase angle is

$$\theta = (t_p / T) \times 360^\circ.$$

3. If the peak of **$v_1(t)$ occurs first**, we say that **$v_1(t)$ leads $v_2(t)$** or that $v_2(t)$ lags $v_1(t)$.

$v_1(t)$ leads $v_2(t)$ by θ (60°).

$$\theta = (t_p/T) \times 360^\circ.$$

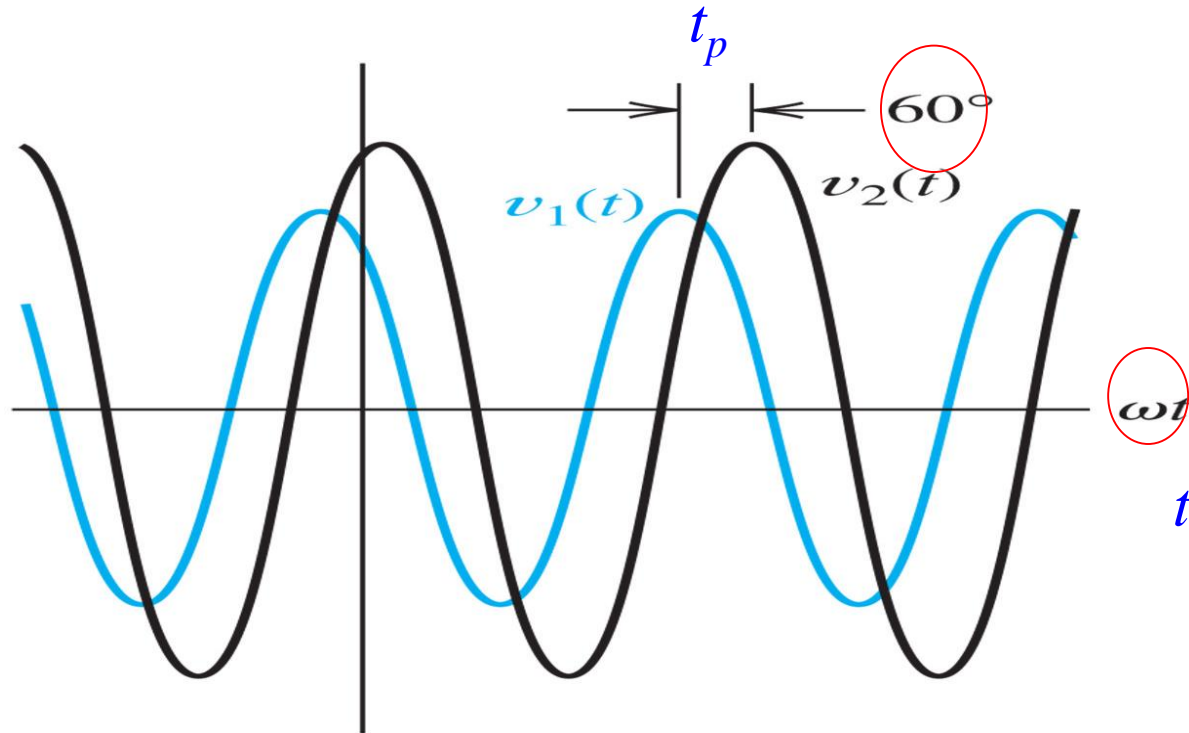

Exercise 5.5


$$v_1(t) = 10 \cos(\omega t - 30^\circ)$$

$$v_2(t) = 10 \cos(\omega t + 30^\circ)$$

$$v_3(t) = 10 \sin(\omega t + 45^\circ)$$

State the phase relationship between each pair of voltages.

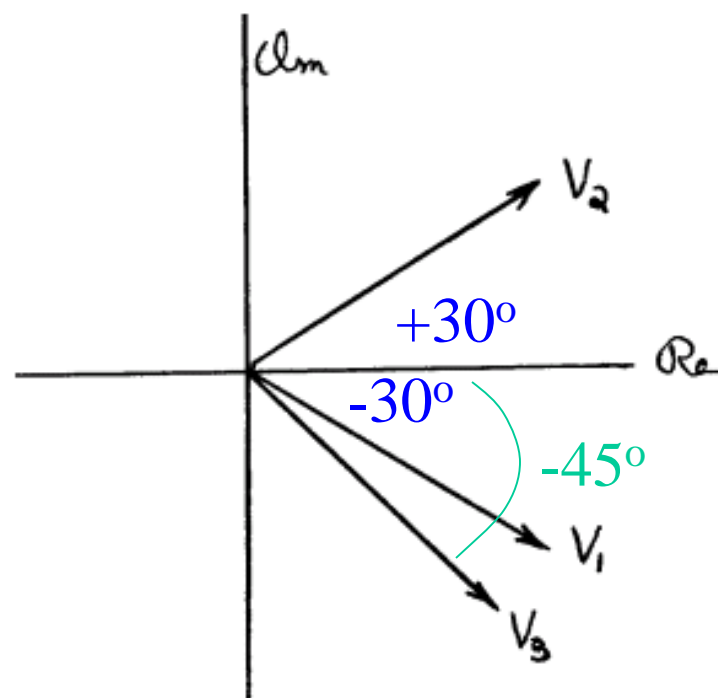The phasors are $V_1 = 10 \angle -30^\circ$ $V_2 = 10 \angle +30^\circ$ and $V_3 = 10 \angle -45^\circ$



v_1 lags v_2 by 60° (or we could say v_2 leads v_1 by 60°)

v_1 leads v_3 by 15° (or we could say v_3 lags v_1 by 15°)

v_2 leads v_3 by 75° (or we could say v_3 lags v_2 by 75°)

5.3 COMPLEX IMPEDANCES (複數阻抗)

Inductance

假設通過電感 L 的 **sinusoidal current** 為

$$i_L(t) = I_m \sin(\omega t + \theta)$$

則電感 L 兩端的voltage為

$$v_L(t) = L \frac{di_L(t)}{dt} = \omega L I_m \cos(\omega t + \theta) \quad (\text{亦為sinusoid})$$


Inductance

Voltage & current 的 phasors 為


$$I_L = I_m \angle \theta - 90^\circ$$

$$V_L = \omega L I_m \angle \theta = V_m \angle \theta$$

→ Current lags the voltage by 90°

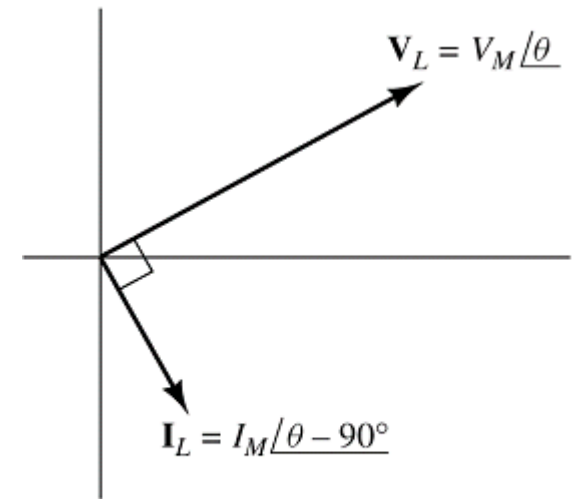

(a) Phasor diagram

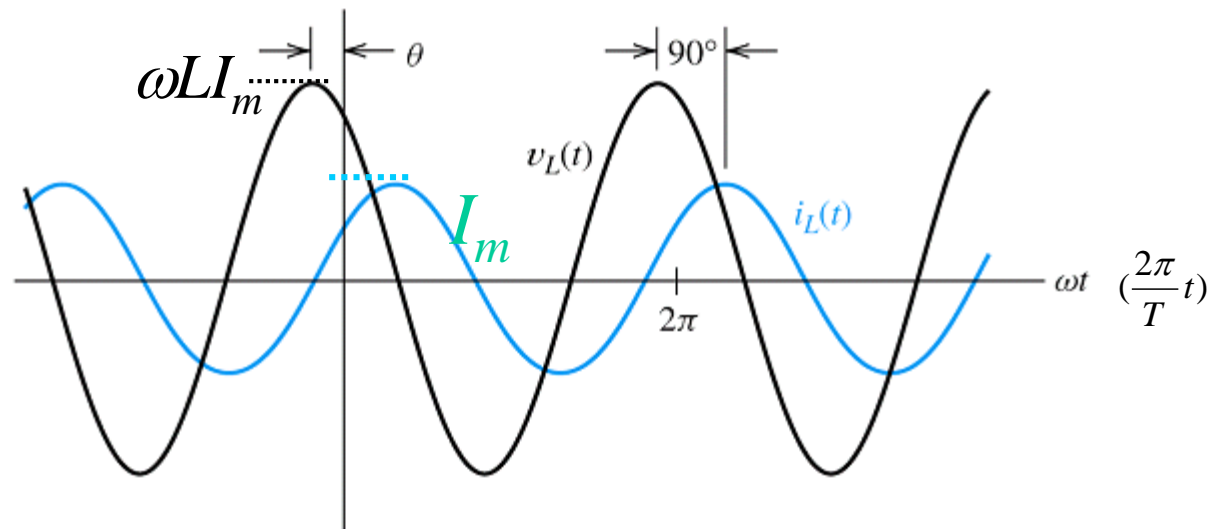

(b) Current and voltage versus time

Ohm's Law

$$V = IR$$

What is the relationship between phasor voltage and phasor current? Does it be similar to Ohm's law?

$$I_L = I_m \angle \theta - 90^\circ$$

$$V_L = \omega L I_m \angle \theta = (\omega L \angle 90^\circ) \times I_m \angle \theta - 90^\circ$$

$$= (\omega L \angle 90^\circ) \times I_L = j\omega L \times I_L$$

$$\left(\because \omega L \angle 90^\circ = \omega L (\cos 90^\circ + j \sin 90^\circ) \right)$$

→ $Z_L = j\omega L = \omega L \angle 90^\circ$ 稱為 L 的阻抗 (impedance)



$$V_L = Z_L \times I_L$$

Phasor voltage = impedance \times phasor current
(similar to Ohm's law)

Note the impedance of an inductance is an
imaginary number 虚數 (called reactance).
Resistance is a real number.

Capacitance

假設通過電容 C 的 sinusoidal voltage 為

$$v_c(t) = V_m \cos(\omega t + \theta)$$

則電容 C 兩端的current為

$$i_c(t) = C \frac{dv_c(t)}{dt} = -\omega C V_m \sin(\omega t + \theta)$$



$$V_C = V_m \angle \theta$$

$$\begin{aligned} I_c &= -\omega C V_m \angle \theta - 90^\circ = \omega C V_m \angle \theta - 90^\circ + 180^\circ \\ &= \omega C V_m \angle \theta + 90^\circ = I_m \angle \theta + 90^\circ \end{aligned}$$

$$\because -1 = \cos(180^\circ)$$

Capacitance

$$Z_c = \frac{V_c}{I_c} = \frac{V_m \angle \theta}{\omega C V_m \angle \theta + 90^\circ} = \frac{1}{\omega C} \angle -90^\circ$$


$$\left(= -j \frac{1}{\omega C} = \frac{1}{j \omega C} \right)$$

$$\therefore V_C = V_m \angle \theta$$


$$I_c = \omega C V_m \angle \theta + 90^\circ$$

→ Current leads the voltage by 90°

Capacitance

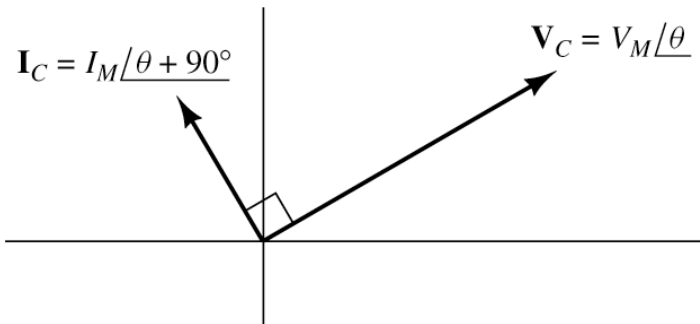

(a) Phasor diagram

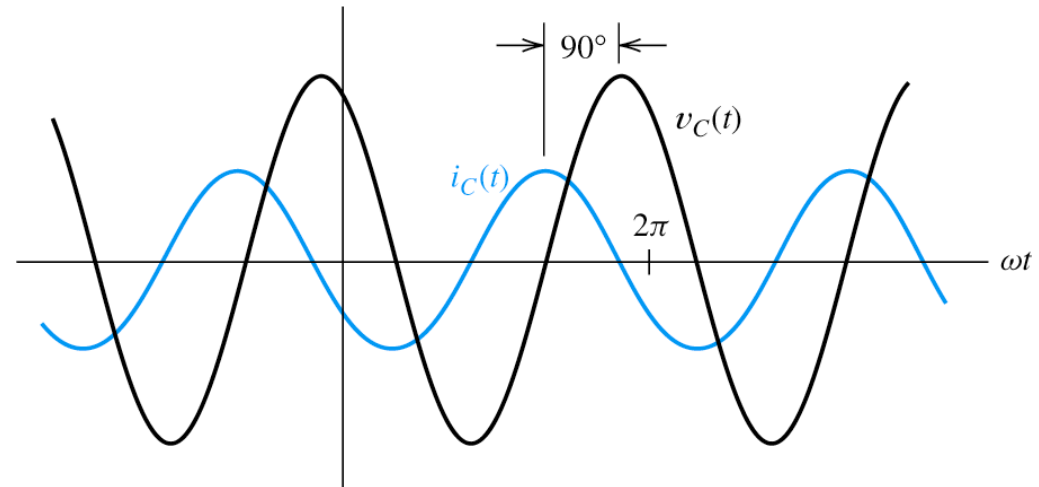

(b) Current and voltage versus time

Figure 5.8 Current leads voltage by 90° in a pure capacitance.

Resistance

$$V_R = RI_R$$

The current and voltage are in phase. (同相位)


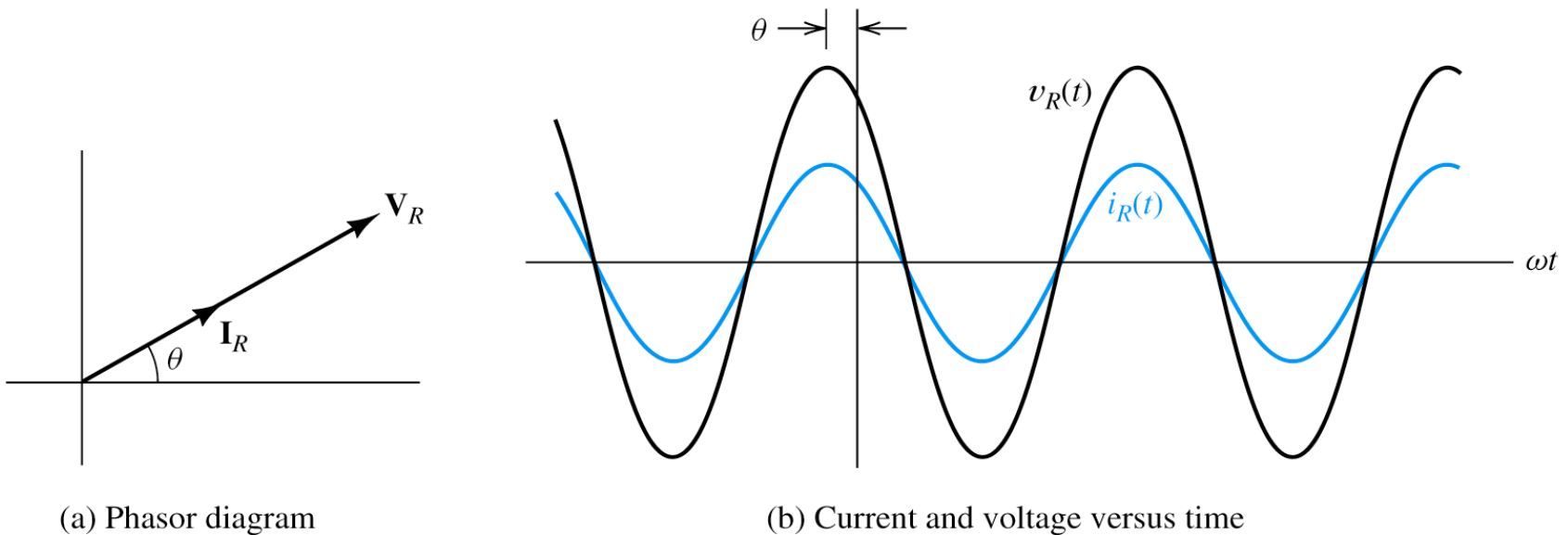


Figure 5.9 For a pure resistance, current and voltage are in phase.

電容阻抗

$$Z_c = -j \frac{1}{\omega C}$$


Current **leads** voltage by 90°

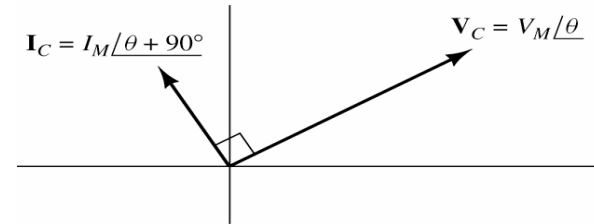

電感阻抗

$$Z_L = j\omega L$$


Current **lags** voltage by 90°

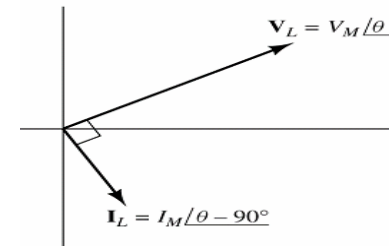

電阻

$$Z_R = R$$

Current and voltage are **in phase**

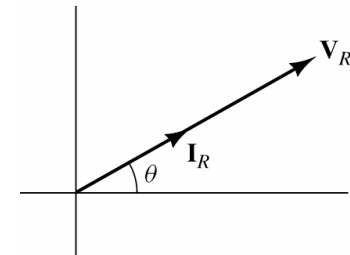

5.4 Circuit Analysis with Phasors and Complex Impedances

Kirchhoff's Laws in Phasor Form

We can apply **KVL** directly to **phasors**.
The sum of the **phasor voltages** equals zero for any closed path.


KCL-The sum of the **phasor currents** entering a node must equal the sum of the phasor currents leaving.

Circuit Analysis Using Phasors and Impedances

1. Replace the time descriptions of the **voltage and current** sources with the corresponding **phasors**. (All of the sources must have the **same frequency**.)
2. Replace **inductances** by their complex impedances $Z_L = j\omega L$. Replace **capacitances** by their complex impedances $Z_C = 1/(j\omega C)$ or $-j(1/\omega C)$. Resistances have impedances equal to their resistances.

3. Analyze the circuit using any of the techniques studied earlier in Chapter 2, performing the calculations with complex arithmetic.


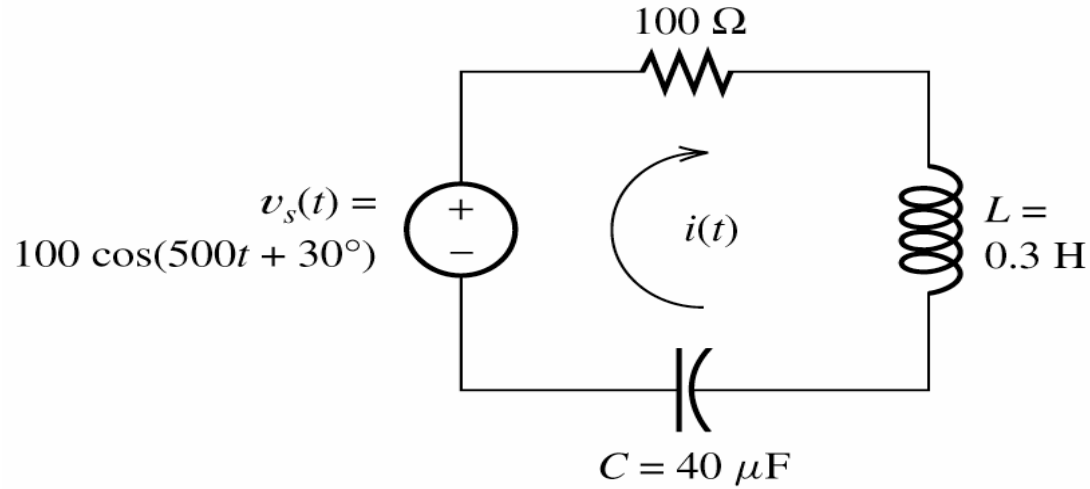
Example 5.4 Steady-state AC Analysis of a Series Circuit



$I?$
 $V_R?$
 $V_L?$
 $V_C?$

1. Phasors

$$V_s = 100 \angle 30^\circ$$

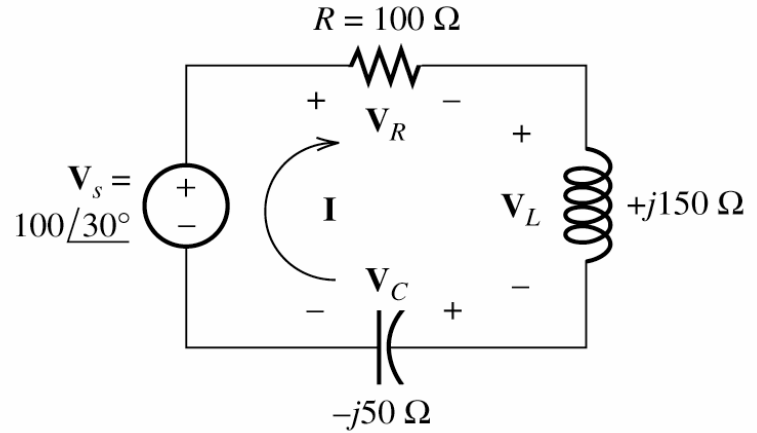
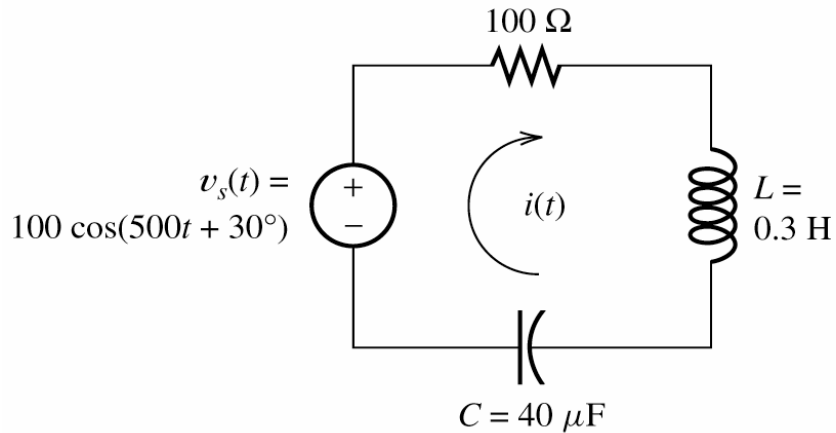


2. Complex impedances

$$Z_L = j\omega L = j500 \times 0.3 = j150\Omega$$

$$Z_C = -j \frac{1}{\omega C} = -j \frac{1}{500 \times 40 \times 10^{-6}} = -j50\Omega$$

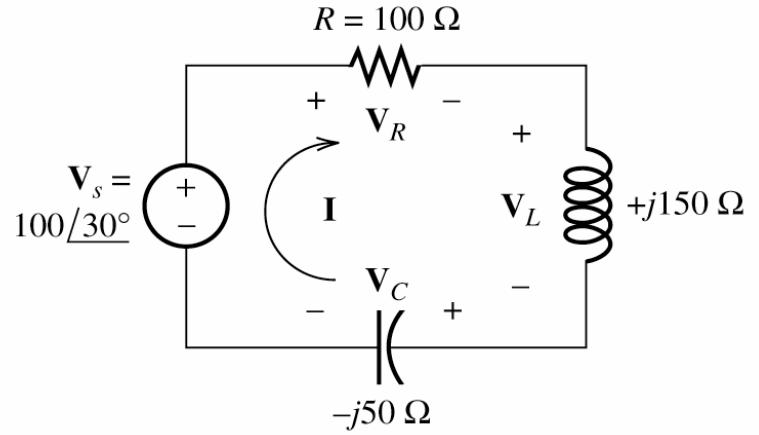
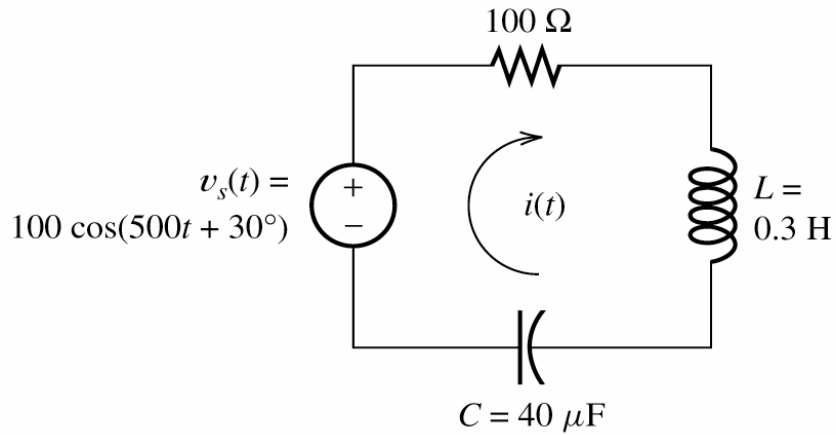
$$\begin{aligned} Z_{eq} &= R + Z_L + Z_C = 100 + j150 - j50 = 100 + j100 \\ &= 141.4 \angle 45^\circ \quad \left(\sqrt{100^2 + 100^2} \angle \arctan \frac{100}{100} \right) \end{aligned}$$



3. Circuit Analysis

$$I = \frac{V_s}{Z_{eq}} = \frac{100 \angle 30^\circ}{141.4 \angle 45^\circ} = \frac{100}{141.4} \angle (30^\circ - 45^\circ) = 0.707 \angle -15^\circ$$

→ $i(t) = 0.707 \cos(500t - 15^\circ)$

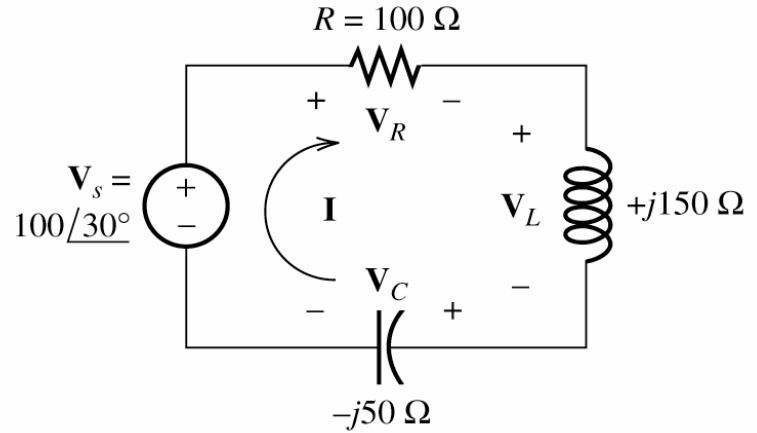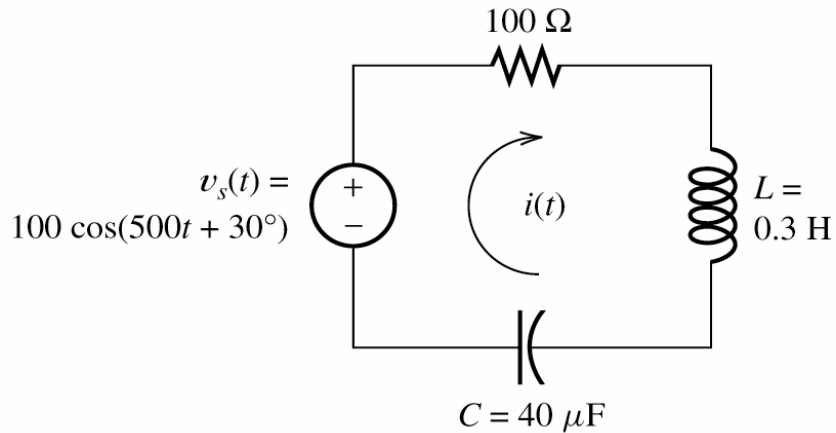

3. Circuit Analysis

$$\mathbf{V}_R = R \times \mathbf{I} = 100 \times 0.707 \angle -15^\circ = 70.7 \angle -15^\circ$$

$$\begin{aligned} \mathbf{V}_L &= j\omega L \times \mathbf{I} = \omega L \angle 90^\circ \times \mathbf{I} = 150 \angle 90^\circ \times 0.707 \angle -15^\circ \\ &= 106.1 \angle 75^\circ \end{aligned}$$

$$\begin{aligned} \mathbf{V}_C &= -j \frac{1}{\omega C} \times \mathbf{I} = \frac{1}{\omega C} \angle -90^\circ \times \mathbf{I} = 50 \angle -90^\circ \times 0.707 \angle -15^\circ \\ &= 35.4 \angle -105^\circ \end{aligned}$$

Note $j = \angle 90^\circ, -j = \angle -90^\circ$


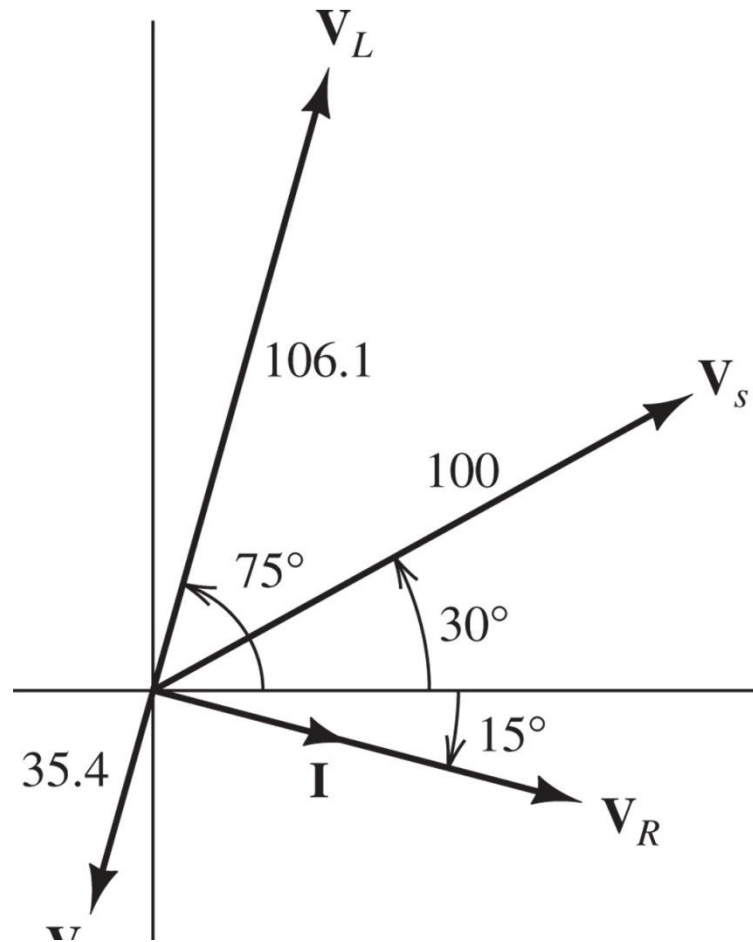


Figure 5.13 Phasor diagram for Example 5.4.


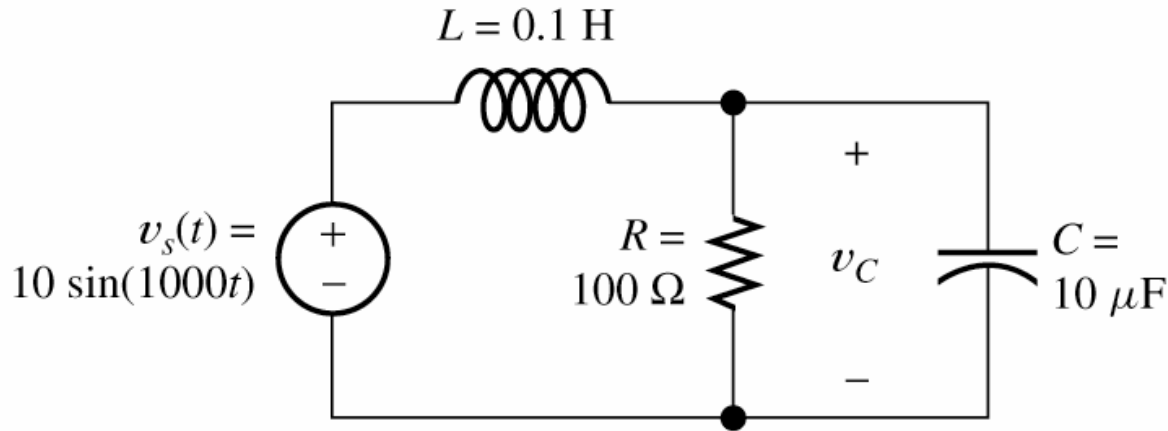
Example 5.5 Series and Parallel Combinations of Complex Impedances.



$V_C?$
 $I_L?$
 $I_R?$
 $I_C?$

1. Phasors

$$V_s = 10 \angle -90^\circ$$

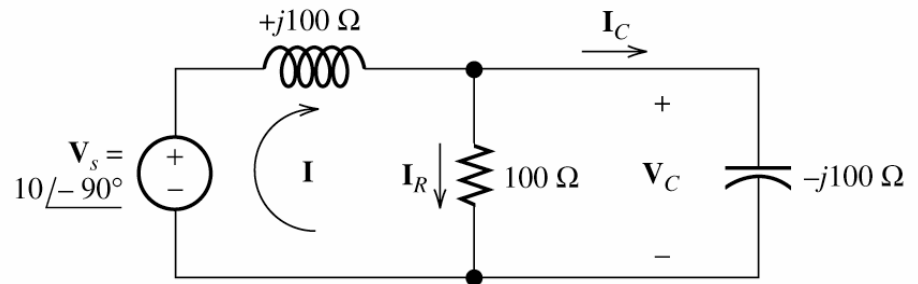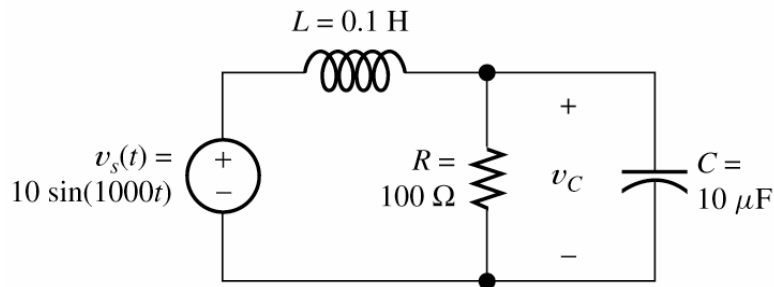

2. Complex impedances

$$Z_L = j\omega L = j1000 \times 0.1 = j100\Omega$$


$$Z_C = -j \frac{1}{\omega C} = -j \frac{1}{1000 \times 10 \times 10^{-6}} = -j100\Omega$$

$$Z_{RC} = \frac{1}{1/R + 1/Z_C} = \frac{1}{1/100 + 1/(-j100)} = \frac{1}{0.01 + j0.01}$$

$$= \frac{1 \angle 0^\circ}{0.01414 \angle 45^\circ} = 70.71 \angle -45^\circ = 70.71(\cos -45^\circ + j \sin -45^\circ) = 50 - j50$$

$$\text{Or } \frac{1}{0.01 + j0.01} = \frac{1}{0.01 + j0.01} \cdot \frac{0.01 - j0.01}{0.01 - j0.01} = 50 - j50$$

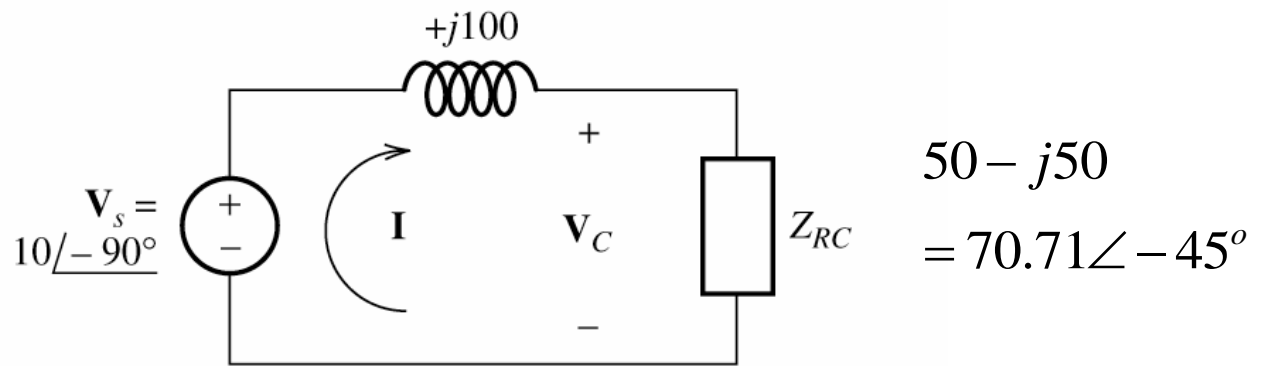
$$= \sqrt{50^2 + 50^2} \angle \arctan \frac{-50}{50} = 70.71 \angle -45^\circ$$



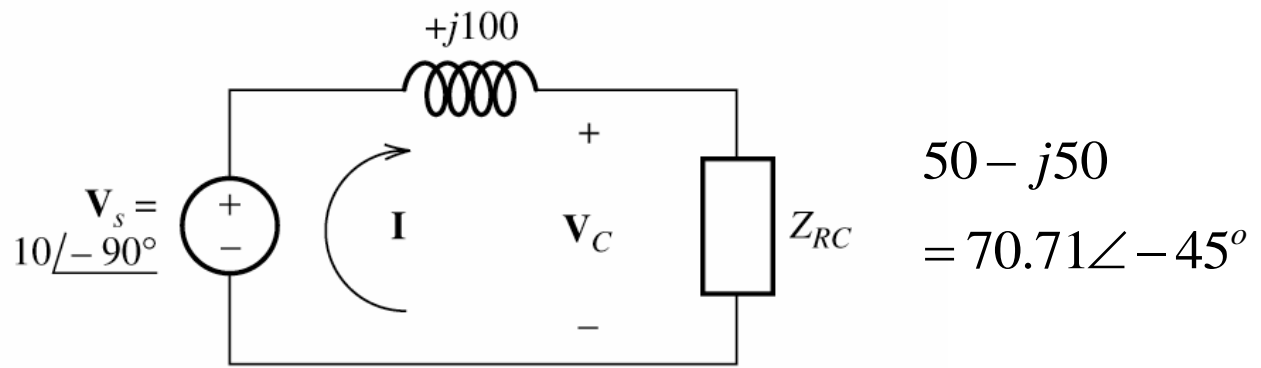3. Circuit Analysis

$$\begin{aligned}
 V_C &= V_s \frac{Z_{RC}}{Z_L + Z_{RC}} = 10\angle -90^\circ \frac{70.71\angle -45^\circ}{j100 + 50 - j50} \\
 &= 10\angle -90^\circ \frac{70.71\angle -45^\circ}{50 + j50} = 10\angle -90^\circ \frac{70.71\angle -45^\circ}{70.71\angle 45^\circ} \\
 &= 10\angle -180^\circ
 \end{aligned}$$


$$v_C(t) = 10\cos(1000t - 180^\circ) = -10\cos(1000t)$$




$$I = \frac{V_s}{Z_L + Z_{RC}} = \frac{10\angle -90^\circ}{j100 + 50 - j50} = \frac{10\angle -90^\circ}{50 + j50} = \frac{10\angle -90^\circ}{70.71\angle 45^\circ} = 0.1414\angle -135^\circ$$

$$I_R = \frac{V_C}{R} = \frac{10\angle -180^\circ}{100} = 0.1\angle -180^\circ$$

$$I_C = \frac{V_C}{Z_C} = \frac{10\angle -180^\circ}{-j100} = \frac{10\angle -180^\circ}{100\angle -90^\circ} = 0.1\angle -90^\circ$$

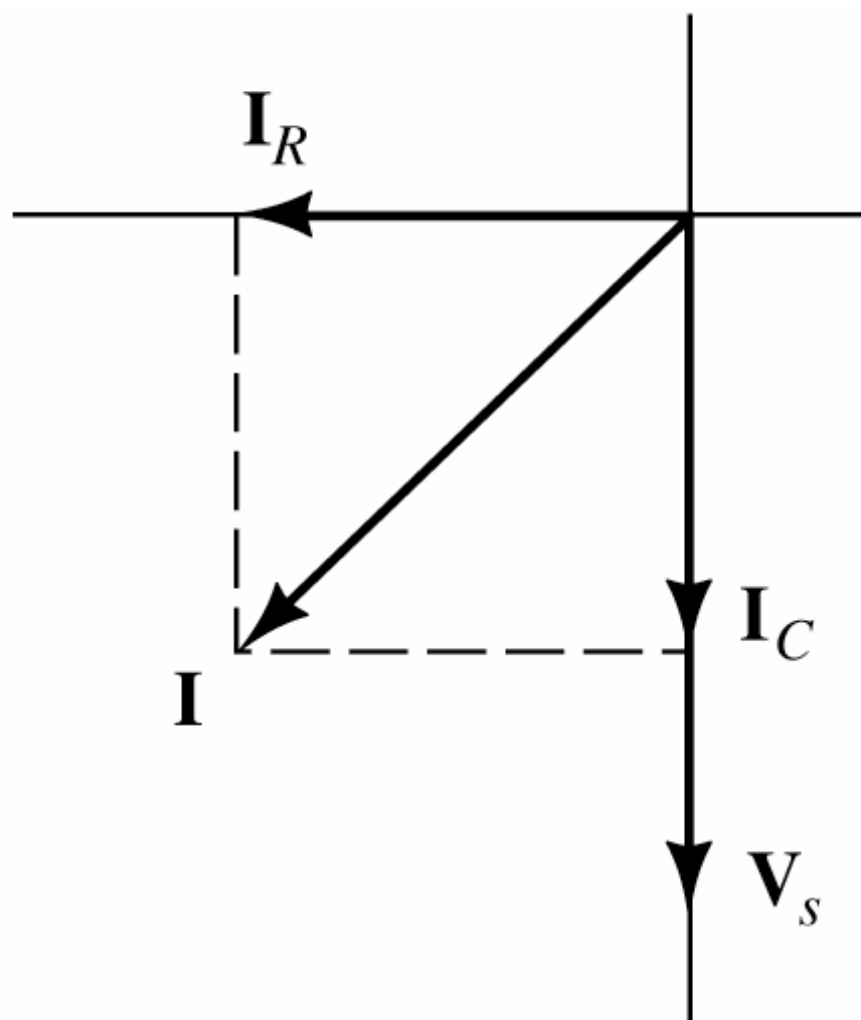

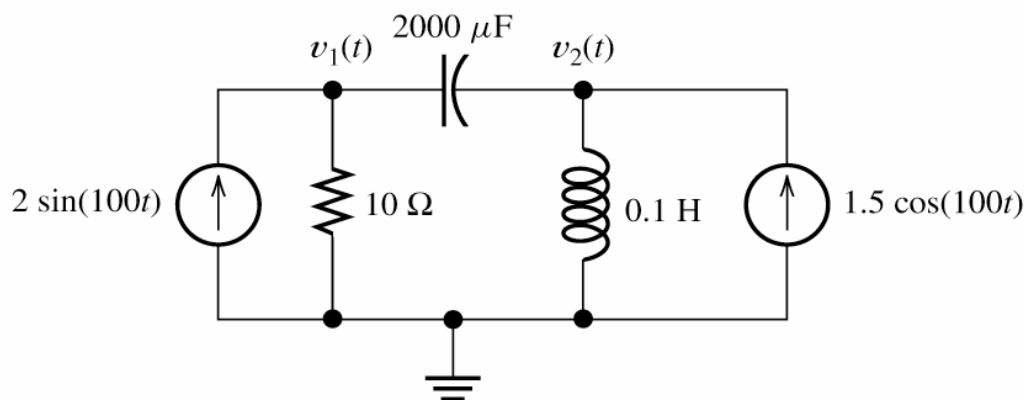Example 5.6 Steady-State AC Node-Voltage Analysis



$v_1(t)$?

1. Phasors


$$2 \sin(100t) = 2 \angle -90^\circ$$


$$1.5 \cos(100t) = 1.5 \angle 0^\circ$$

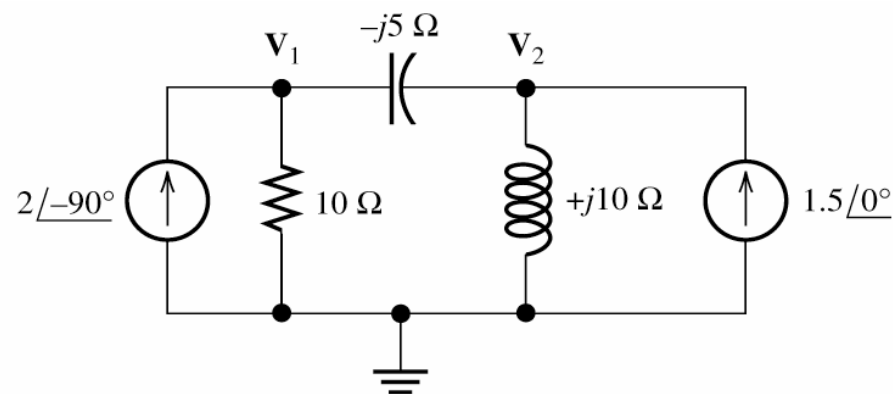2. Complex impedances

$$j\omega L = j100 \times 0.1 = j10$$

$$-j \frac{1}{\omega C} = -j \frac{1}{100 \times 2000 \times 10^{-6}} = -j5$$



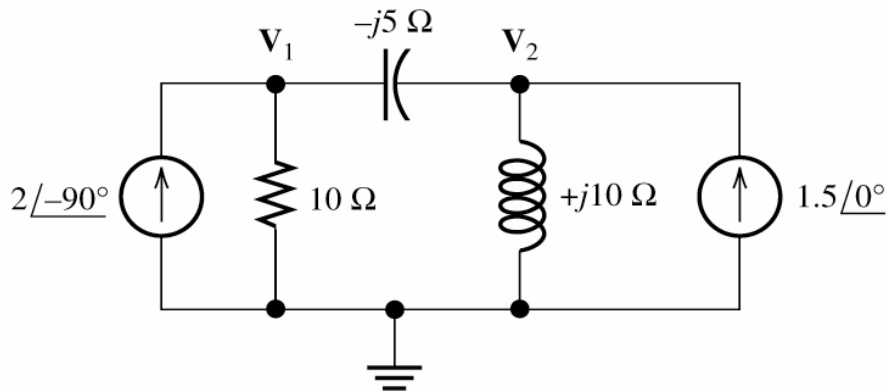

3. Circuit Analysis


KCL Node 1
$$\frac{V_1}{10} + \frac{V_1 - V_2}{-j5} = 2\angle -90^\circ$$

KCL Node 2
$$\frac{V_2}{j10} + \frac{V_2 - V_1}{-j5} = 1.5\angle 0^\circ$$

$$(0.1 + j0.2)V_1 - j0.2V_2 = -j2 \quad \because \quad \boxed{\frac{1}{-j5} = \frac{1}{-j5} \cdot \frac{j}{j} = j0.2}$$

$$-j0.2V_1 + j0.1V_2 = 1.5$$


→
$$(0.1 - j0.2)V_1 = 3 - j2$$

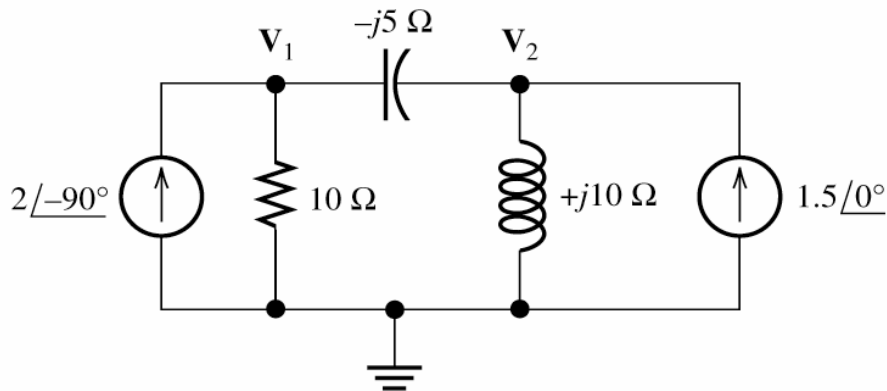

$$\begin{aligned}
 V_1 &= \frac{3 - j2}{0.1 - j0.2} = \frac{3 - j2}{0.1 - j0.2} \cdot \frac{0.1 + j0.2}{0.1 + j0.2} \\
 &= \frac{0.7 + j0.4}{0.05} = 14 + j8 = 16.1 \angle 29.7^\circ
 \end{aligned}$$

$$\rightarrow v_1(t) = 16.1 \cos(100t + 29.7^\circ)$$

5.5 Power in AC Circuits

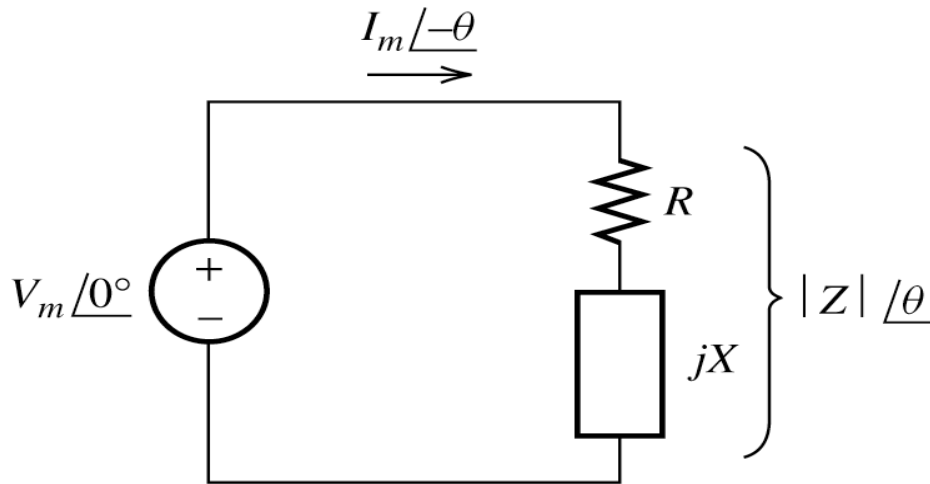

A voltage source delivering power to a load impedance $Z = R + jX$.

阻抗有實數(電阻)或虛數(電感, 電容), 功率有無實虛?

$$Z = R + jX = |Z| \angle \theta$$

$$I = \frac{V}{Z} = \frac{V_m}{|Z|} \angle -\theta = I_m \angle -\theta$$

$$I_m = \frac{V_m}{|Z|}$$

1. If $X=0 \rightarrow$ 實阻抗(純電阻)

$$v(t) = V_m \cos(\omega t)$$

$$i(t) = I_m \cos(\omega t)$$

$$p(t) = v(t)i(t) = V_m I_m \cos^2(\omega t)$$

$$Z = R,$$

$$\theta = 0$$

(參考Ch5.1)

$$p_{avg} > 0$$



實功率
(real power)

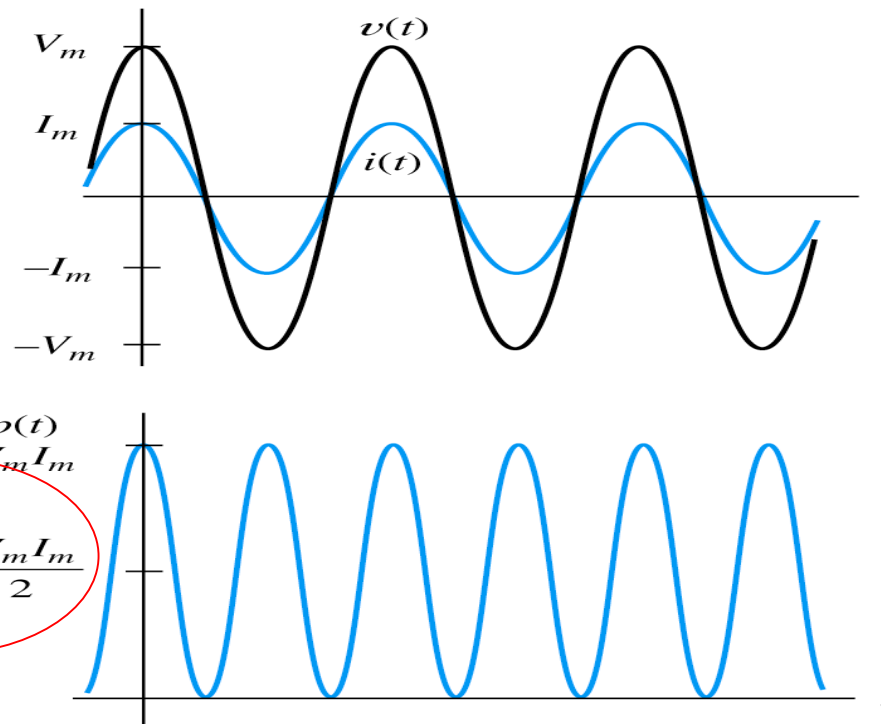


Figure 5.20 Current, voltage, and power versus time for a purely resistive load.

1. If $X=0 \longrightarrow$ 實阻抗(純電阻)

$$P_{avg} = \frac{V_{rms}^2}{R} = I_{rms}^2 R$$

$$P_{avg}^2 = \frac{V_{rms}^2}{R} \cdot I_{rms}^2 R = V_{rms}^2 \cdot I_{rms}^2$$

$$P_{avg} = V_{rms} \cdot I_{rms} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}} = \frac{V_m I_m}{2}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

2. If $R=0$, $X>0 \rightarrow$ 虛阻抗 (電感性)

$$v(t) = V_m \cos(\omega t)$$

$$i(t) = I_m \cos(\omega t - 90^\circ) = I_m \sin(\omega t)$$



$$p(t) = v(t)i(t) = V_m I_m \cos(\omega t) \sin(\omega t) = \frac{V_m I_m}{2} \sin(2\omega t)$$

$$p_{avg} = 0$$

$$Z = jX,$$

$$\theta = 90^\circ$$

\rightarrow 虛功率 or 無效功率
(Reactive power)

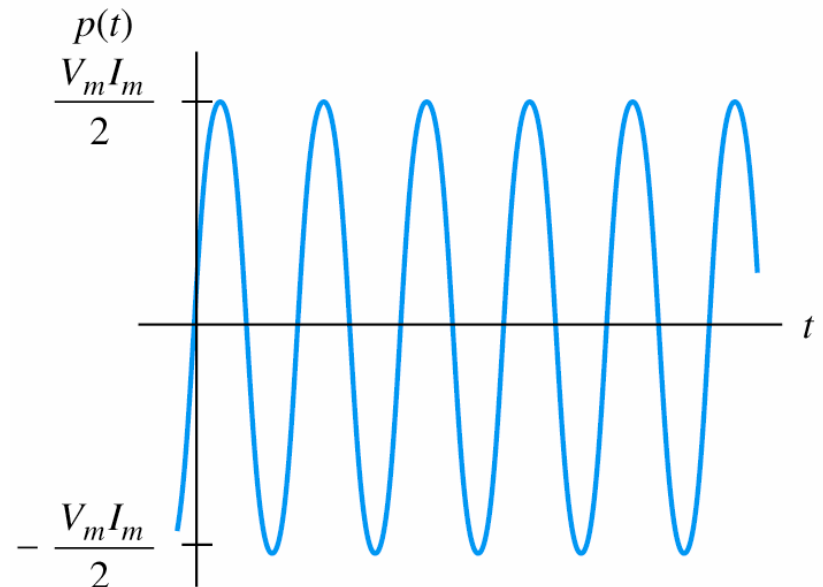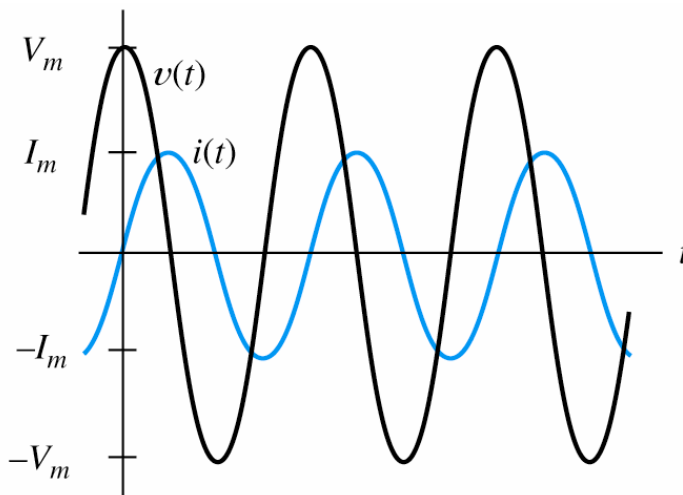

3. If $R=0$, $X<0 \longrightarrow$ 虛阻抗 (電容性)

$$v(t) = V_m \cos(\omega t)$$

$$i(t) = I_m \cos(\omega t + 90^\circ) = -I_m \sin(\omega t)$$



$$Z = jX,$$

$$\theta = -90^\circ$$

$$p(t) = v(t)i(t) = -V_m I_m \cos(\omega t) \sin(\omega t) = -\frac{V_m I_m}{2} \sin(2\omega t)$$

$$p_{avg} = 0$$

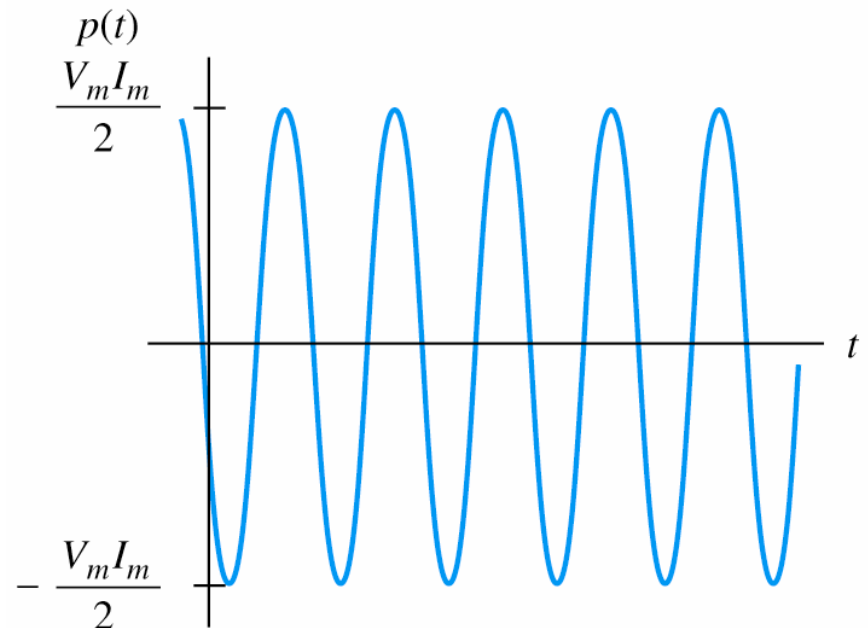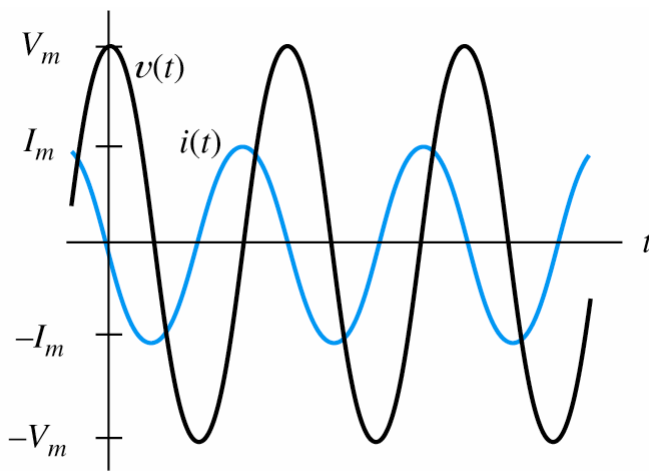\longrightarrow 虛功率 or 無效功率
(Reactive power)



Power for a General Load

一般狀況 $R \neq 0$ 且 $X \neq 0$, RLC 電路 (有實與虛阻抗)

$$v(t) = V_m \cos(\omega t)$$

$$Z = R + jX, \quad -90^\circ < \theta < 90^\circ$$

$$i(t) = I_m \cos(\omega t - \theta)$$

$$p(t) = V_m I_m \cos(\omega t) \cos(\omega t - \theta)$$

$$= V_m I_m \cos(\theta) \cos^2(\omega t) + V_m I_m \sin(\theta) \cos(\omega t) \sin(\omega t)$$

$$(\because \cos(\omega t - \theta) = \cos(\theta) \cos(\omega t) + \sin(\theta) \sin(\omega t))$$

$$= \frac{V_m I_m}{2} \cos(\theta) [1 + \cos(2\omega t)] + \frac{V_m I_m}{2} \sin(\theta) \sin(2\omega t)$$

$$(\because \cos^2(\omega t) = \frac{1}{2}(1 + \cos(2\omega t)), \quad \cos(\omega t) \sin(\omega t) = \frac{1}{2} \sin(2\omega t))$$

$$P_{avg} = \frac{1}{T} \int_0^T p(t) dt$$

$$= \frac{1}{T} \int_0^T \frac{V_m I_m}{2} \cos(\theta) [1 + \underbrace{\cos(2\omega t)}_{\text{積分為0}}] + \frac{V_m I_m}{2} \sin(\theta) \underbrace{\sin(2\omega t)}_{\text{積分為0}} dt$$

$$= \frac{V_m I_m}{2} \cos(\theta)$$

$$\therefore V_{rms} = \frac{V_m}{\sqrt{2}}, I_{rms} = \frac{I_m}{\sqrt{2}}$$

$$\longrightarrow P_{avg} = V_{rms} I_{rms} \cos(\theta)$$

$P_{avg} = P = V_{rms} I_{rms} \cos(\theta)$ 為real power (有效功律or 實功率)
單位為W


$\cos(\theta)$ 為power factor, PF (功率因子)

$\theta = \theta_v - \theta_i$ 為power angle (功率角)代表電流lags電壓的角度


$V_{rms} I_{rms}$ 為apparent power (視出功律) 單位為VA(volt-amperes)



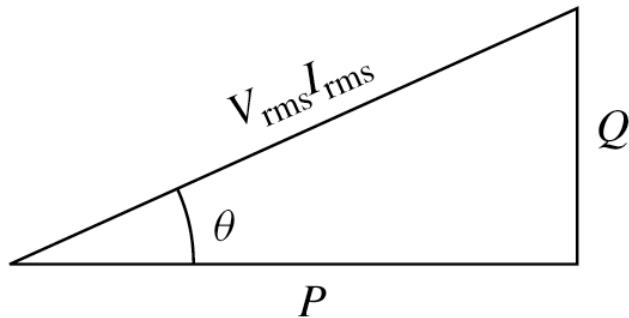$Q = V_{rm} I_{rms} \sin(\theta)$ 為reactive power (無效功律or 虛功率), 單位為
VAR (volt amperes reactive)



(a) Inductive load (θ positive)

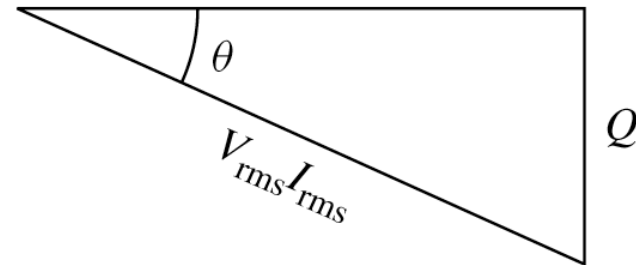

(b) Capacitive load (θ negative)

Power triangles for inductive and capacitive loads.

AC Power Calculations

$$P = V_{\text{rms}} I_{\text{rms}} \cos(\theta) \quad (\text{W})$$

$$\text{PF} = \cos(\theta)$$

$$\theta = \theta_v - \theta_i$$

$$Q = V_{\text{rms}} I_{\text{rms}} \sin(\theta) \quad (\text{VAR})$$

$$V_{\text{rms}} I_{\text{rms}} = \sqrt{P^2 + Q^2} \quad (\text{VA})$$

$$\sqrt{P^2 + Q^2} = V_{\text{rms}} I_{\text{rms}} \quad (\text{VA})$$

$$P = I_{\text{rms}}^2 R \quad (\text{W})$$

$$Q = I_{\text{rms}}^2 X \quad (\text{VAR})$$

$$P = I_{rms}^2 R$$

Proof:

$$\cos(\theta) = \frac{R}{|Z|}$$

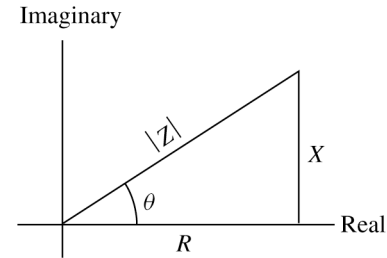


Figure 5.23 The load impedance in the complex plane.

$$P = I_{rms} V_{rms} \cos \theta = I_{rms} \frac{V_m}{\sqrt{2}} \frac{R}{|Z|} = I_{rms} \frac{I_m}{\sqrt{2}} R = I_{rms}^2 R$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I = \frac{V}{Z}, I_m = \frac{V_m}{|Z|}$$

$$Q = I_{rms}^2 X$$

Proof:

$$Q = I_{rms} V_{rms} \sin \theta = I_{rms} \frac{V_m}{\sqrt{2}} \frac{X}{|Z|} = I_{rms} \frac{I_m}{\sqrt{2}} X = I_{rms}^2 X$$


Appendix A

Complex Numbers

Basic Complex-Number Concepts

- Complex numbers involve the imaginary number(虛數) $j = \sqrt{-1}$
- $Z=x+jy$ has a **real part** (實部) x and an **imaginary part** (虛部) y , we can represent complex numbers by points in the **complex plane** (複數平面)
- The complex numbers of the form $x+jy$ are in **rectangular form** (直角座標)

Imaginary

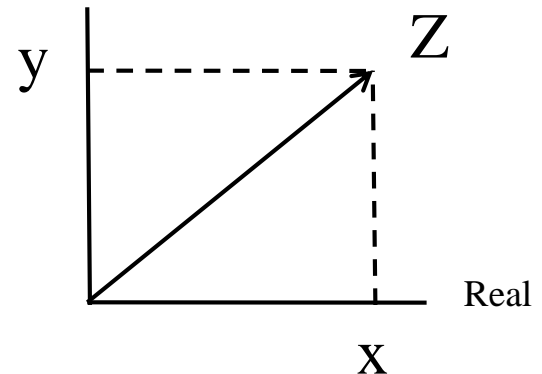

- The **complex conjugate** (共軛複數) of a number in rectangular form is obtained by **changing the sign of the imaginary part**.
- For example if $Z_2 = 3 - j4$ then the complex conjugate of Z_2 is

$$Z_2^* = 3 + j4$$

- $j^2 = -1$

Example A.1 Complex Arithmetic in Rectangular Form

Given that $Z_1 = 5 + j5$ and $Z_2 = 3 - j4$, reduce $Z_1 - Z_2$, $Z_1 Z_2$, Z_1 / Z_2 to rectangular form

- Solution:

For the sum, we have

$$Z_1 + Z_2 = (5 + j5) + (3 - j4) = 8 + j1$$

The difference is

$$Z_1 - Z_2 = (5 + j5) - (3 - j4) = 2 + j9$$

Example A.1 Complex Arithmetic in Rectangular Form

For the product , we get

$$\begin{aligned} Z_1 Z_2 &= (5 + j5)(3 - j4) \\ &= 15 - j20 + j15 - j^2 20 \\ &= 15 - j20 + j15 + 20 \\ &= 35 - j5 \end{aligned}$$

To divide the numbers, we obtain

$$\frac{Z_1}{Z_2} = \frac{5 + j5}{3 - j4}$$

We can reduce this expression to rectangular form by multiplying the numerator and denominator by the complex conjugate of the denominator


$$\begin{aligned}\frac{Z_1}{Z_2} &= \frac{5 + j5}{3 - j4} \times \frac{Z_2^*}{Z_2^*} \\ &= \frac{5 + j5}{3 - j4} \times \frac{3 + j4}{3 + j4} \\ &= \frac{15 + j20 + j15 + j^2 20}{9 + \cancel{j12 - j12} - j^2 16} \\ &= \frac{15 + j20 + j15 - 20}{9 + j12 - j12 + 16} \\ &= \frac{-5 + j35}{25} \\ &= -0.2 + j1.4\end{aligned}$$

Complex Numbers in Polar Form(極座標)


- Complex numbers can be expressed in **polar form (極座標)**.
Examples of complex numbers in polar form are :

$$Z_3 = 5 \angle 30^\circ \quad \text{and} \quad Z_4 = 10 \angle -45^\circ$$

The **length of the arrow** that represents a complex number Z is denoted as $|Z|$ and is called the **magnitude** (幅值 or 大小) of the complex number.

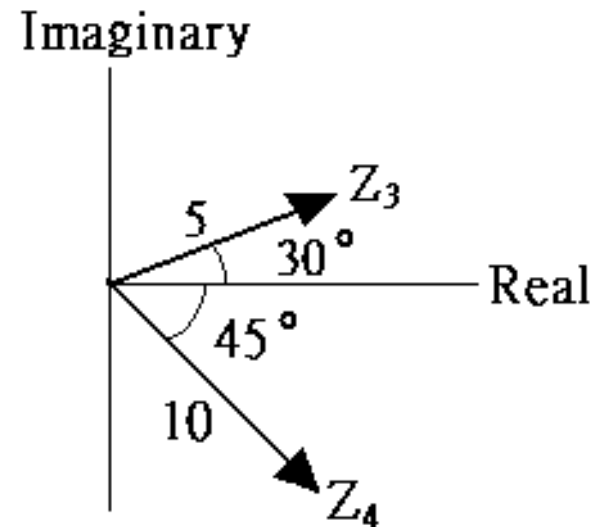

- Using the magnitude $|Z|$, the real part x , and the imaginary part y form a right triangle (直角三角形).

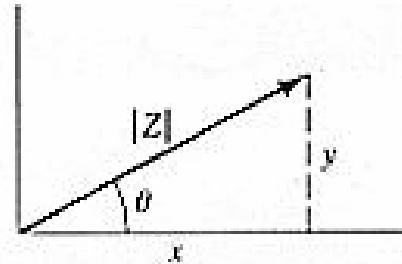

- Using trigonometry, we can write the following relationships:

$$|Z|^2 = x^2 + y^2 \quad (\text{A.1})$$

$$\tan(\theta) = \frac{y}{x} \quad (\text{A.2})$$

$$x = |Z| \cos(\theta) \quad (\text{A.3})$$

$$y = |Z| \sin(\theta) \quad (\text{A.4})$$

These equations can be used to convert numbers from polar to rectangular form.

Example A.2 Polar-to Rectangular Conversion

Convert $Z_3 = 5\angle 30^\circ$ to rectangular form

Solution :

Using Equation A.3 and A.4 (pre. page) \Rightarrow

$$x = |Z| \cos(\theta) = 5 \cos(30^\circ) = 4.33$$

$$y = |Z| \sin(\theta) = 5 \sin(30^\circ) = 2.5$$

$$\therefore Z_3 = 5\angle 30^\circ = x + jy = 4.33 + j2.5$$

Example A.3 Rectangular-to-Polar Conversion

Convert $Z_5 = 10 + j5$ and $Z_6 = -10 + j5$ to polar form.

Solution :

First, using Equation A.1 to find the magnitudes of each of the numbers

$$|Z_5| = \sqrt{x_5^2 + y_5^2} = \sqrt{10^2 + 5^2} = 11.18$$

$$|Z_6| = \sqrt{x_6^2 + y_6^2} = \sqrt{(-10)^2 + 5^2} = 11.18$$

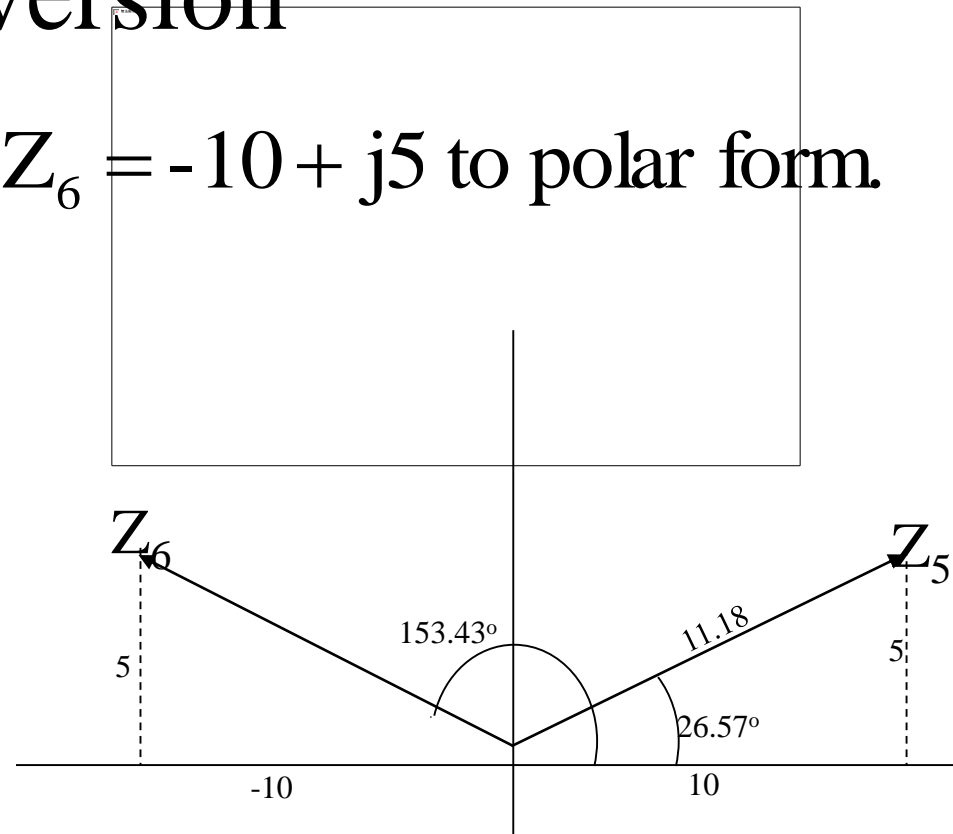


Figure A.4

To find the angles, we use Equation A.2.

For Z_5

$$\tan(\theta_5) = \frac{y_5}{x_5} = \frac{5}{10} = 0.5$$

$$\theta_5 = \arctan(0.5) = 26.57^\circ$$

$$\begin{aligned}\therefore Z_5 &= 10 + j5 \\ &= 11.18 \angle 26.57^\circ\end{aligned}$$

For Z_6

$$\tan(\theta_6) = \frac{y_6}{x_6} = \frac{5}{-10} = -0.5$$

$$\theta_6 = 180 + \arctan\left(\frac{y_6}{x_6}\right)$$

$$= 180 - 26.57 = 153.43^\circ$$

$$\begin{aligned}\therefore Z_6 &= 10 + j5 \\ &= 11.18 \angle 153.43^\circ\end{aligned}$$

- The procedures that we have illustrated in Examples A.2 and A.3 can be carried out with a relatively simple calculator. However, if we find the angle by taking the arctangent of y/x , we must consider the fact that the **principal value** of the arctangent is the true angle **only if the real part x is positive**. If x is negative, we have:

$$\theta = \arctan\left(\frac{y}{x}\right) \pm 180^\circ$$

Euler's Identities


- The connection between sinusoidal signals and complex number is through Euler's identities, which state that

$$\cos(\theta) = \frac{e^{j\theta} + e^{-j\theta}}{2} \quad \text{and} \quad \sin(\theta) = \frac{e^{j\theta} - e^{-j\theta}}{2j}$$

- Another form of these identities is

$$e^{j\theta} = \cos(\theta) + j \sin(\theta) \quad \text{and} \quad e^{-j\theta} = \cos(\theta) - j \sin(\theta)$$

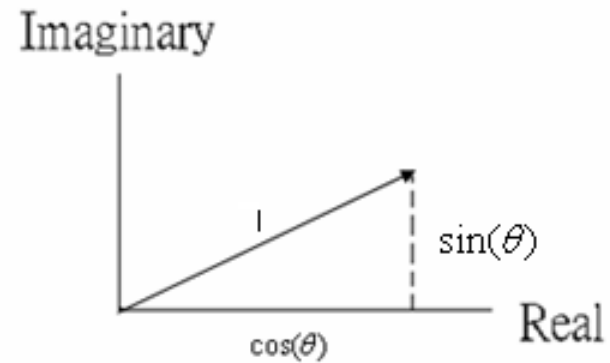- $e^{j\theta}$ is a complex number having a **real part** of $\cos(\theta)$ and an **imaginary part** of $\sin(\theta)$



- The **magnitude** is

$$|e^{j\theta}| = \sqrt{\cos^2(\theta) + \sin^2(\theta)} = 1$$

- The angle of $e^{j\theta}$ is θ

$$e^{j\theta} = 1\angle\theta = \cos(\theta) + j\sin(\theta)$$

$$e^{-j\theta} = 1\angle-\theta = \cos(\theta) - j\sin(\theta)$$

- A complex number such as $A\angle\theta$ can be written as
$$A\angle\theta = A \times (1\angle\theta) = Ae^{j\theta} = A\cos(\theta) + jA\sin(\theta)$$
- We call $Ae^{j\theta}$ the **exponential form** (指數形式) of a complex number.

- Given complex number can be written in three forms:
 - The rectangular form
 - The polar form
 - Exponential form

Example A.4 Exponential Form of a Complex Number


Express the complex number $Z = 10\angle 60^\circ$ in exponential and rectangular forms.

Sketch the number in the complex plane

- Solution:

$$Z = 10\angle 60^\circ = 10e^{j60^\circ}$$
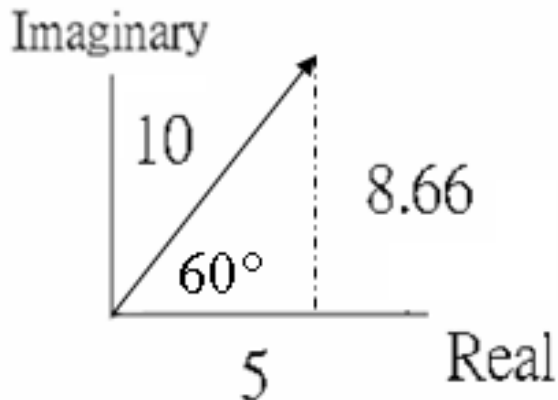
$$Z = 10 \times (e^{j60^\circ}) = 10 \times [\cos(60^\circ) + j \sin(60^\circ)] = 5 + j8.66$$



Arithmetic Operations in Polar and Exponential Form

- To **add (or subtract)** complex numbers, we must first convert them to **rectangular form**. Then, we add (or subtract) real part to real part and imaginary to imaginary.

- Two complex numbers in exponential form:

$$Z_1 = |Z_1|e^{j\theta_1} \quad \text{and} \quad Z_2 = |Z_2|e^{j\theta_2}$$

- The polar forms of these numbers are

$$Z_1 = |Z_1| \angle \theta_1 \quad \text{and} \quad Z_2 = |Z_2| \angle \theta_2$$

- For multiplication of numbers in exponential form, we have $Z_1 \times Z_2 = |Z_1|e^{j\theta_1} \times |Z_2|e^{j\theta_2} = |Z_1||Z_2|e^{j(\theta_1+\theta_2)}$

- In polar form, this is $Z_1 \times Z_2 = |Z_1|\angle\theta_1 \times |Z_2|\angle\theta_2 = |Z_1||Z_2|\angle\theta_1 + \theta_2$

Proof:

$$\begin{aligned}
 Z_1 \times Z_2 &= |Z_1|(\cos \theta_1 + j \sin \theta_1) \times |Z_2|(\cos \theta_2 + j \sin \theta_2) \\
 &= |Z_1||Z_2|(\cos \theta_1 \cos \theta_2 - \sin \theta_1 \sin \theta_2 + j(\sin \theta_1 \cos \theta_2 + \sin \theta_2 \cos \theta_1)) \\
 &= |Z_1||Z_2|(\cos(\theta_1 + \theta_2) + j \sin(\theta_1 + \theta_2))
 \end{aligned}$$

$$\left(\begin{aligned} \sin(\alpha \pm \beta) &= \sin\alpha\cos\beta \pm \cos\alpha\sin\beta \\ \cos(\alpha \pm \beta) &= \cos\alpha\cos\beta \mp \sin\alpha\sin\beta \end{aligned} \right)$$

- Now consider division: $\frac{Z_1}{Z_2} = \frac{|Z_1|e^{j\theta_1}}{|Z_2|e^{j\theta_2}} = \frac{|Z_1|}{|Z_2|}e^{j(\theta_1-\theta_2)}$
- In polar form, this is $\frac{Z_1}{Z_2} = \frac{|Z_1|\angle\theta_1}{|Z_2|\angle\theta_2} = \frac{|Z_1|}{|Z_2|}\angle\theta_1 - \theta_2$

Example A.5

Complex Arithmetic in Polar Form

Given $Z_1 = 10\angle 60^\circ$ and $Z_2 = 5\angle 45^\circ$, find $Z_1 Z_2$, Z_1/Z_2 , and $Z_1 + Z_2$ in polar form.

- Solution:

$$Z_1 \times Z_2 = 10\angle 60^\circ \times 5\angle 45^\circ = 50\angle 105^\circ$$

$$\frac{Z_1}{Z_2} = \frac{10\angle 60^\circ}{5\angle 45^\circ} = 2\angle 15^\circ$$

Before we can add (or subtract) the numbers, we must convert them to **rectangular form**.

$$Z_1 = 10\angle 60^\circ = 10\cos(60^\circ) + j10\sin(60^\circ) = 5 + j8.66$$

$$Z_2 = 5\angle 45^\circ = 5\cos(45^\circ) + j5\sin(45^\circ) = 3.54 + j3.54$$

The sum as Z_s :

$$Z_s = Z_1 + Z_2 = 5 + j8.66 + 3.54 + j3.54 = 8.54 + j12.2$$

Convert the sum to polar form:

$$|Z_s| = \sqrt{(8.54)^2 + (12.2)^2} = 14.9$$

$$\tan \theta_s = \frac{12.2}{8.54} = 1.43 \quad \theta_s = \arctan(1.43) = 55^\circ$$

Because the real part of Z_s is positive, the correct angle is the principal value of the arctangent.

$$Z_s = Z_1 + Z_2 = 14.9 \angle 55^\circ$$