

國立成功大學 工程科學系 試題

電子電路 (總分 100 分)

學號 _____ 姓名 _____ 2018/1/15

計算題 5 題(100 分, 共 3 頁) 推導過程須要詳細寫出來, 若觀念正確, 才能斟酌給分。

1. The CG amplifier circuit shown in Fig.1 have $g_m = 2\text{mA/V}$, $r_o = \infty$, and $C_{gs} = 1\text{pF}$, $C_{gd} = 2\text{pF}$. Please determine the midband gain $A_M \equiv \frac{v_o}{v_{sig}}$, and the upper 3-dB frequency f_H in case $R_{sig} = 2\text{k}\Omega$, $R_L = 10\text{k}\Omega$, and $C_L = 10\text{pF}$, and neglect r_o .(20%)

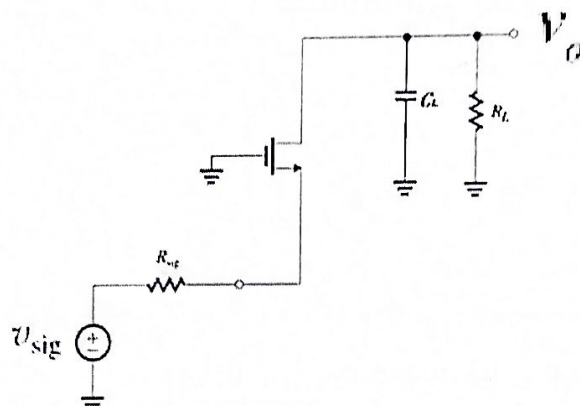


Fig.1

2. For the circuit in Fig.2, let $\beta = 100$, $C_\mu = 2\text{pF}$, $C_\pi = 6\text{pF}$, and neglect r_o . Calculate the midband gain $A_M \equiv \frac{v_o}{v_{sig}}$, and the upper 3-dB frequency f_H . (20%)

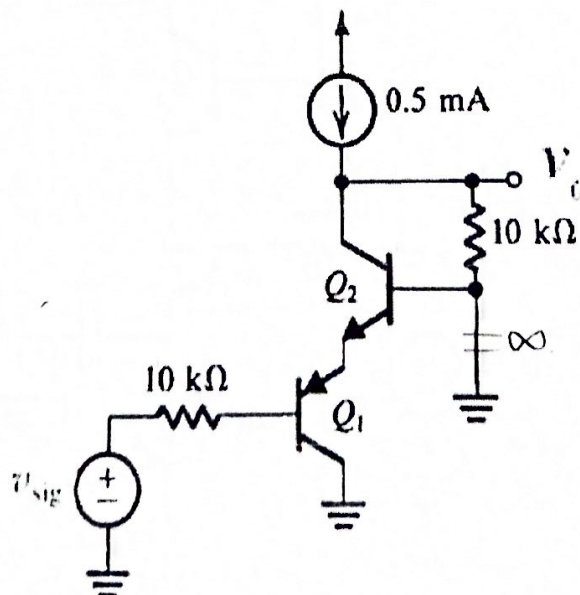


Fig.2

3. The CS amplifier in Fig.3 has $g_m = 2\text{mA/V}$, $C_{gs} = C_{gd} = 1\text{pF}$, $R = 100\text{k}\Omega$, $R_G = 1.2\text{M}\Omega$, $R_L = 12\text{k}\Omega$, and neglect r_o . Use the method of open-circuit time constants to obtain f_H . (20%)

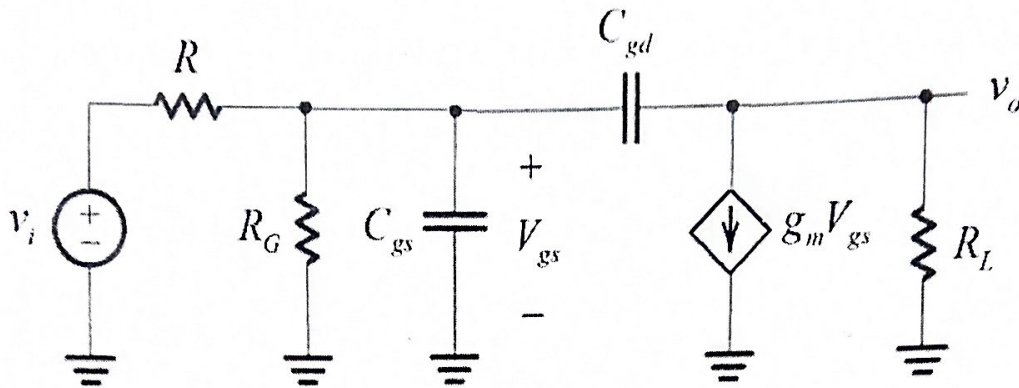


Fig.3

4. In the Fig.4, let $\beta = 100$, $C_\mu = 2\text{pF}$, $C_\pi = 6\text{pF}$, and neglect r_o . Please calculate the midband gain A_M and 3-dB frequency f_H . (20%)

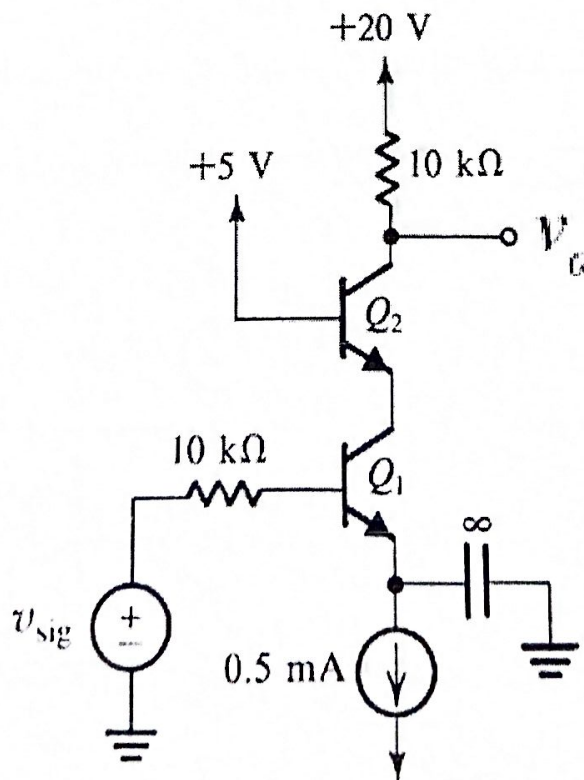


Fig.4

5. Consider the common-emitter amplifier of Fig.5 under the following conditions:

$$R_{sig} = 5\text{k}\Omega, R_1 = 33\text{k}\Omega, R_2 = 22\text{k}\Omega, R_E = 3.9\text{k}\Omega, R_C = 4.7\text{k}\Omega, R_L = 6\text{k}\Omega,$$

$$V_{CC} = 5\text{V}, \beta = 100, \text{ and neglect } r_o.$$

(a) Calculate the mid-band voltage gain.

(b) If $C_{C1} = C_{C2} = C_E = 1\mu\text{F}$, determine the lower 3-dB frequency.

(c) If the BJT is $C_\pi = 2.4\text{ pF}$, and $C_\mu = 1\text{ pF}$, determine the upper 3-dB frequency.

(Using Miller theorem, $f_H \approx \text{Miller's dominant pole}$).

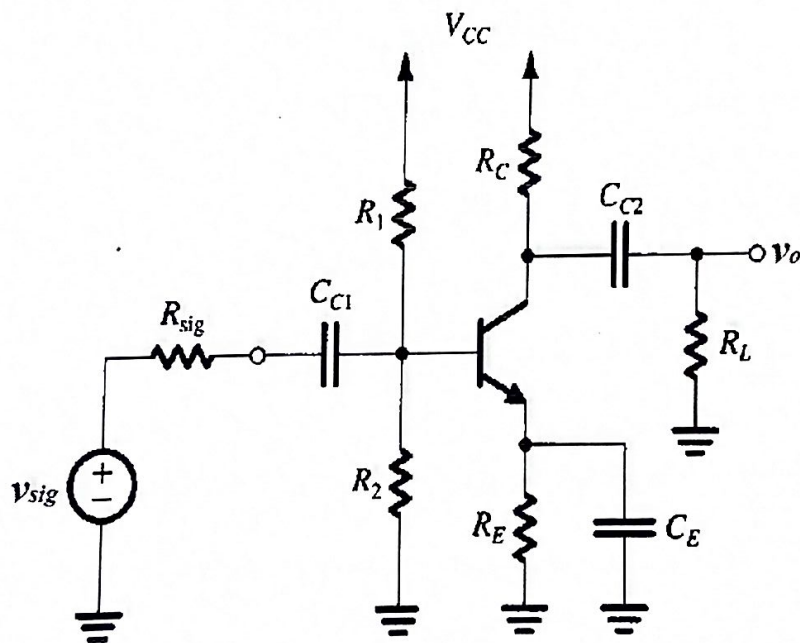


Fig.5