

Final Exam. of Logic Design course (2007)

All of your solution must give the detail design procedures.

1. Implement a T type Flip-Flop from a JK type Flip-Flop. (10%)
2. Give the characteristic table, the excitation table, the state transition diagram, and the next state equation of a JK Flip-Flop. (10%)
3. Design a counter which can provide the following counting sequence by using D type Flip-Flops and assume each Flip-Flop with the Preset and Reset PINs. (20%)

ABC

0 0 0

1 0 0

1 1 0

1 1 1

0 1 1

0 0 1

0 0 0

$$Q(t+1) = \gamma(t)$$

4. Design a module 5 asynchronous counter by using JK type Flip-Flops. (20%)
5. Use T type Flip-Flops design a three bit up/down counter with the counting sequence $0 \leftrightarrow 2 \leftrightarrow 3 \leftrightarrow 1 \leftrightarrow 4 \leftrightarrow 6 \leftrightarrow 5 \leftrightarrow 7 \leftrightarrow 0$. (20%)
6. For the state diagram shown in Figure 1, give the corresponding table for presenting the relations of present-next states, input, and output, then design the logic circuits using T type Flip-Flops. (20%)

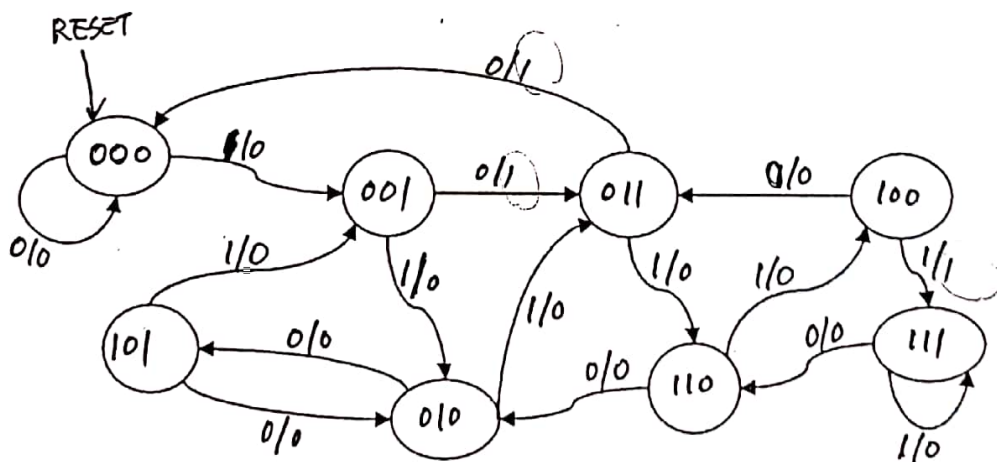


Figure 1