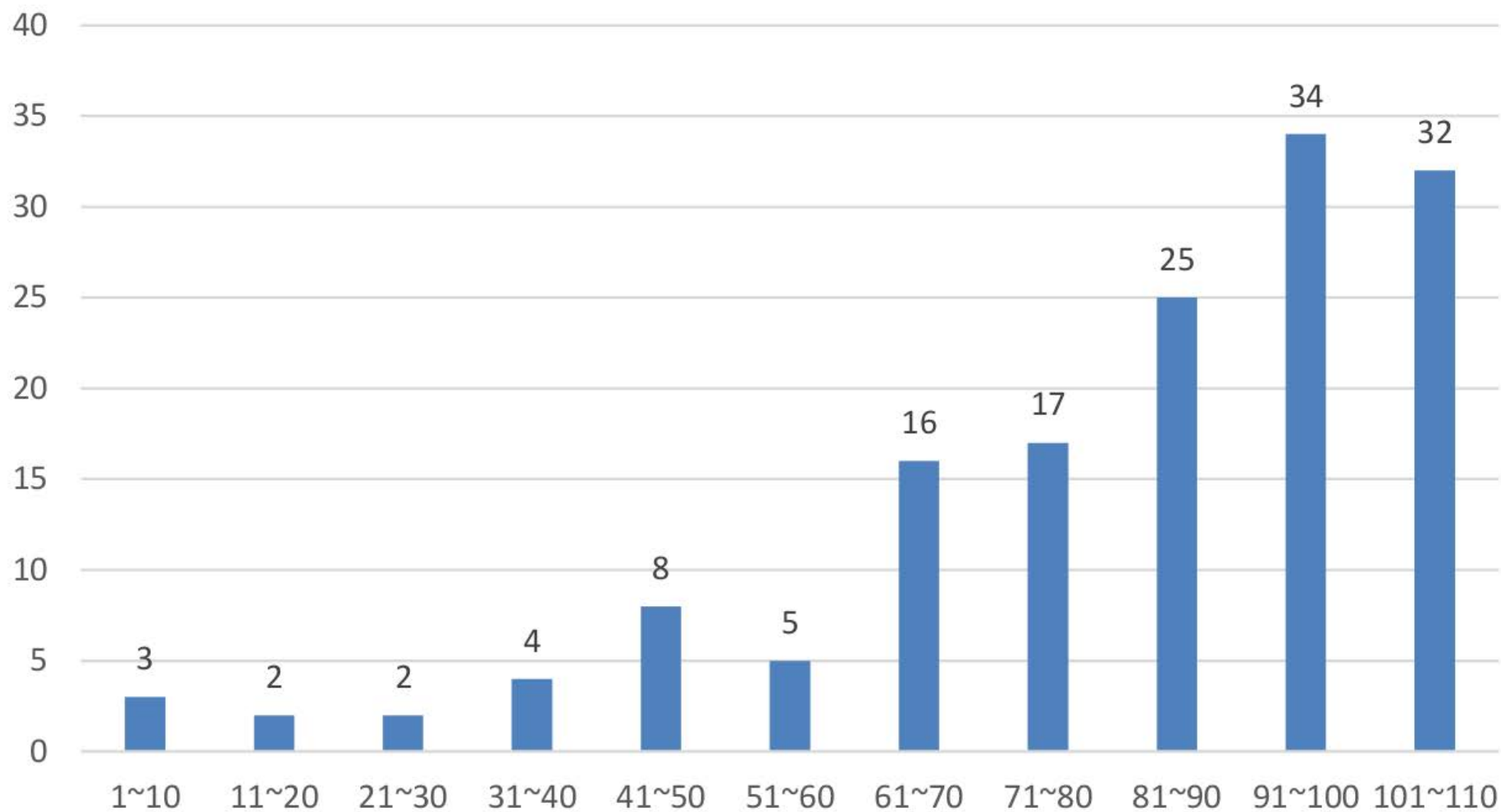


# 電子電工學

## Lecture 10



## 期中考二



Average 79.8  
Std deviation 23.6

# Chapter 9

## AC Circuits


交流

直流
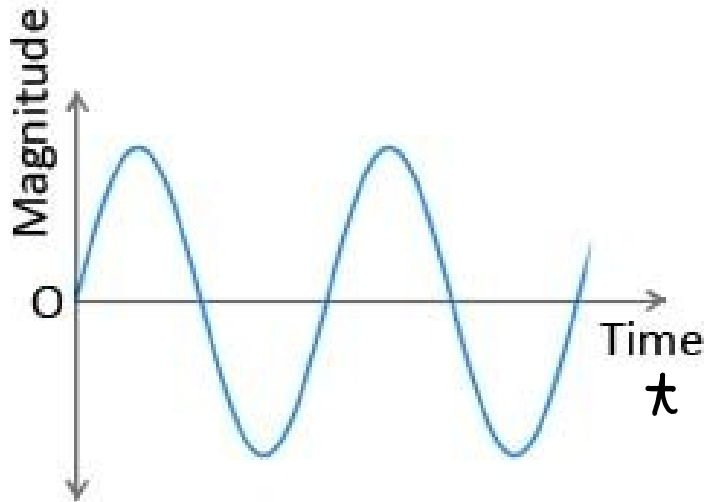
# Alternating current vs Direct current


Periodically  
Change direction

$\left. \begin{matrix} \cos(\omega t) \\ \sin(\omega t) \end{matrix} \right\}$  sinusoidal wave



Alternating Current



Constant  
Flow in one direction

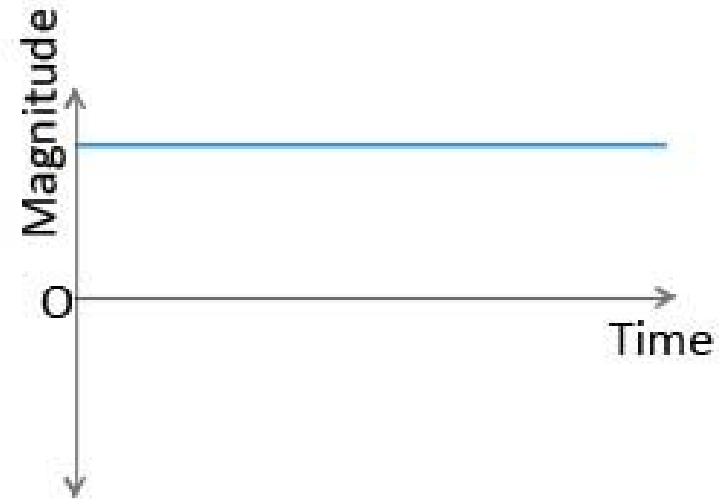


Direct Current

# Alternating current

$$I \propto \cos(\omega t)$$

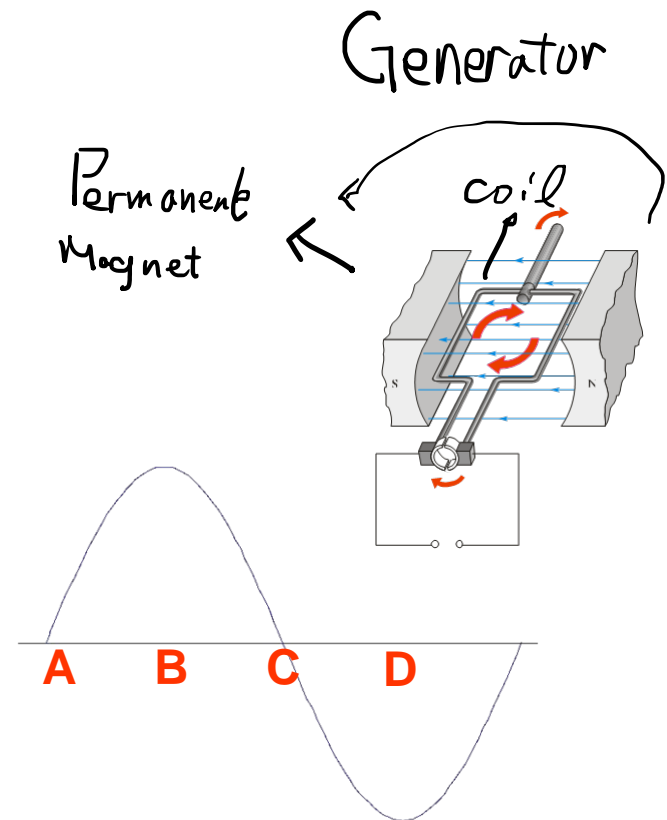
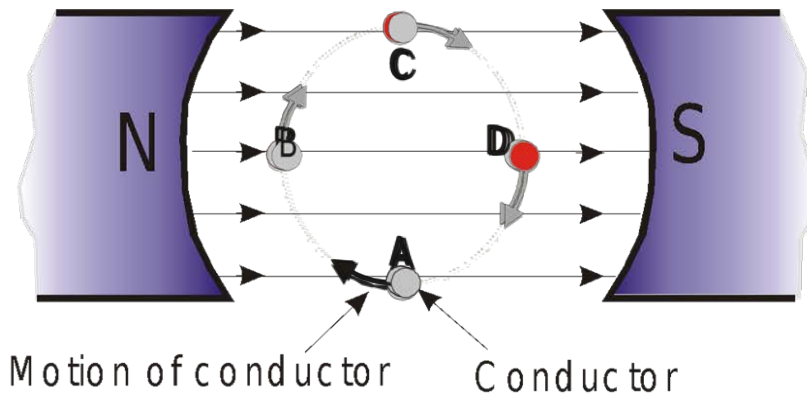


# Sinusoidal waves

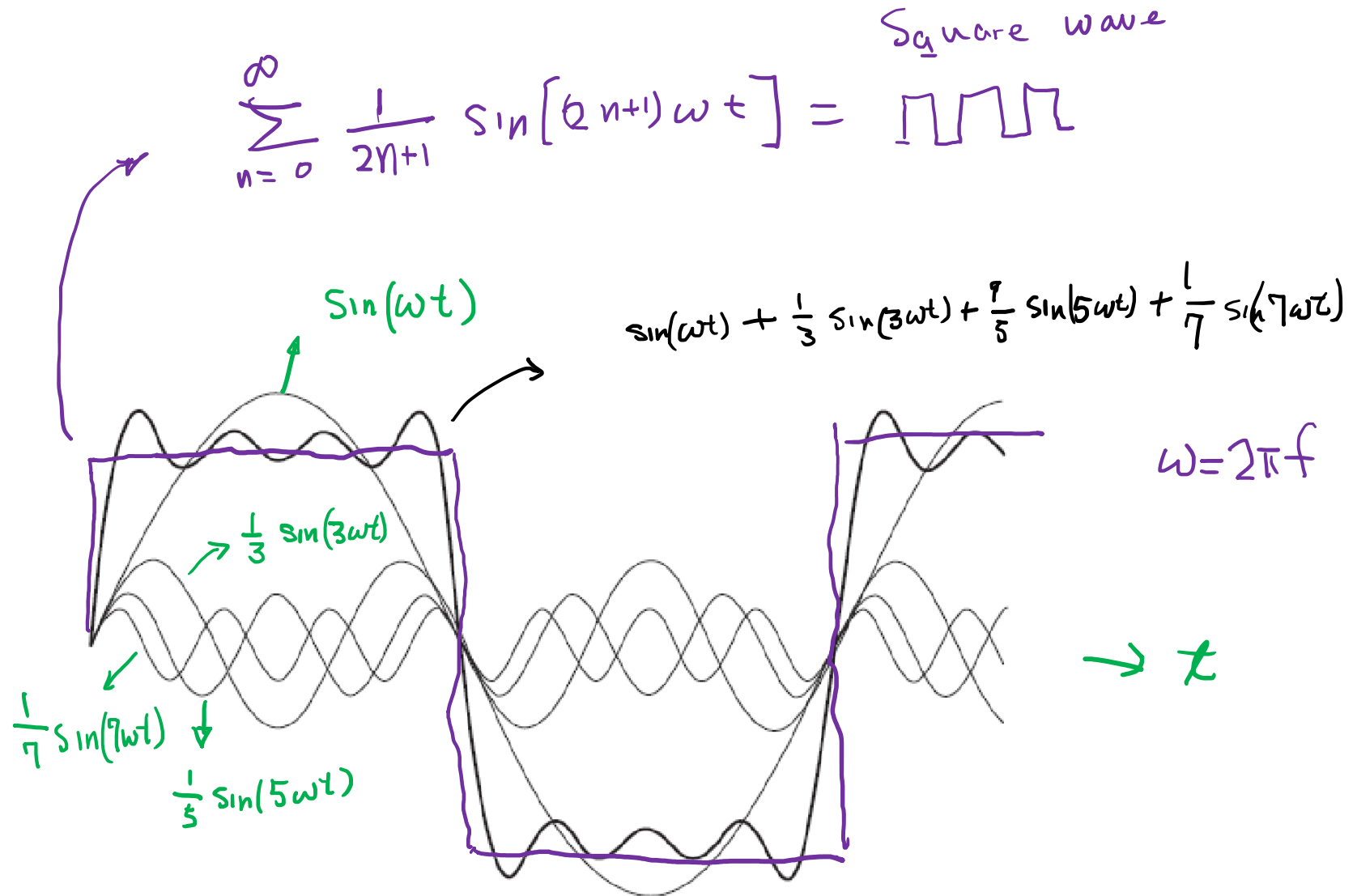

**Figure 9.1** The addition of four sinewaves of relative amplitudes 1, 1/3, 1/5 and 1/7, and relative frequencies  $\omega$ ,  $3\omega$ ,  $5\omega$  and  $7\omega$  (light-lines) yields an approximation (bold line) to a square waveform.

# Sine waves vs square wave

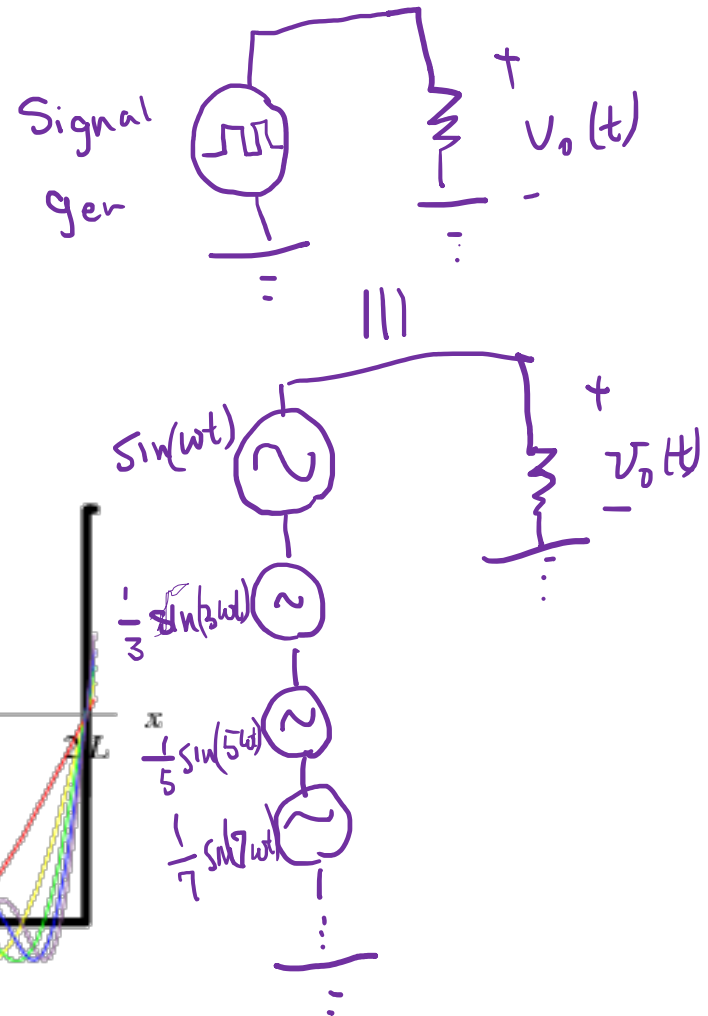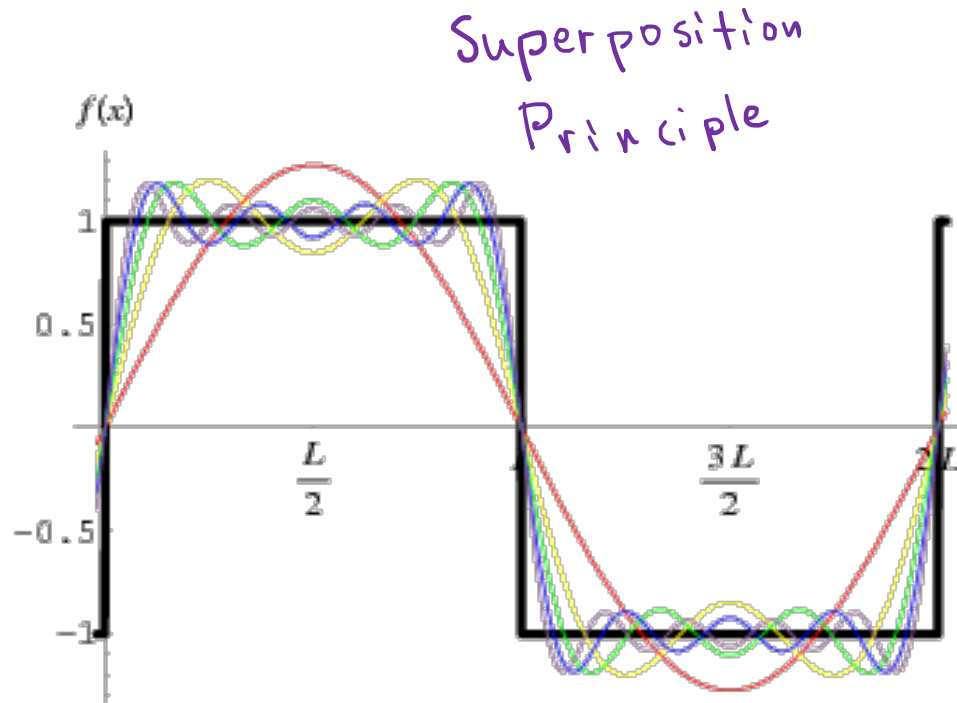




# Fourier series expansion

$$f(x) = a_0 + \sum_{n=1}^{\infty} \left[ a_n \cos\left(\frac{n\pi x}{L}\right) + b_n \sin\left(\frac{n\pi x}{L}\right) \right]$$

$$a_0 = \frac{1}{L} \int_0^L f(x) dx$$

$$a_n = \frac{2}{L} \int_0^L f(x) \cos\left(\frac{n\pi x}{L}\right) dx$$
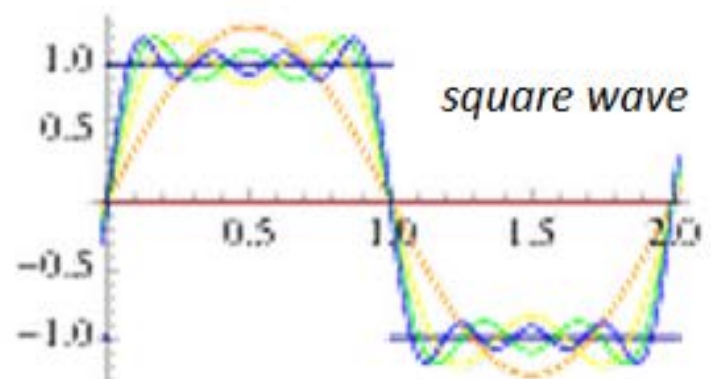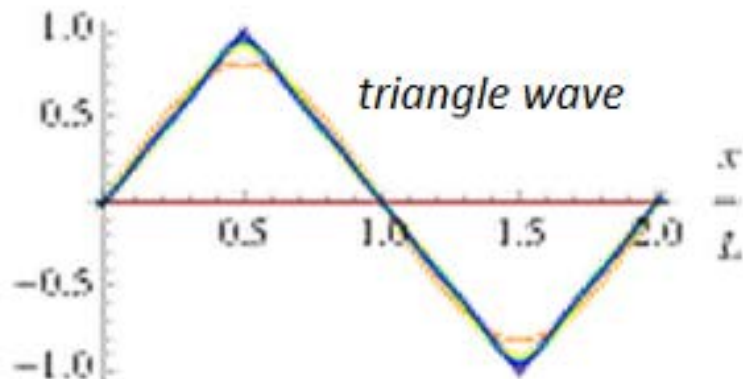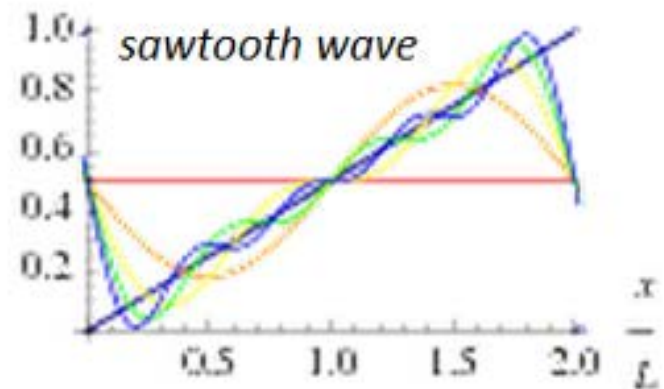
$$b_n = \frac{2}{L} \int_0^L f(x) \sin\left(\frac{n\pi x}{L}\right) dx$$





# Basic Waves

$$A \cos(\omega \underline{2\pi f} t)$$

$$\longrightarrow A \cos(2\pi f t + \phi)$$


$A$  : Amplitude

$f$  : Frequency

$\omega = 2\pi f$  (Radian freq.)

$1/f$  : period

$\phi$  : phase 相角

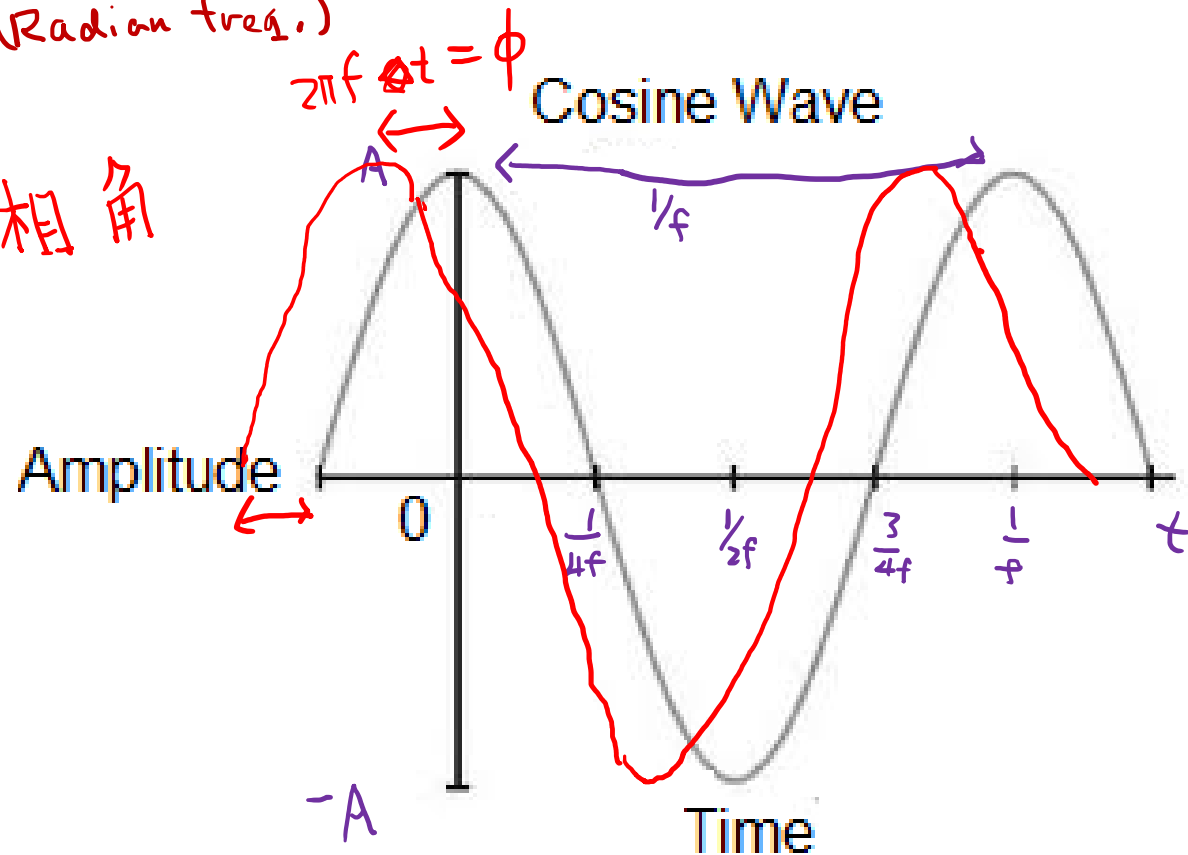


# Capacitor

$$i(t) = C \frac{dv(t)}{dt} \quad \leftarrow \quad \dot{i}(t) = \frac{d q(t)}{dt}$$

Source  $v(t) = V \cos(\omega t)$


$$\Rightarrow i(t) = C V \left[ -\omega \overset{\frac{d}{dt}}{\sin(\omega t)} \right]$$
$$= \underline{-\omega C V \sin(\omega t)}$$

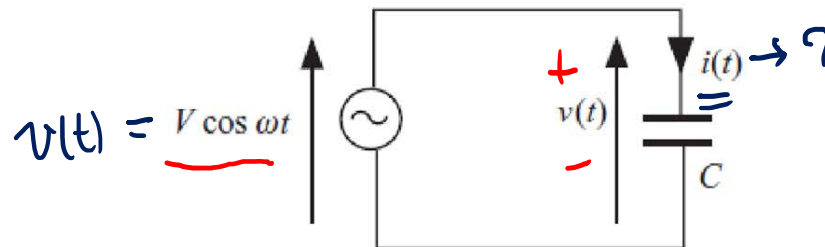


**Figure 9.2** A capacitor with its voltage defined by a sinusoidal voltage source of radian frequency  $\omega$

# Capacitor

$$-\sin(\omega t) = \cos\left(\omega t + \frac{\pi}{2}\right)$$

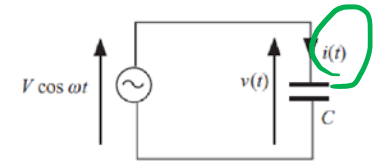

**Figure 9.2** A capacitor with its voltage defined by a sinusoidal voltage source of radian frequency  $\omega$

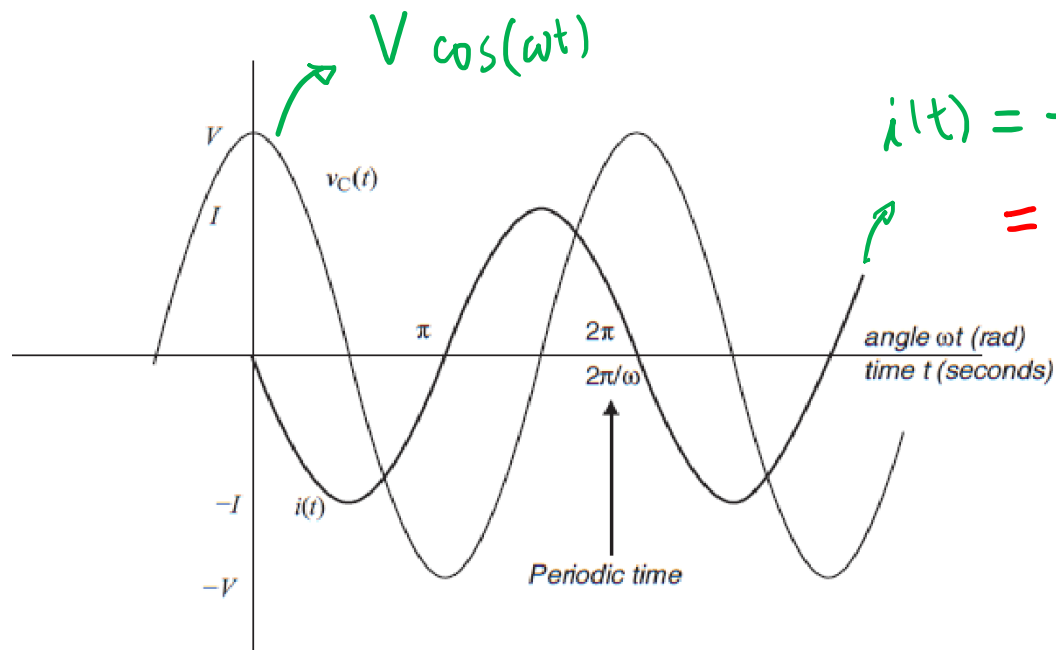


$$i(t) = -\omega C V \sin(\omega t)$$

$$= \omega C V \cos\left(\omega t + \frac{\pi}{2}\right)$$

**Figure 9.3** The waveforms of sinusoidal voltage across, and sinusoidal current through, a capacitor
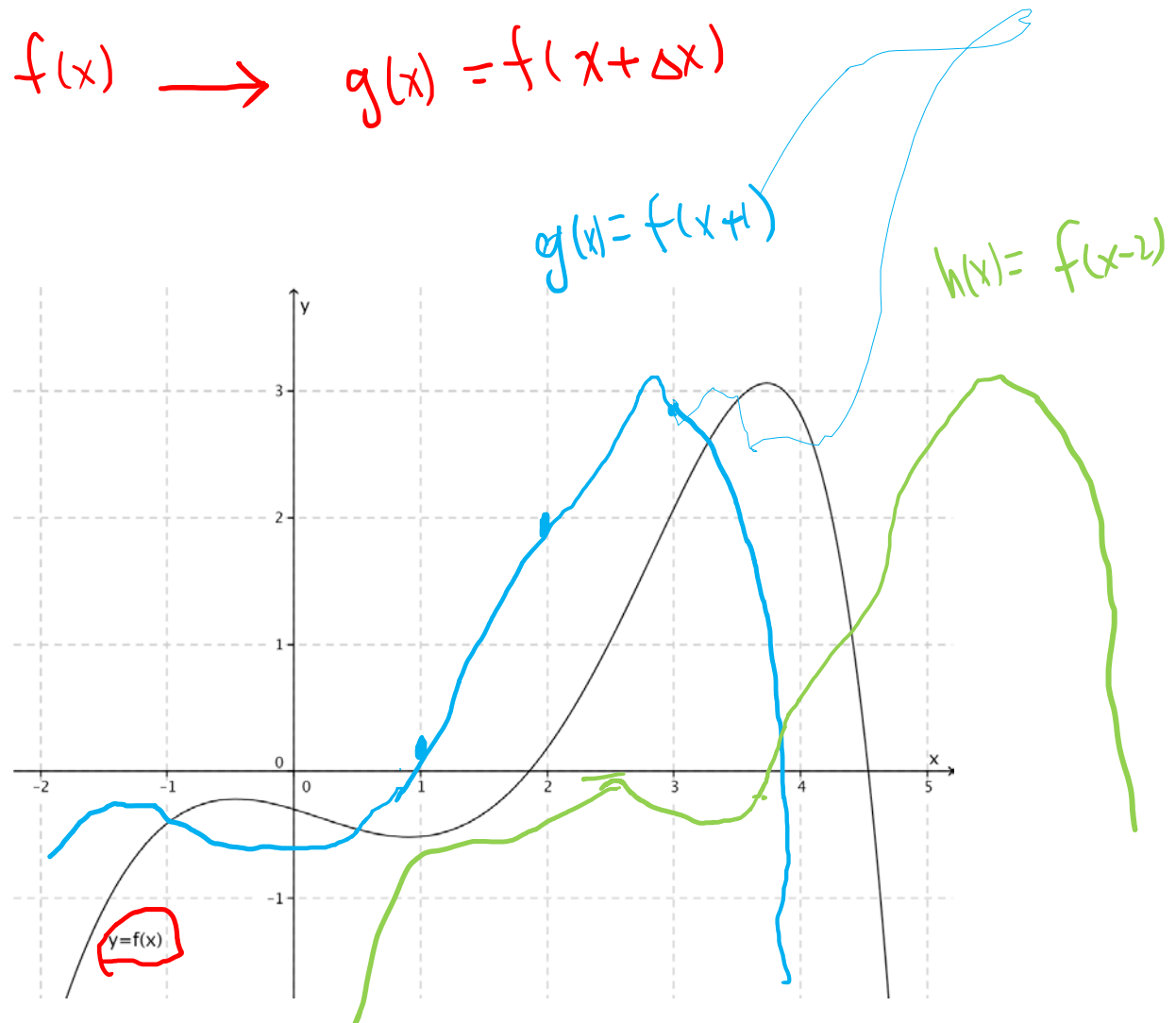
# Review: function shift


$$y = f(x) \rightarrow g(x) = f(x + \Delta x)$$



# Voltage vs Currents

$$v(t) = \underline{V} \cos(\omega t) \qquad i(t) = \underline{I} \cos\left(\omega t + \frac{\pi}{2}\right)$$

1. Frequency : same  $\omega = 2\pi f$
2. Amplitude :  $I = \omega C V$
3. Phase :  $i(t)$  leads  $v(t)$  by  $\pi/2$  ( $90^\circ$ )  
 $v(t)$  lags  $i(t)$

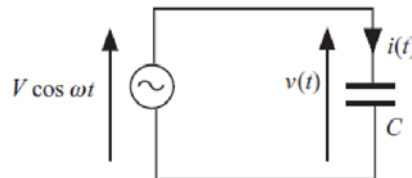

**Figure 9.2** A capacitor with its voltage defined by a sinusoidal voltage source of radian frequency  $\omega$

## Example 9.1


$$v(t) = 4 \cos(2\pi \cdot 159 \cdot t)$$

$$= 4 \cos(1000t)$$

$$i(t) = C \cdot \frac{dv(t)}{dt}$$


$$= \omega C \cdot 4 \cos(1000t + \pi/2)$$

$$= 4 \times 10^{-3} \cos(1000t + \pi/2)$$

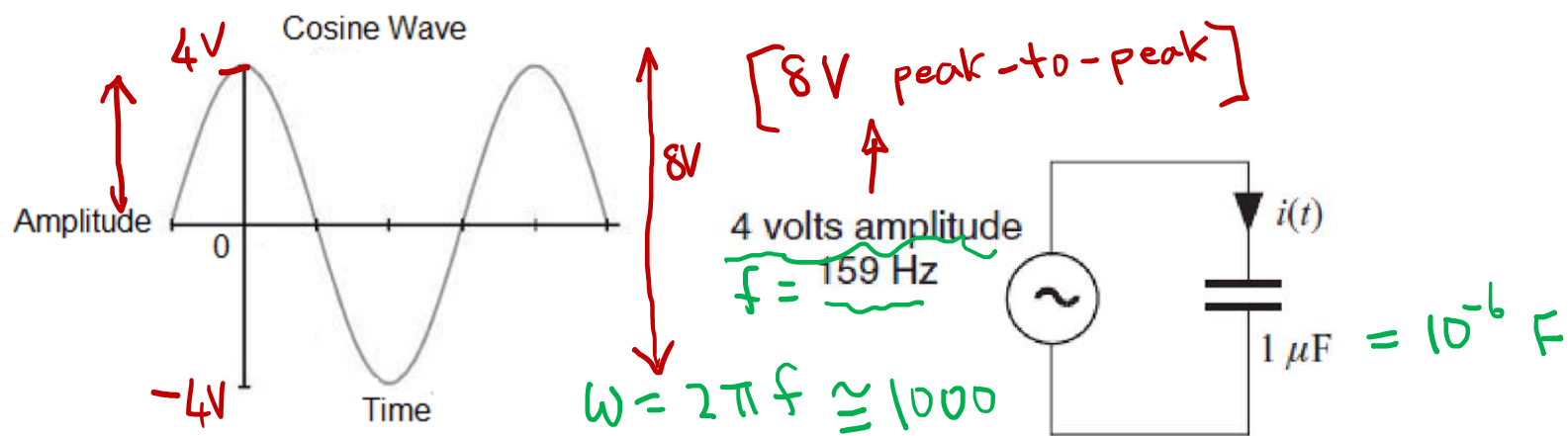

**Figure 9.4** A capacitor with its voltage defined by a sinusoidal voltage source of frequency 159 Hz


## Inductor

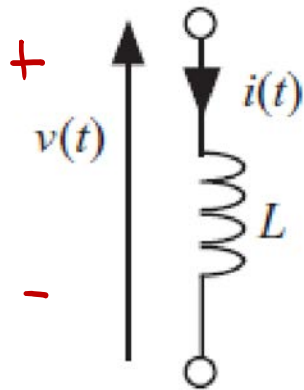

$$\left\{ \begin{aligned} v(t) &= L \cdot \frac{di(t)}{dt} \\ i(t) &= \frac{1}{L} \int_{-\infty}^t v(\tau) d\tau \end{aligned} \right.$$

\* An inductor resists a change in current.

**Figure 9.5** An inductor

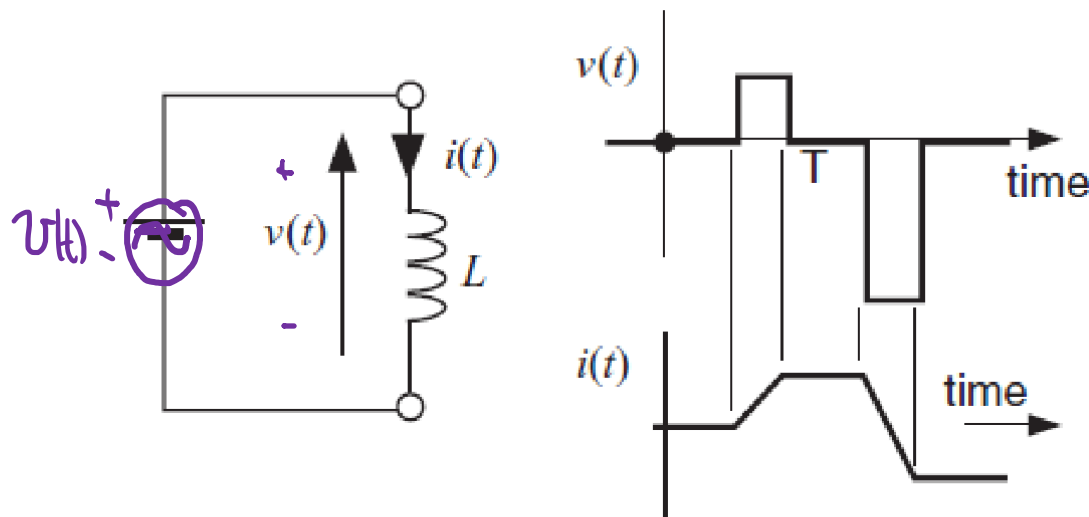


**Figure 9.6** Response of an inductor to a time-varying voltage source

# Inductor

Current src  $i(t) = I \cos(\omega t + \theta)$

$$\begin{aligned} \Rightarrow v(t) &= L \frac{di(t)}{dt} \\ &= -\omega L I \sin(\omega t + \theta) \\ &= \underbrace{\omega L I}_{V = \omega L I} \cos\left(\omega t + \theta + \frac{\pi}{2}\right) \end{aligned}$$

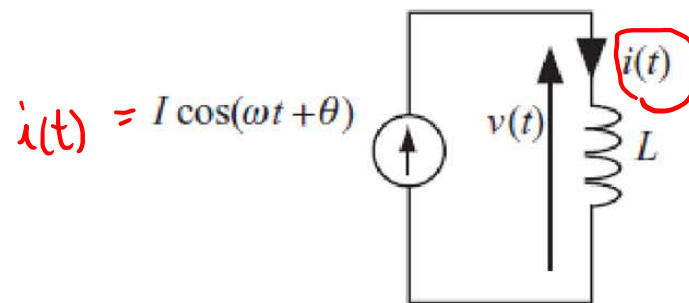

**Figure 9.7** An inductor with its current defined by a sinusoidal current source of radian frequency  $\omega$





# Inductor

voltage vs current

1. Frequency : Same  $\omega = 2\pi f$

2. Amplitude :  $V = \omega L I$

3. phase:  $v(t)$  leads  $i(t)$   
by  $\pi/2$

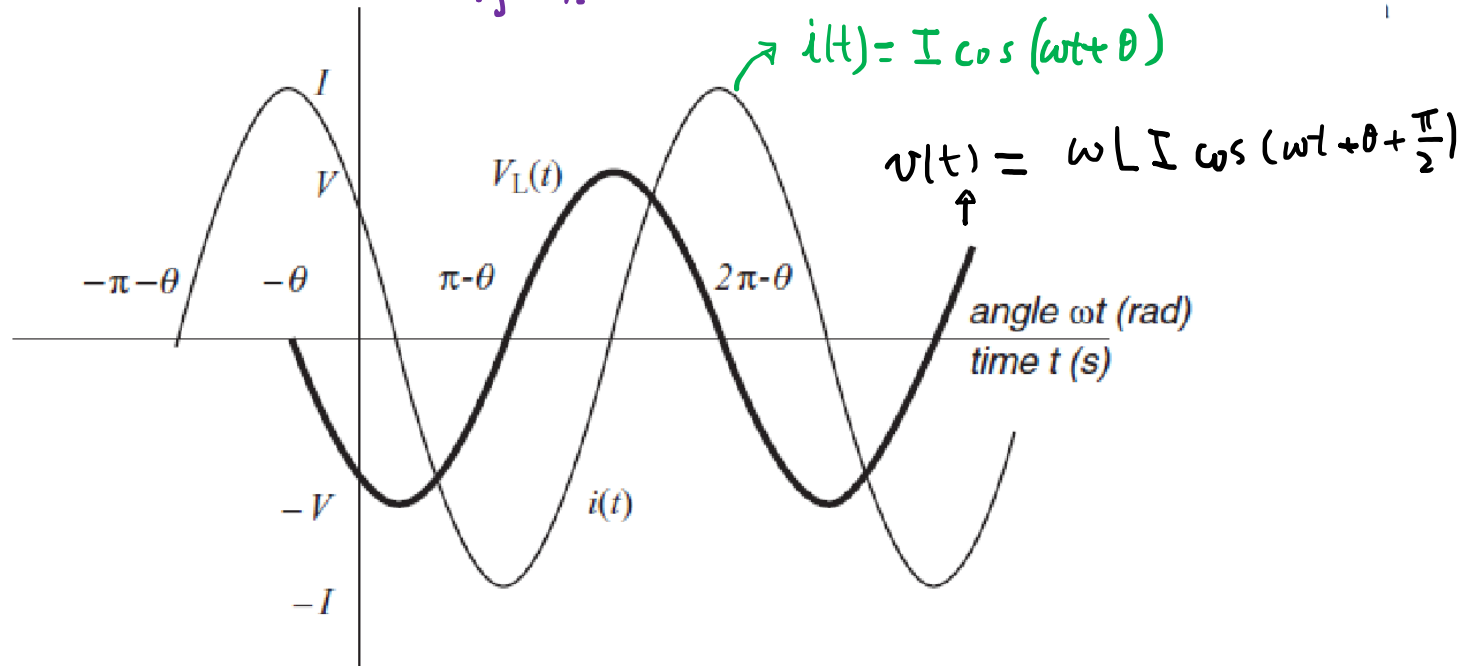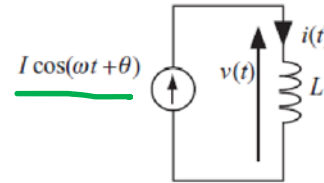

**Figure 9.8** The waveforms of sinusoidal current through, and sinusoidal voltage across, an inductor

# Resistor

Source  $v(t) = V \cos \omega t$


By Ohm's Law:  $i(t) = \frac{1}{R} v(t)$   
 $= \frac{V}{R} \cos(\omega t)$

Voltage vs Current

Freq: same  $\omega = 2\pi f$


Amp:  $I = V/R$

Phase: same  $\Delta\phi = 0$

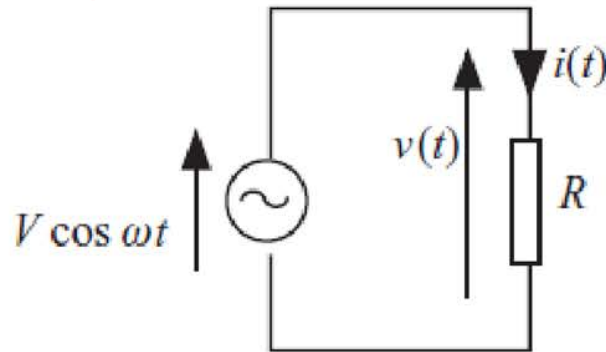


**Figure 9.9** A resistor with its voltage defined by a sinusoidal voltage source of radian frequency  $\omega$

# Summary: passive components

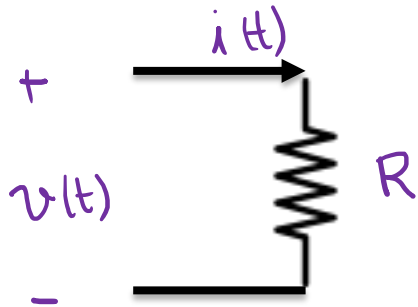


$$v(t) = V \cos(\omega t)$$
$$i(t) = I \cos(\omega t)$$

$$V = RI$$

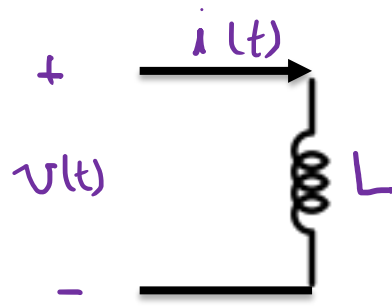

$$i(t) = I \cos(\omega t)$$
$$v(t) = V \cos(\omega t + \frac{\pi}{2})$$

$$V = \omega L I$$

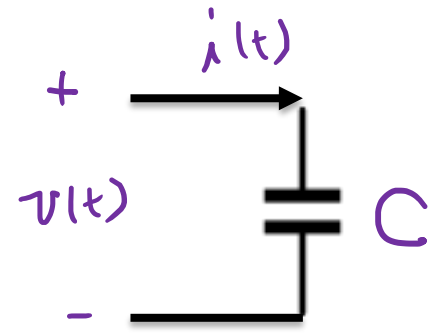

$$v(t) = V \cos(\omega t)$$
$$i(t) = I \cos(\omega t + \frac{\pi}{2})$$


$$I = \omega C V$$

$$V = (\frac{1}{\omega C}) I$$

## Example 9.2

$$\text{KCL: } i_R(t) = i_L(t) = i_S(t) = 2 \cos(1000t + 20^\circ)$$

$$\begin{aligned} \text{KVL: } v_S(t) &= v_R(t) + v_L(t) \\ &= \underset{\substack{\downarrow \\ 100\ \Omega}}{R} \cdot i_S(t) + \underset{\substack{\downarrow \\ 100\ \text{mH} \\ = 0.1\ \text{H}}}{L} \cdot \frac{di_S(t)}{dt} \end{aligned}$$

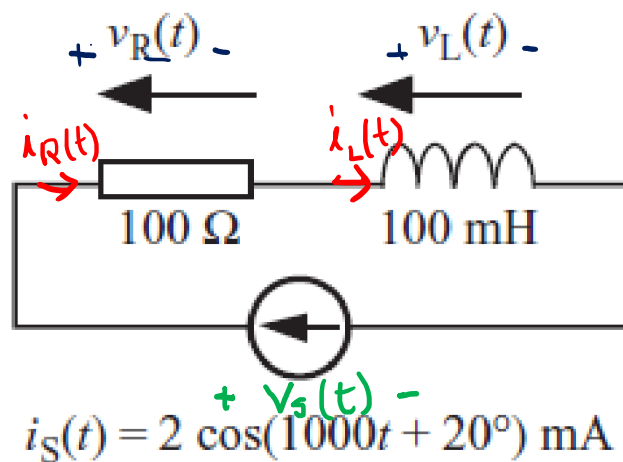

**Figure 9.10** The circuit discussed in Example 9.2

## Example 9.2

$$v_R(t) = R \cdot i_S(t) = 200 \cos(1000t + 20^\circ)$$


$$v_L(t) = L \frac{di_S(t)}{dt} = 200 \cos(1000t + 20^\circ + 90^\circ)$$

$$v_S(t) = v_R(t) + v_L(t)$$

$$= 200 \left[ \cos(1000t + 20^\circ) + \cos(1000t + 110^\circ) \right]$$

Apply Sum-to-product

rule

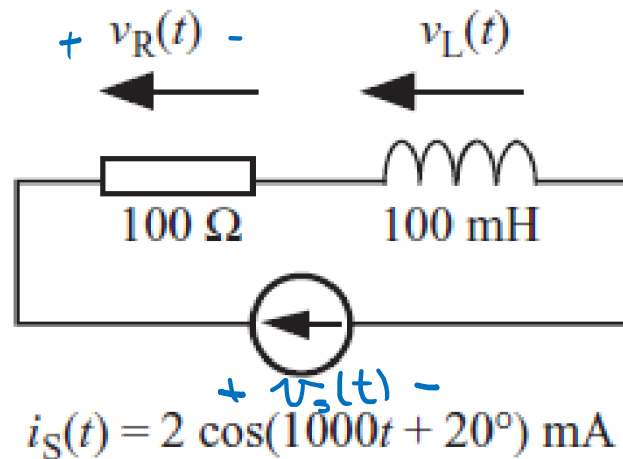

**Figure 9.10** The circuit discussed in Example 9.2

# Trigonometric Identities

$$\begin{aligned} & \cos(1000t + 20^\circ) + \cos(1000t + 110^\circ) \\ &= 2 \cos(1000t + 65^\circ) \cos(45^\circ) \\ &= \sqrt{2} \cos(1000t + 65^\circ) \end{aligned}$$

## Sum to Product Formula

$$\cos x + \cos y = 2 \cos \frac{x+y}{2} \cos \frac{x-y}{2}$$

$$\cos x - \cos y = -2 \sin \frac{x+y}{2} \sin \frac{x-y}{2}$$

$$\sin x + \sin y = 2 \sin \frac{x+y}{2} \cos \frac{x-y}{2}$$

$$\sin x - \sin y = 2 \cos \frac{x+y}{2} \sin \frac{x-y}{2}$$

## Product to Sum Formula

$$2 \cos x \cos y = \cos(x+y) + \cos(x-y)$$


$$-2 \sin x \sin y = \cos(x+y) - \cos(x-y)$$

$$2 \sin x \cos y = \sin(x+y) + \sin(x-y)$$

$$2 \cos x \sin y = \sin(x+y) - \sin(x-y).$$

## Example 9.2

$$v_s(t) = 200 \times \sqrt{2} \cos(1000t + 65^\circ)$$
$$\approx 282.8 \cos(1000t + 65^\circ)$$

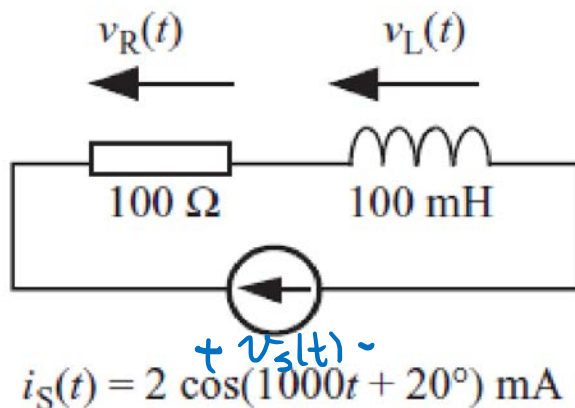

**Figure 9.10** The circuit discussed in Example 9.2

# R-L circuit

Given  $V(t) = V \cos(\omega t)$

Find  $i(t) = ?$  unknown


KCL, KVL

$$V(t) = V_R(t) + V_L(t)$$

$$= R \cdot i(t) + L \frac{di(t)}{dt}$$

$$V \cos(\omega t) = R i(t) + L i'(t)$$

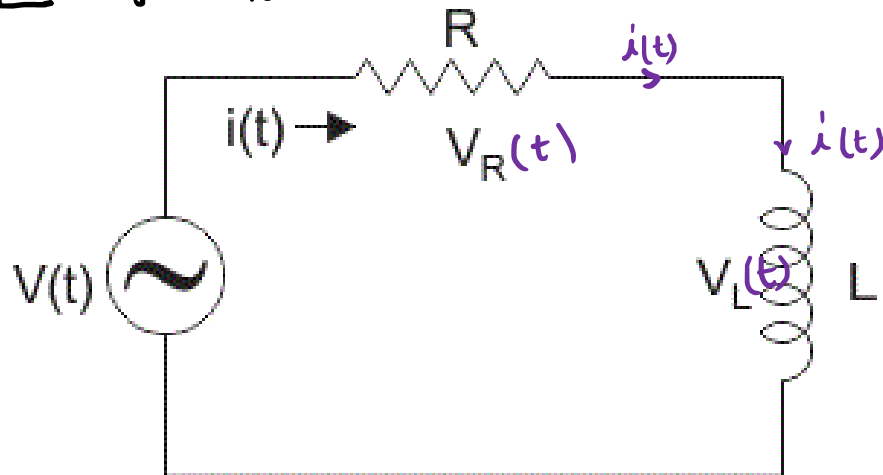ODE for  $i(t) \Rightarrow i'(t) + \frac{R}{L} i(t) = \frac{V}{L} \cos(\omega t)$






## Quiz

Suppose the initial current is  $i(0)=0$  for the circuit shown in the figure below.

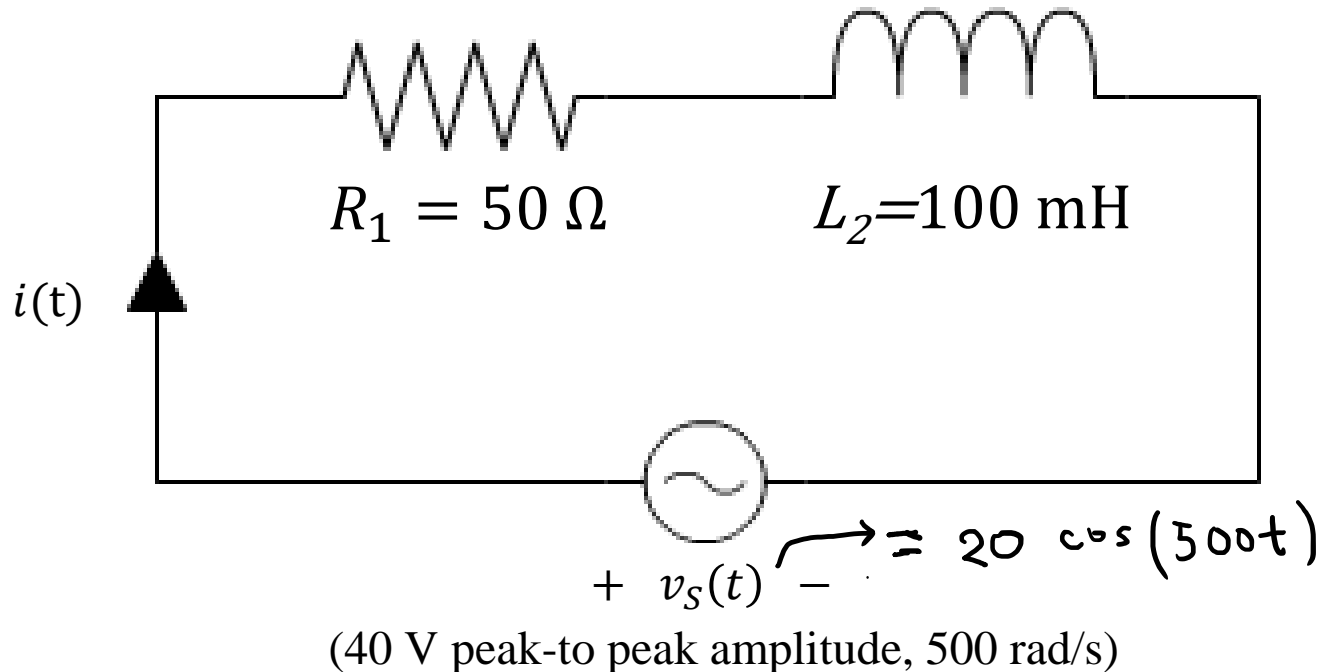1. Write a differential equation for the current  $i(t)$ .
2. Apply the knowledge you learned from Engineering Math to solve  $i(t)$  for  $t>0$ .



# Quiz Review

(1) KVL:  $V_s(t) = R_1 i(t) + L_2 \frac{di(t)}{dt}$

$\downarrow$   
 $20 \cos(500t)$

$\downarrow$   
 $50$

$\downarrow$   
 $0.1$


$\rightarrow 0.1 i'(t) + 50 i(t) = 20 \cos(500t)$

$i'(t) + 500 i(t) = 200 \cos(500t)$

(2) Solve

Method 1. Integrating Factor  $\times e^{-500t}$

2. Undetermined coefficient

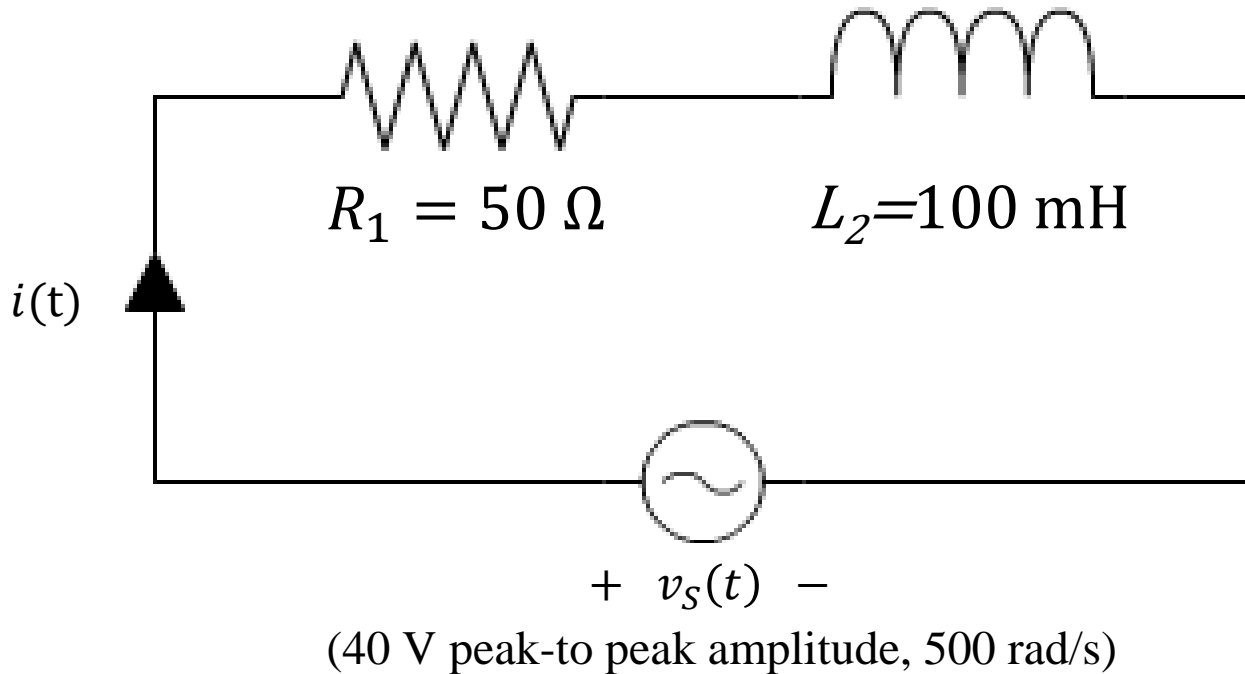

# Quiz Review

Let  $i(t) = i_h(t) + i_p(t)$  →  $i_h(t) = k e^{-500t}$


$$\begin{cases} i_h'(t) + 500 i_h(t) = 0 \\ i_p'(t) + 500 i_p(t) = 200 \cos(500t) \end{cases} \leftarrow$$

Let  $i_p(t) = A \cos(500t) + B \sin(500t)$

↳  $A = B = 0.2$

⇒  $i(t) = k e^{-500t} + 0.2 \cos(500t) + 0.2 \sin(500t)$

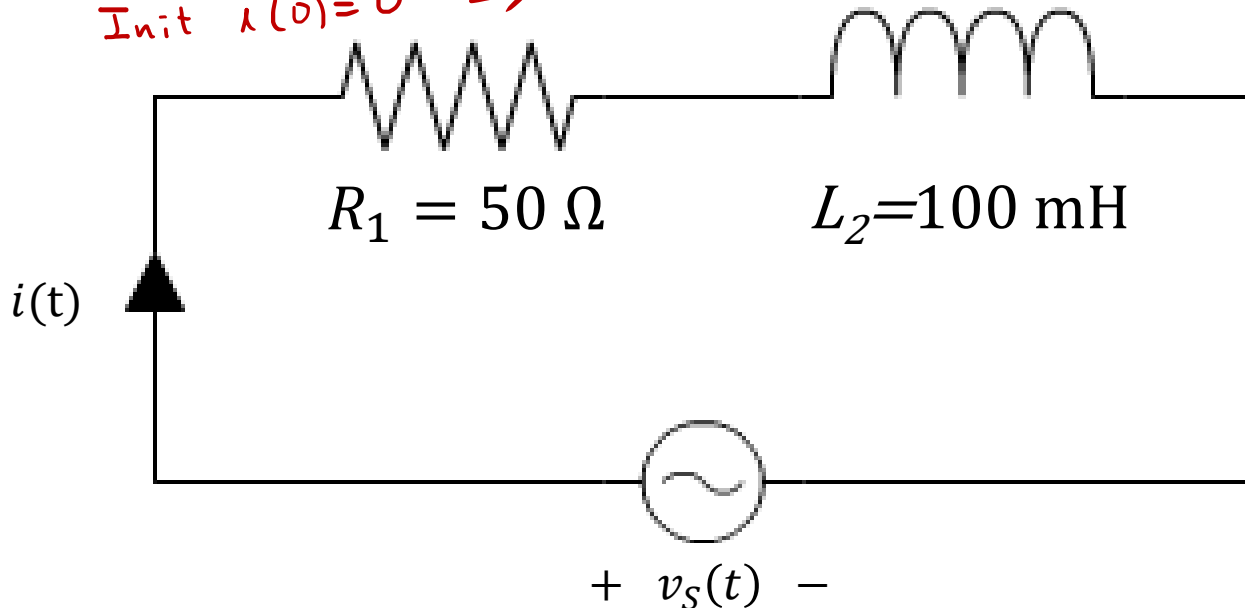Init  $i(0) = 0 \Rightarrow k + 0.2 = 0 \Rightarrow k = -0.2$



(40 V peak-to-peak amplitude, 500 rad/s)

# Summary

1. AC vs DC

2.  $\cos(\omega t)$

3. Component

$$\omega, \phi = \pm \frac{\pi}{2}, \begin{cases} V = \omega L I \\ V = RI \\ V = \frac{1}{\omega C} I \end{cases}$$

4. KCL, KVL

→ Sum-to-product  
Differential Equation

→ Simplify!

→ Phasor Diagram