

5. An amplifier in Fig. 5 with an input resistance $R_i = 3\text{k}\Omega$, when driven by a current source $i_s = 1\text{mA}$ and a source resistance $R_s = 15\text{k}\Omega$, has a short-circuit output current of 2mA and an open-circuit output voltage of 10V . If the amplifier is used to drive a $5\text{k}\Omega$ load R_L , find the values of the

- (a) $A = ?$ (4%)
- (b) voltage gain v_o / v_i (4%)
- (b) current gain i_o / i_i (4%)
- (c) overall current gain i_o / i_s (4%)
- (d) power gain (P_o / P_i) . (4%)

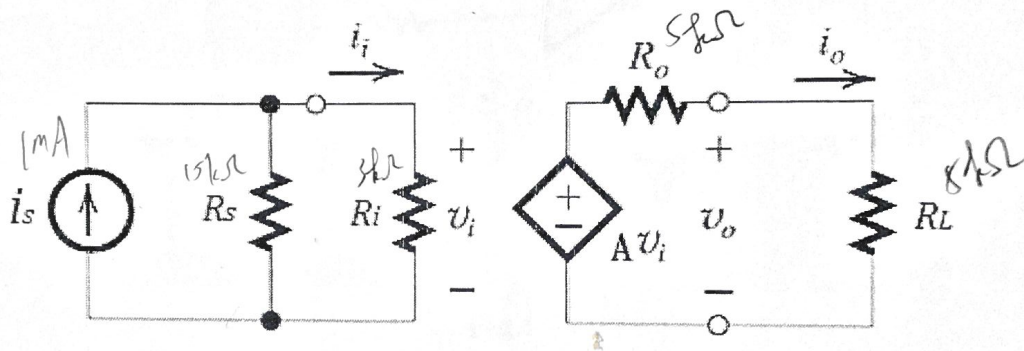


Fig. 5

$$R_o = \frac{10}{2\text{mA}} = 5\text{k}\Omega$$

$$V_o =$$