

考試時間: 100 Mins

作弊一律零分計算

Name: \_\_\_\_\_ ID: \_\_\_\_\_

一、10pts 解釋何謂組合電路？何謂序向電路？並各舉兩個例子。

Combinational means "memory-less", a digital circuit is combinational if its output values only depend on its input values.

Ex: AND gate, OR gate.

Sequential systems exhibit behaviors (output values) that depend not only on the current input values, but also on previous input values.

Ex: R-S latch, J-K flip flop.

二、10pts **Prove** (by any means you like) the equation:  $AB+BC+A'C=AB+A'C$ 



A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

	AB		A	
C	0	1	0	1
0	0	0	1	0
1	1	1	1	0
	B			

$$F=AB+A'C$$

三、15pts Given  $F_0 = B'C'$   $F_1 = AB+A'C$   $F_2 = B'C'+AB$   $F_3 = A'C+B$ ,

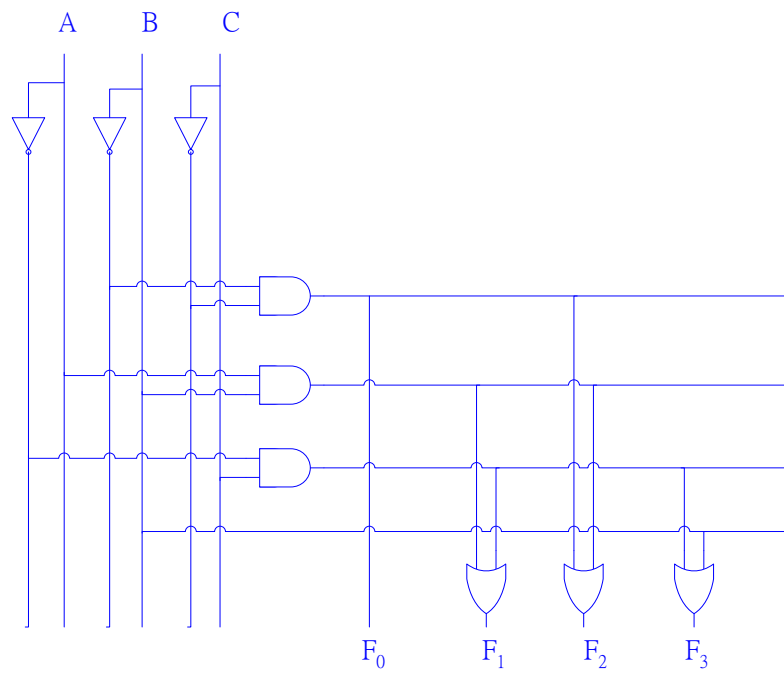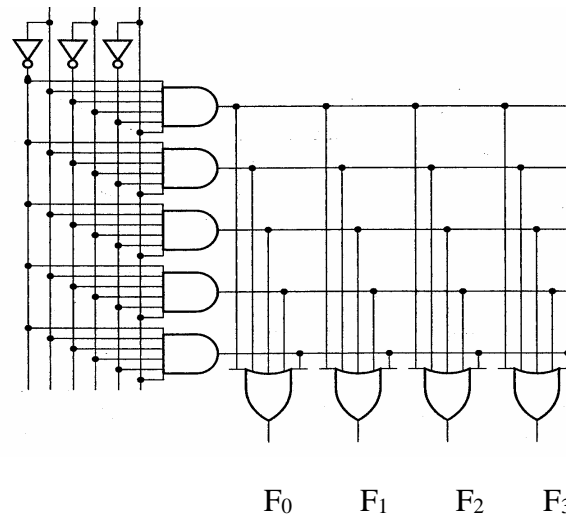Use the PLA of Fig.1 to implement the above four functions, i.e. by taking out those fuses that you don't need and draw the final configuration.



四、15pts (a) Draw the state diagram (including the race condition) for the R-S latch.


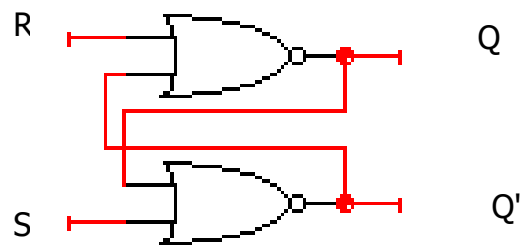



Fig.2

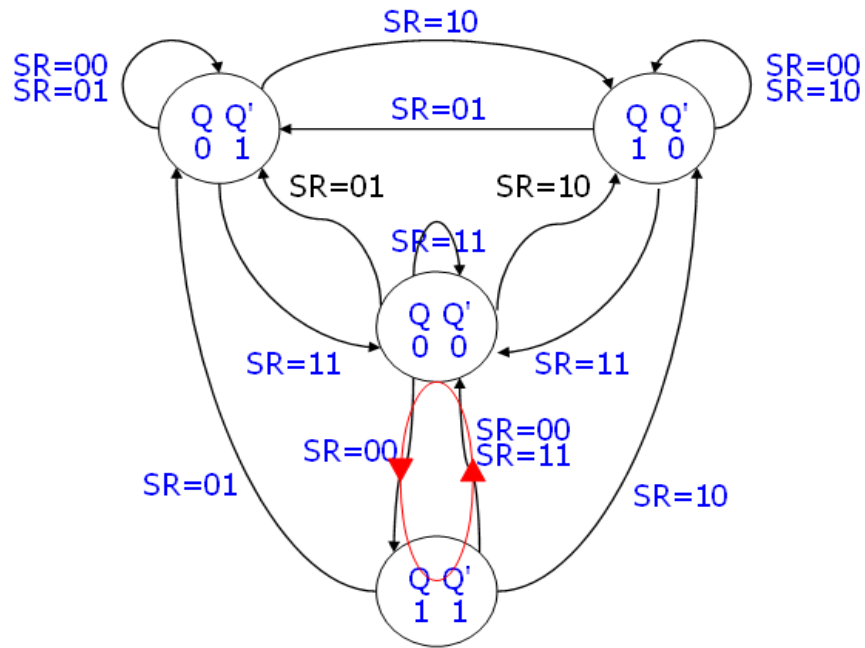

possible oscillation between states 00 and 11

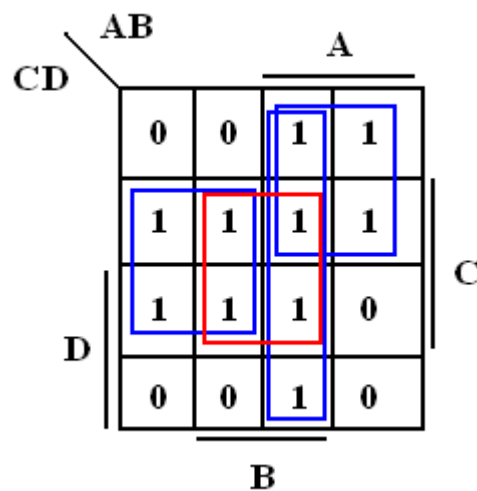- (b) **Explain** the condition under which the R-S latch starts the race-condition (i.e. oscillation).  
 (請由推論電路圖之流程來解釋，故在此省略說明。)

五、15pts  $F(A,B,C,D)=\Sigma m(1,3,5,7,8,9,12,13,14,15)$ , implement a hazard-free design for F.



$$F=AB+AD+A'C$$

According to avoid hazard,  
 $F=AB+AD'+A'C+BC$

六、15pts Complete the waveform for  $Q_0$  and  $Q_1$ .

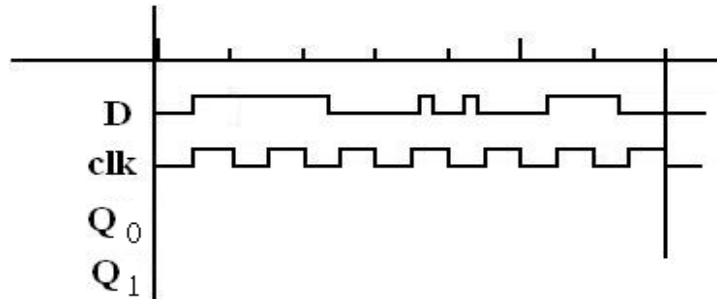


Fig.3


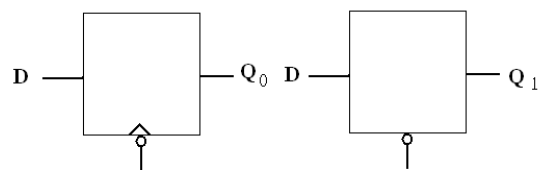


Fig.4

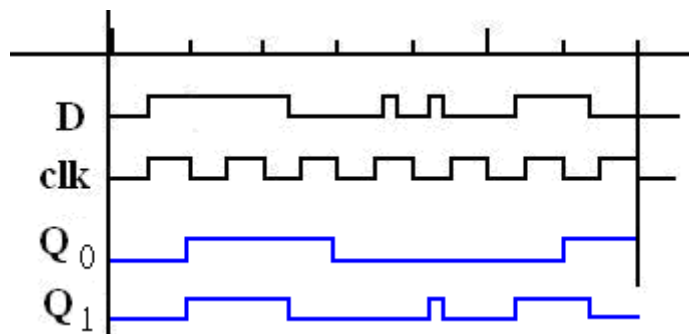

七、20pts Given a 2-bit right-shift register in Fig.5

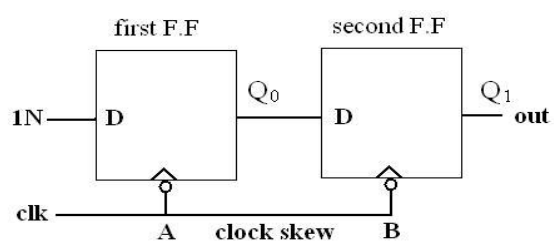


Fig.5

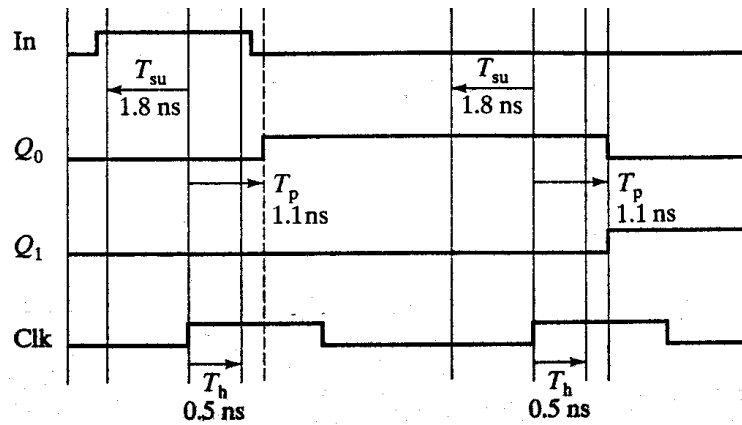


Fig.6

- (a) **Explain** why  $T_p > T_h$  is a must-be-true condition for the 2-bit shift register to work properly.

因為若  $T_p < T_h$ ， $Q_0$  輸出給 second F.F 的 D 之值可能已經改變，無法達到“shift register”之效果。

- (b) Assume the wire length between A and B is so long that it adds a clock delay  $T_{skew}$  to the second FF (Flip Flop). In that case, how the condition in (a) should be changed so that the shift register can work properly?

$$T_p > T_h + T_{skew}$$

- (c) According to (b) and the parameters in Fig.6, calculate  $\max(T_{skew}) = ?$

$$T_{skew} < T_p - T_h = 1.1 - 0.5 = 0.6 \text{ ns}$$