

3. The circuit in Fig.3:

(a) Find the resistances looking into node 1,  $R_1$ ; node 2,  $R_2$ ; node 3,  $R_3$ . (6%)

(b) Find the currents  $I_1$ ,  $I_2$ ,  $I_3$ , in term of the input current  $I$ . (6%)

(c) Find the voltages at nodes 1, 2, and 3, that is,  $V_1$ ,  $V_2$ , and  $V_3$  in term of  $IR$ . (6%)

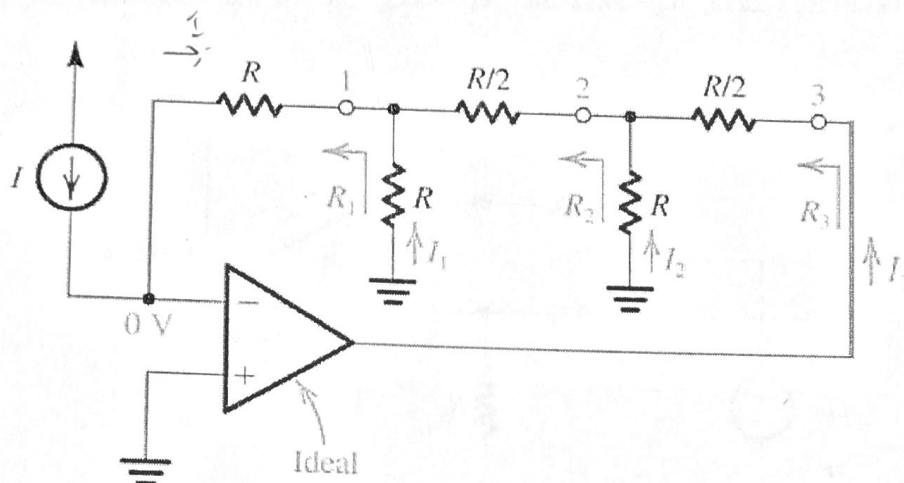


Fig.3

4. For the circuit in Fig.4, find the transfer function  $T(s) = \frac{V_i(s)}{V_s(s)}$ , and arrange it in the appropriate standard form from the frequency response of STC networks.

(a) What is its DC gain? (4%)

(b) What is the corner frequency  $\omega_0$ ? (4%)

(c) Is this a high-pass or a low-pass network? (4%)

(d) For the case of  $R_s = 10 \text{ k}\Omega$ ,  $R_i = 40 \text{ k}\Omega$ , and  $C_i = 5 \text{ pF}$ , find  $f_0$ . (5%)

(e) What is the value of  $|T(j\omega_0)|$ ? (5%)

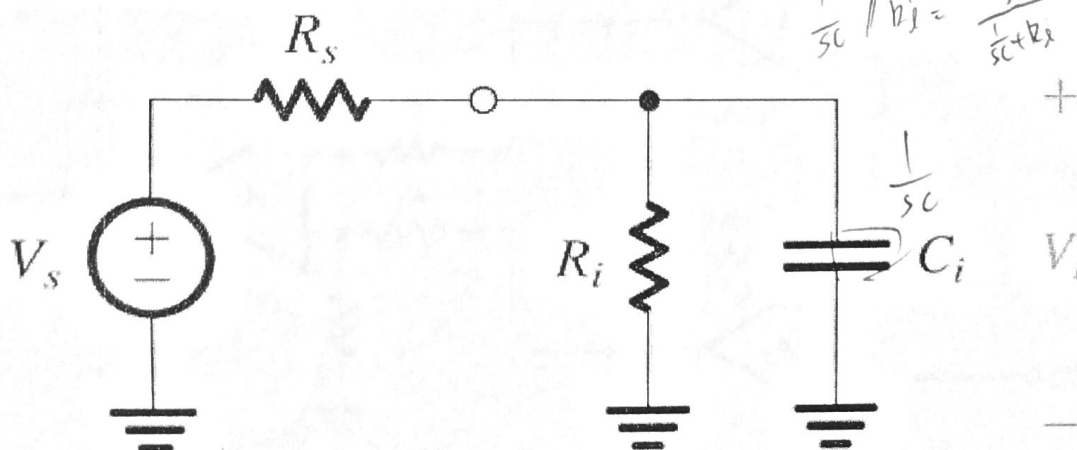


Fig.4