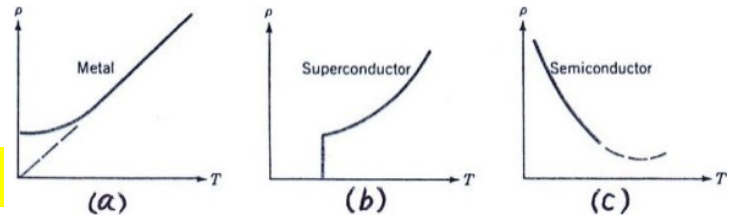


用上式解釋  $\rho(T)$  :


- (a) 導體  $T \uparrow \Rightarrow v_{rms} \uparrow \Rightarrow \tau \downarrow \Rightarrow \rho \uparrow$  .  
 (b) 超導體  $\tau = \infty$  when  $T < T_c$  .  
 (c) 半導體  $T \uparrow \Rightarrow n \uparrow$  (holes)  $\Rightarrow \rho \downarrow$  ,  
 ( 參考 :  $n \uparrow$  的原因見右下圖。 )



For copper,  $\tau = m/ne^2\rho = 2.5 \times 10^{-14} s$   
 $\Rightarrow \lambda = v_{rms}\tau = 2.5 \times 10^{-9} m$  at 300 K .  
 ( 原子間距  $\approx 0.25 \times 10^{-9} m$  )

If  $\lambda$  is fixed, then  $\tau = \lambda/v_{rms} \propto 1/\sqrt{T} \Rightarrow$   
 $\rho \propto \sqrt{T}$ , which is wrong.  $\therefore \lambda$  is not fixed.

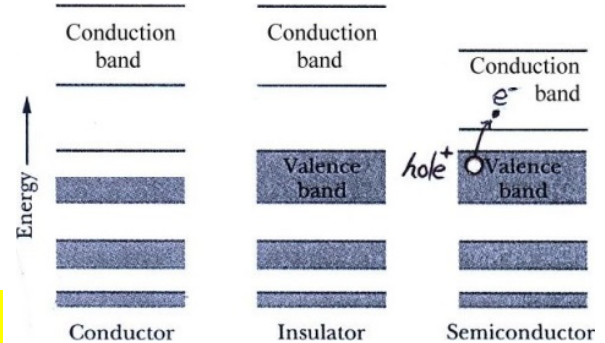In fact  $\lambda \approx 1 mm$  at low temp. , 古典物理不能解釋。



**Power**  $P = dU/dt = V_{ab} dq/dt = V_{ab} I = (IR)I = I^2 R = V_{ab} (V_{ab}/R) = V_{ab}^2 / R$  .

H.W. : Ex. 12, 39; Prob. 4, 5.

本章後 Special topic: Atmospheric Electricity ( 關於晴天電場、雷電的產生，非常有趣 )

## Ch. 28 Direct Current Circuit





**Electromotive force** ( Emf , 電動勢 ):

把正電荷自低電位推到高電位，在發電機是磁力；在 Van de Graaff 加速器是 moving belt；在化學電池是擴散。

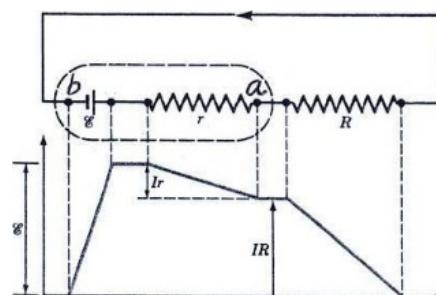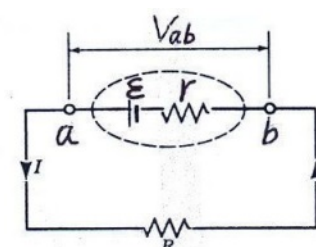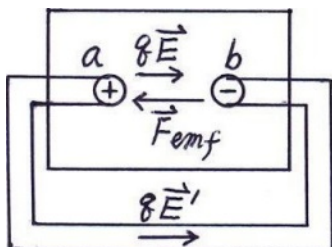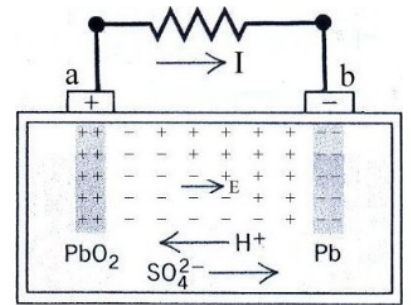例：鉛酸電池  $Pb(s) + PbO_2(s) + 4H^+(aq) + 2SO_4^{2-} \rightleftharpoons 2PbSO_4(s) + 2H_2O$  (  $\approx 2V$  ) .

$H^+$  (  $SO_4^{2-}$  ) 在正極  $PbO_2$  ( 負極  $Pb$  ) 被抓掉，

正 ( 負 ) 極附近濃度降低造成擴散，且擴散電流  $>$  漂移電流  $J = \sigma E$ ，而有向左的淨電流。正電荷憑機率逆電場而上  
 所需能量來自化學釋出的熱能。





電動勢  $\mathcal{E} = \int_b^a \vec{F}_{emf} \cdot d\vec{s} / q$  ( $\vec{F}_{emf}$  作功); 電位差  $V_{ab} = \int_{a' \text{ 內}}^b \vec{E} \cdot d\vec{s} = \int_{a \text{ 外}}^b \vec{E}' \cdot d\vec{s}$ 。

$\vec{F}_{emf} > q\vec{E}$  時表示有內電阻  $r$ ， $\mathcal{E} > V_{ab}$ ， $Ir \equiv \mathcal{E} - V_{ab} = \int_b^a [(\vec{F}_{emf}/q) + \vec{E}] \cdot d\vec{s}$ 。

$\mathcal{E} - Ir = V_{ab} = IR$ ，故  $I = \mathcal{E}/(R + r)$ 。又  $\therefore$  energy output  $dU = V_{ab} dq$ ，  
 $\therefore$  power  $P = dU/dt = V_{ab} dq/dt = V_{ab} I = (IR)I = I^2 R = V_{ab} (V_{ab}/R) = V_{ab}^2 / R$ 。


Kirchhoff's junction rule:  $\sum I_{in} = \sum I_{out}$  for any junction  
 (否則接點會有電荷累積)。

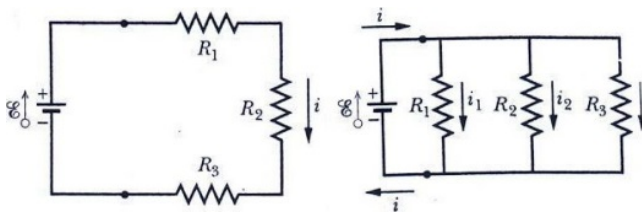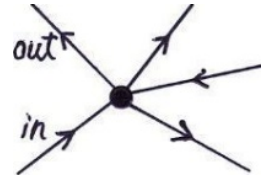Kirchhoff's loop rule:  $\sum \Delta V_i = 0$  for any closed loop。



串聯:  $\mathcal{E} - iR_1 - iR_2 - iR_3 = 0 \Rightarrow$   
 $i = \mathcal{E}/(R_1 + R_2 + R_3) \Rightarrow R_{eq} = R_1 + R_2 + R_3$ 。  
 並聯:  $i = i_1 + i_2 + i_3 = \mathcal{E}/R_1 + \mathcal{E}/R_2 + \mathcal{E}/R_3$   
 $\Rightarrow 1/R_{eq} = i/\mathcal{E} = 1/R_1 + 1/R_2 + 1/R_3$ 。

例:

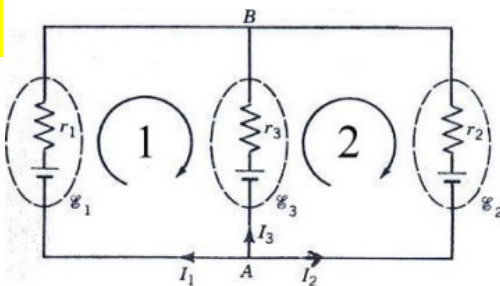

j-rule  $\Rightarrow I_1 + I_2 + I_3 = 0 \Rightarrow I_3 = -I_1 - I_2$ 。

Loop 1:  $\mathcal{E}_1 - I_1 r_1 + (-I_1 - I_2) r_3 - \mathcal{E}_3 = 0$ 。


Loop 2:  $\mathcal{E}_3 - (-I_1 - I_2) r_3 + I_2 r_2 - \mathcal{E}_2 = 0$ 。

(1)  $(r_1 + r_3)I_1 + r_3 I_2 = \mathcal{E}_1 - \mathcal{E}_3$ ，

(2)  $r_3 I_1 + (r_2 + r_3)I_2 = \mathcal{E}_2 - \mathcal{E}_3$ 。

$$D = \begin{vmatrix} r_1 + r_3 & r_3 \\ r_3 & r_2 + r_3 \end{vmatrix}, \quad I_1 = \frac{1}{D} \begin{vmatrix} \mathcal{E}_1 - \mathcal{E}_3 & r_3 \\ \mathcal{E}_2 - \mathcal{E}_3 & r_2 + r_3 \end{vmatrix}, \quad I_2 = \frac{1}{D} \begin{vmatrix} r_1 + r_3 & \mathcal{E}_1 - \mathcal{E}_3 \\ r_3 & \mathcal{E}_2 - \mathcal{E}_3 \end{vmatrix}.$$

例:

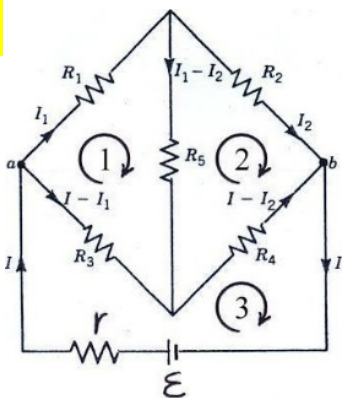

j-rule  $\Rightarrow I_3 = I - I_1$ ,  $I_4 = I - I_2$ ,  $I_5 = I_1 - I_2$ 。

Loop 1:  $-I_1 R_1 - (I_1 - I_2) R_5 + (I - I_1) R_3 = 0$ 。

Loop 2:  $-I_2 R_2 + (I - I_2) R_4 + (I_1 - I_2) R_5 = 0$ 。

Loop 3:  $\mathcal{E} - Ir - (I - I_1) R_3 - (I - I_2) R_4 = 0$ 。

(1)  $(R_1 + R_3 + R_5)I_1 - R_5 I_2 - R_3 I = 0$ ;

(2)  $-R_5 I_1 + (R_2 + R_4 + R_5)I_2 - IR_4 = 0$ ;

(3)  $-R_3 I_1 - R_4 I_2 + (r + R_3 + R_4)I = \mathcal{E}$ 。


$$D = \begin{vmatrix} R_1 + R_3 + R_5 & -R_5 & -R_3 \\ -R_5 & R_2 + R_4 + R_5 & -R_4 \\ -R_3 & -R_4 & r + R_3 + R_4 \end{vmatrix}, \quad I = \frac{1}{D} \begin{vmatrix} R_1 + R_3 + R_5 & -R_5 & 0 \\ -R_5 & R_2 + R_4 + R_5 & 0 \\ -R_3 & -R_4 & \mathcal{E} \end{vmatrix}.$$

$R_{eq} = \varepsilon/I$ . (另一作法：以 (1) & (2) 解得  $I_1 = \alpha I$  ,  $I_2 = \beta I$  , 則  
 $\varepsilon = Ir + \alpha IR_1 + \beta IR_2 \Rightarrow R_{eq} = \varepsilon/I = r + \alpha R_1 + \beta R_2$  . )

In general, assign one loop current to each independent loop,

$\therefore$  (# of ind. loop currents) = (# of ind. equations),

$\therefore$  the solution is unique.

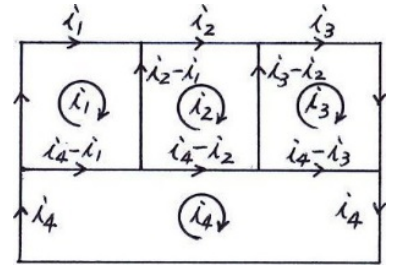


### Matching of Resistance


$\therefore i = \varepsilon/(R+r)$ ,  $\therefore$  power in  $R$ :  $P = I^2 R = \varepsilon^2 R / (R+r)^2$ .

Maximum  $P$  at  $dP/dR = \varepsilon^2 [1/(R+r)^2 - 2R/(R+r)^3] = 0$ ,

i.e.  $R+r = 2R$ ,  $\therefore R = r$ .

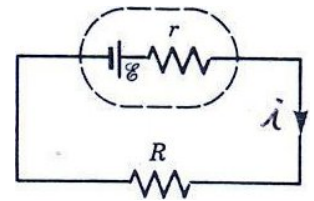


### Measuring Instruments

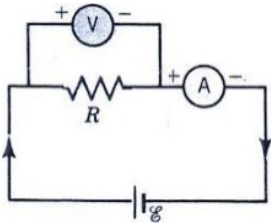


$R_A \ll R$   
 (使得  $V_A \ll V$ );

$R_V \gg R$   
 (使得  $I_V \ll I$ ).

### Galvanometer

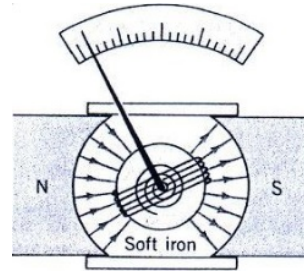

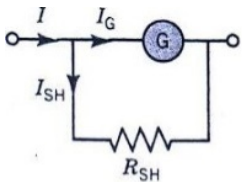$R_G = 20\Omega$  ,  
 滿額 (full scale)  
 $I_G = 1\text{ mA}$  ,  
 $V_G = 0.020\text{ volts}$  .  
 (=  $(10^{-3}\text{ A}) \times 20\Omega$ )



**Ammeter** : 滿額  $I = 10\text{ A}$  ,  $R_{sh} = ?$

$R_{sh} = V_G / (I - I_G) = 0.020\text{ V} / (10 - 10^{-3})\text{ A} = 0.0020\Omega$ .

$R_A = R_G R_{sh} / (R_G + R_{sh}) \approx 0.0020\Omega$ .




**Voltmeter** : 滿額  $V = 10\text{ volts}$  ,  $R_s = ?$

$R_s = (V - V_G) / I_G = (10 - 0.020)\text{ V} / 10^{-3}\text{ A} = 9980\Omega$ .

$R_V = R_s + R_G = 10000\Omega$ .

### Ohmmeter

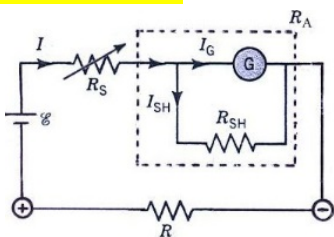


Meter 內  $\varepsilon$  固定，有好幾組  $(R_s, R_{sh})$  以適用不同  
 電阻範圍 ( $R_s \sim R$ ) 與電流範圍 ( $i \sim \varepsilon/R$ ) .

$R_A = R_G R_{sh} / (R_G + R_{sh})$  ,


$i = \varepsilon / (R_s + R_A + R)$ ,  $i_G / i = R_{sh} / (R_G + R_{sh})$  .

歸零：  $R = 0$  時，調  $R_s$  直到  $G$  電流達滿額  $I_G$ ，而得  $i$  的  
 滿額  $I = \varepsilon / (R_s + R_A)$  . 當然  $I_G / I = i_G / i$  .

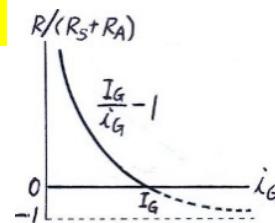放上  $R$  :  $I/i = (R_s + R_A + R)/(R_s + R_A) = 1 + R/(R_s + R_A)$  ,  
故  $R = [(I/i) - 1](R_s + R_A) = [(I_G/i_G) - 1](R_s + R_A)$  。



## Potentiometer

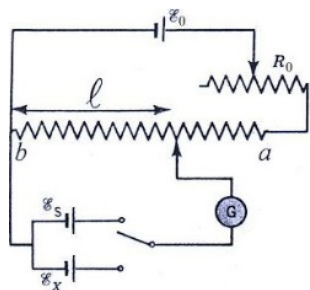

$\varepsilon_X$  待測， $\varepsilon_s$  是標準電池 ( 珍貴 )， $\varepsilon_0$  是便宜的電池。  
 $R_0$  用來調出適當的  $V_{ab}$  (  $V_{ab} > \varepsilon_X, \varepsilon_s$  )。  
放上  $\varepsilon_s$ ，調  $l$  直到  $i_G = 0$ ，而得  $l = l_s$ ；  
換上  $\varepsilon_X$ ，調  $l$  直到  $i_G = 0$ ，而得  $l = l_X$ 。  
 $\varepsilon_X = (l_X/l_s)\varepsilon_s$ 。

## R-C Circuit

### (a) Discharge

$$q/C - iR = 0, \therefore dq/dt = -i = -q/RC.$$



$$\int_{q(0)}^{q(t)} dq'/q' = -(1/RC) \int_0^t dt' \Rightarrow \ln[q(t)/q(0)] = -t/RC$$

$$\Rightarrow q(t) = q(0)e^{-t/RC} = q(0)e^{-t/\tau}, \tau \equiv RC \text{ time constant.}$$

$$q(\tau) = q(0)e^{-1} = 0.37q(0), \text{ i.e. } \tau = T_{1/e} \text{ (1/e life).}$$

$$T_{1/2}: q(0)/2 = q(0)e^{-T_{1/2}/\tau} \Rightarrow T_{1/2} = \tau \ln 2 = 0.693\tau.$$
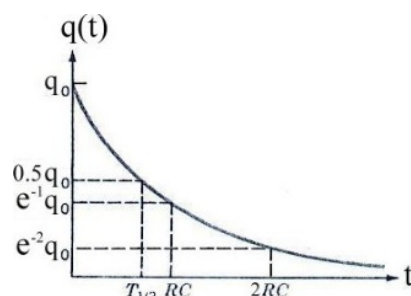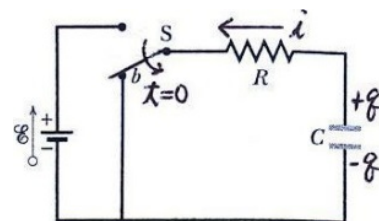
$$i = -dq/dt = [q(0)/RC]e^{-t/RC} = i(0)e^{-t/\tau}.$$



### (b) charging

$$\varepsilon - iR - q/C = 0, \text{ with } q(0) = 0.$$

$$dq/dt = i = (\varepsilon - q/C)/R = -(q - C\varepsilon)/RC.$$

$$\int_{q(0)=0}^{q(t)} dq'/(q' - C\varepsilon) = -(1/RC) \int_0^t dt' \Rightarrow$$

$$\ln[(q(t) - C\varepsilon)/(0 - C\varepsilon)] = -t/RC \Rightarrow$$

$$q(t) - C\varepsilon = -C\varepsilon e^{-t/RC} \Rightarrow q(t) = C\varepsilon(1 - e^{-t/RC}) = C\varepsilon(1 - e^{-t/\tau}).$$

$$i = dq/dt = C\varepsilon(1/RC)e^{-t/RC} = (\varepsilon/R)e^{-t/\tau} = i(0)e^{-t/\tau}.$$

$\varepsilon$  提供能量  $q(\infty)\varepsilon$ ，但  $C$  只儲存  $QV/2 = q(\infty)\varepsilon/2$ ，故有一半被  $R$  消耗掉。

