

Mid Term II

E927500

Circuit Analysis

May 18, 2016

A. (5×8=40 points) Answer each of the following statements.

1. To explain "The total instantaneous power in a balanced three-phase system is constant."
2. To explain "If same power loss is tolerated in both system, three-phase system use only 75% of materials of a single-phase system."
3. To use the red, black, and white wires for "120-V connection" and "240-V connection" in household system.
4. Comparison between "self-inductance" and "mutual-inductance".
5. To derive $M = k\sqrt{L_1 L_2}$, where coupling coefficient $k = c_M / \sqrt{c_1 c_2}$.
6. Comparison between "linear transform" and "ideal transformer".
7. Describe the function of the isolation transformer in Fig. 1. Why?
8. Describe the function of the isolation transformer & the rectifier in Fig. 2.

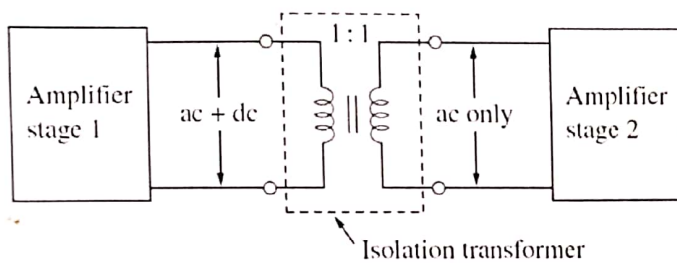


Fig. 1

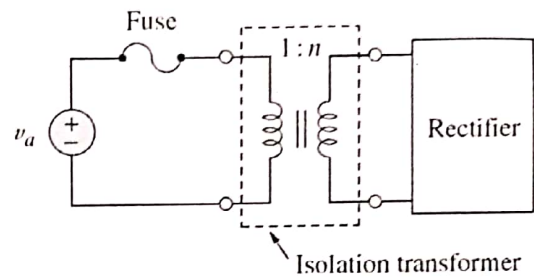


Fig. 2

B. (8+6=14 points) Balanced Wye-Delta Connection + Power in a Balanced System: In Fig. 3, one line voltage of a balanced Y-connected source is $V_{AB} = 120\angle -20^\circ$ V. Assume the *abc* sequence. If the source is connected to a Δ -connected load of $20\angle 40^\circ \Omega$,

1. Find the phase and line currents.
2. Find the average power delivered to the load.

C. (15 points) Mutual Inductance: Find current I_o in Fig. 4.

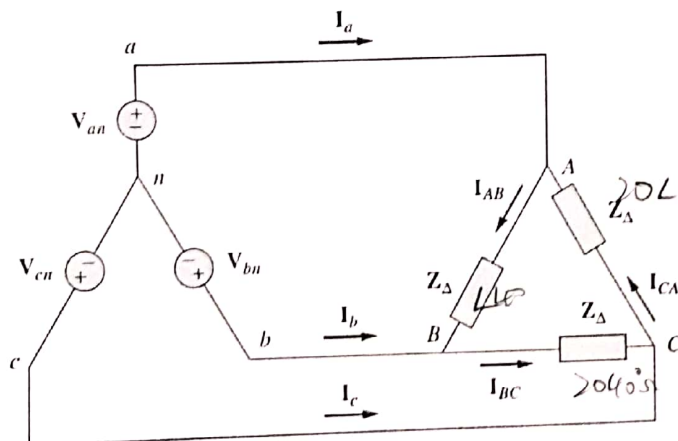


Fig. 3

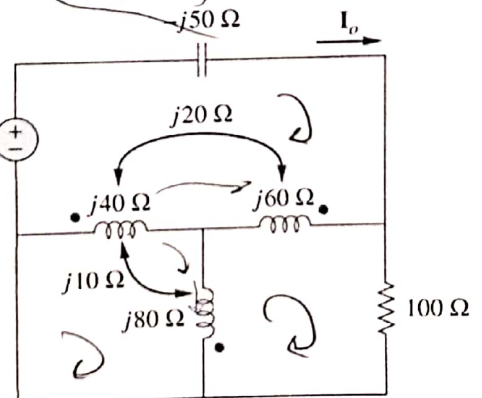


Fig. 4