

國立成功大學 工程科學系 試題

電子電路 (總分 100 分)

學號_____姓名_____

2017/12/11

計算題 4 題(100 分, 共 3 頁)。推導過程須要詳細寫出來, 若觀念正確, 才能斟酌給分。

1. The differential amplifier circuit shown in Fig.1 has $|V_{BE}| = 0.7V$, $\beta \gg 1$, and r_o is neglected.

(a) For $v_1 = \frac{v_{id}}{2}$ and $v_2 = \frac{-v_{id}}{2}$, find the differential gain $\left| \frac{v_o}{v_{id}} \right|$. (7%)

(b) For $v_1 = v_2 = v_{icm}$, find the common-mode gain $\left| \frac{v_o}{v_{icm}} \right|$ and CMRR. (13%)

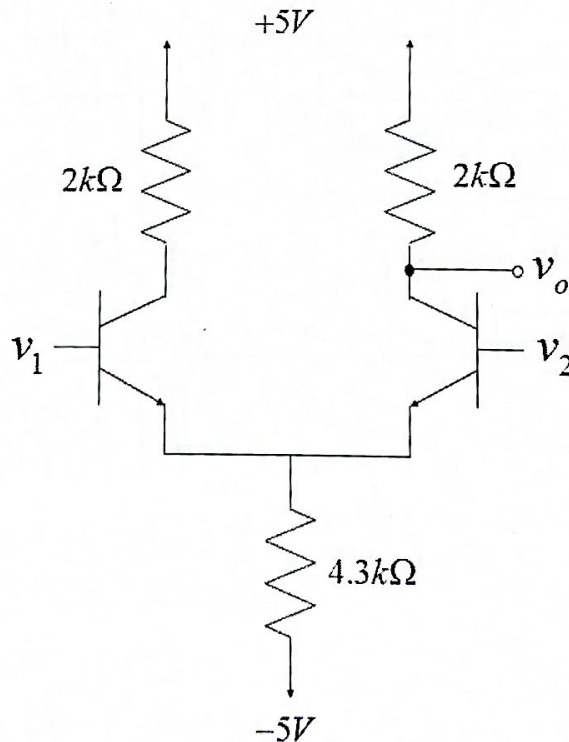


Fig.1

下頁還有題目

2. In the four-stage OP amplifier as shown in Fig.2, all transistors have $\beta = 99$, $|V_{BE}| = 0.7\text{V}$, and r_o is neglected. Note that Q_6 has two times the EBJ area of those of Q_3 and Q_9 .

(a) Find the value of DC current $I_1 \sim I_4$. (you can assume $\beta = \infty$). (8%)

(b) Find the gain of stage1 $A_1 \equiv \frac{v_{o1}}{v_{id}}$. (10%)

(c) Find the gain of stage2 $A_2 \equiv \frac{v_{o2}}{v_{o1}}$. (10%)

(d) Find the overall gain $A_d \equiv \frac{v_o}{v_{id}}$. (12%)

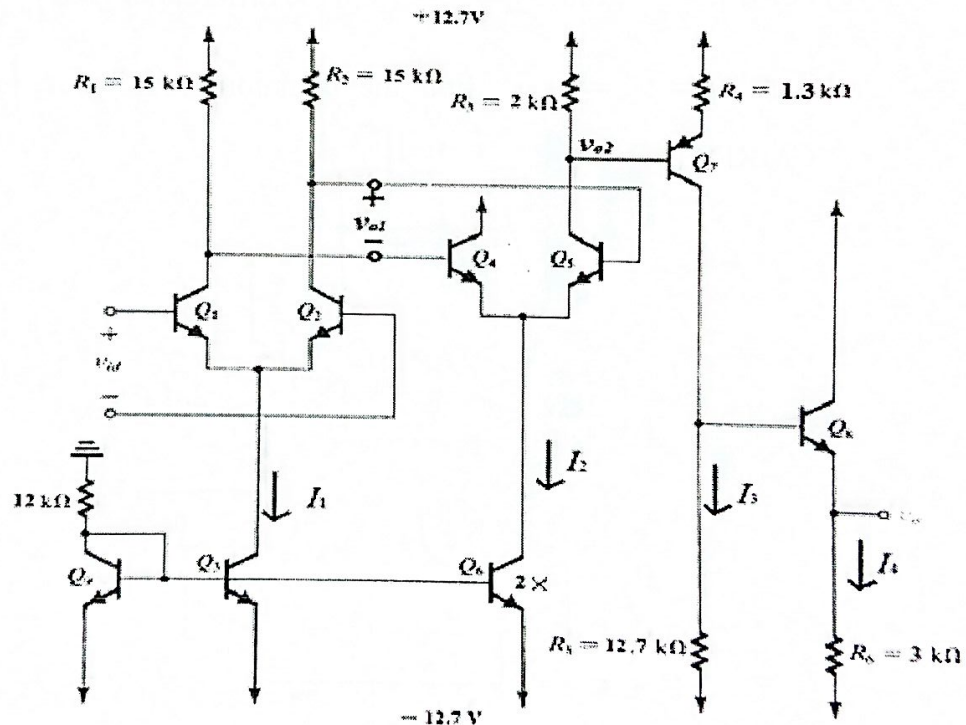


Fig.2

3. For the BJT differential amplifier shown in Fig.3,
 $\beta_1 = \beta_2 = 100$, the current source has an output resistance of
 $200\text{k}\Omega$. (r_o is neglected)

(a) Find $R_{id} \equiv \frac{v_{id}}{i_{id}}$, $|A_d| \equiv \left| \frac{v_o}{v_{id}} \right|$. (10%)

(b) Find $R_{icm} \equiv \frac{v_{icm}}{i_{icm}}$, $|A_{cm}| \equiv \left| \frac{v_o}{v_{icm}} \right|$, and CMRR. (15%)

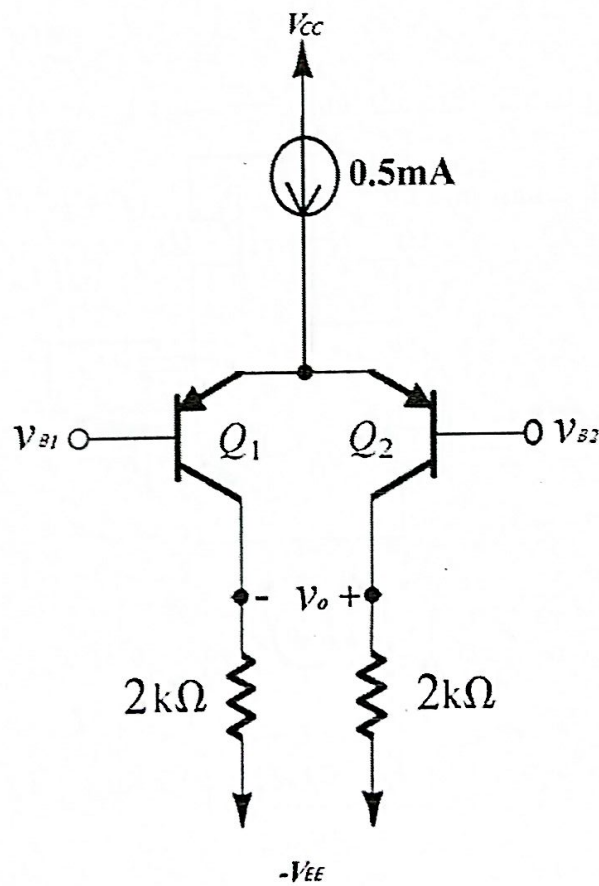


Fig.3

4. A current-mirror-loaded MOS differential amplifier shown in

Fig.4 is specified as follows: $(W/L)_n = 200$, $(W/L)_p = 200$,

$\mu_n C_{ox} = 2\mu_p C_{ox} = 0.2\text{mA/V}^2$, $V_{An} = |V_{Ap}| = 40\text{V}$, and $I =$

1.6mA . Calculate $G_m \equiv \frac{i_o}{v_{id}}$ (neglect r_o), R_o , and $A_d \equiv$

$|\frac{v_o}{v_{id}}|$. (15%)

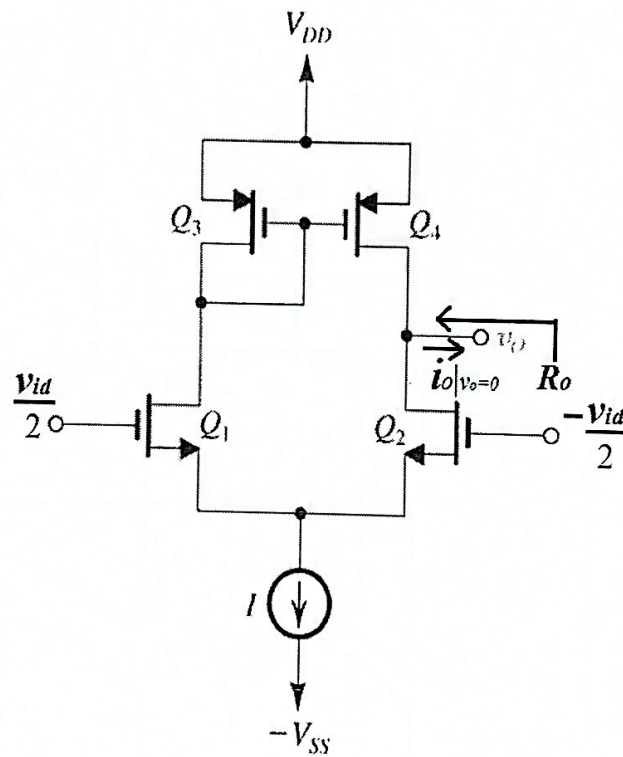


Fig.4