


Midterm Exam I

October 21, 2019


Rules and Regulations: It is permitted to bring one paper of A4 size with handwritten formulas. There is a time limit of one hour and fifty minutes.

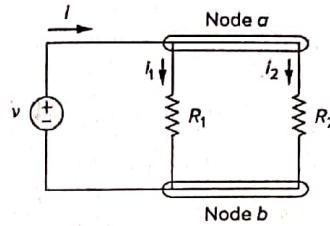Problems for Solution:


- Please determine whether each of the following statements is *True* or *False*.
 - (4%) The system $y = 2x + 1$ is linear where x is the input and y is the output.
 - (4%) If $R_1 \gg R_2$ in the following circuit, then $i_2 \approx 0$.



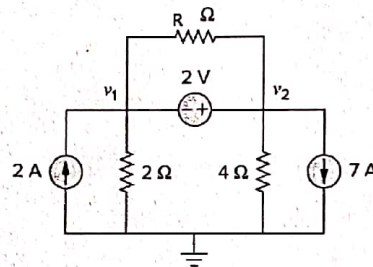
- (4%) In the following circuit, the node voltage v_1 will not change if the R - Ω resistor is replaced by a $2R$ - Ω resistor.



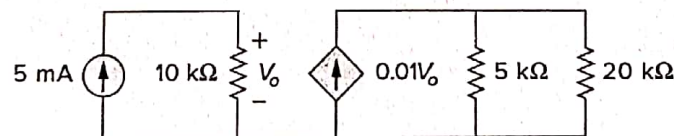
- (4%) The power of any element in a circuit should be positive.
 - (4%) A direct current (DC) can be time varying.
- (10%) For the network as given below, find the power absorbed by the 20 k Ω resistor.



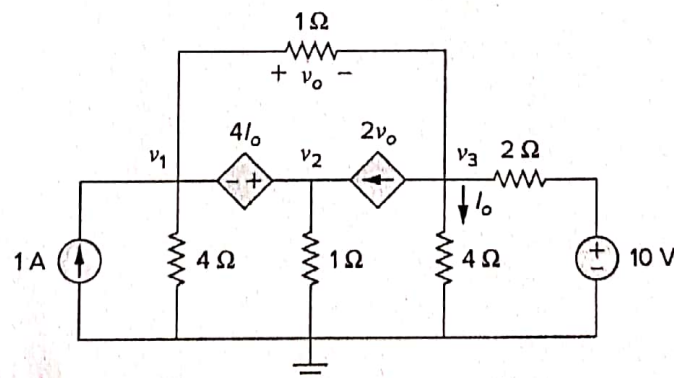
- (20%) Find the node voltages v_1 , v_2 , and v_3 in the following circuit.



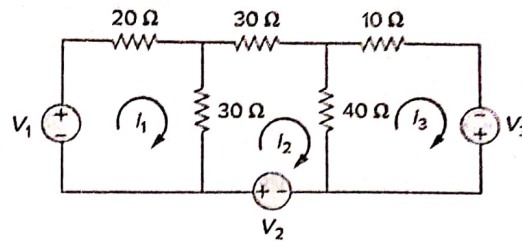
4. (10%) Determine the mesh currents in the following circuit if $V_1 = 6\text{ V}$, $V_2 = 4\text{ V}$, and $V_3 = 3\text{ V}$.



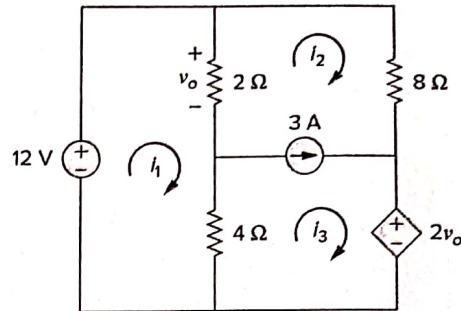5. (20%) Use mesh analysis to find i_1 , i_2 , and i_3 in the following circuit.



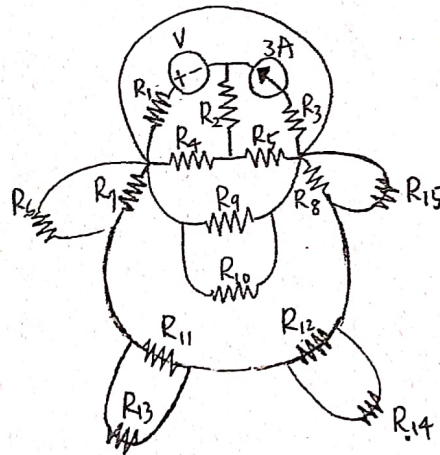6. (10%) 感謝出題王盧子晴、黃淑微同學提供此題目。 If $R_1 = 4\ \Omega$, $R_2 = R_4 = R_5 = 3\ \Omega$, $R_3 = 9\ \Omega$, $R_6 = R_{13} = R_{14} = R_{15} = 17\ \Omega$, $R_7 = R_{11} = R_{12} = R_8 = 19\ \Omega$, $R_9 = 5\ \Omega$, and $R_{10} = 7\ \Omega$, find $V = ?$



7. (10%) 感謝出題王陳立得、林宜伯同學提供此題目。 Find the equivalent resistance R_{eq} if $R_1 = 1\ \Omega$.

