

# 電子電工學

## Lecture 2



# Recap

- Basic quantities

- Charge ✓  $Q$
- Voltage ✓  $V$
- Current ✓  $I$
- Power ✓  $P = VI$


- Electrical components

- Resistor  $R$
- Capacitor  $C$
- Inductor  $L$


- Circuit diagrams

Interconnection of components.

# Recap: Electronics to circuits

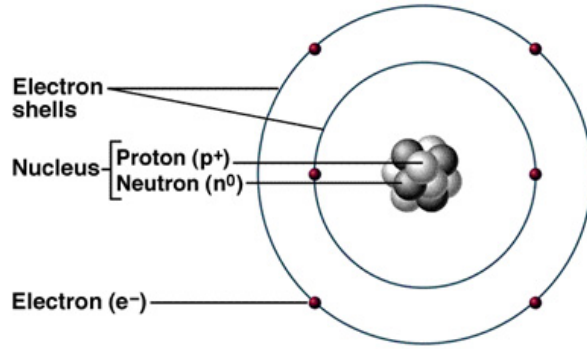

Free e<sup>-</sup> flow  
circuits.

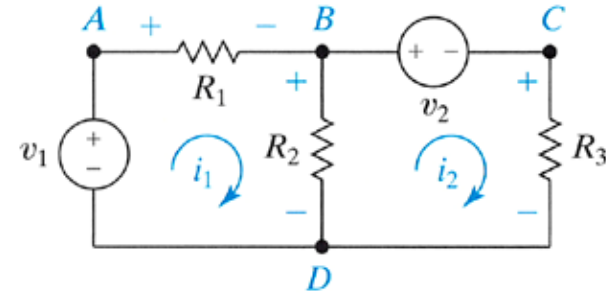

**TABLE 7-2**  
**Maxwell's Equations**

Differential Form	Integral Form	Significance
$\nabla \times \mathbf{E} = -\frac{\partial \mathbf{B}}{\partial t}$	$\oint_C \mathbf{E} \cdot d\boldsymbol{\ell} = -\frac{d\Phi}{dt}$	Faraday's law
$\nabla \times \mathbf{H} = \mathbf{J} + \frac{\partial \mathbf{D}}{\partial t}$	$\oint_C \mathbf{H} \cdot d\boldsymbol{\ell} = I + \int_S \frac{\partial \mathbf{D}}{\partial t} \cdot d\mathbf{s}$	Ampère's circuital law
$\nabla \cdot \mathbf{D} = \rho$	$\oint_S \mathbf{D} \cdot d\mathbf{s} = Q$	Gauss's law
$\nabla \cdot \mathbf{B} = 0$	$\oint_S \mathbf{B} \cdot d\mathbf{s} = 0$	No isolated magnetic charge

# Chapter 3. Circuit Laws and Equivalences

Goal: For each component, find


Voltage  $V$

Current  $I$



Power  $P$

Essential laws:

1. Ohm's law
2. Kirchhoff's laws

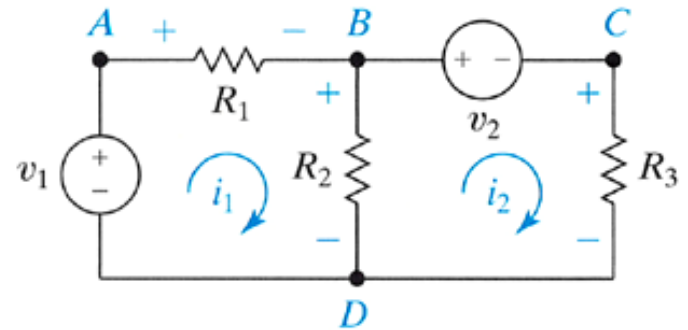

# Electrical component

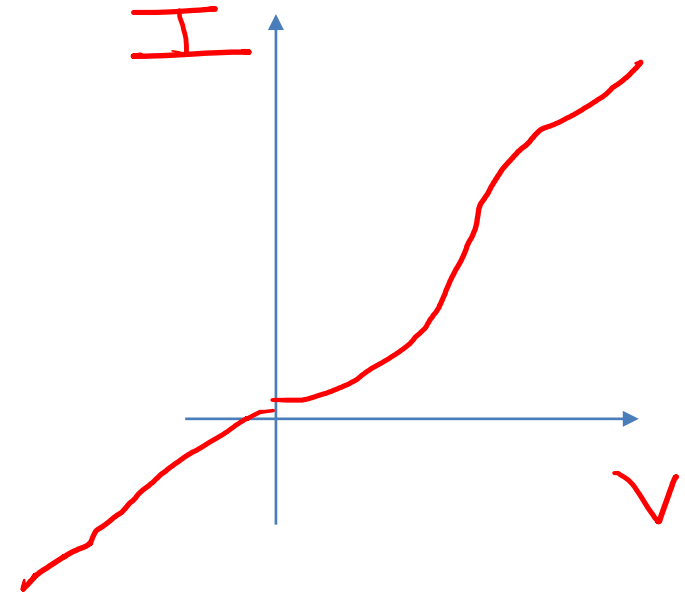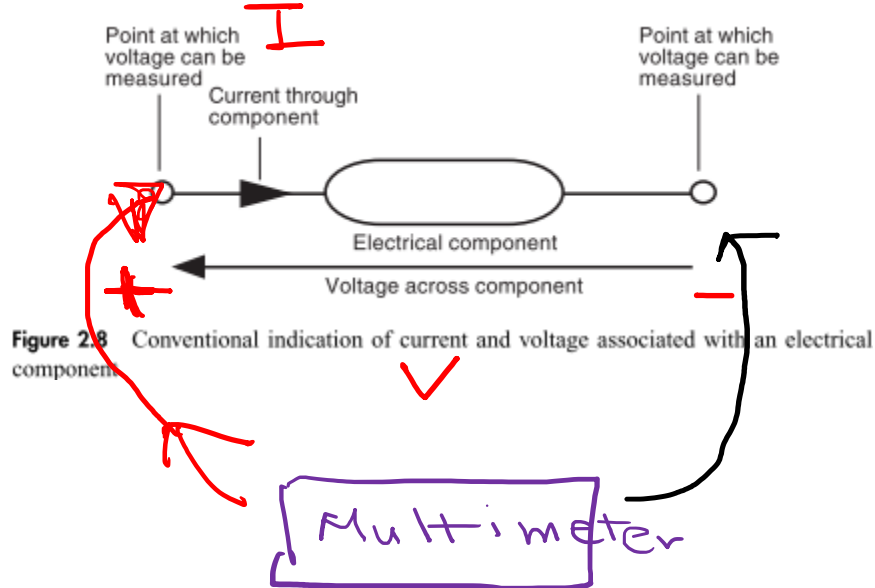

I-V Characteristic

# Electrical component

$R$  : Resistor  $\Omega$  (ohm)

$L$  : Inductor  $H$  (henry)

$C$  : Capacitor  $F$  (Farad)

Resistor




Symbol:

Inductor



Capacitor

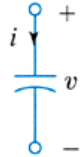

Relationship:  $v = iR$

$$v = L \frac{di}{dt}$$


$$v = \frac{1}{C} \int i dt$$

or

$$i = \frac{1}{R} v$$


$$i = \frac{1}{L} \int v dt$$

$$i = C \frac{dv}{dt}$$

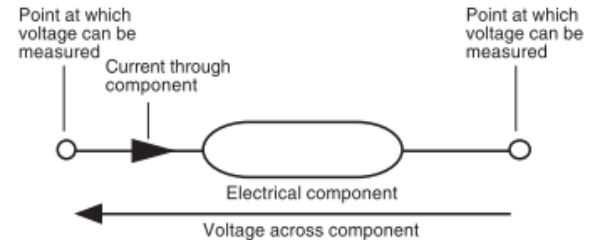

**Figure 2.8** Conventional indication of current and voltage associated with an electrical component

# Resistance

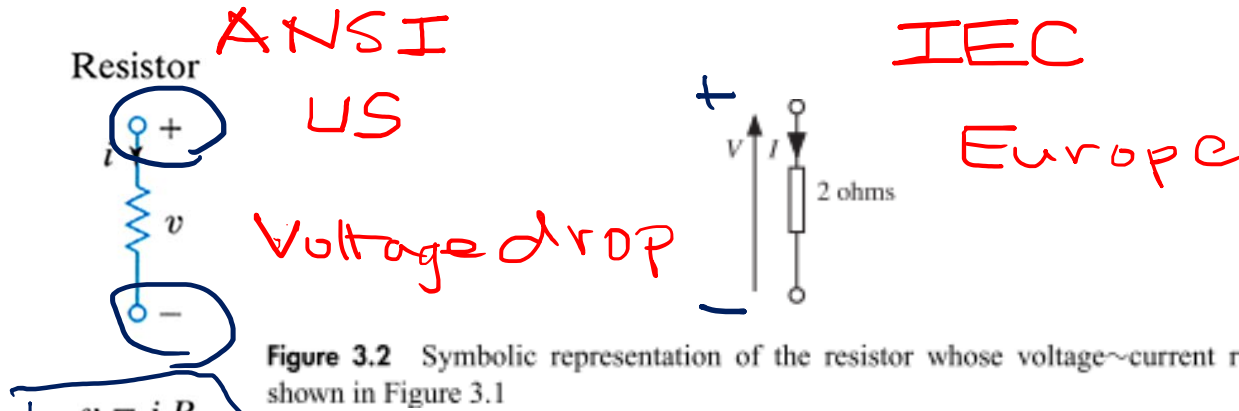

$$R = 2\Omega$$

Ohm's Law

$R$ : resistance ( $\Omega$ )

$$i = \frac{1}{R} v$$

$= G v$

Conductance ( $\text{S}$ )  $\frac{1}{\Omega}$ , mho



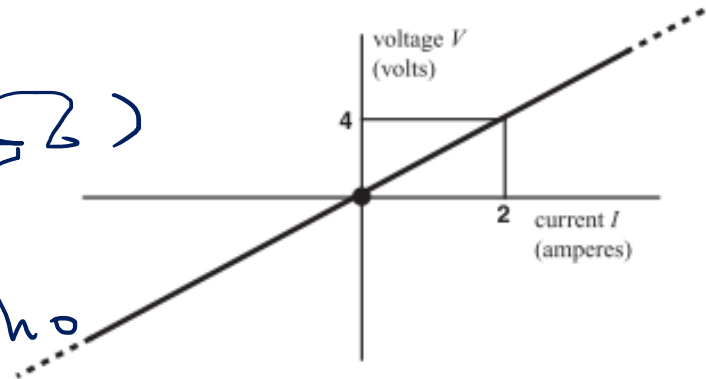


Figure 3.1 The result of measuring the current through, and the voltage across, a resistor

$$v(t) = R i(t)$$

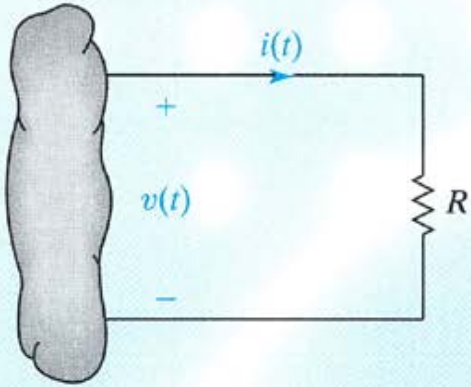

(a)

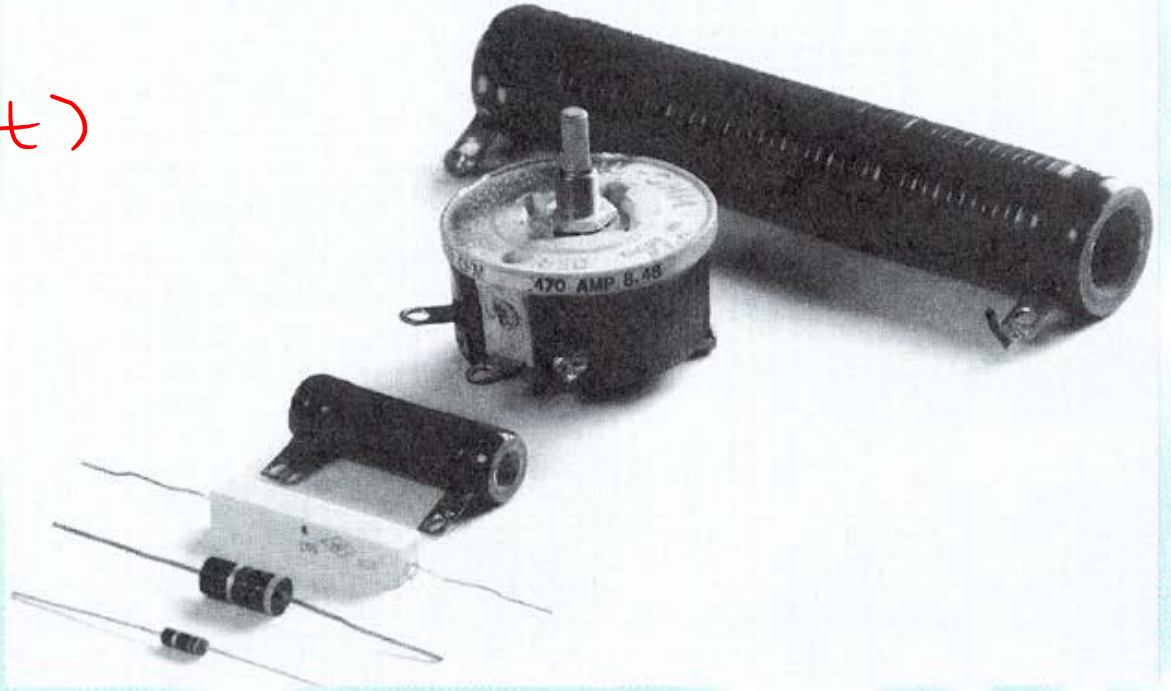

(b)

**FIGURE 2.1** (a) The symbol for a resistor, and (b) some examples of typical carbon or wirewound resistors.



# Resistors



Color  
Code

# Conductance

Resistor



$$v = iR$$

$$i = \frac{1}{R}v$$

$$i = Gv$$

Conductance

( $\Omega^{-1}$ , mho)  
(S, siemens)

$$R = 2\ \Omega \leftrightarrow G = 0.5\ S$$



**Figure 3.3** Alternative symbolic representation of the resistor whose voltage~current relation is shown in Figure 3.1


# Current directions

[ Reference  
Direction ]




**Figure 3.4** The reference direction for current can be arbitrary, and does not necessarily indicate the actual direction of flow

Actual Direction  
(Sign)

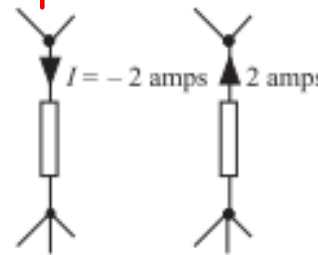

**Figure 3.5** If the value of  $I$  in Figure 3.4 is negative, that can be represented in either of the two ways shown here

# Current directions

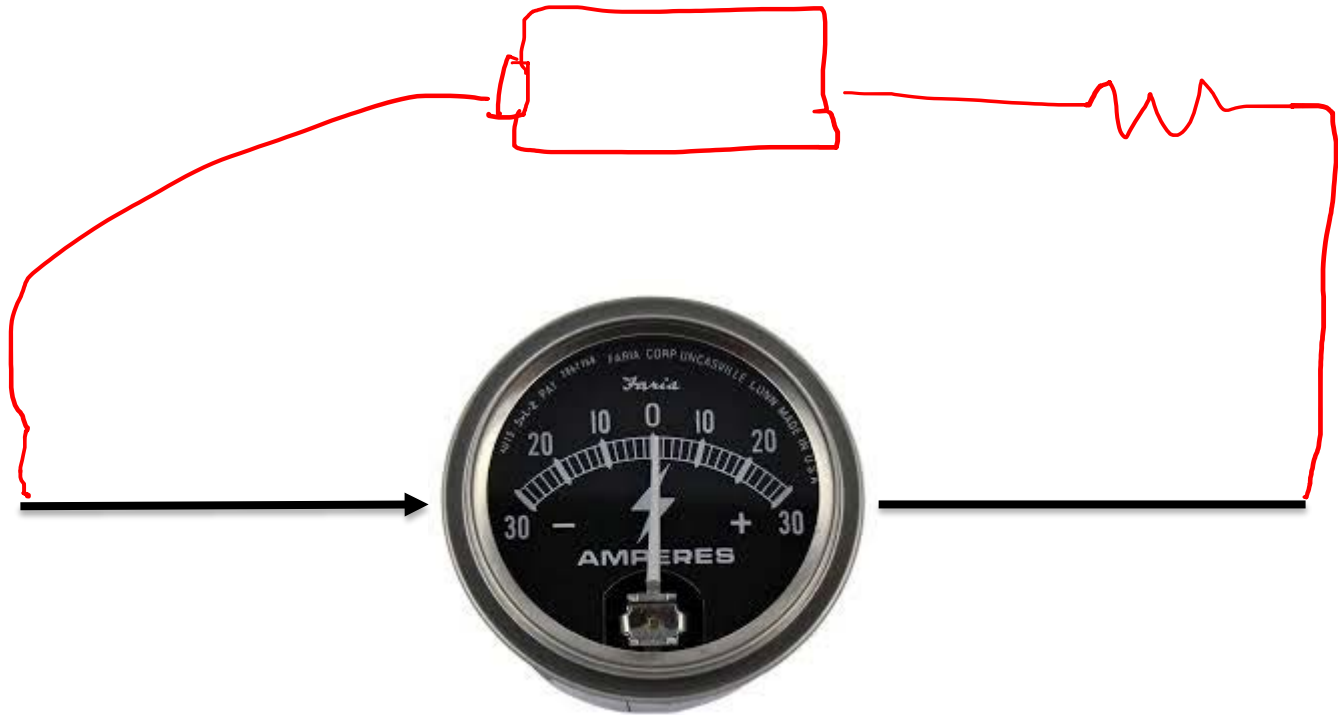

Voltage source

直流

Direct Current (DC)

Ideal

⇒ Enforce constant voltage.

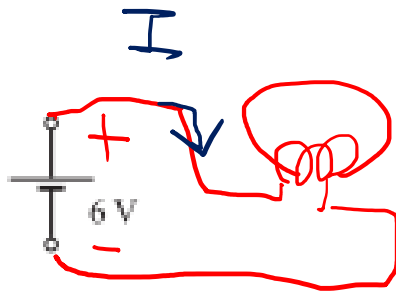
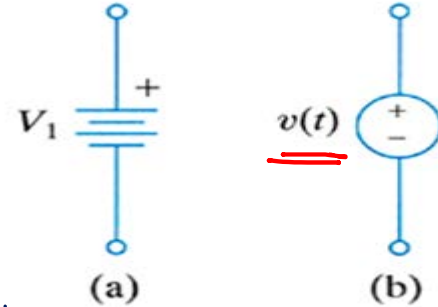


Figure 3.7 Representation of an ideal voltage source of 6 V


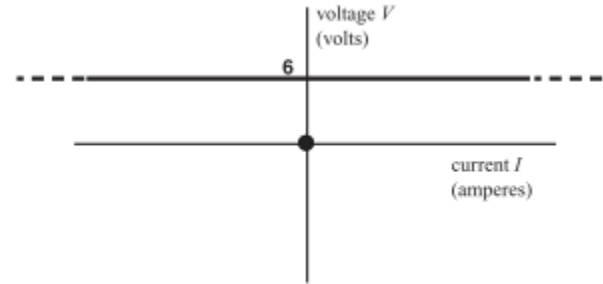


Figure 3.6 The result of measuring the current through, and the voltage across, an ideal voltage source

# Short circuit

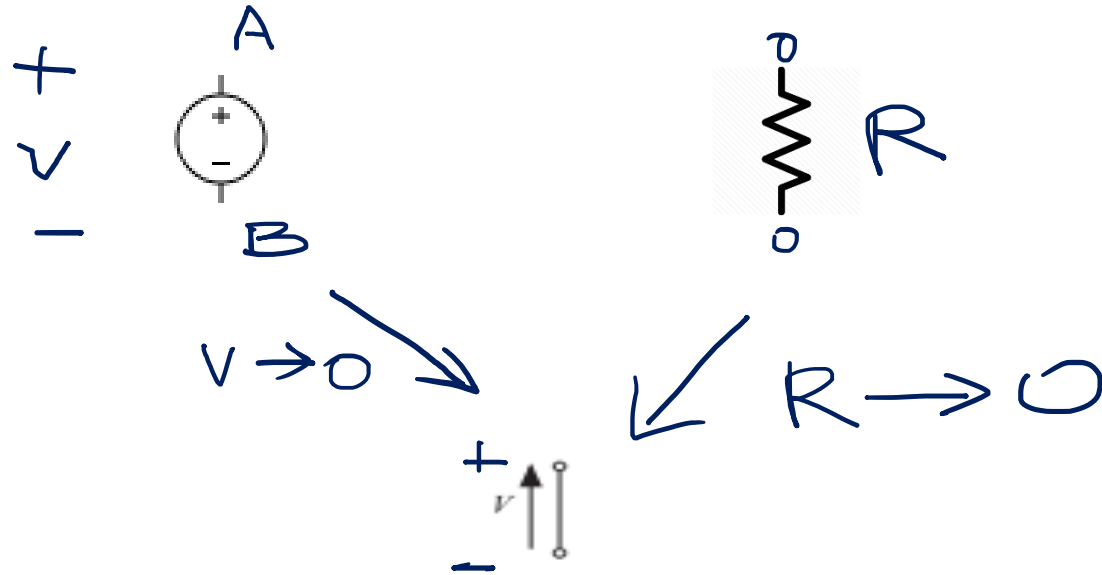

**Figure 3.8** A short-circuit. The voltage  $V$  between the terminals is zero whatever the value of the current through it

# Current source

Ideal

Enforce a constant current,  
irrespective of the voltage  
across it.

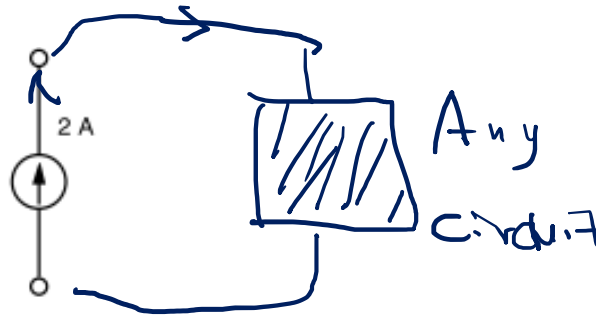


Figure 3.10 Representation of an ideal current source of 2 A

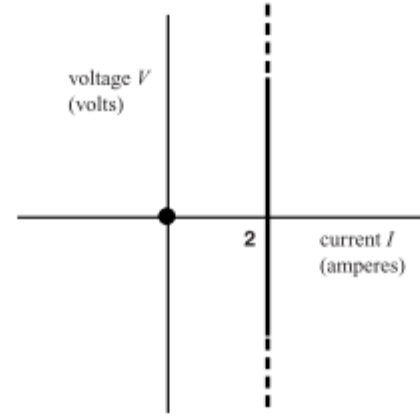
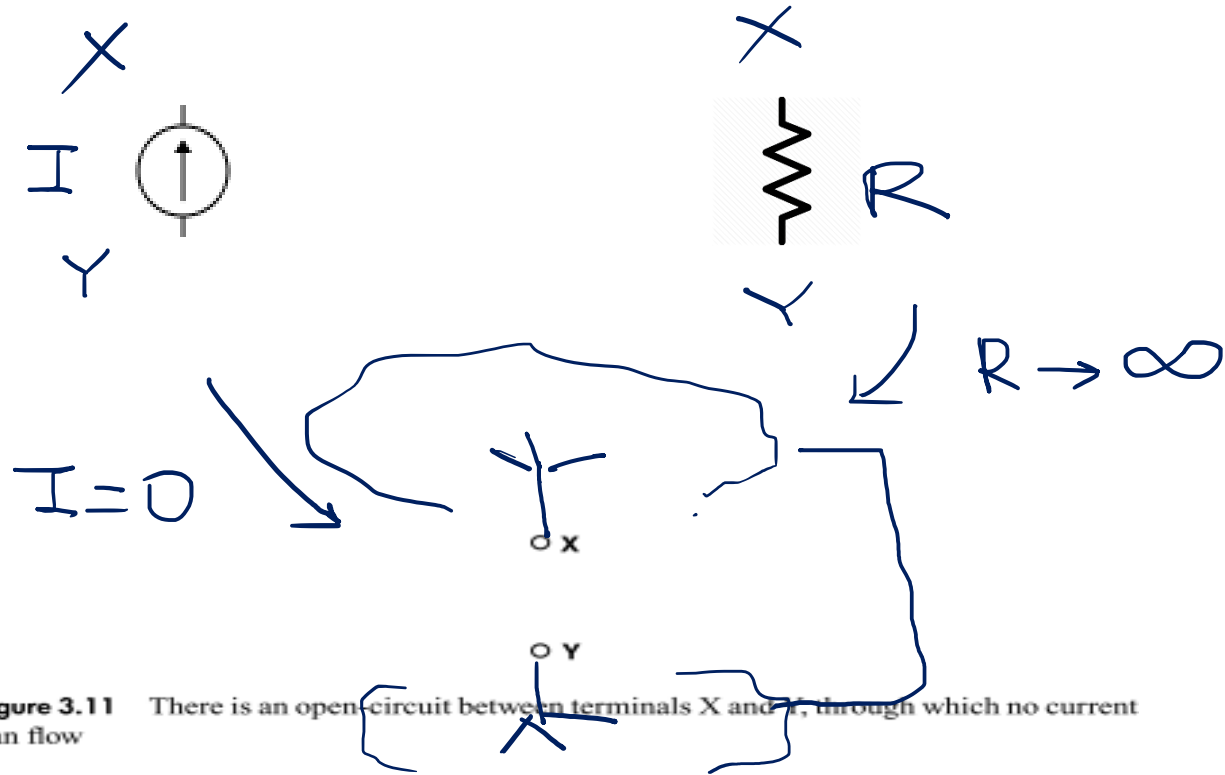


Figure 3.9 The result of measuring the current through, and the voltage across, an ideal current source

# Open circuit

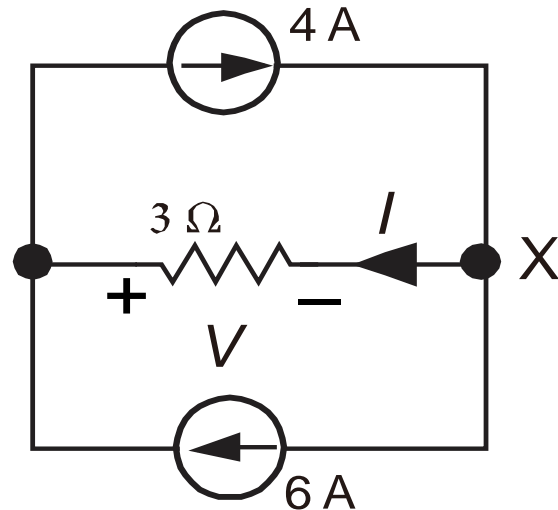


**Figure 3.11** There is an open circuit between terminals  $X$  and  $Y$ , through which no current can flow



## Quiz 1

1. For the circuit shown in Fig. 1, find the current  $I$  and  $V$  across the resistor.
2. Let  $i(t) = A \cos(\pi t + \theta)$ , what is  $\frac{di}{dt}$  ?
3. Evaluate  $\int_0^4 e^{-t/2} dt$  .
4. Let  $i = \sqrt{-1}$  , simplify  $\frac{1+2i}{3+4i}$  to the form of  $a+bi$ .
5. Evaluate the absolute value  $\left| \frac{1+2i}{3+4i} \right|$ .




## Quiz 1 Review

1. For the circuit shown in Fig. 1, find the current  $I$  and  $V$  across the resistor.

$$I = -2 \text{ A}$$

$$V = 6 \text{ V}$$

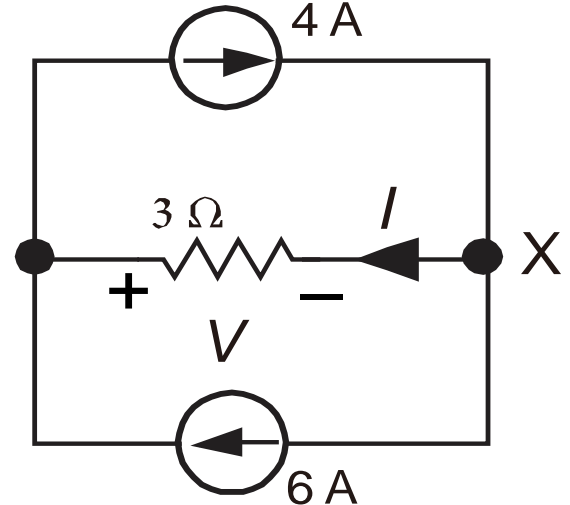

## Quiz 1 Review

2. Let  $i(t) = \underline{A} \cos(\underline{\pi}t + \underline{\theta})$ , what is  $\frac{di}{dt}$ ?

3. Evaluate  $\int_0^4 e^{-t/2} dt$ .

$$2. \frac{di(t)}{dt} = -\pi A \sin(\pi t + \theta)$$

$$\begin{aligned} 3. \int_0^4 e^{-t/2} dt &= -2 e^{-t/2} \Big|_0^4 \\ &= -2 [e^{-2} - 1] \\ &= 2(1 - e^{-2}) \end{aligned}$$

## Quiz 1 Review

4. Let  $i = \sqrt{-1}$ , simplify  $\frac{1+2i}{3+4i}$  to the form of  $a+bi$ .

5. Evaluate the absolute value  $\left| \frac{1+2i}{3+4i} \right|$ .


$$4. \quad \frac{1+2i}{3+4i} = \frac{(1+2i)(3-4i)}{(3+4i)(3-4i)} = \frac{11+2i}{25}$$

$$a = \frac{11}{25}$$

$$b = \frac{2}{25}$$

$$5. \quad \left| \frac{1+2i}{3+4i} \right| = \frac{\sqrt{5}}{5} = \frac{1}{\sqrt{5}}$$

# Switch

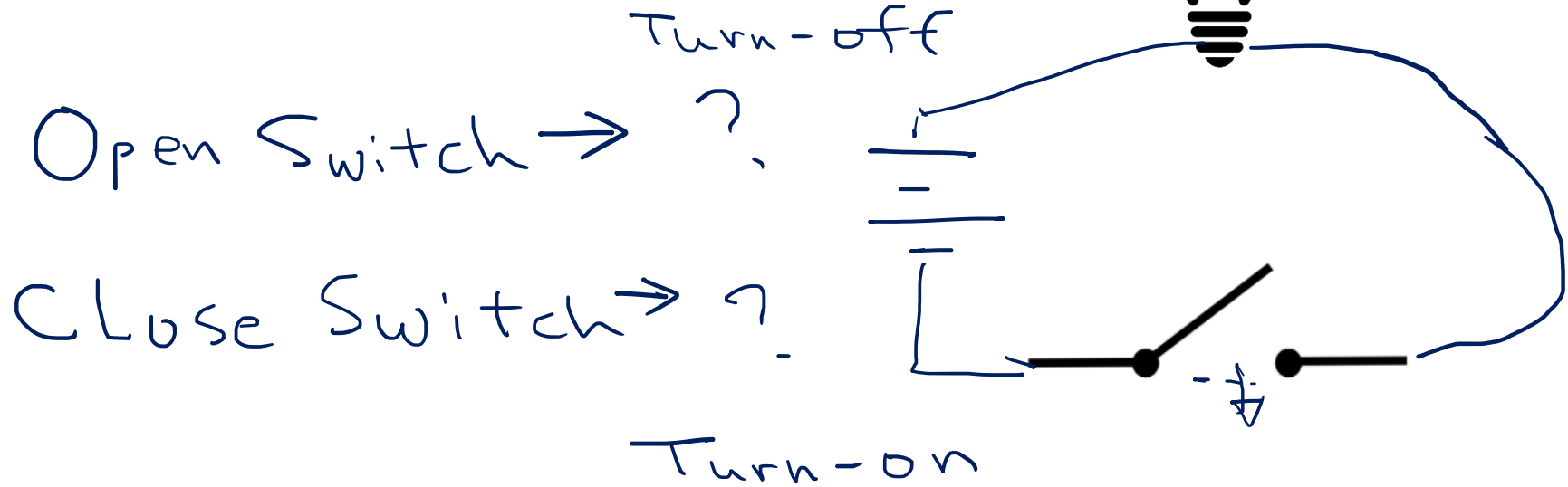


# Power

$$P = VI$$


$VI > 0$  Absorb power

(Passive component)

$VI < 0$  Supply power  
(Active component)

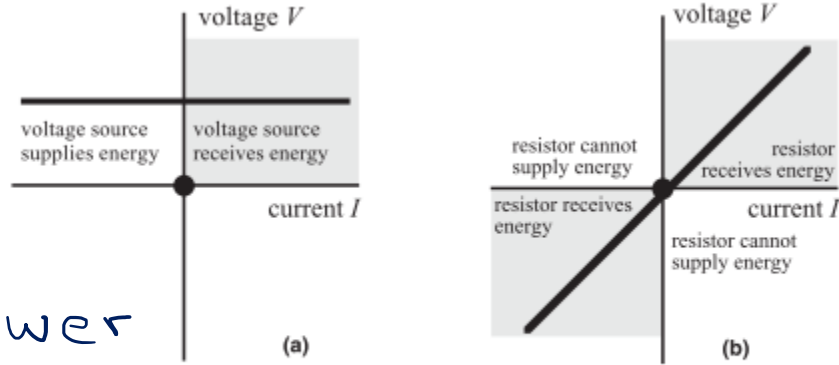

**Figure 3.13** A voltage source can supply energy because the product of  $V$  and  $I$  can be negative. With a resistor the product of  $V$  and  $I$  is always positive, so it can only receive energy

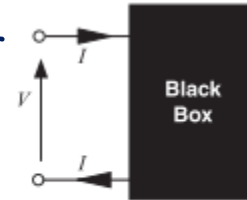

**Figure 3.12** The power supplied to a black box is the product of  $V$  and  $I$  provided the current  $I$  enters at the terminal with the highest voltage (i.e., the positive reference for  $V$ )

# Kirchhoff's Current Law (KCL) Interconnection

For any node (junction)


$$\sum_{n \in \text{Branch}(n)} I_n = 0$$

Inward as positive.

$$I_1 + I_2 + I_3 = 0$$



Conservative  
of  
charge  
(Mass)

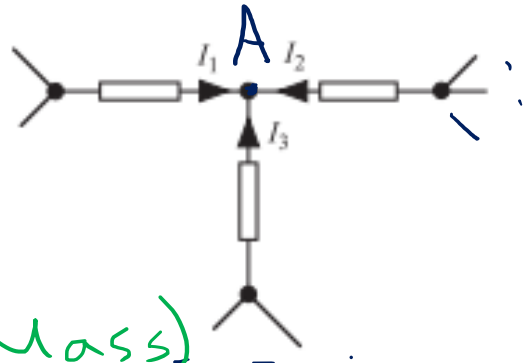


Simplify  $\nabla \times H = J + \frac{\partial D}{\partial t}$   
 $\mu$  const. (Ampere's Law)

Figure 3.14 Three resistors are connected to the same terminal

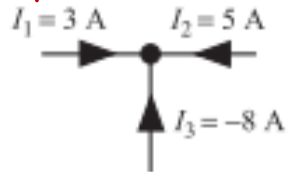
# Kirchhoff's Current Law (KCL)

$$\begin{aligned} I_1 + I_2 + I_3 &= 3 + 5 + (-8) \\ &= 0 \text{ A} \end{aligned}$$
$$\left. \begin{aligned} \sum \text{Outward } I &= \sum \text{Inward } I \\ I_3 &= I_1 + I_2 \end{aligned} \right\}$$



"Total current into a node is zero"

(a)

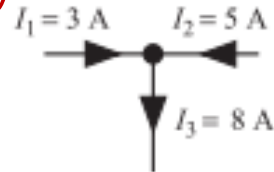

"Total current in equals total current out"

(b)

Figure 3.15 Alternative expressions of Kirchhoff's current law



# Kirchhoff's Voltage Law (KVL)

Loop

$a \rightarrow b \rightarrow c \rightarrow d \rightarrow a$

$$V_{ba} + V_{cb} + V_{dc} + V_{ad} = 0$$

$$V_A + V_B + V_X + V_Y = 0$$

$$\sum_{i \in \text{Loop}} V_i = 0$$

Voltage drop

Conservative  
or  
Energy

Maxwell's  
 $\nabla \times E = -\frac{\partial B}{\partial t}$   
Faraday's Law

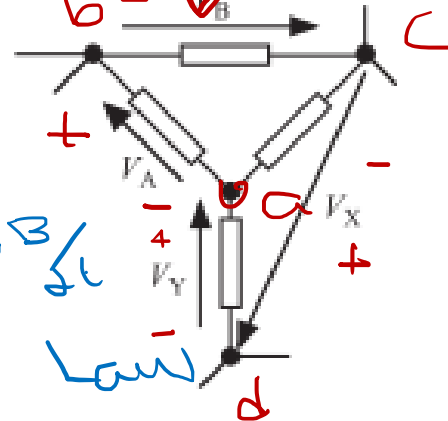


Figure 3.16 A closed loop is formed by the voltages  $V_A$ ,  $V_B$ ,  $V_X$  and  $V_Y$

# Kirchhoff's Voltage Law (KVL)

Loop  $a-b-c-d-a$

$$\text{KVL: } V_{ba} + V_{cb} + V_{dc} + V_{ad} = 0$$

$$\Rightarrow V_C + (-V_D) + V_R + (-V_S) = 0$$

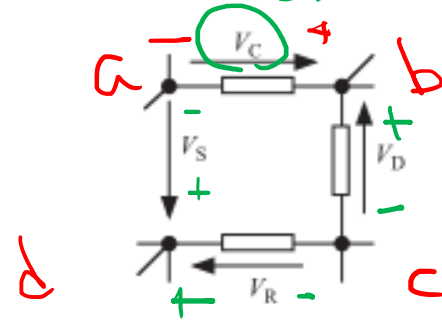







Figure 3.17 Four voltages forming a closed loop within a circuit

# DC circuits

**Table 3.1** Summary of the relations describing DC circuits



FEATURES OF A CIRCUIT	SYMBOLIC REPRESENTATION	RELATION
<u>Components</u>	  	<u>Ohm's Law</u> constant V constant I
<u>Connection at a node</u>		$\sum I_n = 0$ <u>Kirchhoff's Current Law (KCL)</u>
<u>Connection to form a loop</u>		$\sum V_n = 0$ <u>Kirchhoff's Voltage Law (KVL)</u>

$I-V$  curve

## Equivalent circuits


2 resistors  $\rightarrow$  1 resistor

Same  
I-V characteristic

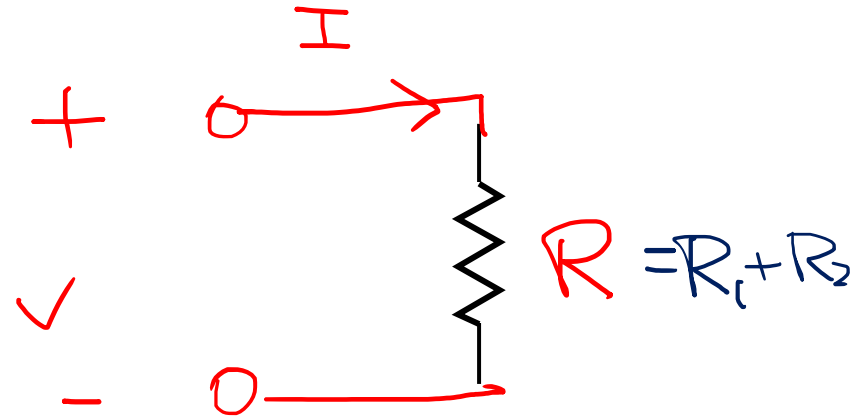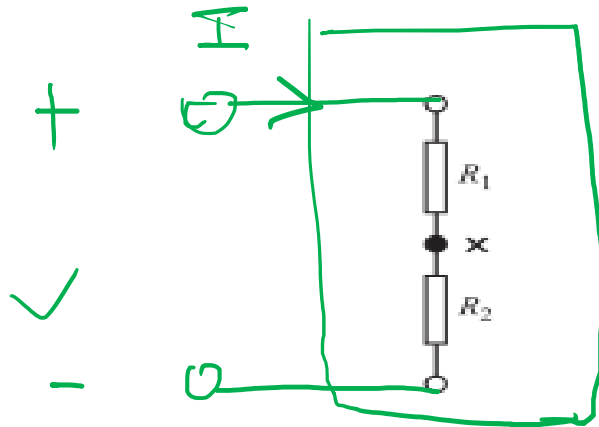

**Figure 3.18** The series connection of two resistors. Note that there is nothing else connected to point  $X$

# Equivalent circuits

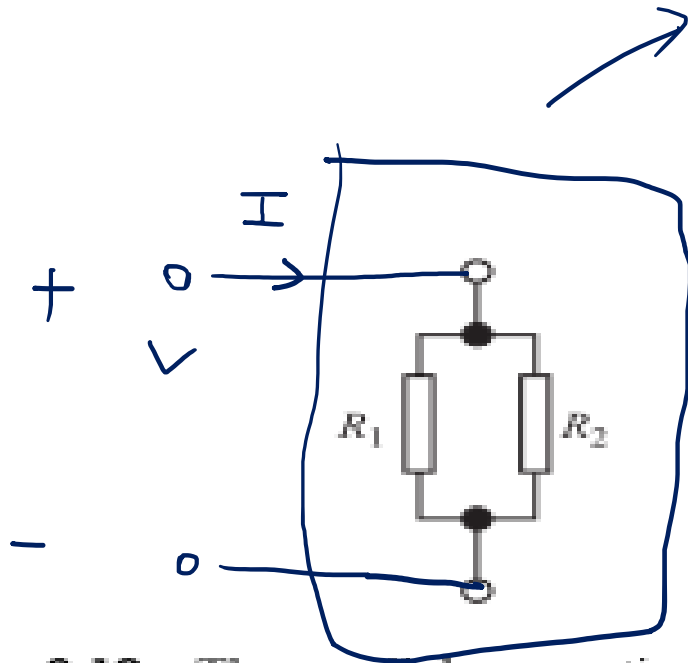

Same  
I-V  
Characteristic

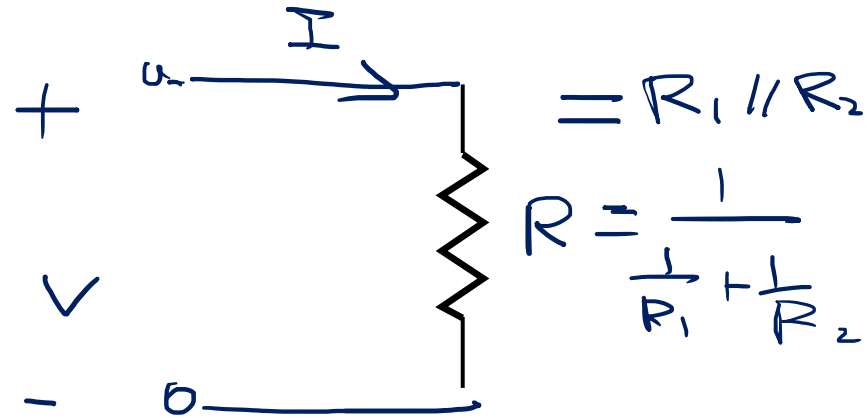


Figure 3.19 The parallel connection of two resistors

Equivalent circuits

Apply source  $V$

KCL

$$\left. \begin{array}{l} \text{node Y: } I = I_1 \\ \text{node X: } I_1 = I_2 \\ \text{node Z: } I = I_3 \end{array} \right\} I = I_1 = I_2 = I_3$$

Ohm's Law  $I, I_1, I_2, I_3$

$$\left. \begin{array}{l} R_1: V_{R_1} = R_1 I_1 \\ R_2: V_{R_2} = R_2 I_2 \end{array} \right\} V_{R_1}, V_{R_2}$$

KVL: Loop Z-A-B-Y-X-Z

$$\Rightarrow V - V_{R_1} - V_{R_2} = 0$$

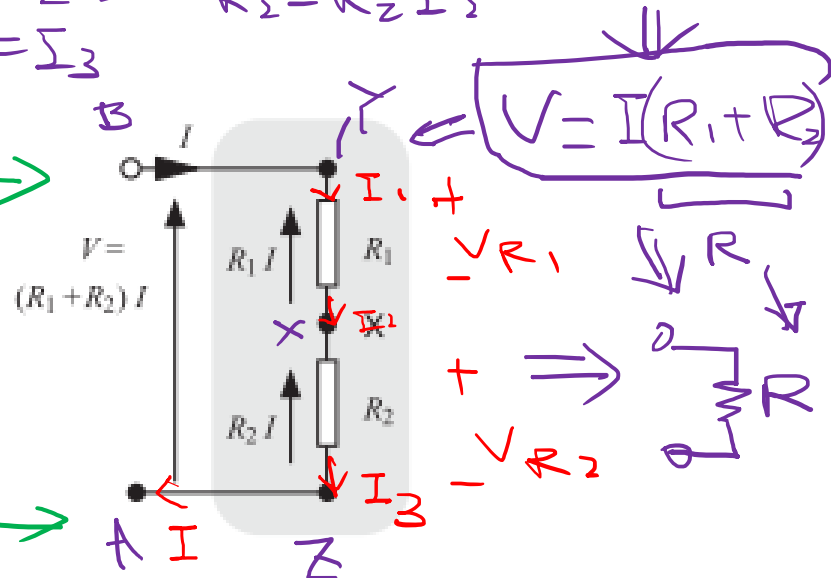


Figure 3.20 Derivation of the equivalent resistance of two resistors connected in series

# Equivalent circuits

[Apply current  $s_{rc}$ ]

KCL@A

$$I = I_1 + I_2$$

$$= G_1 V + G_2 V$$

$$I = (G_1 + G_2) V$$

$$I = G V$$

Ohm's Law

$$\begin{cases} I_1 = G_1 V \\ I_2 = G_2 V \end{cases}$$

$$G = 1/R$$

$$R = R_1 \parallel R_2$$

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$G = G_1 + G_2$$

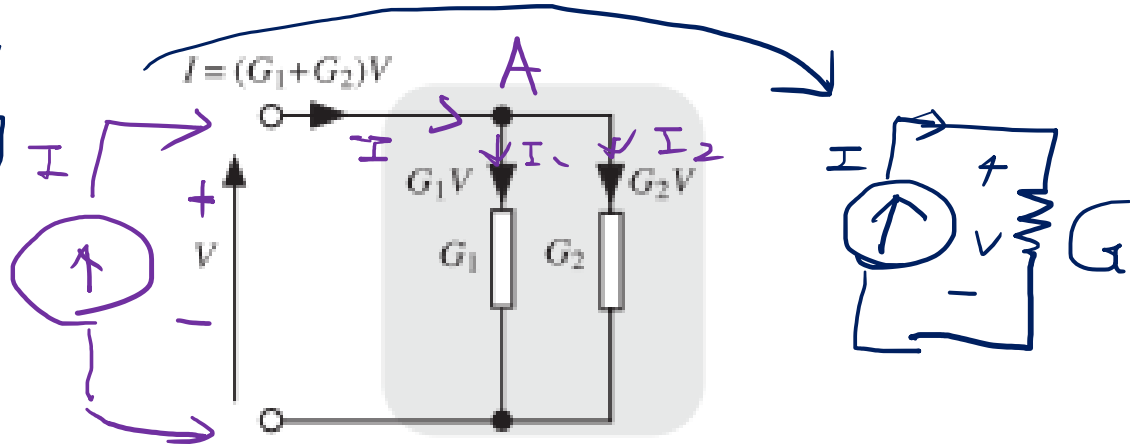


Figure 3.21 Derivation of the equivalent conductance of two resistors connected in parallel