

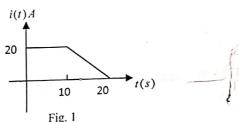
- 1. (10%) Please give the answer for the following statements. State your reasoning.
 - (1) A network with a branches, and b independent loops, and c nodes will satisfy the fundamental theorem of network topology: a = b + c 1. (true or false)
 - (2) For a graph, what is a tree? A tree is also a loop. (true or false)
 - (3) A mesh is a dependent loop. Also, the mesh current is equal to the branch current. (true or false)
 - (4) Kirchhoff's current law can state that the algebraic sum of currents entering a closed boundary is zero. (true or false)
 - (5) Nodal analysis applies KCL to find unknown currents in a given circuit, while mesh analysis applies KVL to find unknown voltages. (true or false)
- (15%) (a) (5%) The current that enters an element is shown in Fig. 1. Find the charge q(18).



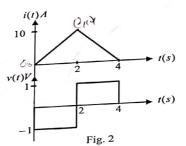- (b) (10%) Fig. 2 shows the current through and the voltage across an element
 - (i) Sketch the power in the element for $t \ge 0$.
 - (ii) Find the energy absorbed by the element at t=1 and t=3.




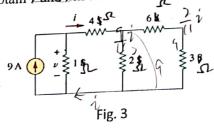3. (10%) Obtain v and i in the circuit in Fig. 3.


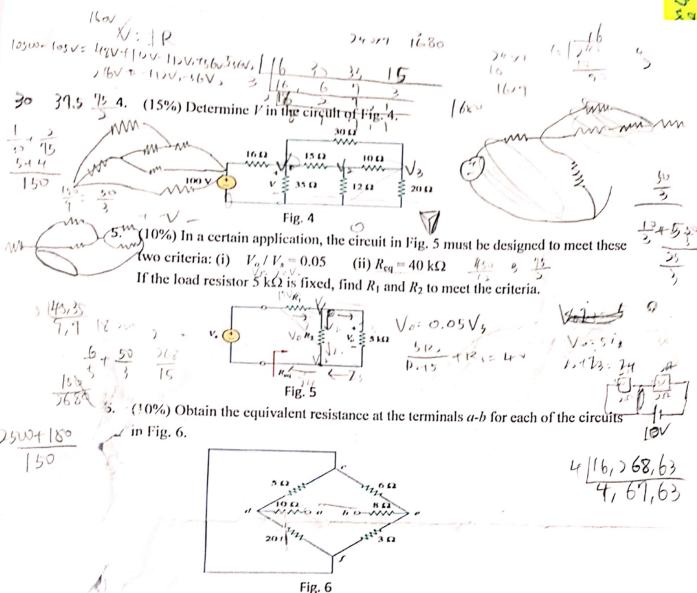
$$\frac{(1+\frac{1}{4}-\frac{9+3}{8}-\frac{1}{18})}{(8+\frac{1}{18}-\frac{1}{18})} = \frac{(1+\frac{1}{8}-\frac{1}{18})}{(1+\frac{1}{8}-\frac{1}{18}-\frac{1}{18})}$$
Go to next page =>





7. (15%) For the circuit in Fig. 7, find currents i_1 and i_2 using the mesh analysis.

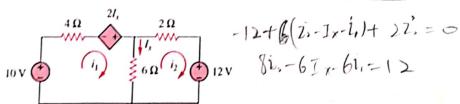


Fig. 7

8. (15%) For the circuit in Fig. 8, find v_1 , v_2 , and v_3 using nodal analysis.

