


考試時間: 100 mins

姓名:

注意: 總分 120 分, 作弊一律以零分計

學號:

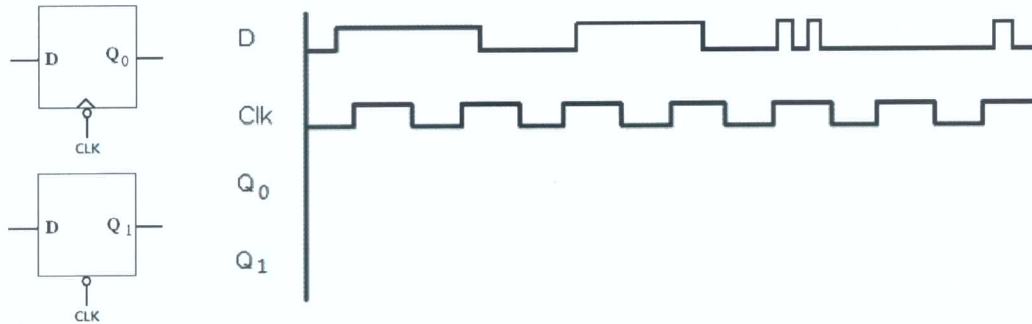一. (10pts) Complete the waveforms of  $Q_0$  and  $Q_1$



二. (10pts) Explain briefly at least four reasons that digital circuits are more advantageous over analog circuits.

三. (30pts) (a) Use Quine-McCluskey method to minimize  $F(A,B,C,D) = \sum m(4,5,6,8,10,13) + d(0,2,7,9,15)$ . (b) Draw the all NAND gates circuit corresponding to the minimized SOP form in (a). (c) if input=0111 to the circuit in (b), what will be the output?

四. (30pts) Design an optimal 3-bit sequence recognizer by use the implication chart method for detecting 010 or 101.

五. (25pts) Design 3-bit counters with cycling sequence of 1, 7, 5, 2 by using JK flip flops. **Note: Use the symbols in order of CBA.**

六. (15pts) (a) What logic function does the circuit perform in Fig.1? Explain by drawing the truth table

(b) Given a Flip-Flop (one bit memory cell, FF) as in Fig.2, it is known that the equivalent circuit of FF is shown in Fig. 3, identify the two NOT gates  $I_1$  and  $I_2$  by using transistors  $M_1, M_2, M_3, M_4$ , that is, in Fig.3 which transistors constitute  $I_1$  and  $I_2$  respectively?

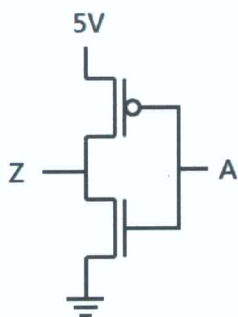


Fig.1

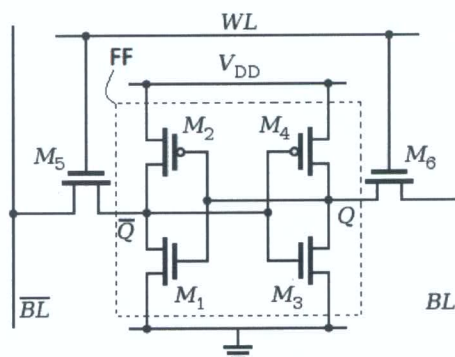


Fig.2


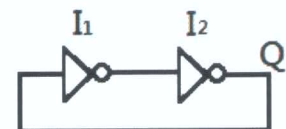


Fig.3

10

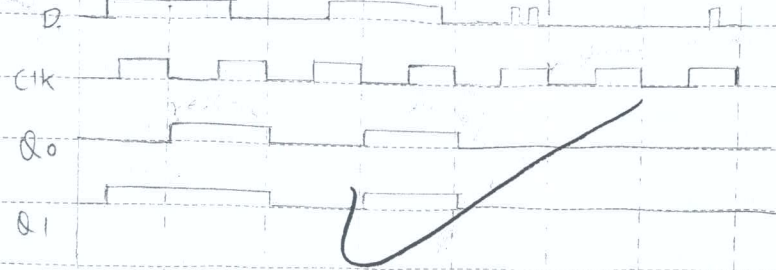

2. 模組化

可用軟體編輯, 自動化

可去除雜訊, 不失真

防竊資訊理論

3.

ABCD F

0000	X
0001	0
0010	X
0011	0
0100	1
0101	1
0110	1
0111	X
1000	1
1001	X
1010	1
1011	0
1100	0
1101	1
1110	0
1111	X



I	II	III
0000 0	00-0 0,2	0--0 0,2,4,6 *
0010 2	0-00 0,4	-0-0 0,2,8,10 *
0100 4	-000 0,8	
1000 8	0-10 2,6	01-- 4,5,6,7 *
0101 5	-010 2,10	
0110 6	01-0 4,5	-1-1 5,7,13,15 *
0111 7	01-0 4,6	
1001 9	100- 8,9 *	
1010 10	10-0 8,10	
0111 7	01-1 5,7	
1101 13	-101 5,13	
1111 15	011- 6,7	
	1-01 9,13 *	
	-111 3,15	
	11-1 13,15	

4 + 6 + 8 + 10 + 13


$\checkmark$  0--0 X  
 $\checkmark$  -0-0 X  
 $\checkmark$  01-- X  
 $\checkmark$  -1-1 X  
 $\checkmark$  01-1 X  
 $\checkmark$  -101 X  
 $\checkmark$  011- X  
 $\checkmark$  1-01 X  
 $\checkmark$  -111 X  
 $\checkmark$  11-1 X

解  $F = B'D' + BD + A'D'$   
 或  $F = B'D' + BD + A'B$

(b) 取第一種解

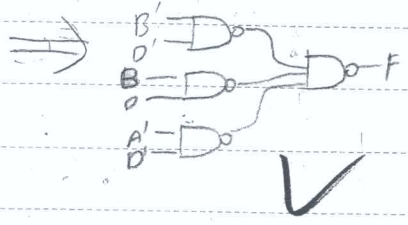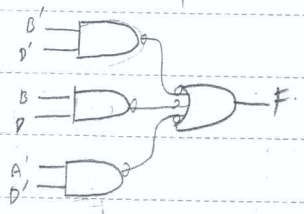


(c)

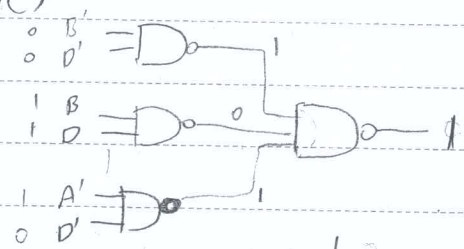

output = 1

✓

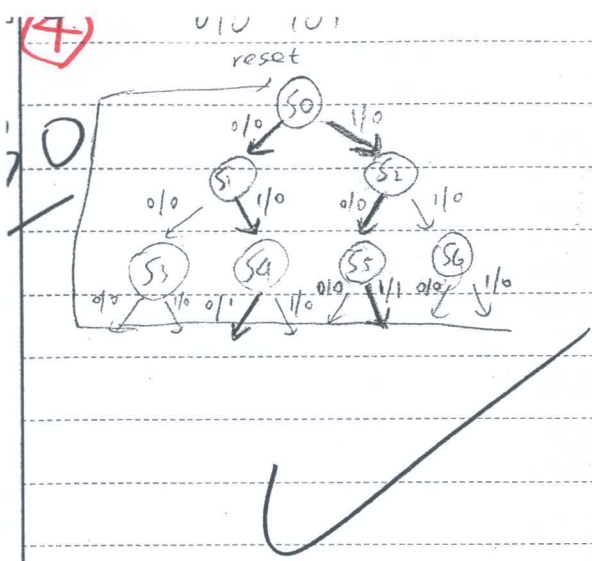

input sequence	present state	next state	output
		$X_0 X_1$	$X_2 X_3$
reset	$S_0$	$S_1 S_2$	0 0
0	$S_1$	$S_3 S_4$	0 0
1	$S_2$	$S_5 S_6$	0 0
00	$S_3$	$S_0 S_0$	0 0
01	$S_4$	$S_0 S_0$	1 0
10	$S_5$	$S_0 S_0$	0 1
11	$S_6$	$S_0 S_0$	0 0

$S_1$	$S_1 = S_3$ $S_2 = S_4$				
$S_2$	$S_1 = S_3$ $S_2 = S_4$	$S_3 = S_5$ $S_4 = S_6$			
$S_3$	$S_1 = S_3$ $S_2 = S_4$	$S_3 = S_5$ $S_4 = S_6$	$S_5 = S_0$ $S_6 = S_0$		
$S_4$	X	X	X	X	
$S_5$	X	X	X	X	X
$S_6$	$S_1 = S_3$ $S_2 = S_4$	$S_3 = S_5$ $S_4 = S_6$	$S_5 = S_0$ $S_6 = S_0$	X	X
	$S_0$	$S_1$	$S_2$	$S_3$	$S_4$

$S_0 = S_0$   
 $S_3 = S_6$


6  
1st

A	Z
0	5
1	0

(b)

$M_1, M_2$  取代  $I_1$   
 $M_3, M_4$  取代  $I_2$

NOT gates

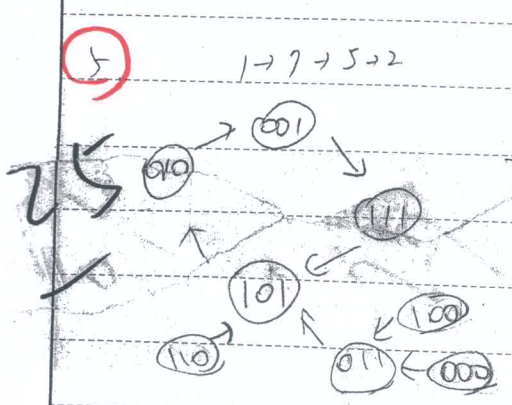

CBA	$C^+B^+A^+$	$J_C K_C$	$J_B K_B$	$J_A K_A$
000	xxx	xx	xx	xx
001	111	1x	1x	x0
010	001	0x	x1	1x
011	xxx	xx	xx	xx
100	xxx	xx	xx	xx
101	010	x1	1x	x1
110	xxx	xx	xx	xx
111	101	x0	x1	x0

0→1 1x  
0→0 0x  
1→0 x1  
1→1 x0

$J_C$	A	00 01 11 10
0	x	0 1 1 0
1	x	1 0 0 1

$J_C = A$

$K_C$	A	00 01 11 10
0	x	1 0 1 0
1	x	0 1 0 1

$K_C = B'$

$J_B$	A	00 01 11 10
0	x	1 0 1 0
1	x	0 1 0 1

$J_B = 1$

$K_B$	A	00 01 11 10
0	x	1 0 1 0
1	x	0 1 0 1

$K_B = 1$

$J_A$	A	00 01 11 10
0	x	1 0 1 0
1	x	0 1 0 1

$J_A = 1$

$K_A$	A	00 01 11 10
0	x	1 0 1 0
1	x	0 1 0 1

$K_A = C B'$